



NODE ANALYSIS METHOD

CIRCUIT ANALYSIS METHOD

prepared by:

Gyro A. Madrona
Electronics Engineer

TOPIC OUTLINE

Node Voltage


Node Analysis Method



NODE ANALYSIS METHOD



NODE VOLTAGE

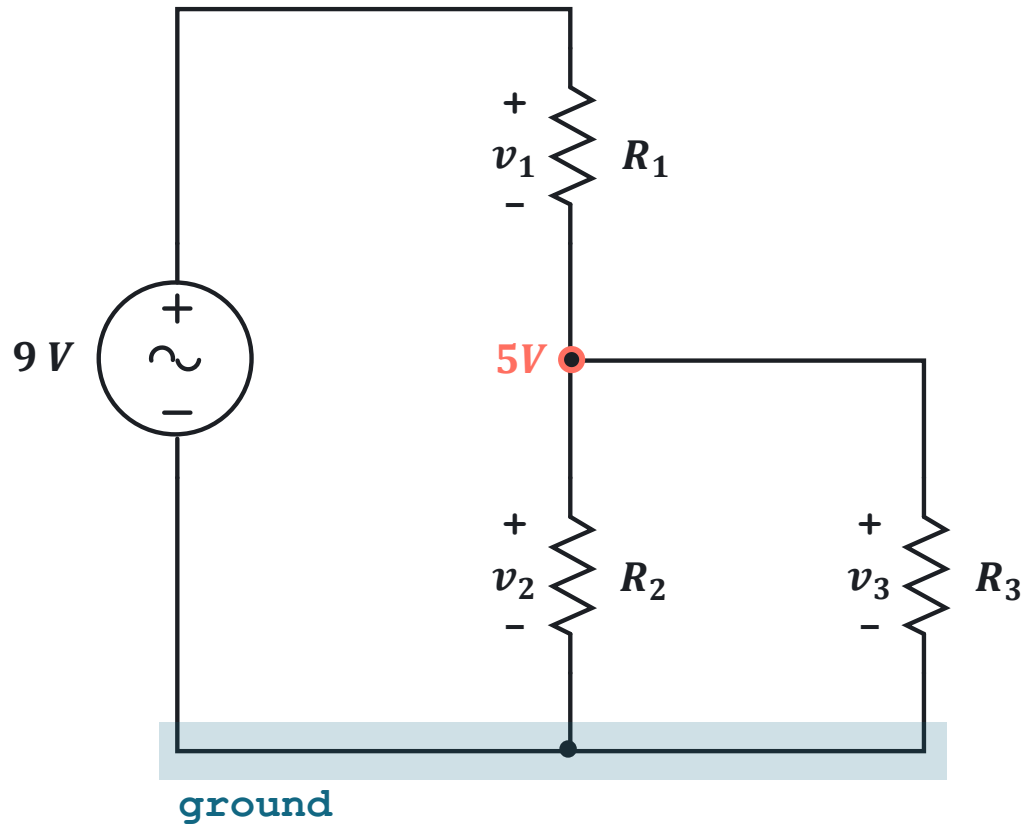

Node Voltage is the electrical potential difference between a given node and a reference node (ground) in a circuit.

Example:


$$v_1 = 9V - 5V$$

$$v_2 = 5V - 0$$

$$v_3 = 5V - 0$$




NODE ANALYSIS METHOD

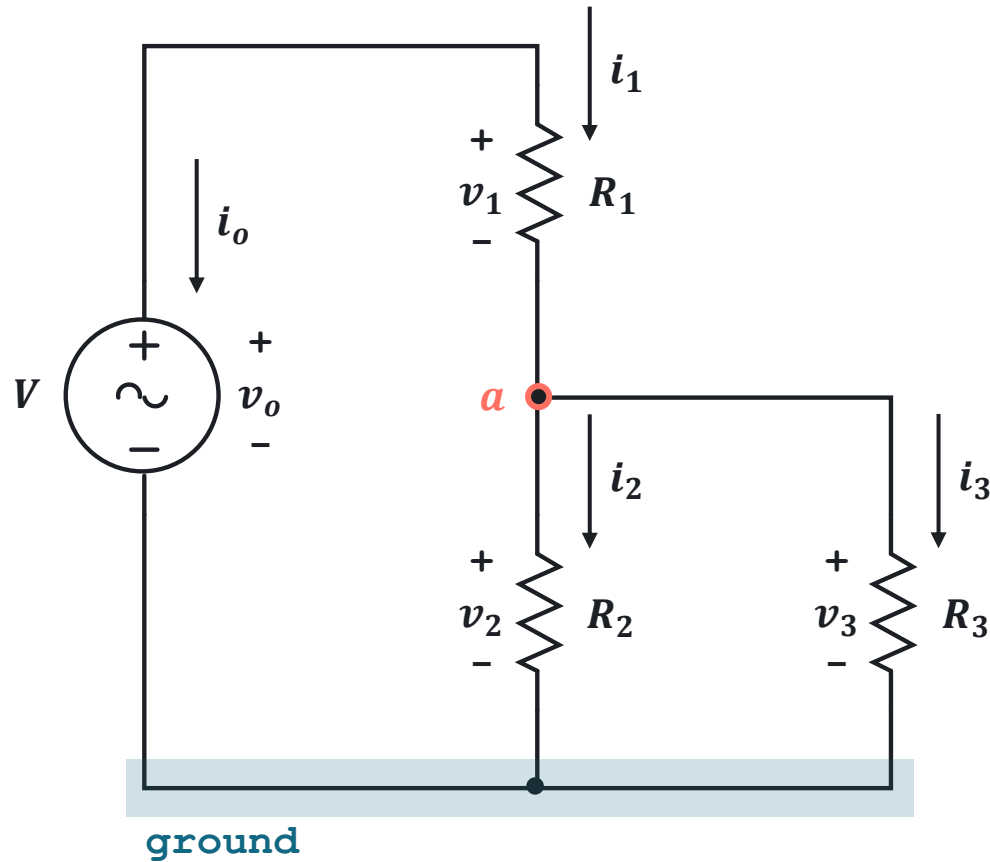

The node analysis method is based on Kirchhoff's Current Law (KCL), which is implicitly applied to establish voltage-current relationships forming a system of equations to solved for the unknown node voltages.



NODE ANALYSIS METHOD

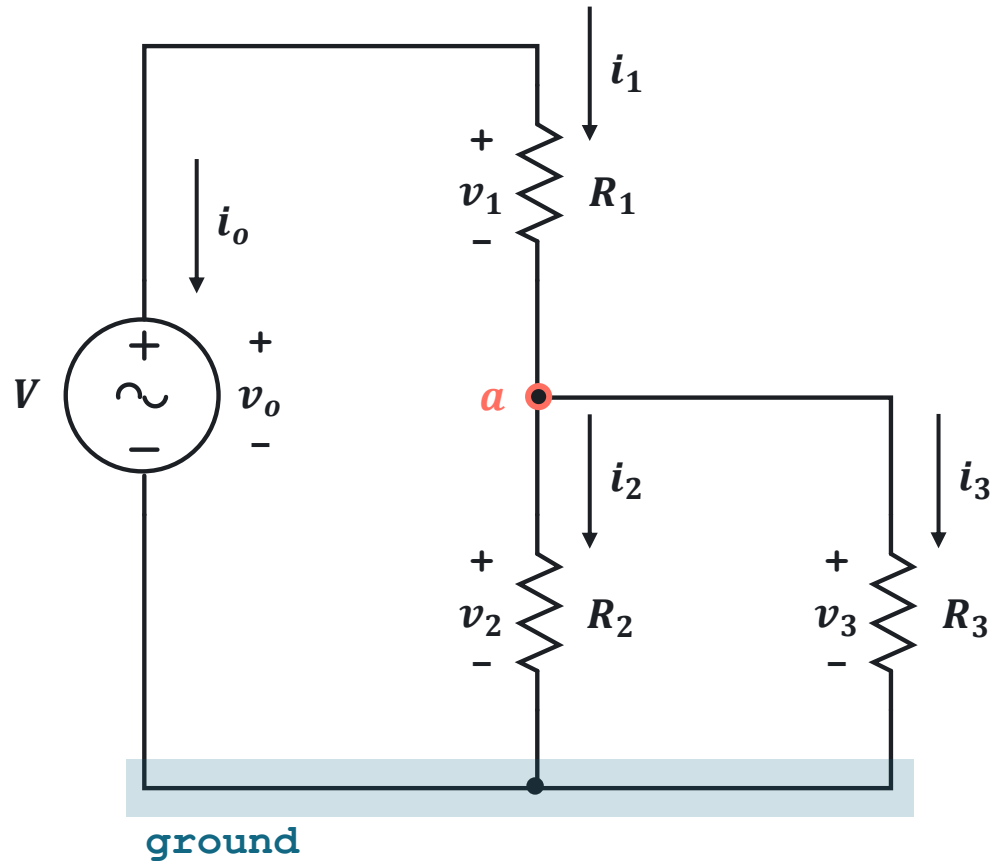

KCL @a:

$$-i_1 + i_2 + i_3 = 0$$

$$-\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} = 0$$


$$-\frac{v_o - v_a}{R_1} + \frac{v_a - 0}{R_2} + \frac{v_a - 0}{R_3} = 0$$

$$-v_o G_1 + v_a G_1 + v_a G_2 + v_a G_3 = 0$$

$$v_a(G_1 + G_2 + G_3) = v_o G_1$$



ELECTRICAL POWER

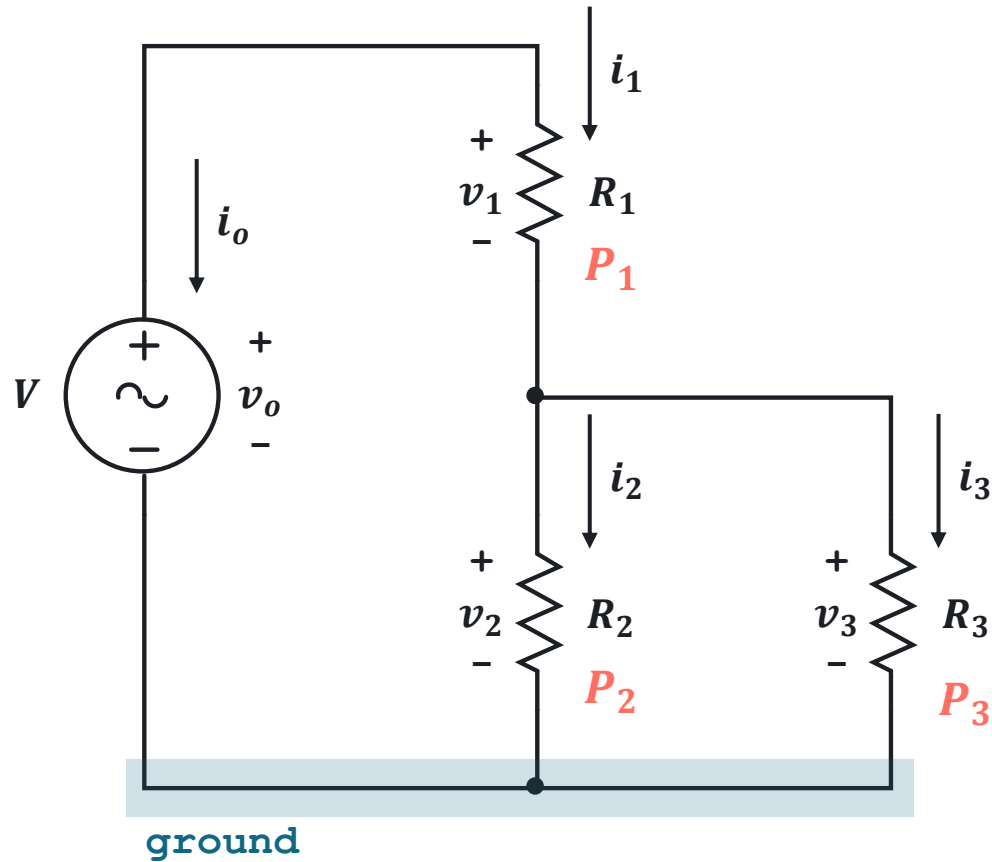

Electrical power refers to the rate at which electrical energy is transferred or converted per unit time.

Formulas:

$$P = vi$$

$$P = i^2 R$$

$$P = \frac{v^2}{R}$$

$$P_{total} = P_1 + P_2 + P_3 + \cdots P_n$$


unit: Watt (**W**)



EXERCISE

Determine the current flowing through each resistor, the voltage drop across each resistor, and the total power in the given circuit.


Solution:

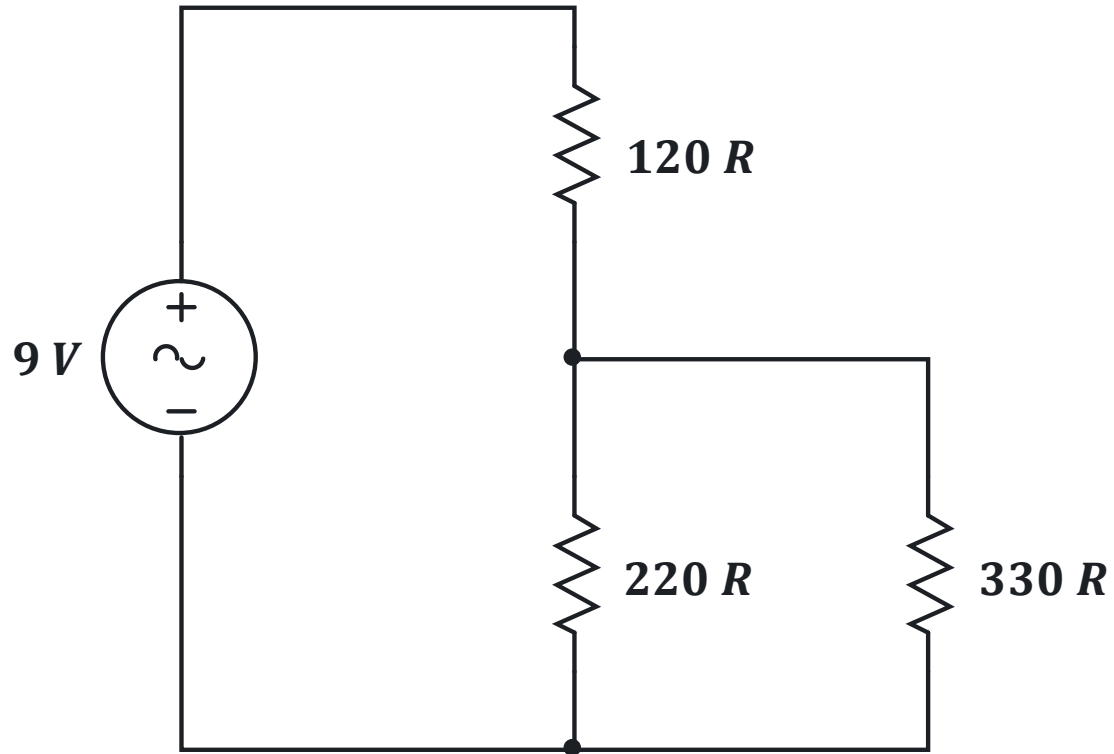

EXERCISE

Determine the current flowing through each resistor, the voltage drop across each resistor, and the total power in the given circuit.

Solution:

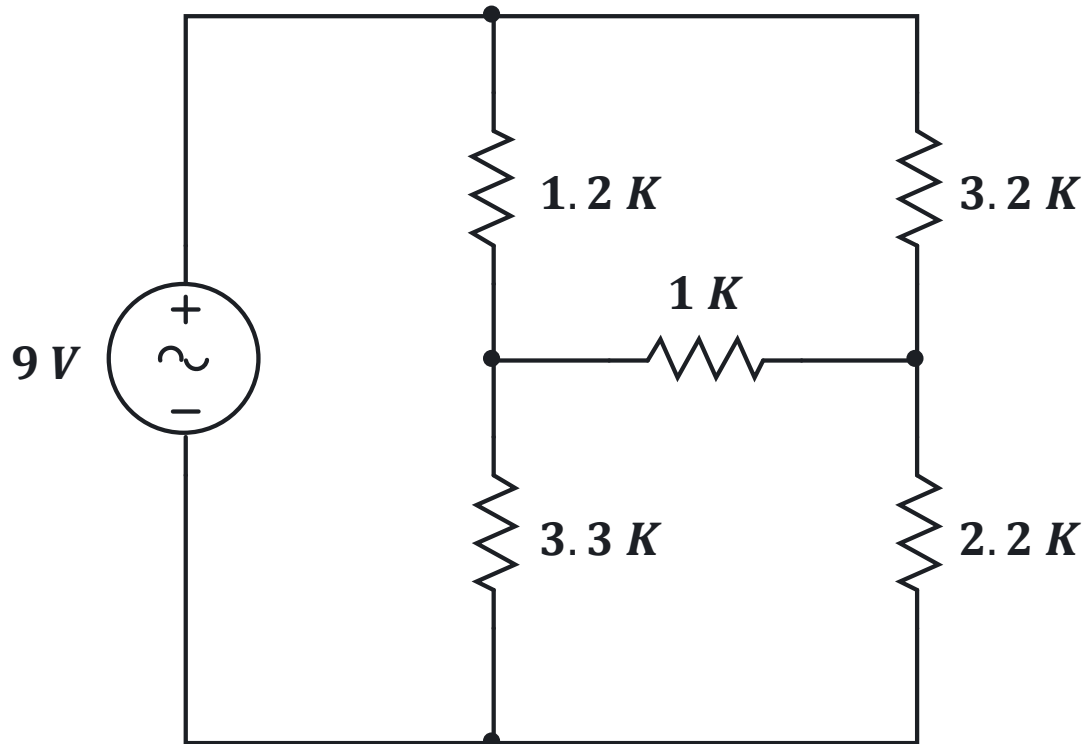

LABORATORY

