



# OPERATIONAL AMPLIFIER

## INTRODUCTION

---

*prepared by:*

**Gyro A. Madrona**  
Electronics Engineer

# TOPIC OUTLINE

Op-Amp Abstraction


Ideal Op-Amp

Non-inverting Op-Amp



# LUMPED CIRCUIT ABSTRACTION

Physics Law

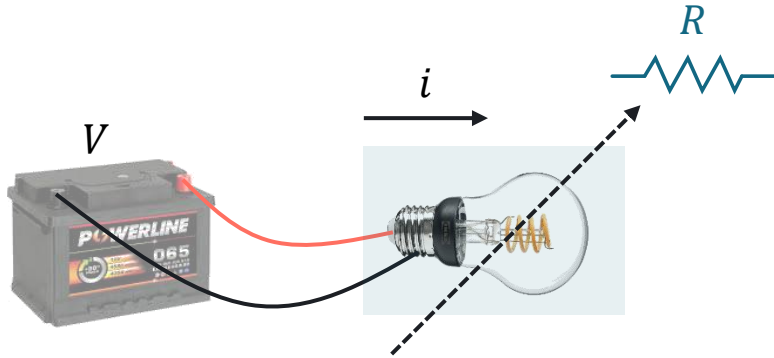


Maxwell's Equation

$$\nabla \cdot E = -\frac{\partial B}{\partial t} \xrightarrow{0}$$



$$\nabla \cdot J = -\frac{\partial \rho}{\partial t} \xrightarrow{0}$$

$$\nabla \cdot E = \frac{\rho}{\epsilon_0} \xrightarrow{0}$$

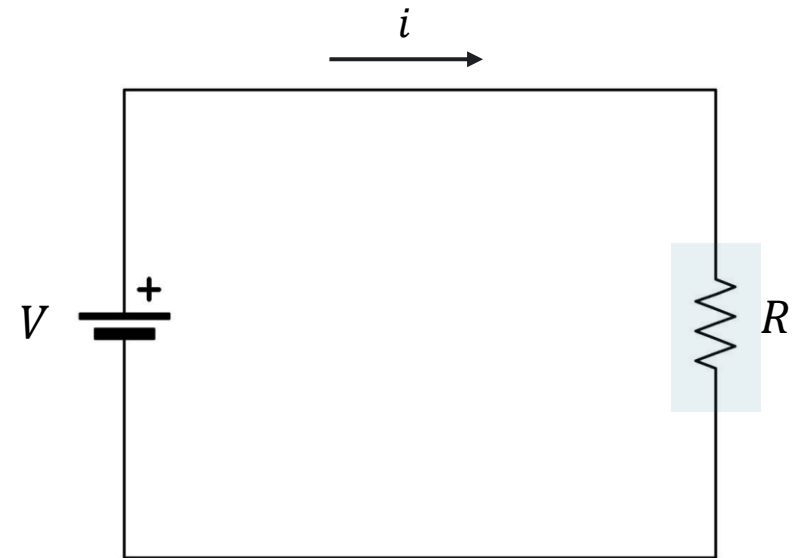R is a lumped element abstraction for the bulb



# DIGITAL ABSTRACTION

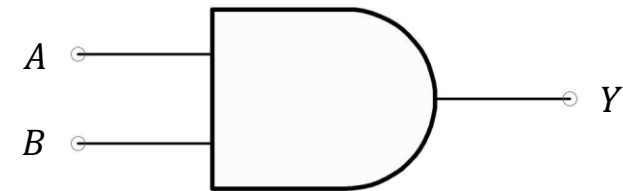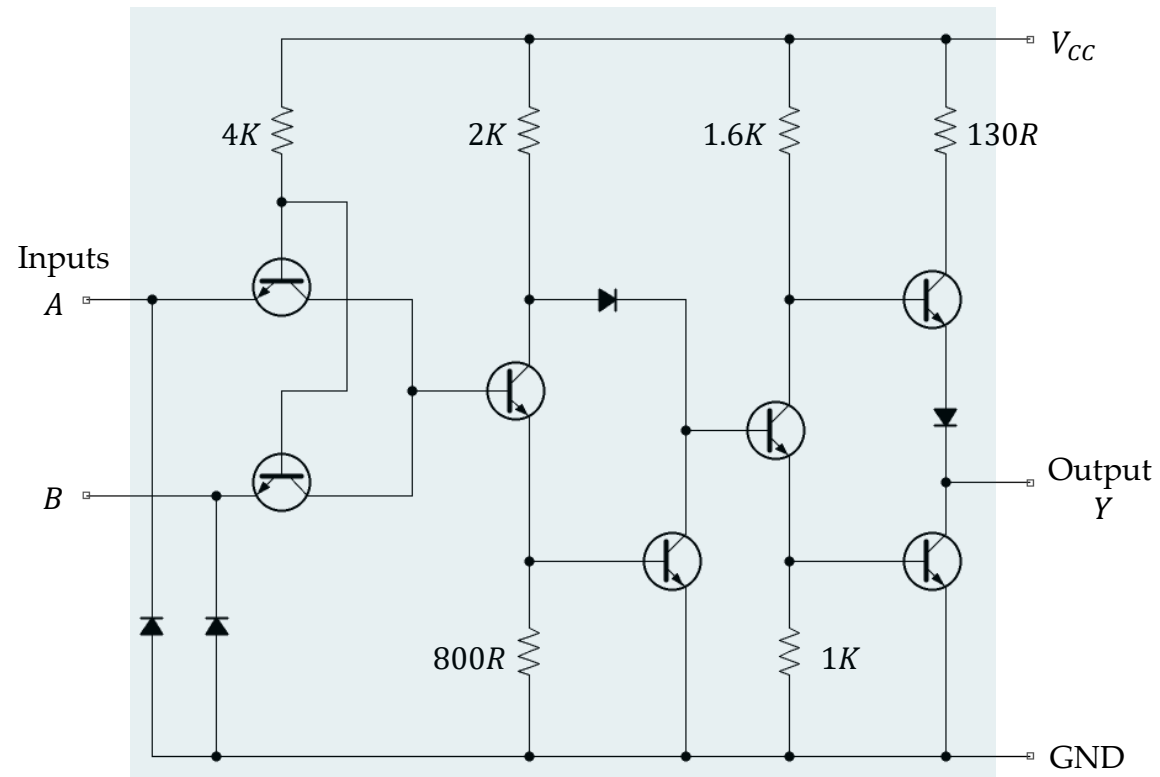

# LANGUAGE ABSTRACTION

---

```
#include <libioP.h>
#include <stdarg.h>
#include <stdio.h>

#undef printf

/* Write formatted output to stdout from the format string
FORMAT.  */
/* VARARGS1 */
int
__printf (const char *format, ...)
{
    va_list arg;
    int done;

    va_start (arg, format);
    done = vfprintf (stdout, format, arg);
    va_end (arg);

    return done;
}



#undef _IO_printf
ldbl_strong_alias (__printf, printf);
/* This is for libg++.  */
ldbl_strong_alias (__printf, _IO_printf);
```



**printf()**



# OP-AMP ABSTRACTION

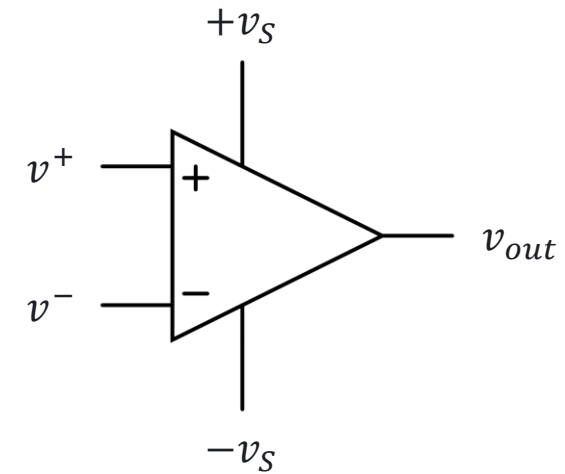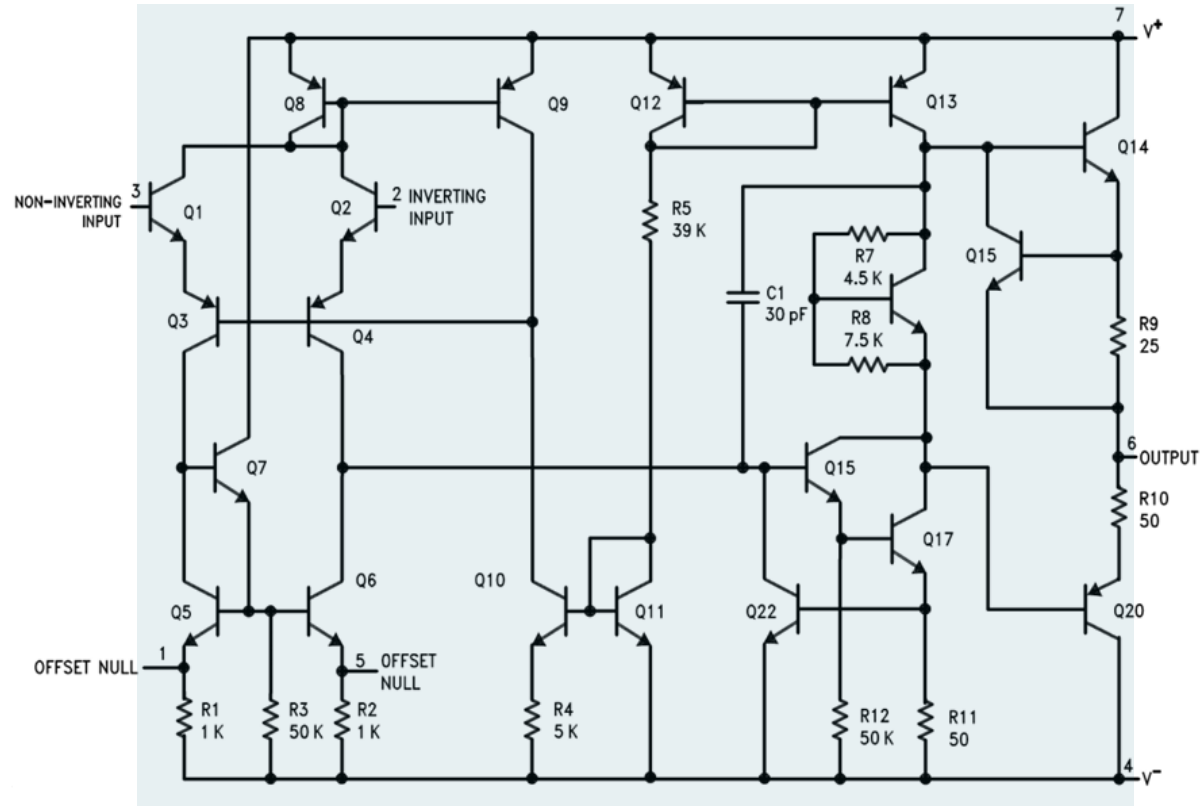


# IDEAL OP-AMP




# IDEAL OP-AMP

## Abstract representation

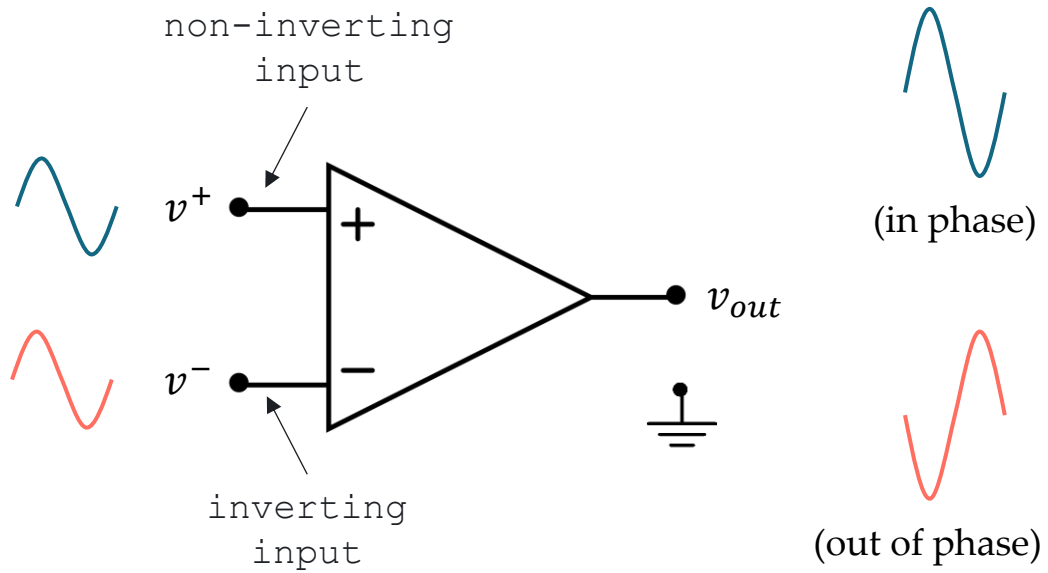

## Circuit model

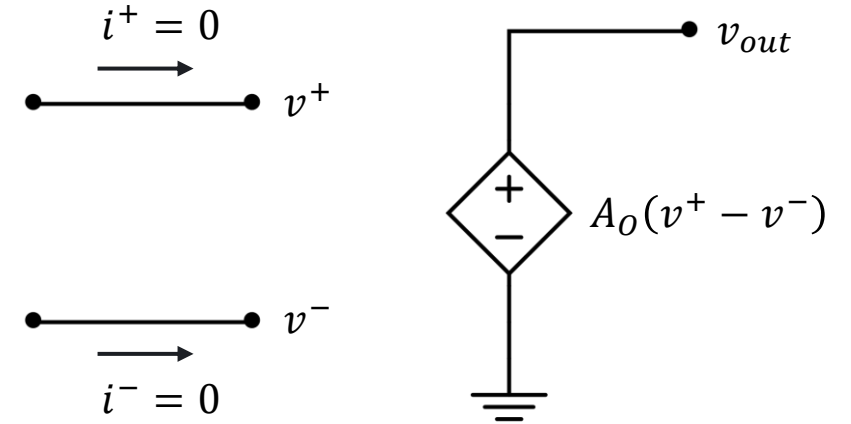




# IDEAL OP-AMP

## Properties of an ideal op-amp


- ( $R_{in} \rightarrow \infty$ ) Infinite input resistance
- ( $R_{out}$ ) Zero output resistance
- ( $A_o \rightarrow \infty$ ) Infinite open-loop gain
- ( $v_{out} \rightarrow \infty$ ) No saturation

## Circuit model

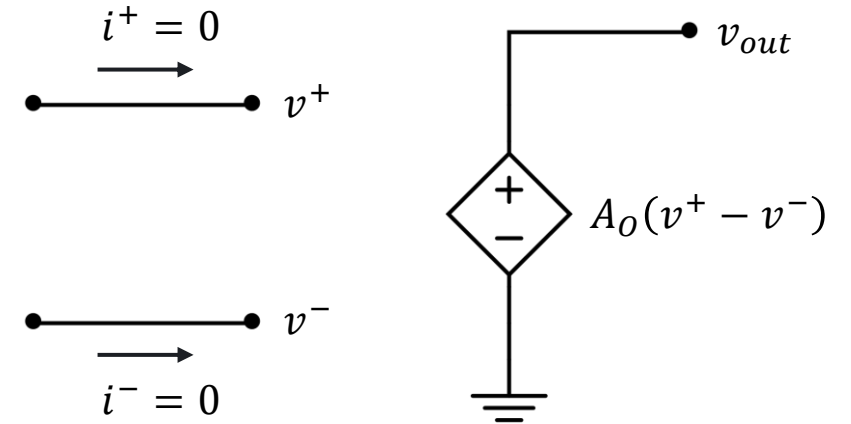


# SATURATION REGION

## Abstract representation

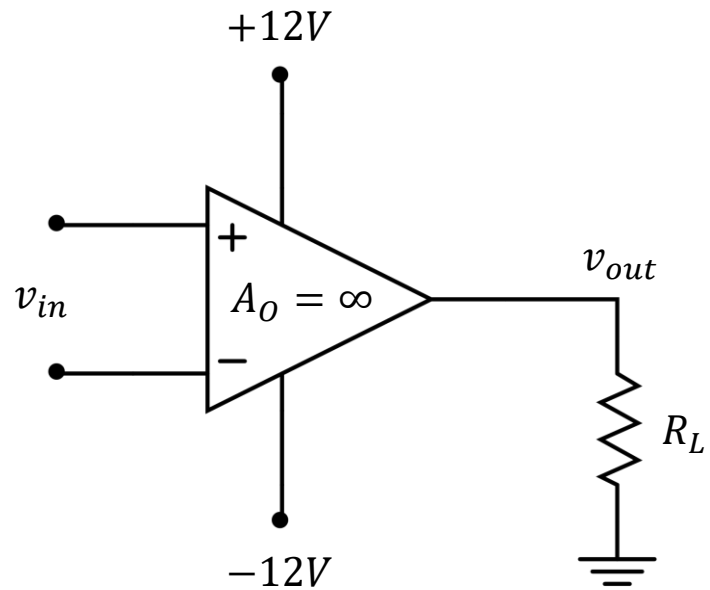

## Transfer characteristic

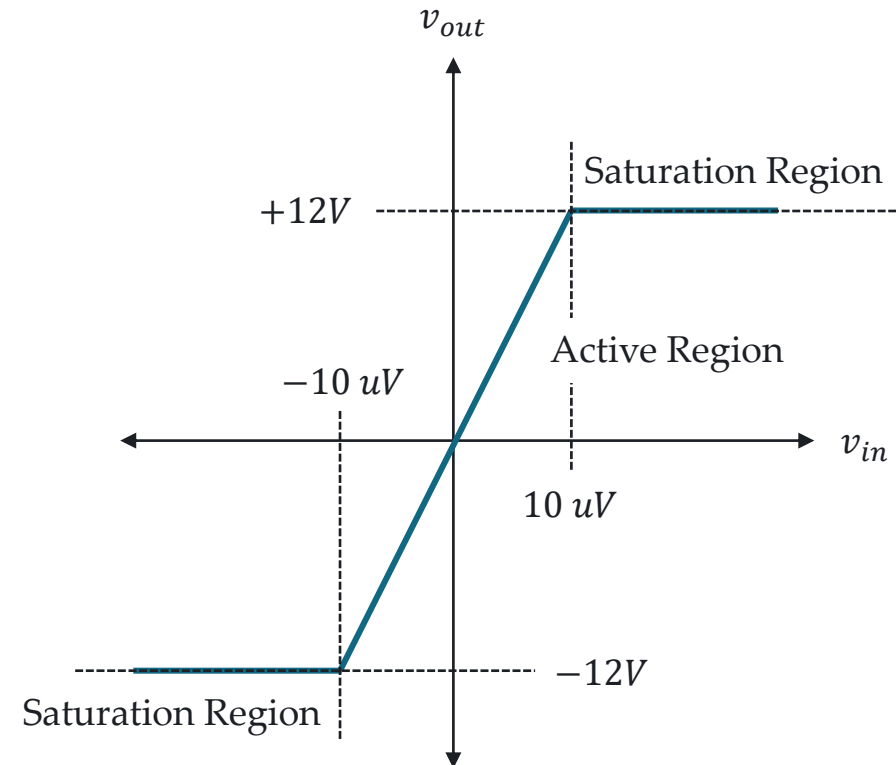


# NON-INVERTING OP-AMP



# NON-INVERTING OP-AMP

## Abstract representation

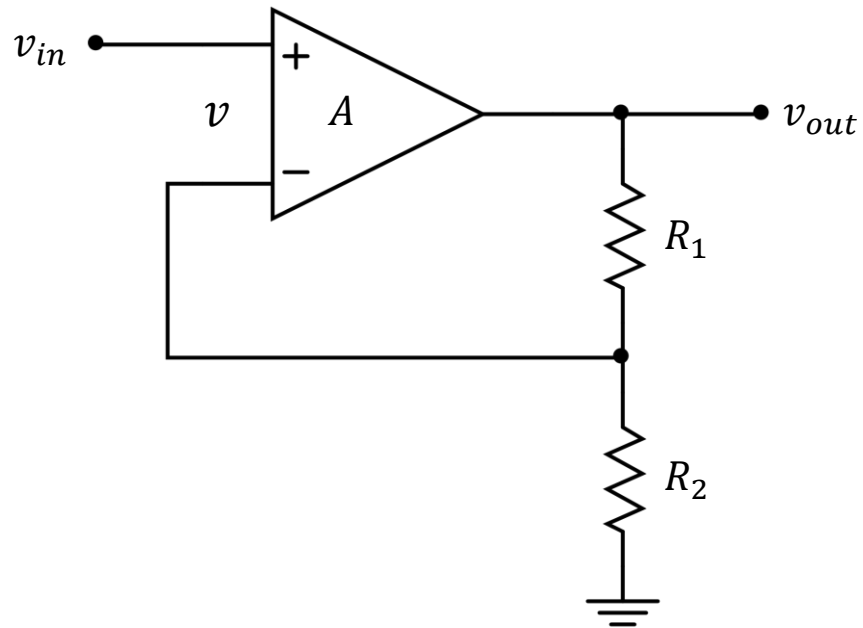


## note

$A$  = closed-loop gain


$A_o$  = open-loop gain ( $\infty$ )

## Circuit model

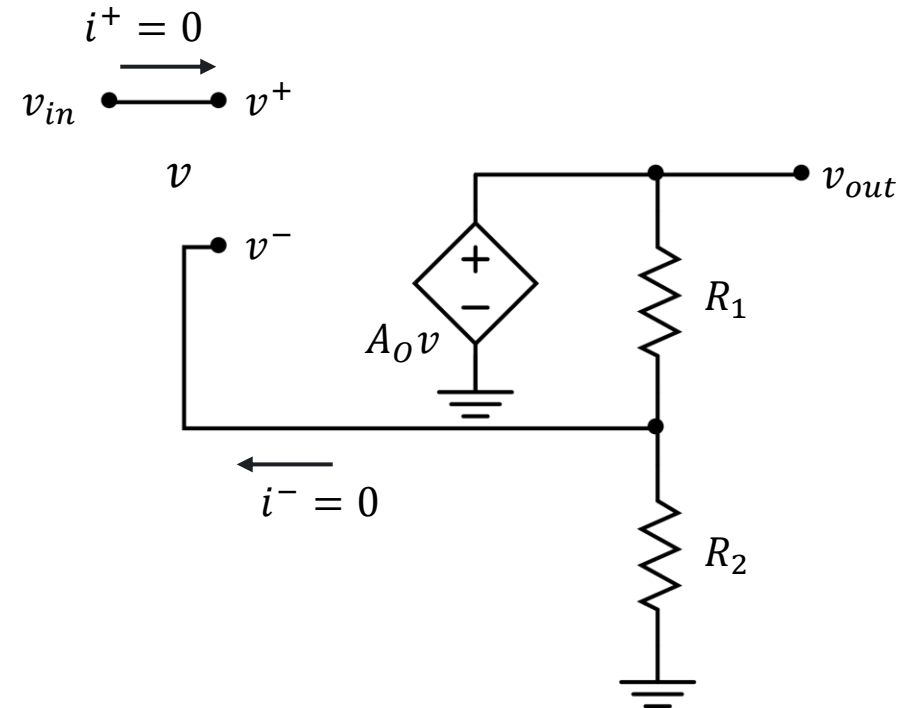

# NEGATIVE FEEDBACK

## Abstract representation

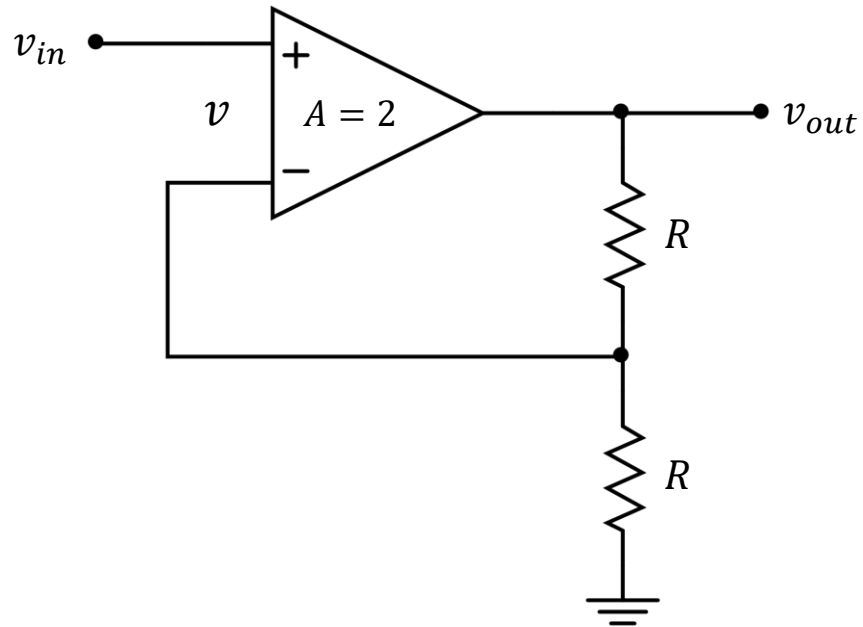

## Insightful analysis

- $v^+ \approx v^-$
- $i^+ = 0$
- $i^- = 0$



# LABORATORY

