

# KIRCHHOFF'S CURRENT AND VOLTAGE LAW

## BASIC CIRCUIT ANALYSIS METHOD

---

*prepared by:*

**Gyro A. Madrona**

Electronics Engineer

## **TOPIC OUTLINE**

**Circuit Convention**

**Kirchhoff's Current Law (KCL)**

**Kirchhoff's Voltage Law (KVL)**



# CIRCUIT CONVENTION



# CONVENTION

---

A convention is a widely accepted practice, method, or behavior that is followed by common agreement or tradition, rather than by formal rules.

example

## Color coding in Offices

red – urgent documents

blue – general files

green – financial records

This is a common practice but not formally regulated.



# STANDARD

---

A standard is a formal, established guideline, rule, or specification that is often mandatory and enforced by an authoritative body or organization.

example

## IEC 60062 Resistor Color Code

black – 0

brown – 1

red – 2

.

.

.

white – 9

Resistors have colored bands that represent specific digits, multipliers, and tolerance values.



# LABELING VARIABLES

## Steps in Labeling Variables

### 1. Label the Reference Node (ground)

Select a reference node with the most connections or the negative (-) terminal of a voltage source.

### 2. Label Node Voltages


Mark higher potentials as positive (+) relative to the reference node.

### 3. Label Currents

Entering the positive (+) terminal of a component.

### 4. Create a voltage loop

Follow the defined current directions.

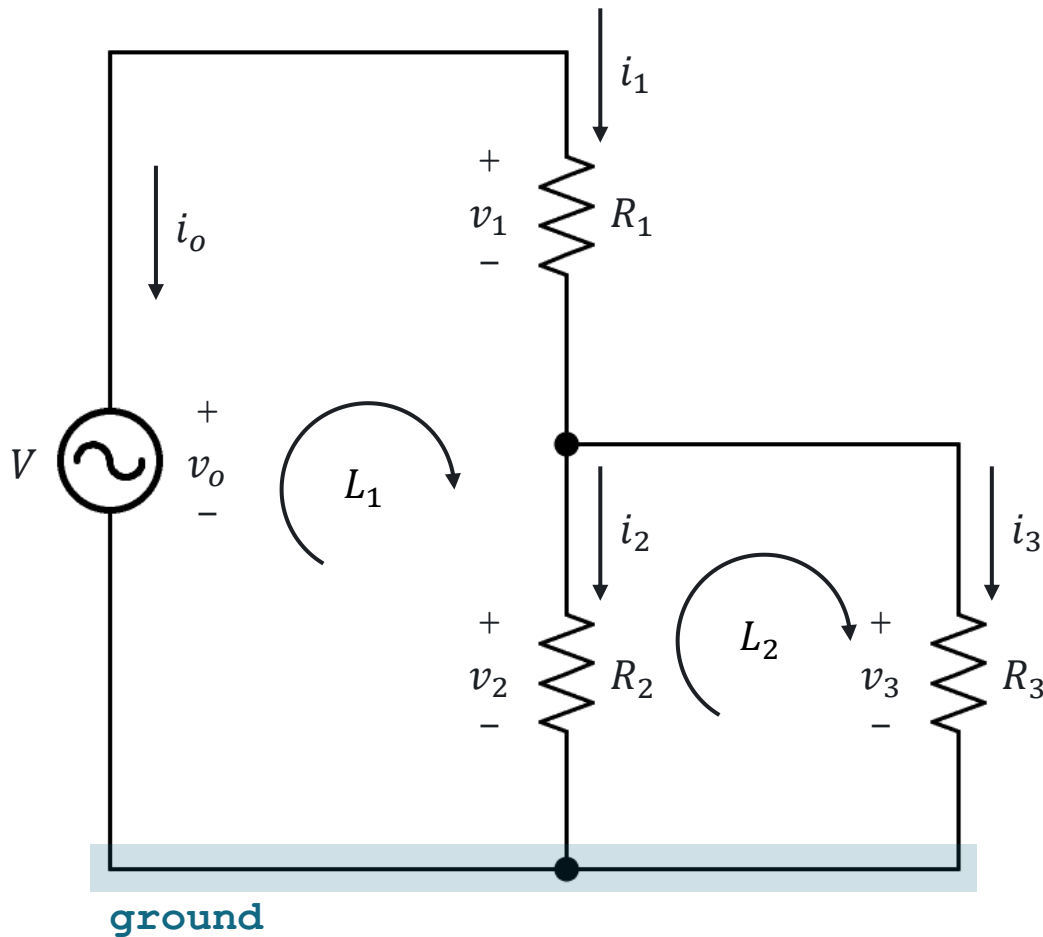

# CIRCUIT CONVENTION

## Current Flow Convention

- Current entering a node is negative  $(-)$
- Current leaving a node is positive  $(+)$

@a

$-i_1$


$+i_2$

$+i_3$

@b

$+i_o$


$+i_1$

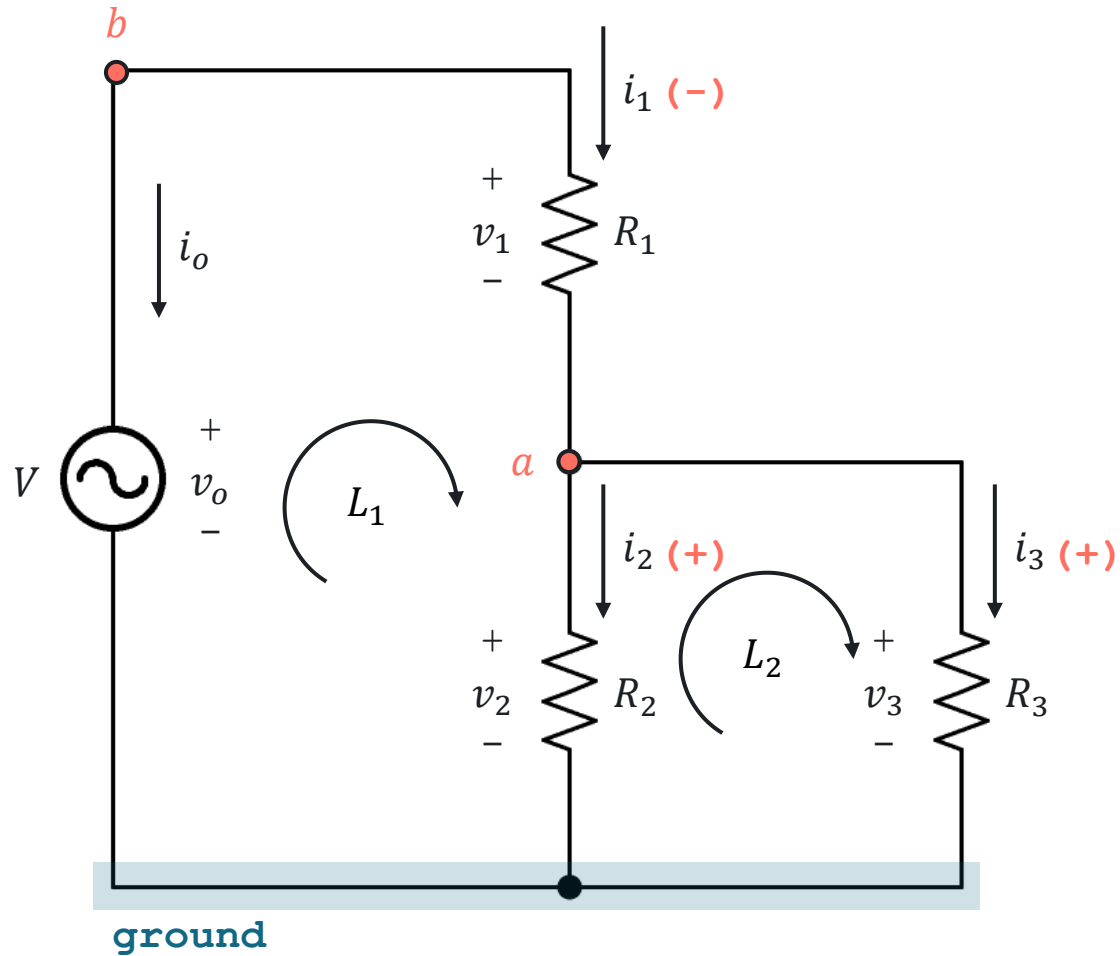

# CIRCUIT CONVENTION
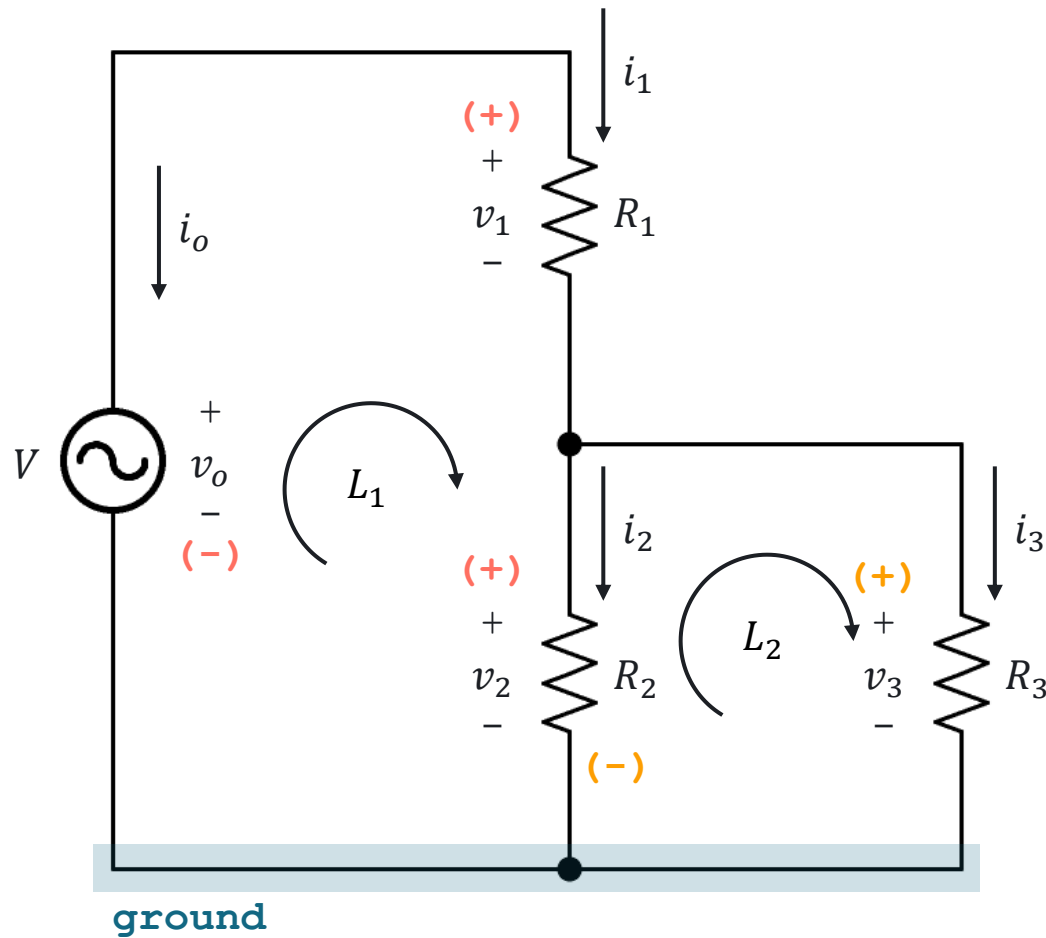
## Voltage Loop Convention

The “sign” of voltage of the element is the first sign the loop encounters.



@ $L_1$

$-v_o$

$+v_1$

$+v_2$

@ $L_2$

$-v_2$

$+v_3$





# KIRCHHOFF'S CURRENT AND VOLTAGE LAW



# KIRCHHOFF'S CURRENT LAW

Kirchhoff's current law states that summation of currents going-in and going-out a node is zero.


$$\sum i_j = 0$$

KCL @a

$$-i_1 + i_2 + i_3 = 0$$

KCL @b

$$i_o + i_1 = 0$$

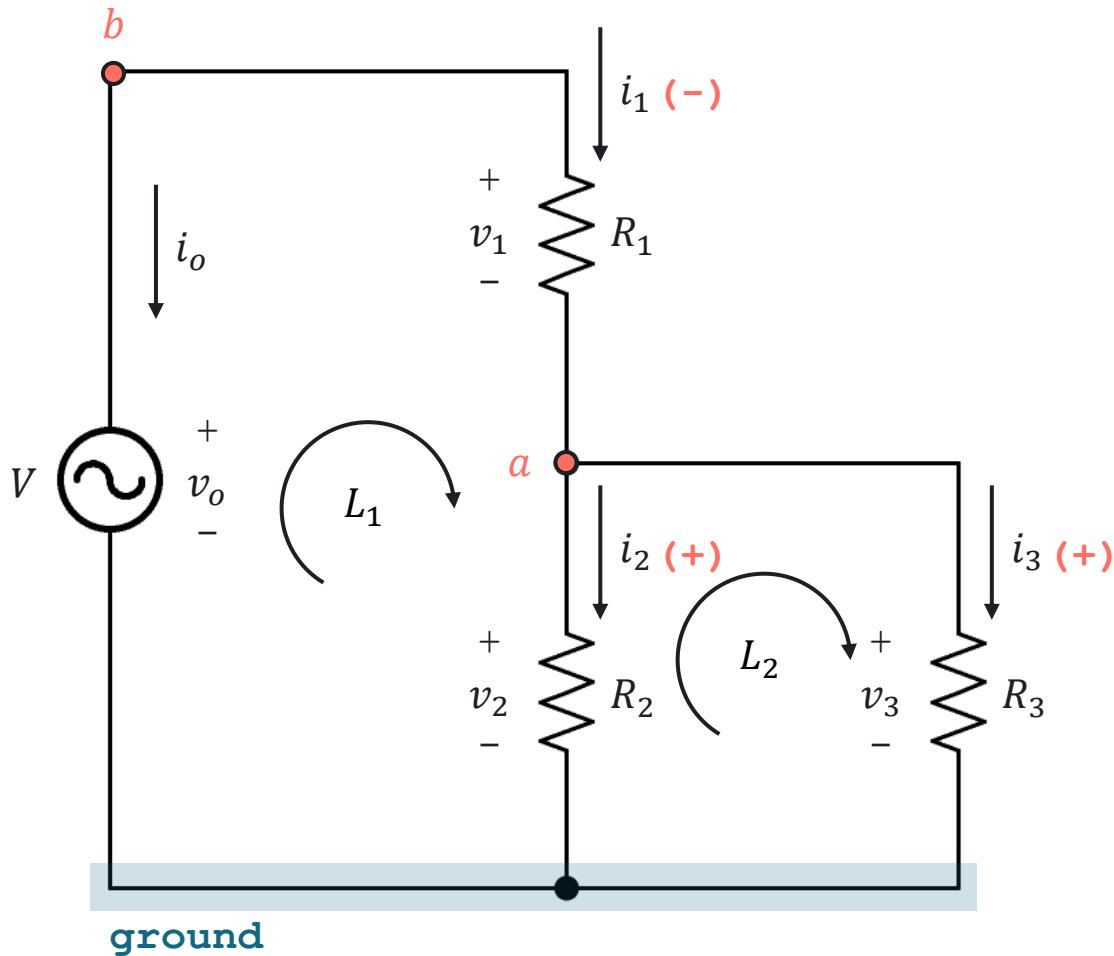

# KIRCHHOFF'S VOLTAGE LAW

Kirchhoff's voltage law states that the summation of voltages in a closed-loop is zero.


$$\sum v_j = 0$$

KVL @  $L_1$

$$-v_o + v_1 + v_2 = 0$$


KVL @  $L_2$

$$-v_2 + v_3 = 0$$

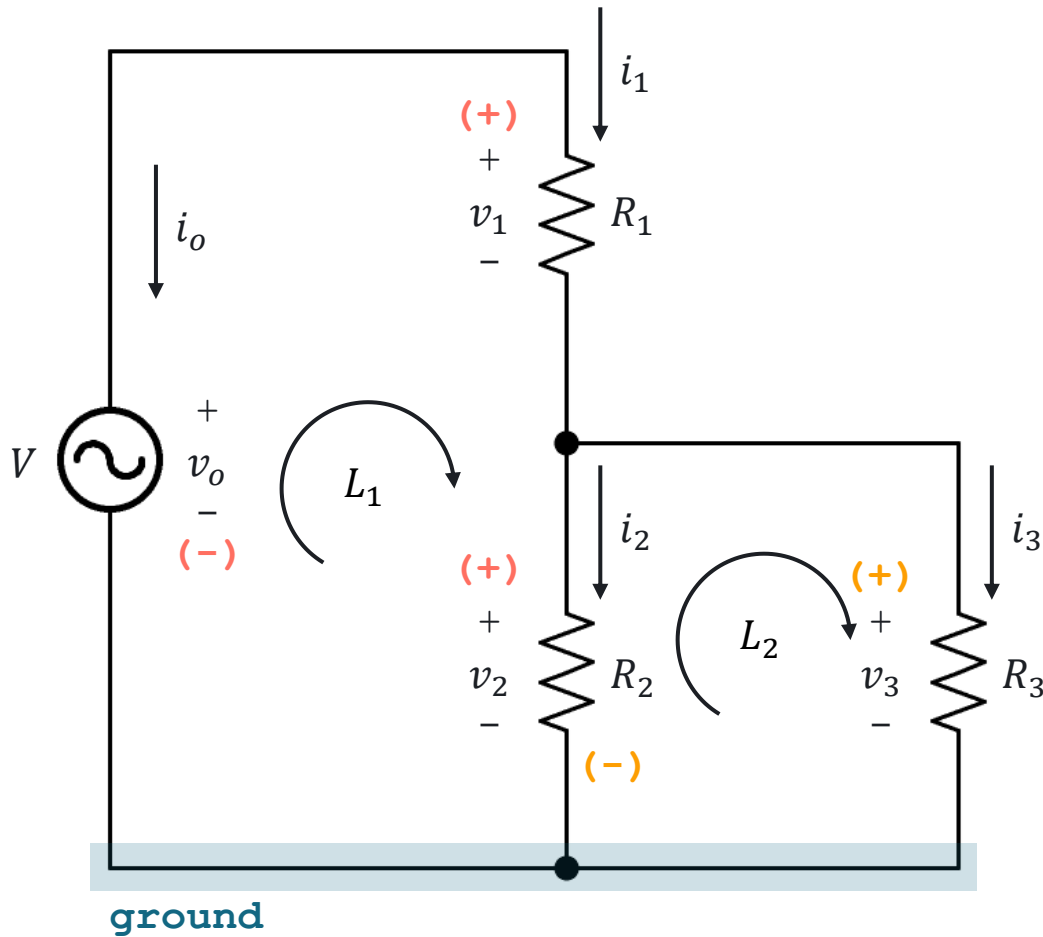
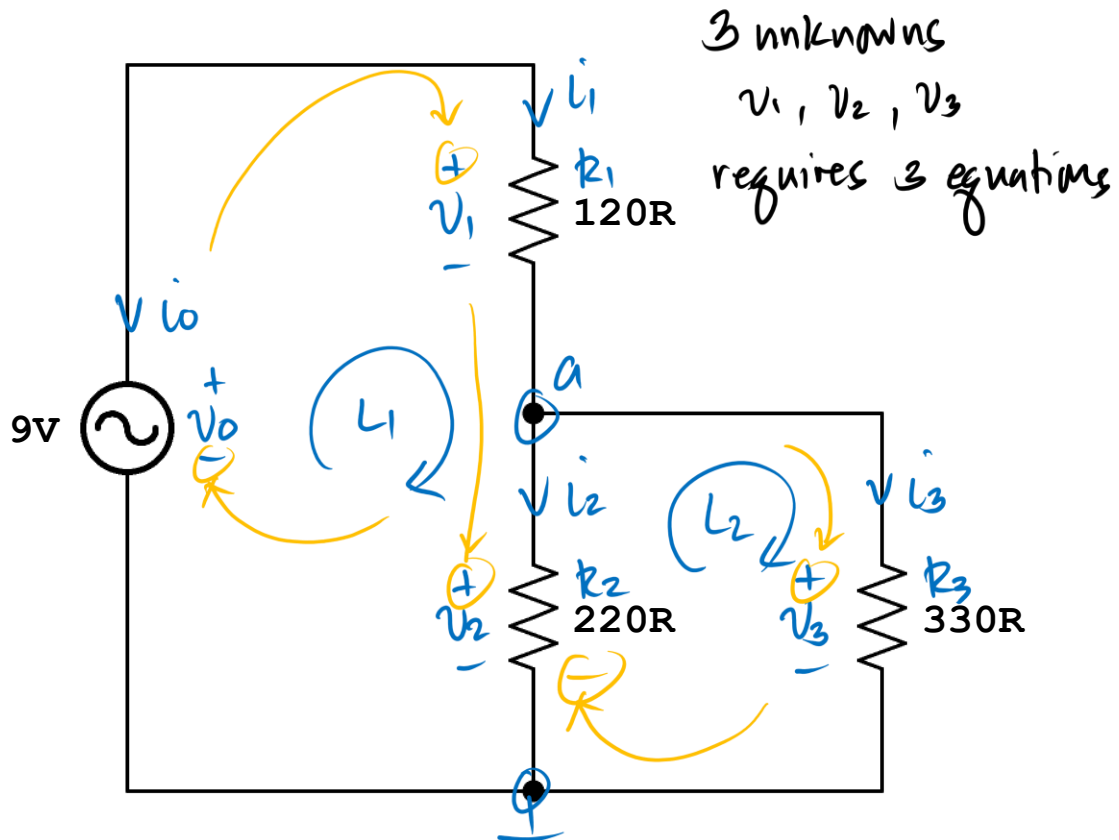
## EXERCISE

Analyze the given circuit to determine both the current through and the voltage drop across each resistor.



Solution

KCL @ a

$$-i_1 + i_2 + i_3 = 0$$

$$-\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} = 0$$

$$-v_1 G_1 + v_2 G_2 + v_3 G_3 = 0 \quad \text{eq ①}$$

KVL @ L1

$$-v_0 + v_1 + v_2 = 0$$

$$v_1 + v_2 = v_0 \quad \text{eq ②}$$

KVL @ L2

$$-v_2 + v_3 = 0 \quad \text{eq ③}$$

# EXERCISE

## Gaussian elimination method

$v_1$	$v_2$	$v_3$	
<del><math>-\frac{1}{120}</math></del>	<del><math>\frac{1}{220}</math></del>	<del><math>\frac{1}{330}</math></del>	0 $r_1$
①	1	0	9 $r_2$
0	-1	1	0 $r_3$

## System of linear equations

$$\underline{-v_1 G_1 + v_2 G_2 + v_3 G_3 = 0} \quad \text{eq ①}$$

$$\underline{v_1 + v_2 = v_0} \quad \text{eq ②}$$

$$\underline{-v_2 + v_3 = 0} \quad \text{eq ③}$$

$$-v_1 \frac{1}{120} + v_2 \frac{1}{220} + \frac{1}{330} = 0 \quad \text{①}$$

$$v_1 + v_2 = 9 \quad \text{②}$$

$$-v_2 + v_3 = 0 \quad \text{③}$$



# EXERCISE

## Gaussian elimination method

$v_1$	$v_2$	$v_3$	
$-\frac{1}{120}$	$\frac{1}{220}$	$\frac{1}{390}$	0 $r_1$
1	1	0	9 $r_2 \leftarrow 120 r_1 + r_2$
0	-1	1	0 $r_3$

## System of linear equations

$v_1$	$v_2$	$v_3$	
$-\frac{1}{120}$	$\frac{1}{220}$	$\frac{1}{390}$	0 $r_1$
0	$\frac{17}{11}$	$\frac{4}{11}$	9 $r_2$
0	-1	1	0 $r_3$



# EXERCISE

## Gaussian elimination method

$v_1$	$v_2$	$v_3$	
$-\frac{1}{120}$	$\frac{1}{220}$	$\frac{1}{330}$	0 $r_1$
0	$\frac{17}{11}$	$\frac{4}{11}$	9 $r_2$
0	0	$\frac{21}{11}$	9 $r_3$

## System of linear equations

$v_1$	$v_2$	$v_3$	
$-\frac{1}{120}$	$\frac{1}{220}$	$\frac{1}{330}$	0 $r_1$
0	$\frac{17}{11}$	$\frac{4}{11}$	9 $r_2$
0	-1	1	0 $r_3 \leftarrow \frac{17}{11} r_3 + r_2$



## EXERCISE

### Gaussian elimination method

$v_1$	$v_2$	$v_3$	
<del><math>-\frac{1}{120}</math></del>	<del><math>\frac{1}{220}</math></del>	<del><math>\frac{1}{330}</math></del>	0 $r_1$
0	$\frac{17}{11}$	$\frac{4}{11}$	9 $r_2$
0	0	$\frac{21}{11}$	9 $r_3$

### System of linear equations

from  $r_3$

$$\frac{21}{11} v_3 = 9$$

$$v_3 = \frac{9(11)}{21}$$

$$v_3 = 4.71 \text{ V}$$


ans




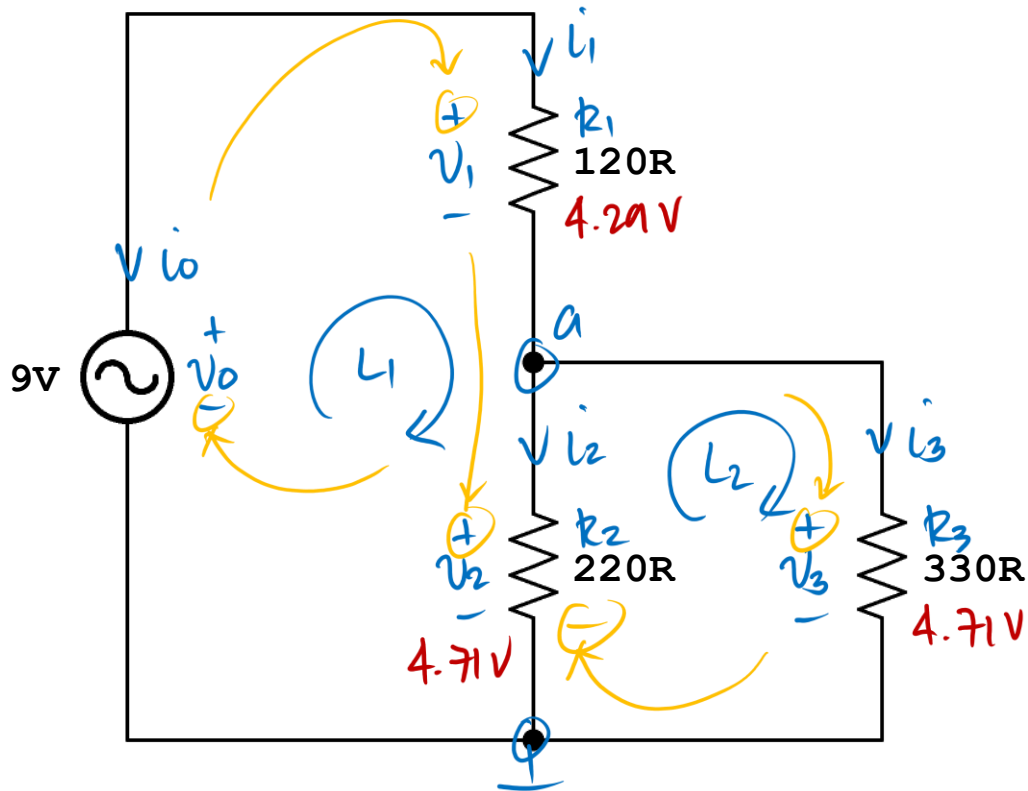
## EXERCISE

Analyze the given circuit to determine both the current through and the voltage drop across each resistor.



Solution

KVL @  $L_2$

$$-v_2 + v_3 = 0$$

$$v_2 = v_3$$

$$\boxed{v_2 = 4.71 \text{ V}}$$

ans

KVL @  $L_1$

$$-v_0 + v_1 + v_2 = 0$$


$$\begin{aligned} v_1 &= v_0 - v_2 \\ &= 9 - 4.71 \end{aligned}$$

$$\boxed{v_1 = 4.29 \text{ V}}$$

ans
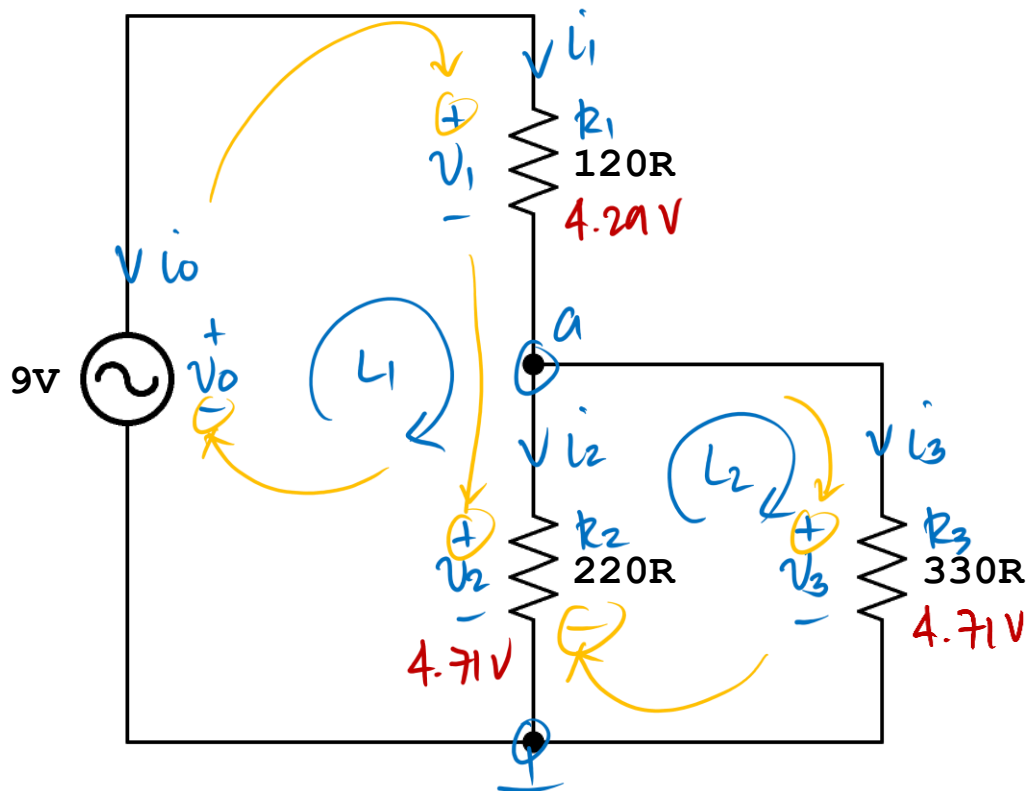
## EXERCISE

Analyze the given circuit to determine both the current through and the voltage drop across each resistor.



Solution

$$i_1 = \frac{v_1}{R_1} = \frac{4.29}{120}$$

$$i_1 = 35.75 \text{ mA}$$

ans

$$i_2 = \frac{v_2}{R_2} = \frac{4.71}{220}$$

$$i_2 = 21.41 \text{ mA}$$

ans


$$i_3 = \frac{v_3}{R_3} = \frac{4.71}{330}$$
$$i_3 = 14.27 \text{ mA}$$

ans


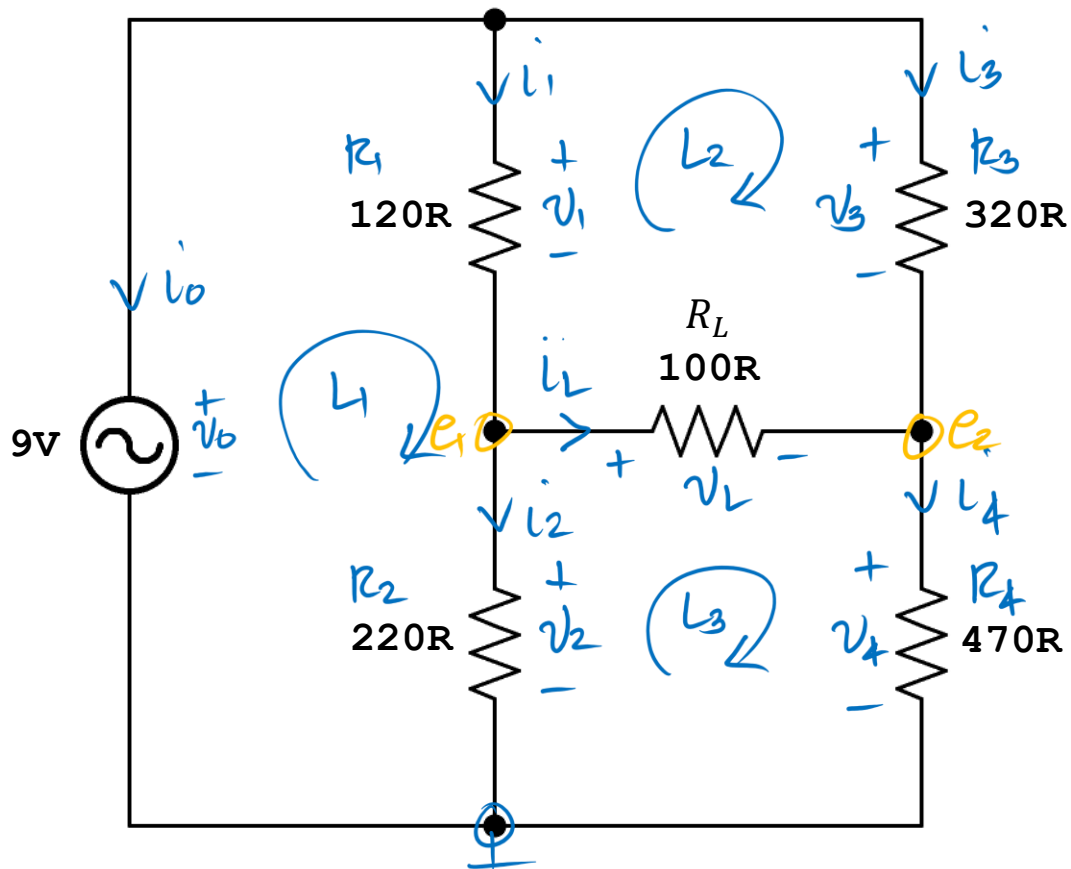
## EXERCISE

Determine the voltage drop across the load resistor and the current flowing through it.



Solution

KCL @ e1

$$-i_1 + i_2 + i_L = 0$$

$$-\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_L}{R_L} = 0$$

$$-v_1 G_1 + v_2 G_2 + v_L G_L = 0 \quad (\text{eq.1})$$

KCL @ e2

$$-i_3 + i_4 - i_L = 0$$


$$-\frac{v_3}{R_3} + \frac{v_4}{R_4} - \frac{v_L}{R_L} = 0$$

$$-v_3 G_3 + v_4 G_4 - v_L G_L = 0 \quad (\text{eq.2})$$


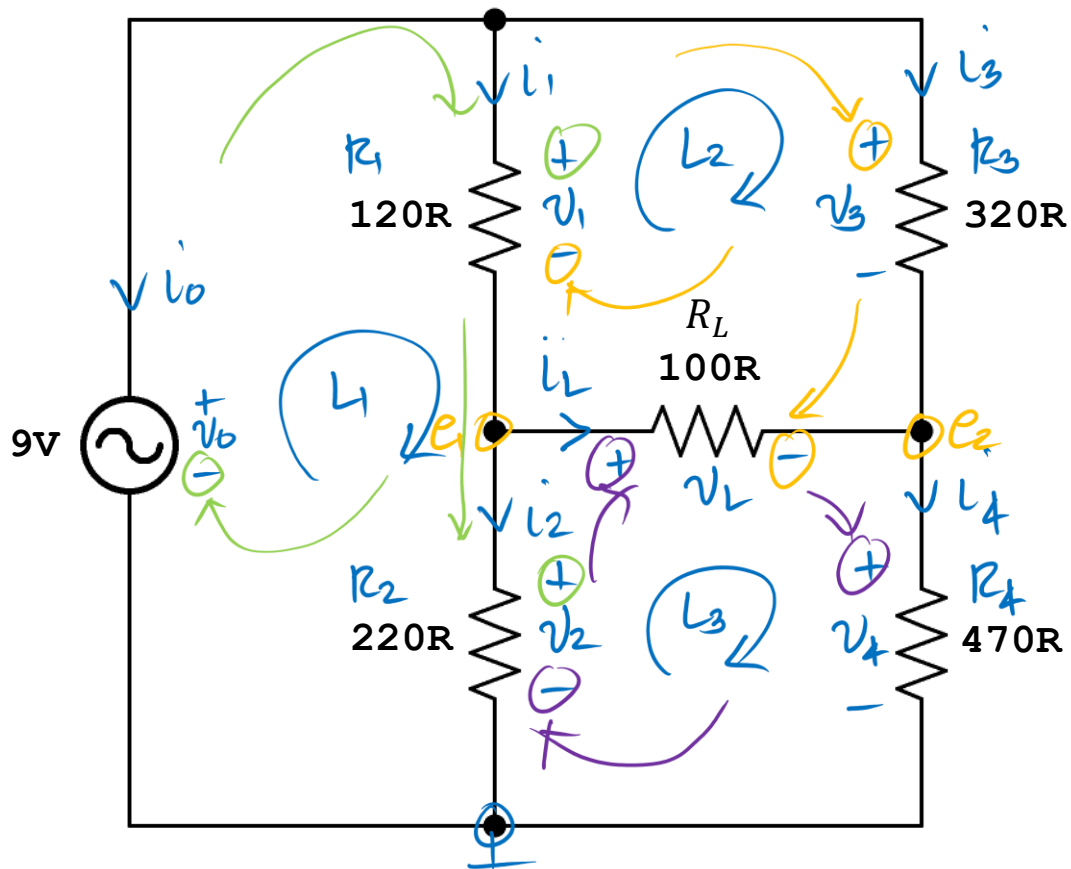
## EXERCISE

Determine the voltage drop across the load resistor and the current flowing through it.



Solution

KVL @ L1

$$-v_0 + v_1 + v_2 = 0$$

$$v_1 + v_2 = v_0 \quad (\text{eq. 3})$$

KVL @ L2

$$-v_1 + v_3 - v_L = 0 \quad (\text{eq. 4})$$

KVL @ L3

$$-v_2 + v_4 + v_L = 0 \quad (\text{eq. 5})$$



# EXERCISE

## Gaussian Elimination Method

$v_1$	$v_2$	$v_3$	$v_4$	$v_L$		
$-\frac{1}{120}$	$\frac{1}{220}$	0	0	$\frac{1}{100}$	0	$r_1$
0	0	$-\frac{1}{320}$	$\frac{1}{470}$	$-\frac{1}{100}$	0	$r_2$
1	1	0	0	0	9	$r_3$
-1	0	1	0	-1	0	$r_4$
0	-1	0	1	1	0	$r_5$

## System of Linear Equations

$$-\cancel{v_1 \frac{1}{120}} + \cancel{v_2 \frac{1}{220}} + \cancel{v_L \frac{1}{100}} = 0 \quad (\text{eq.1})$$

$$-\cancel{v_3 \frac{1}{320}} + \cancel{v_4 \frac{1}{470}} - \cancel{v_L \frac{1}{100}} = 0 \quad (\text{eq.2})$$

$$v_1 + v_2 = \cancel{20}^9 \quad (\text{eq.3})$$

$$-v_1 + v_3 - v_L = 0 \quad (\text{eq.4})$$

$$-v_2 + v_4 + v_L = 0 \quad (\text{eq.5})$$



# EXERCISE

## Gaussian Elimination Method

	$v_1$	$v_2$	$v_3$	$v_4$	$v_L$		
	$-\frac{1}{120}$	$\frac{1}{220}$	0	0	$\frac{1}{100}$	0	$r_1$
SWAP	0	0	$-\frac{1}{320}$	$\frac{1}{470}$	$-\frac{1}{100}$	0	$r_2$
	1	1	0	0	0	9	$r_3$
	-1	0	1	0	-1	0	$r_4$
	0	-1	0	1	1	0	$r_5$

## System of Linear Equations

	$v_1$	$v_2$	$v_3$	$v_4$	$v_L$		
	$-\frac{1}{120}$	$\frac{1}{220}$	0	0	$\frac{1}{100}$	0	$r_1$
	0	-1	0	1	1	0	$r_2$
	0	0	$-\frac{1}{320}$	$\frac{1}{470}$	$-\frac{1}{100}$	0	$r_3$
	-1	0	1	0	-1	0	$r_4$
	1	1	0	0	0	9	$r_5$



# EXERCISE

## Gaussian Elimination Method

$v_1$	$v_2$	$v_3$	$v_4$	$v_L$		
$-\frac{1}{120}$	$\frac{1}{220}$	0	0	$\frac{1}{100}$	0	$r_1$
0	-1	0	1	1	0	$r_2$
0	0	$-\frac{1}{320}$	$\frac{1}{480}$	$-\frac{1}{100}$	0	$r_3$
0	$\frac{6}{11}$	-1	0	$\frac{11}{5}$	0	$r_4$
1	1	0	0	0	9	$r_5$

## System of Linear Equations

$v_1$	$v_2$	$v_3$	$v_4$	$v_L$		
$-\frac{1}{120}$	$\frac{1}{220}$	0	0	$\frac{1}{100}$	0	$r_1$
0	-1	0	1	1	0	$r_2$
0	0	$-\frac{1}{320}$	$\frac{1}{480}$	$-\frac{1}{100}$	0	$r_3$
-1	0	1	0	-1	0	$r_4 \leftarrow 120 r_1 - r_4$
1	1	0	0	0	9	$r_5$



# EXERCISE

## Gaussian Elimination Method

$v_1$	$v_2$	$v_3$	$v_4$	$v_L$		
$-\frac{1}{120}$	$\frac{1}{220}$	0	0	$\frac{1}{100}$	0	$r_1$
0	-1	0	1	1	0	<u><math>r_2</math></u>
0	0	$-\frac{1}{320}$	$\frac{1}{470}$	$-\frac{1}{100}$	0	$r_3$
0	$\frac{6}{11}$	-1	0	$\frac{11}{5}$	0	<u><math>r_4 \leftarrow \frac{6}{11}r_2 + r_4</math></u>
1	1	0	0	0	9	$r_5$

## System of Linear Equations

$v_1$	$v_2$	$v_3$	$v_4$	$v_L$		
$-\frac{1}{120}$	$\frac{1}{220}$	0	0	$\frac{1}{100}$	0	$r_1$
0	-1	0	1	1	0	$r_2$
0	0	$-\frac{1}{320}$	$\frac{1}{470}$	$-\frac{1}{100}$	0	$r_3$
0	0	-1	$\frac{6}{11}$	$\frac{151}{55}$	0	$r_4$
1	1	0	0	0	9	$r_5$





# EXERCISE

## Gaussian Elimination Method

$v_1$	$v_2$	$v_3$	$v_4$	$v_L$		
$-\frac{1}{120}$	$\frac{1}{220}$	0	0	$\frac{1}{100}$	0	$r_1$
0	-1	0	1	1	0	$r_2$
0	0	$-\frac{1}{320}$	$\frac{1}{470}$	$-\frac{1}{100}$	0	$r_3$
0	0	0	$\frac{70}{517}$	$-\frac{327}{55}$	0	$r_4$
1	1	0	0	0	9	$r_5$

## System of Linear Equations

$v_1$	$v_2$	$v_3$	$v_4$	$v_L$		
$-\frac{1}{120}$	$\frac{1}{220}$	0	0	$\frac{1}{100}$	0	$r_1$
0	-1	0	1	1	0	$r_2$
0	0	$-\frac{1}{320}$	$\frac{1}{470}$	$-\frac{1}{100}$	0	$r_3$
0	0	-1	$\frac{6}{11}$	$\frac{151}{55}$	0	$r_4 \leftarrow 320 r_3 - r_4$
1	1	0	0	0	9	$r_5$



# EXERCISE

## Gaussian Elimination Method

$v_1$	$v_2$	$v_3$	$v_4$	$v_L$		
$-\frac{1}{120}$	$\frac{1}{220}$	0	0	$\frac{1}{100}$	0	<u><math>r_1</math></u>
0	-1	0	1	1	0	$r_2$
0	0	$-\frac{1}{320}$	$\frac{1}{470}$	$-\frac{1}{100}$	0	$r_3$
0	0	0	$\frac{70}{517}$	$-\frac{327}{55}$	0	$r_4$
1	1	0	0	0	9	$r_5 \leftarrow 120 r_1 + r_5 \rightarrow$

## System of Linear Equations

$v_1$	$v_2$	$v_3$	$v_4$	$v_L$		
$-\frac{1}{120}$	$\frac{1}{220}$	0	0	$\frac{1}{100}$	0	$r_1$
0	-1	0	1	1	0	$r_2$
0	0	$-\frac{1}{320}$	$\frac{1}{470}$	$-\frac{1}{100}$	0	$r_3$
0	0	0	$\frac{70}{517}$	$-\frac{327}{55}$	0	$r_4$
0	$\frac{17}{11}$	0	0	$\frac{6}{5}$	9	$r_5$



# EXERCISE

## Gaussian Elimination Method

$v_1$	$v_2$	$v_3$	$v_4$	$v_L$		
$-\frac{1}{120}$	$\frac{1}{220}$	0	0	$\frac{1}{100}$	0	$r_1$
0	-1	0	1	1	0	$r_2$
0	0	$-\frac{1}{320}$	$\frac{1}{470}$	$-\frac{1}{100}$	0	$r_3$
0	0	0	$\frac{70}{517}$	$-\frac{327}{55}$	0	$r_4$
0	0	0	$\frac{17}{11}$	$\frac{151}{55}$	9	$r_5$

## System of Linear Equations

$v_1$	$v_2$	$v_3$	$v_4$	$v_L$		
$-\frac{1}{120}$	$\frac{1}{220}$	0	0	$\frac{1}{100}$	0	$r_1$
0	-1	0	1	1	0	$r_2$
0	0	$-\frac{1}{320}$	$\frac{1}{470}$	$-\frac{1}{100}$	0	$r_3$
0	0	0	$\frac{70}{517}$	$-\frac{327}{55}$	0	$r_4$
0	$\frac{17}{11}$	0	0	$\frac{6}{5}$	9	$r_5 \leftarrow \frac{17}{11}r_2 + r_5$



# EXERCISE

## Gaussian Elimination Method

$v_1$	$v_2$	$v_3$	$v_4$	$v_L$		
$-\frac{1}{120}$	$\frac{1}{220}$	0	0	$\frac{1}{100}$	0	$r_1$
0	-1	0	1	1	0	$r_2$
0	0	$-\frac{1}{320}$	$\frac{1}{470}$	$-\frac{1}{100}$	0	$r_3$
0	0	0	$\frac{70}{517}$	$-\frac{327}{55}$	0	$r_4$
0	0	0	$\frac{17}{11}$	$\frac{151}{55}$	9	$r_5$

$$\underline{r_5} \leftarrow \frac{17}{11} r_4 - \frac{70}{517} r_5 \rightarrow$$

## System of Linear Equations

$v_1$	$v_2$	$v_3$	$v_4$	$v_L$		
$-\frac{1}{120}$	$\frac{1}{220}$	0	0	$\frac{1}{100}$	0	$r_1$
0	-1	0	1	1	0	$r_2$
0	0	$-\frac{1}{320}$	$\frac{1}{470}$	$-\frac{1}{100}$	0	$r_3$
0	0	0	$\frac{70}{517}$	$-\frac{327}{55}$	0	$r_4$
0	0	0	0	-9.56	-1.22	$r_5$



# EXERCISE

## Gaussian Elimination Method

from  $r_5$

$$\begin{array}{rcl} -9.56 v_L & = & -1.22 \\ \hline -9.56 & & -9.56 \end{array}$$

$$v_L = 127.62 \text{ mV}$$

ans

## System of Linear Equations

$v_1$	$v_2$	$v_3$	$v_4$	$v_L$		
$-\frac{1}{120}$	$\frac{1}{220}$	0	0	$\frac{1}{100}$	0	$r_1$
0	-1	0	1	1	0	$r_2$
0	0	$-\frac{1}{320}$	$\frac{1}{470}$	$-\frac{1}{100}$	0	$r_3$
0	0	0	$\frac{70}{517}$	$-\frac{327}{55}$	0	$r_4$
0	0	0	0	-9.56	-1.22	$r_5$



# LABORATORY

