

# DESIGN AND SYNTHESIS OF LOGIC CIRCUITS

## COMBINATIONAL LOGIC CIRCUITS

---

*prepared by:*

Gyro A. Madrona

Electronics Engineer

## TOPIC OUTLINE

Synthesis of XOR/XNOR Gate

Synthesis of BCD-to-7-Segment Decoder




# SYNTHESIS OF XOR/XNOR GATE



# EXCLUSIVE-OR GATE


## Logic Symbol

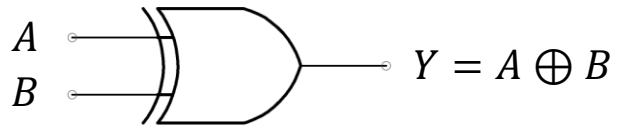

## Truth Table

$A$	$B$	$Y$	Minterm
0	0	0	
0	1	1	$m_1 = \bar{A}B$
1	0	1	$m_2 = A\bar{B}$
1	1	0	

## Equivalent Logic Circuit

 


$$Y = \bar{A}B + A\bar{B}$$



# EXCLUSIVE-NOR GATE


## Logic Symbol

 

## Truth Table

$A$	$B$	$Y$	Minterm
0	0	1	$m_0 = \bar{A}\bar{B}$
0	1	0	
1	0	0	
1	1	1	$m_3 = AB$

## Equivalent Logic Circuit

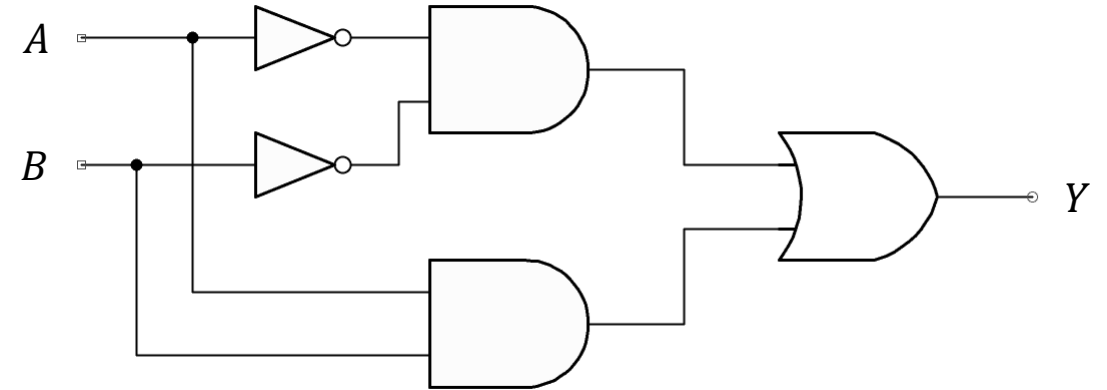

## EXERCISE

---

Develop a logic circuit with four input variables that will only produce a 1 output when exactly three input variables are 1s.

Solution


$ABCD$	Minterm



## EXERCISE


Reduce the combinational logic circuit to a minimum form.

Solution

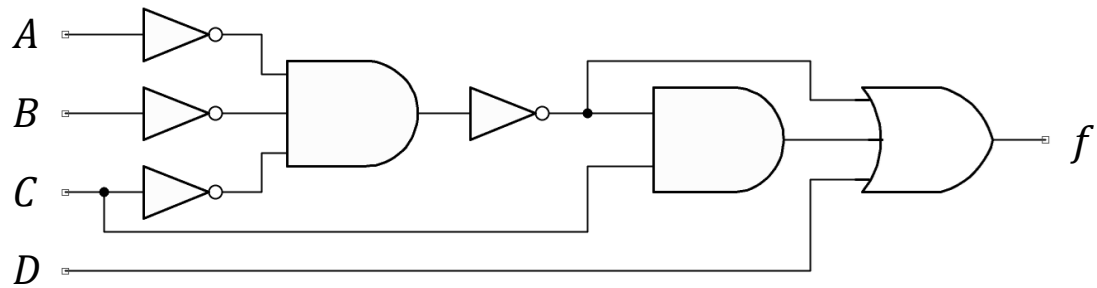
 
## EXERCISE

Reduce the combinational logic circuit to a minimum form.



## Solution

$N$	$ABCD$	$f$
0	0000	
1	0001	
2	0010	
3	0011	
4	0100	
5	0101	
6	0110	
7	0111	
8	1000	

$N$	$ABCD$	$f$
9	1001	
10	1010	
11	1011	
12	1100	
13	1101	
14	1110	
15	1111	





# SYNTHESIS OF BCD-TO- 7-SEGMENT DECODER




# THE 7-SEGMENT DISPLAY

---

A standard 7-segment display consists of seven LEDs (segments) arranged in a rectangular layout to form the number 8. Each segment is labeled from *a* to *g*, and an optional eighth segment (DP) is used for the decimal point.

Segment Arrangement

 


# EXPRESSION FOR SEGMENT A

Truth Table

$N$	$DCBA$	$f_a$
0	0000	
1	0001	
2	0010	
3	0011	
4	0100	
5	0101	
6	0110	
7	0111	
8	1000	

$N$	$DCBA$	$f_a$
9	1001	
10	1010	
11	1011	
12	1100	
13	1101	
14	1110	
15	1111	

Segment Arrangement

 

# EXPRESSION FOR SEGMENT A

Truth Table

$N$	$DCBA$	$f_a$
0	0000	
1	0001	
2	0010	
3	0011	
4	0100	
5	0101	
6	0110	
7	0111	
8	1000	

$N$	$DCBA$	$f_a$
9	1001	
10	1010	
11	1011	
12	1100	
13	1101	
14	1110	
15	1111	

K-Map

$DC \backslash BA$		00	01	11	10
00					
01					
11					
10					



# EXPRESSION FOR SEGMENT A

Truth Table

$N$	$DCBA$	$f_a$
0	0000	
1	0001	
2	0010	
3	0011	
4	0100	
5	0101	
6	0110	
7	0111	
8	1000	

$N$	$DCBA$	$f_a$
9	1001	
10	1010	
11	1011	
12	1100	
13	1101	
14	1110	
15	1111	

QM Method

Group	$DCBA$	Minterm	1 <sup>st</sup> Level



# EXPRESSION FOR SEGMENT A

Prime Implicants Chart

Prime Implicants	$m_0$	$m_2$	$m_3$	$m_5$	$m_7$	$m_8$	$m_9$

QM Method

Group	2 <sup>nd</sup> Level	3 <sup>rd</sup> Level




## EXERCISE

---

Using Karnaugh Map and the Quine-McCluskey method, synthesize the minimized Boolean expressions for each segment (a–g) of a 7-segment display decoder.

Segment Arrangement

 

# LABORATORY

