



THEVENIN'S THEOREM

BASIC CIRCUIT ANALYSIS METHOD

prepared by:

Gyro A. Madrona
Electronics Engineer

TOPIC OUTLINE

Thevenin's Theorem




THEVENIN'S THEOREM



THEVENIN'S THEOREM


Thevenin's theorem states that it is possible to simplify any linear circuit, irrespective of how complex it is, to an equivalent circuit with a single voltage source (v_{TH}) and a series resistance (R_{TH}).

Arbitrary Network

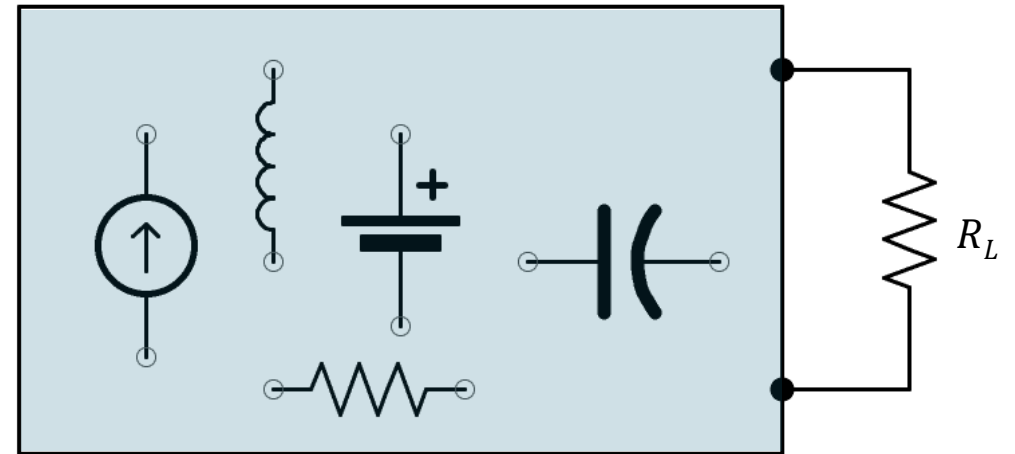


THEVENIN'S THEOREM

Thevenin's Equivalent Circuit

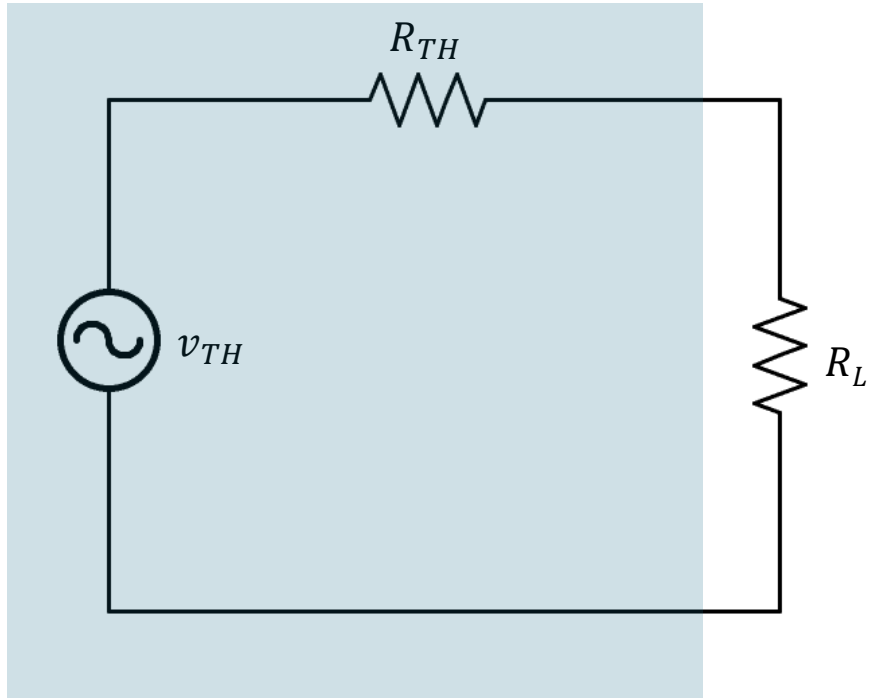


Arbitrary Network

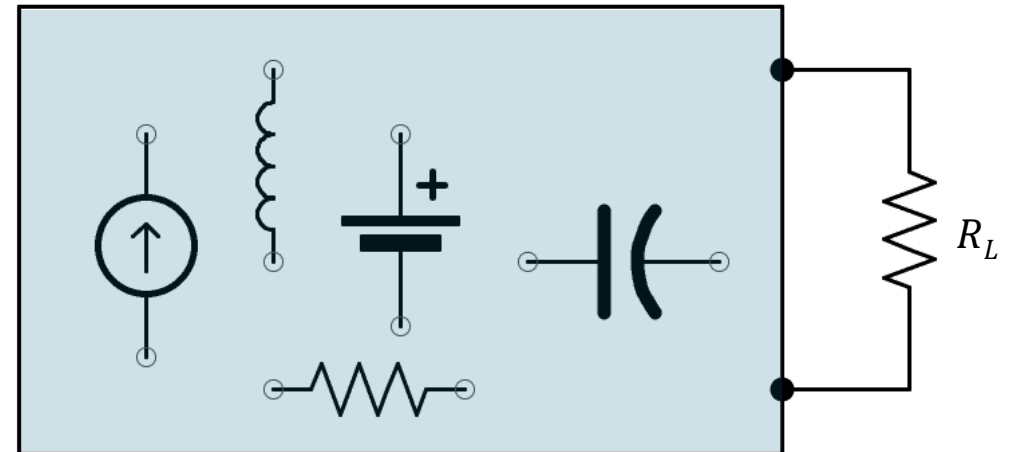


STEPS TO APPLY THEVENIN'S THEOREM

1. Identify the load.

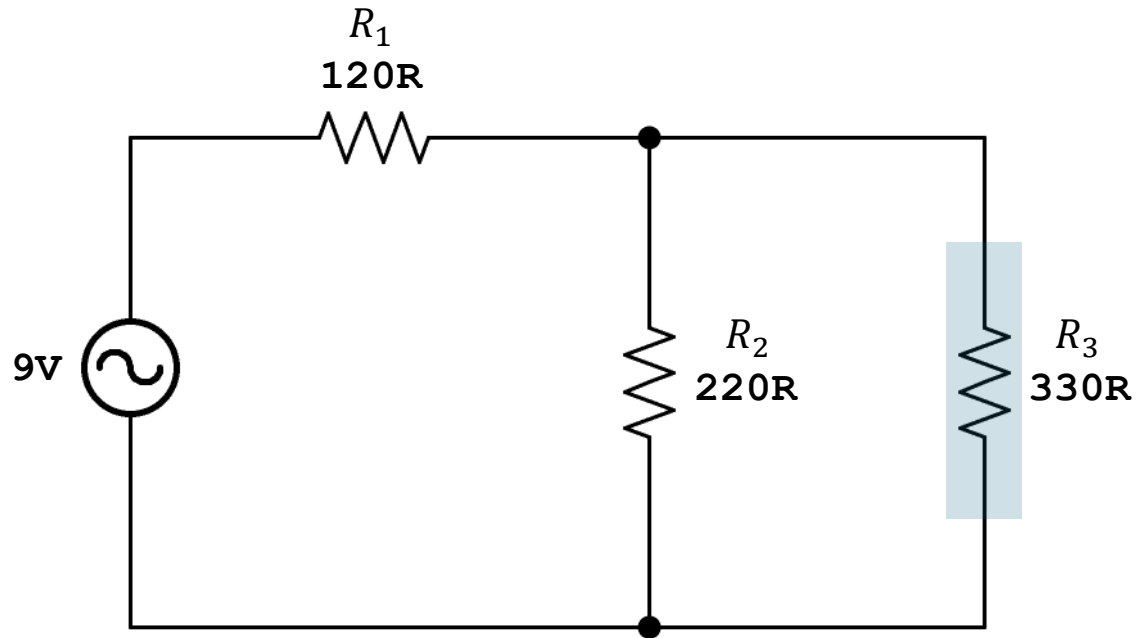


STEPS TO APPLY THEVENIN'S THEOREM

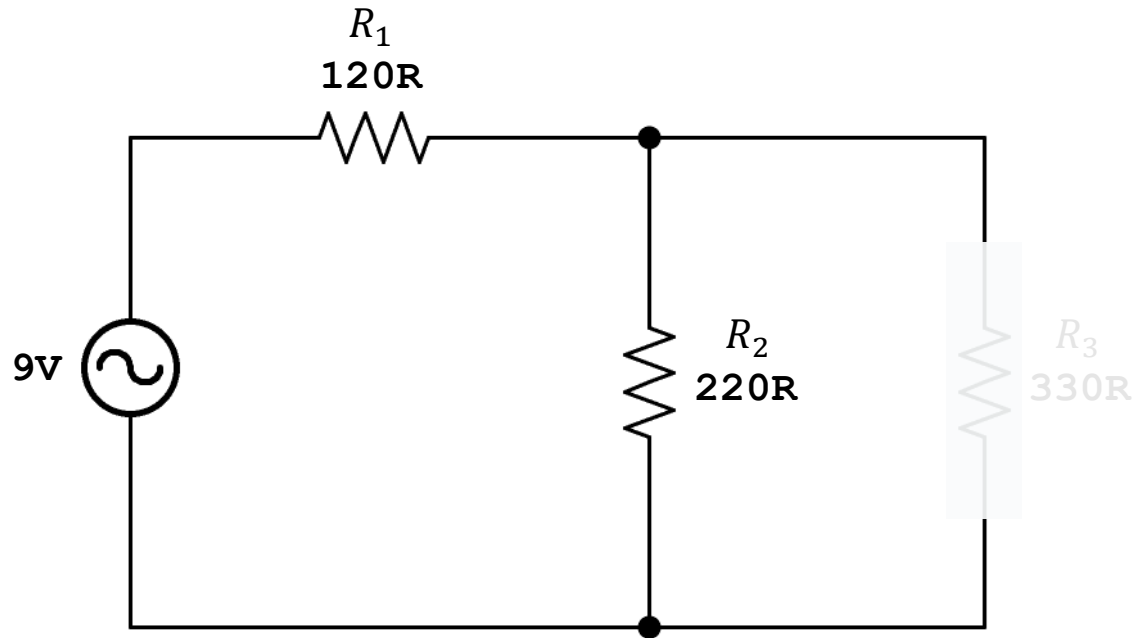

1. Identify the load.
2. Remove the load.




STEPS TO APPLY THEVENIN'S THEOREM

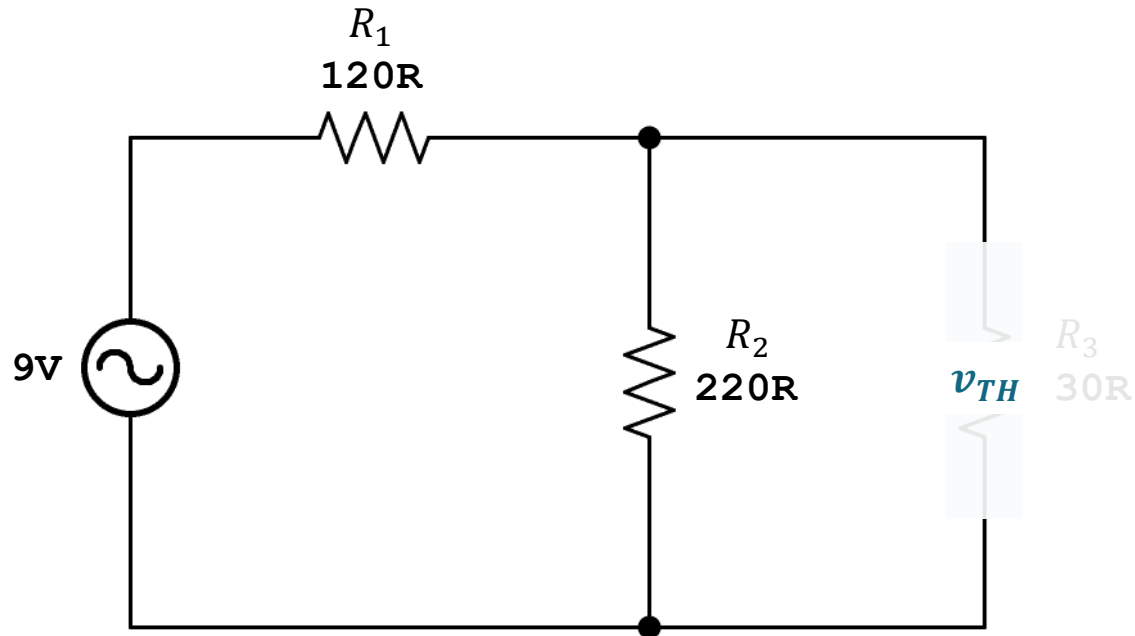

1. Identify the load.
2. Remove the load.
3. Determine the Thevenin voltage (v_{th}):
Calculate the open-circuit voltage across the terminals where the load was connected.



STEPS TO APPLY THEVENIN'S THEOREM

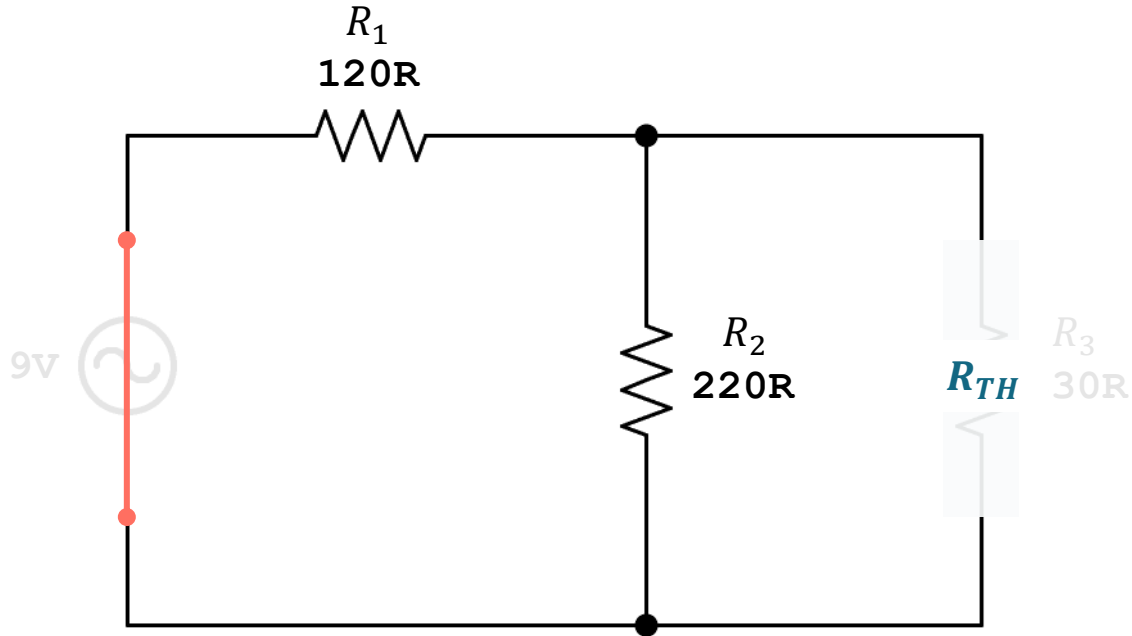


1. Identify the load.
2. Remove the load.
3. Determine the Thevenin voltage (v_{th}):
Calculate the open-circuit voltage across the terminals where the load was connected.
4. Determine the Thevenin Resistance (R_{TH}):
Set all independent sources to zero and calculate the equivalent resistance looking into the terminals where the load was connected.



STEPS TO APPLY THEVENIN'S THEOREM

Thevenin Equivalent Circuit

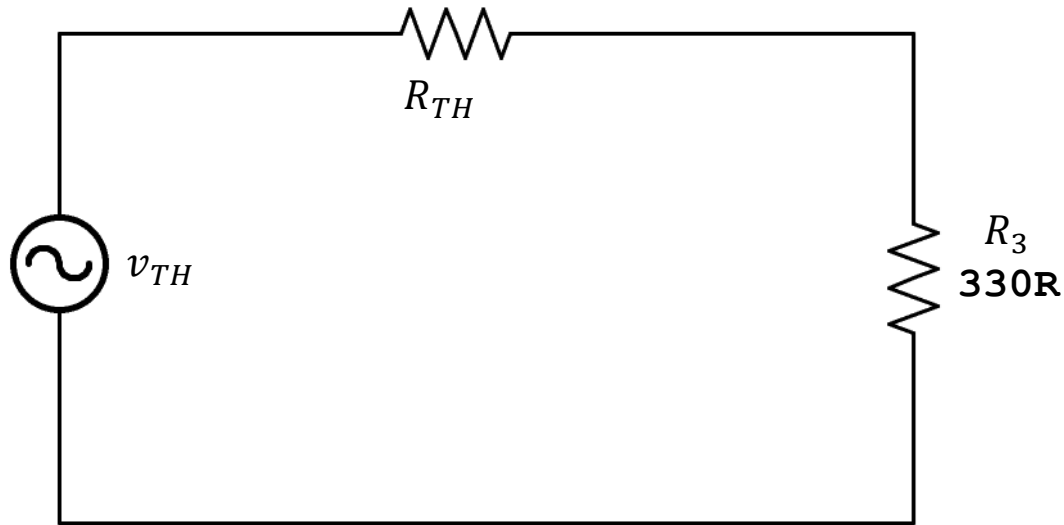


1. Identify the load.
2. Remove the load.
3. Determine the Thevenin voltage (v_{th}):
Calculate the open-circuit voltage across the terminals where the load was connected.
4. Determine the Thevenin Resistance (R_{TH}):
Set all independent sources to zero and calculate the equivalent resistance looking into the terminals where the load was connected.
5. Replace the original circuit with Thevenin equivalent and reconnect the load.



EXERCISE

Use the 2nd approximation diode to calculate the load voltage and load current of the given network.

Solution

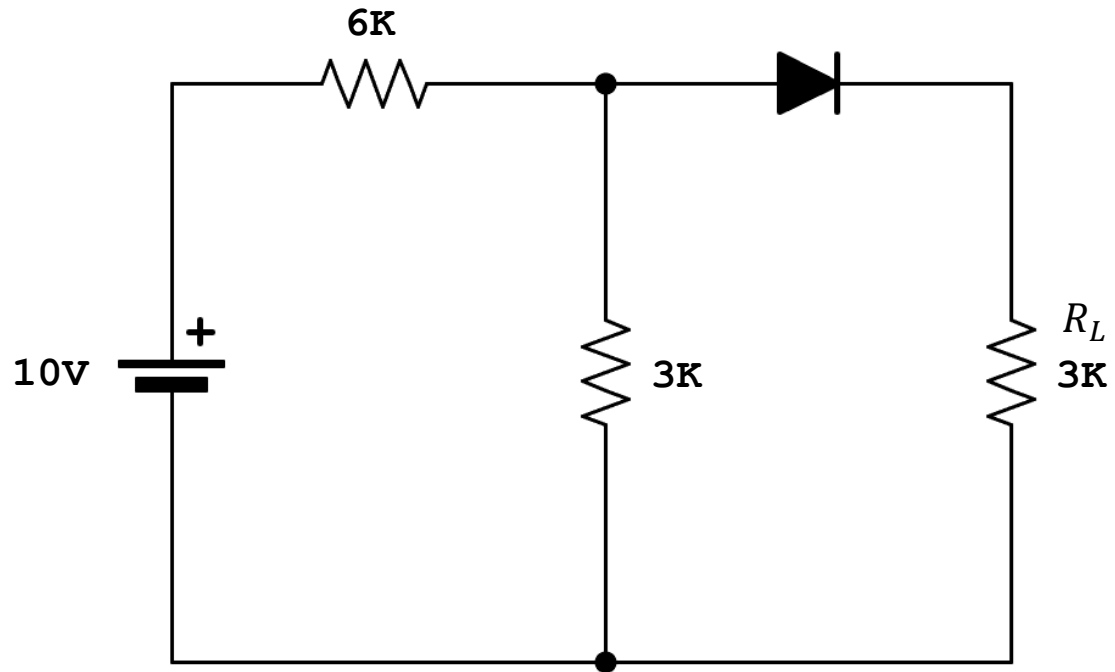

LABORATORY

