



SUBTRACTOR CIRCUIT

COMBINATIONAL LOGIC CIRCUITS

prepared by:

Gyro A. Madrona
Electronics Engineer

TOPIC OUTLINE

Signed-Magnitude Form

1's Complement Form

2's Complement Form



SUBTRACTOR CIRCUIT



SIGNED-MAGNITUDE

0101 (+5)

1101 (-5)

sign

0 - positive

1 - negative

Binary Addition

$$\begin{array}{r} + \quad 1101 \quad (-5) \\ \quad 0010 \quad (+2) \\ \hline \end{array}$$



$$\begin{array}{r} - \quad 101 \quad (5) \\ \quad 010 \quad (2) \\ \hline 1011 \quad (-3) \end{array}$$

$$\begin{array}{r} + \quad 0101 \quad (+5) \\ \quad 1010 \quad (-2) \\ \hline \end{array}$$



$$\begin{array}{r} - \quad 101 \quad (5) \\ \quad 010 \quad (2) \\ \hline 0011 \quad (+3) \end{array}$$

Drawback

To subtract the smaller number from the larger one, logic circuits for **comparison** and **subtraction** are needed.



1's COMPLEMENT

To obtain the 1's complement of a negative binary number, invert each bit – changing all 1s to 0s and all 0s to 1s.

Formula

$$K = (2^n - 1) - P$$

where:

K = negative number

P = positive number

$$K = (2^4 - 1) - 5$$

4-bit ←
+5 ←

$$K = (16 - 1) - 5$$

$$K = 10$$

← Decimal
1010 ← binary of -5

Binary Addition

$$\begin{array}{r} 1010 \quad (-5) \\ + 0010 \quad (+2) \\ \hline 1100 \quad (-3) \\ 0011 \quad (1's) \end{array}$$

$$\begin{array}{r} 0101 \quad (+5) \\ + 1101 \quad (-2) \\ \hline 10010 \\ \text{adjustment} \quad \swarrow \text{1} \\ \hline 0011 \quad (+3) \end{array}$$

Drawback

In some cases, a correction is needed which amounts to an extra addition that must be performed.

1's COMPLEMENT

Equivalent Logic Circuit

To obtain the 1's complement of a negative binary number, invert each bit – changing all 1s to 0s and all 0s to 1s.


Formula

$$K = (2^n - 1) - P$$

where:

K = negative number

P = positive number

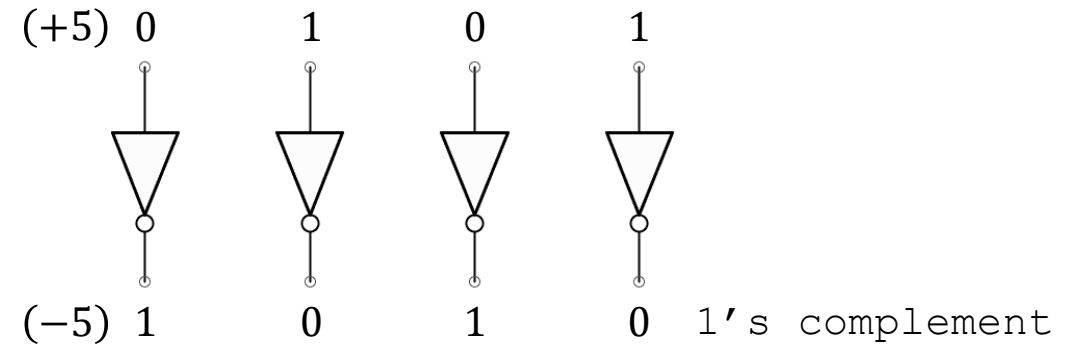

2's COMPLEMENT

To obtain the 2's complement of a negative number, first find its 1's complement (invert all bits), then add 1 to the result.

Formula

$$K = 2^n - P$$

where:

K = negative number

P = positive number

Handwritten notes for $K = 11$:

- $K = 2^4 - 5$ (4-bit, +5)
- $K = 11$ (Decimal)
- 1011 (Binary of -5)

Binary Addition

$$\begin{array}{r} 1011 \quad (-5) \\ + 0010 \quad (+2) \\ \hline 1101 \quad (-3) \\ 0011 \quad (2's) \end{array}$$

$$\begin{array}{r} 0101 \quad (+5) \\ + 1110 \quad (-2) \\ \hline 10011 \quad (+3) \end{array}$$

ignore (pointing to the red 1)

Range

Handwritten notes for Range:

- -2^{n-1} to $2^{n-1} - 1$ (4-bit)
- $\rightarrow -2^{4-1}$ to $2^{4-1} - 1$
- $\rightarrow -8$ to 7

The addition process is the same, regardless of the signs of the operands.

2's COMPLEMENT

To obtain the 2's complement of a negative number, first find its 1's complement (invert all bits), then add 1 to the result.

Formula


$$K = 2^n - P$$

where:

K = negative number

P = positive number

Equivalent Logic Circuit

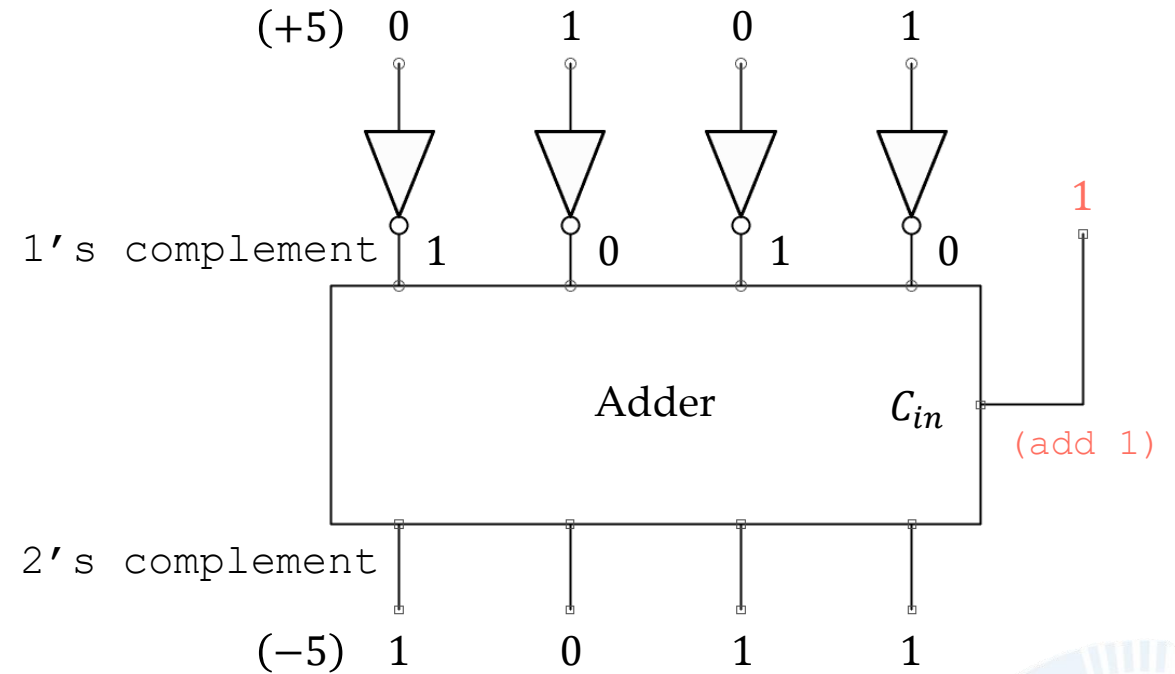

EXERCISE

Create a block-level representation of a 2-bit binary subtractor using 2's complements method.

$$\text{Range} = -2^{n-1} \text{ to } 2^{n-1} - 1$$

$$\text{Range} = -2^{(2-1)} \text{ to } 2^{(2-1)} - 1$$

$$\text{Range} = -2 \text{ to } 1$$

2-bit Signed Integers

$$1 \rightarrow 01$$

$$0 \rightarrow 00$$

$$-1 \rightarrow 11$$

$$-2 \rightarrow 10$$

Solution

$$\begin{array}{r} 2 \\ -1 \\ \hline \end{array} \rightarrow + \begin{array}{r} 2 \\ (-1) \\ \hline 1 \end{array}$$

$$\begin{array}{r} 10 \\ -01 \\ \hline \end{array} \rightarrow + \begin{array}{r} 10 \\ 10 \\ +1 \\ \hline 101 \end{array}$$


overflow

$$\begin{array}{r} C_1 \quad C_0 \\ \downarrow \quad \downarrow \\ A_1 \quad A_0 \\ + \quad \overline{B_1} \quad \overline{B_0} \\ + 1 \\ \hline b_2 \quad b_1 \quad b_0 \end{array}$$

1's
2's

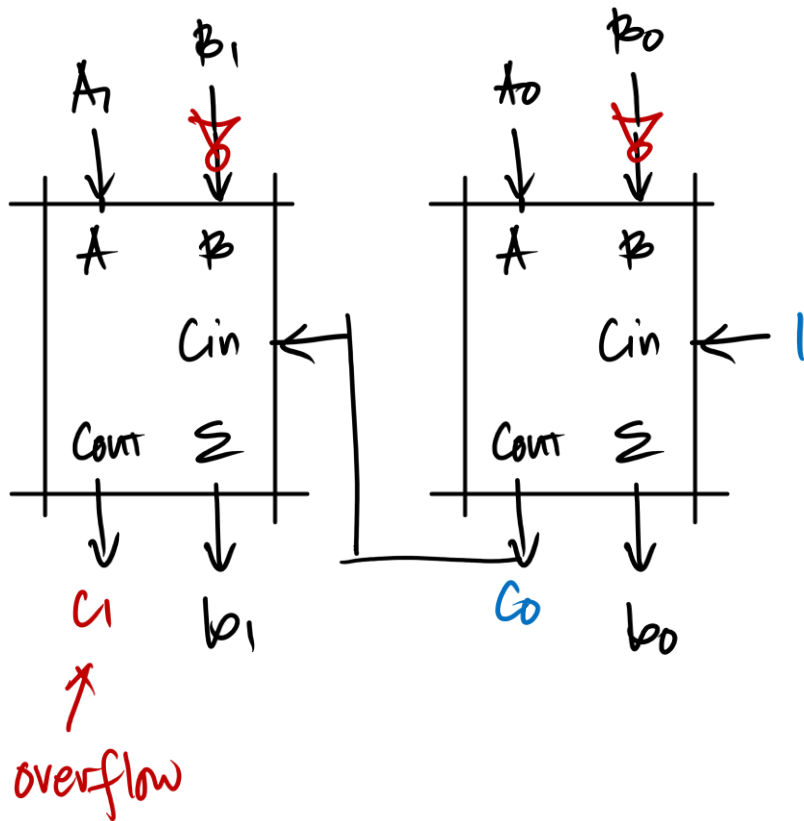EXERCISE

Create a block-level representation of a 2-bit binary subtractor using 2's complements method.



Solution

$$\begin{array}{r} 2 \\ - 1 \\ \hline \end{array} \rightarrow + \begin{array}{r} 2 \\ (-1) \\ \hline 1 \end{array}$$

$$\begin{array}{r} 10 \\ - 01 \\ \hline \end{array} \rightarrow + \begin{array}{r} 10 \\ 10 \\ + 1 \\ \hline 101 \end{array}$$

overflow

$$\begin{array}{r} C_1 \quad C_0 \\ \downarrow \quad \downarrow \\ + \quad A_1 \quad A_0 \\ \quad \bar{B}_1 \quad \bar{B}_0 \\ \quad \quad + 1 \\ \hline b_2 \quad b_1 \quad b_0 \end{array}$$

1's
2's

EXERCISE

Synthesize and implement a 2-bit parallel binary subtractor using 2's complement method.

note

The use of XOR or XNOR gates is not allowed.

Solution



LABORATORY

