



D-MOSFET

MOSFET DC BIASING

prepared by:

Gyro A. Madrona
Electronics Engineer

TOPIC OUTLINE

D-MOSFET Construction

Regions of Operation

D-MOSFET DC Biasing




D-MOSFET CONSTRUCTION




CONSTRUCTION

D-MOSFET

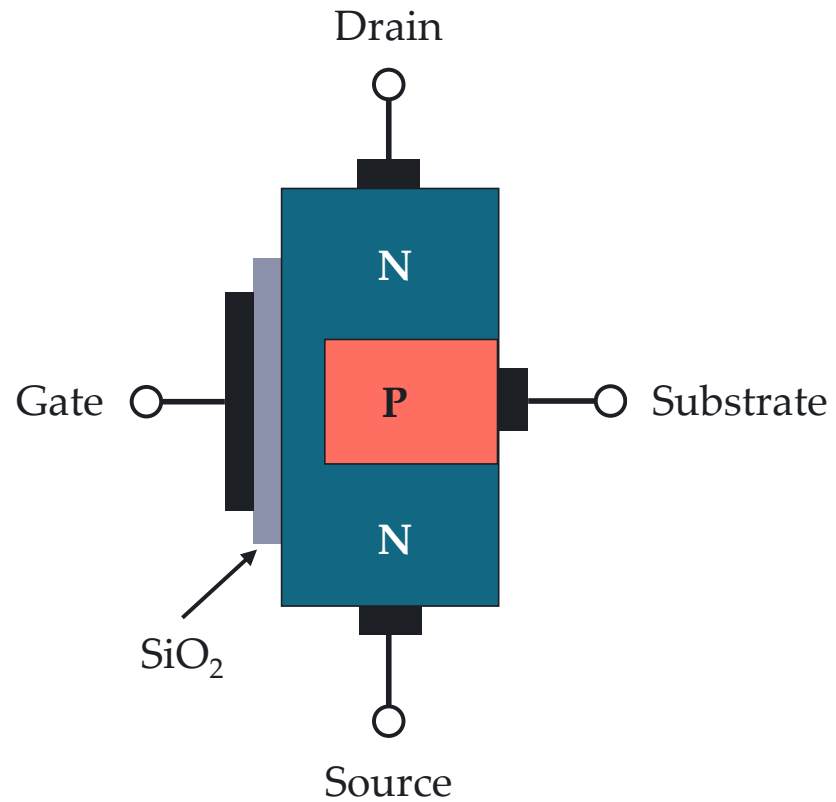Depletion Mode Metal-Oxide Semiconductor Field-Effect Transistor



N-Channel

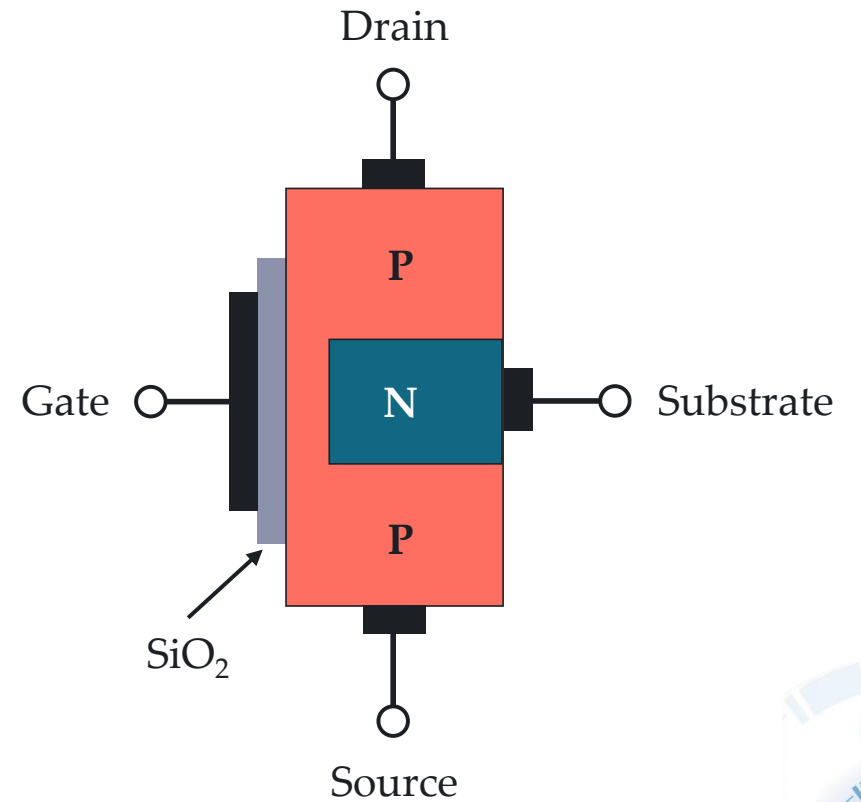


P-Channel


SCHEMATIC SYMBOL

D-MOSFET

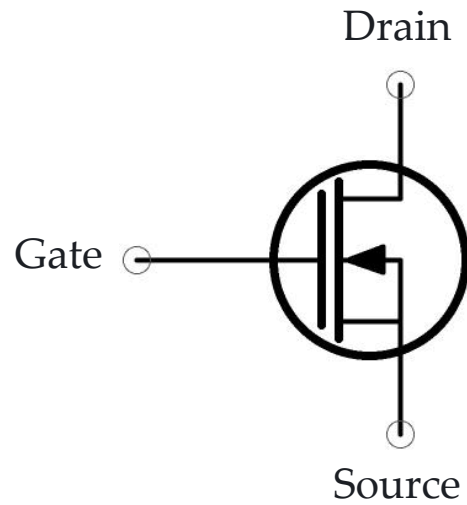Depletion Mode Metal-Oxide Semiconductor Field-Effect Transistor



N-Channel

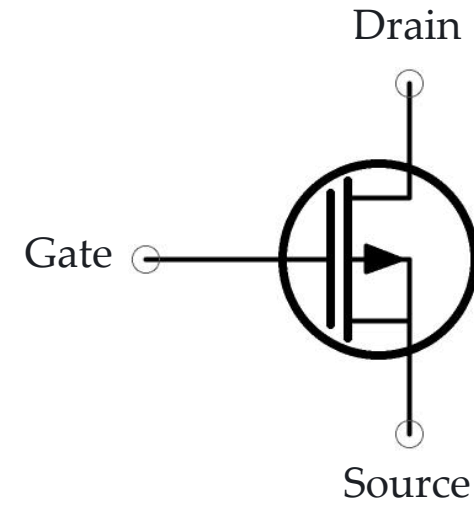


P-Channel



REGIONS OF OPERATION



DRAIN CURVE

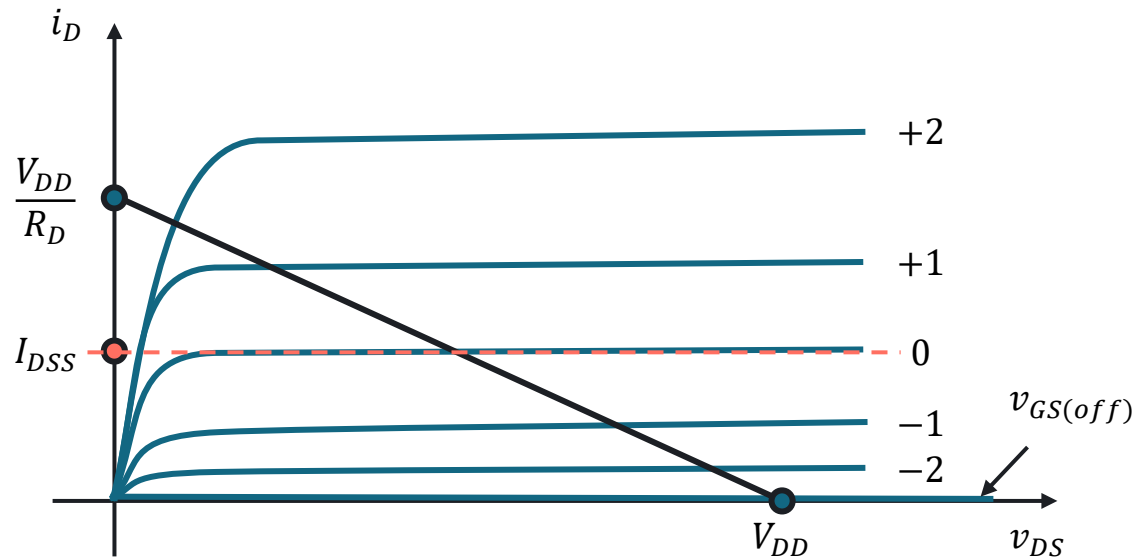


As with a JFET, when $v_{GS} = 0$ V, the drain current will equal I_{DSS} .

This demonstrates that the D-MOSFET is a **normally on** device



TRANSCONDUCTANCE CURVE

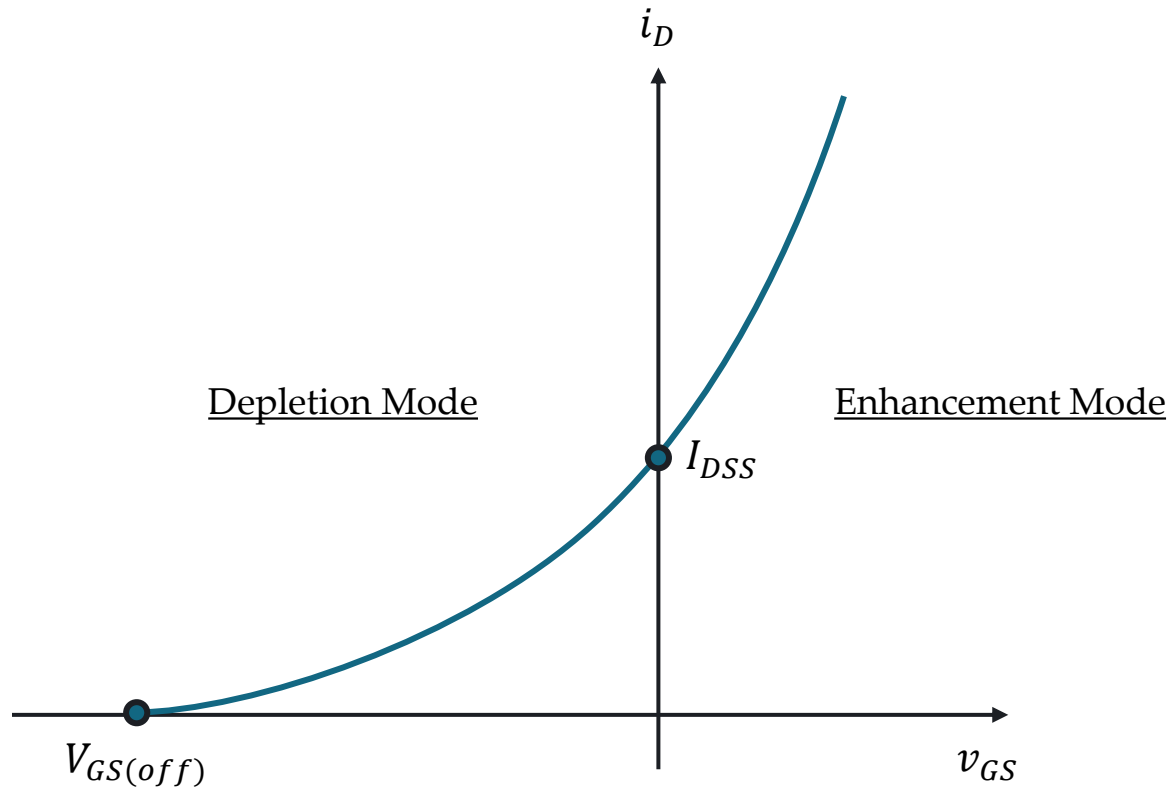

The primary difference between JFET and D-MOSFET is that D-MOSFETs permit operating points with positive values of v_{GS} and levels of i_D that exceeds i_{DSS} .

Shockley's Equation


$$i_D = I_{DSS} \left(1 - \frac{v_{GS}}{V_{GS(off)}} \right)^2$$



D-MOSFET DC BIASING



EXERCISE

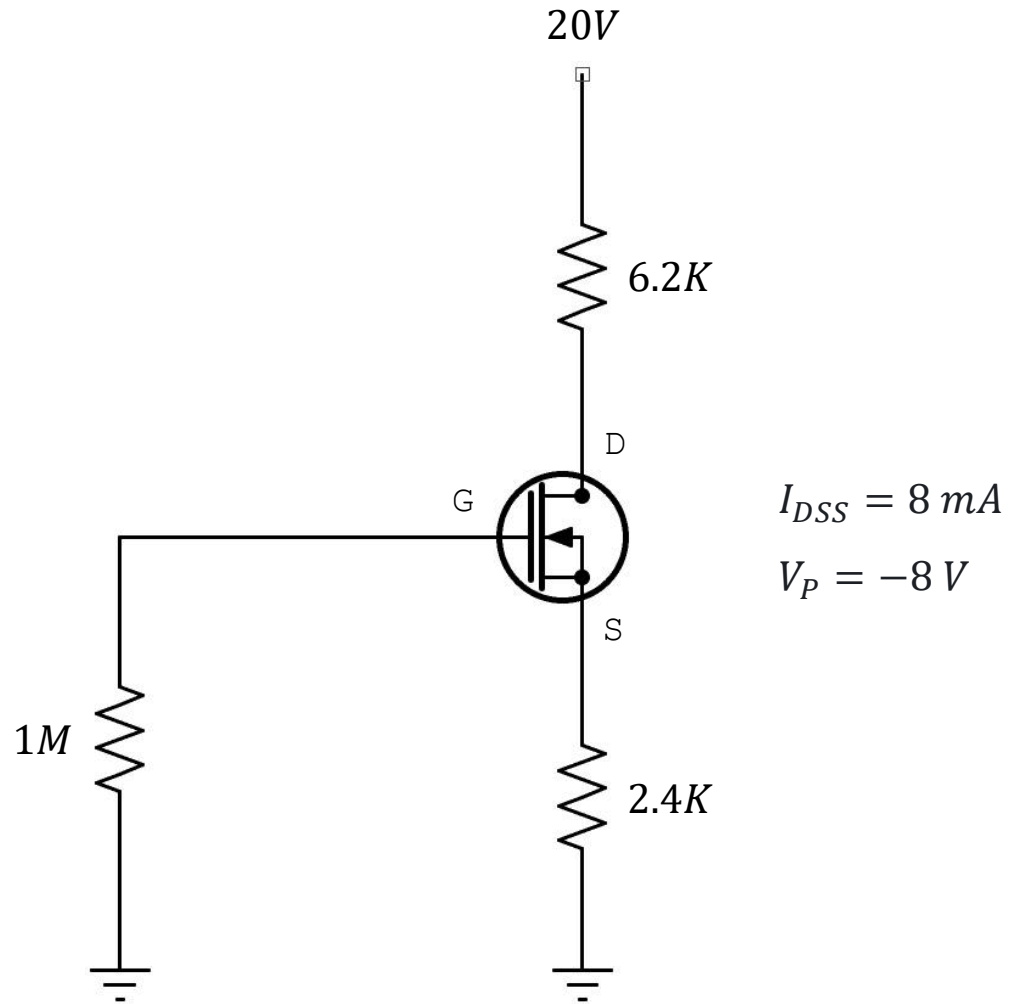


For the given network, determine the following:

- Gate-source voltage (v_{GSQ})
- Drain current (i_{DQ})
- Drain voltage (v_D)


and sketch the transconductance curve.



TRANSCONDUCTANCE CURVE

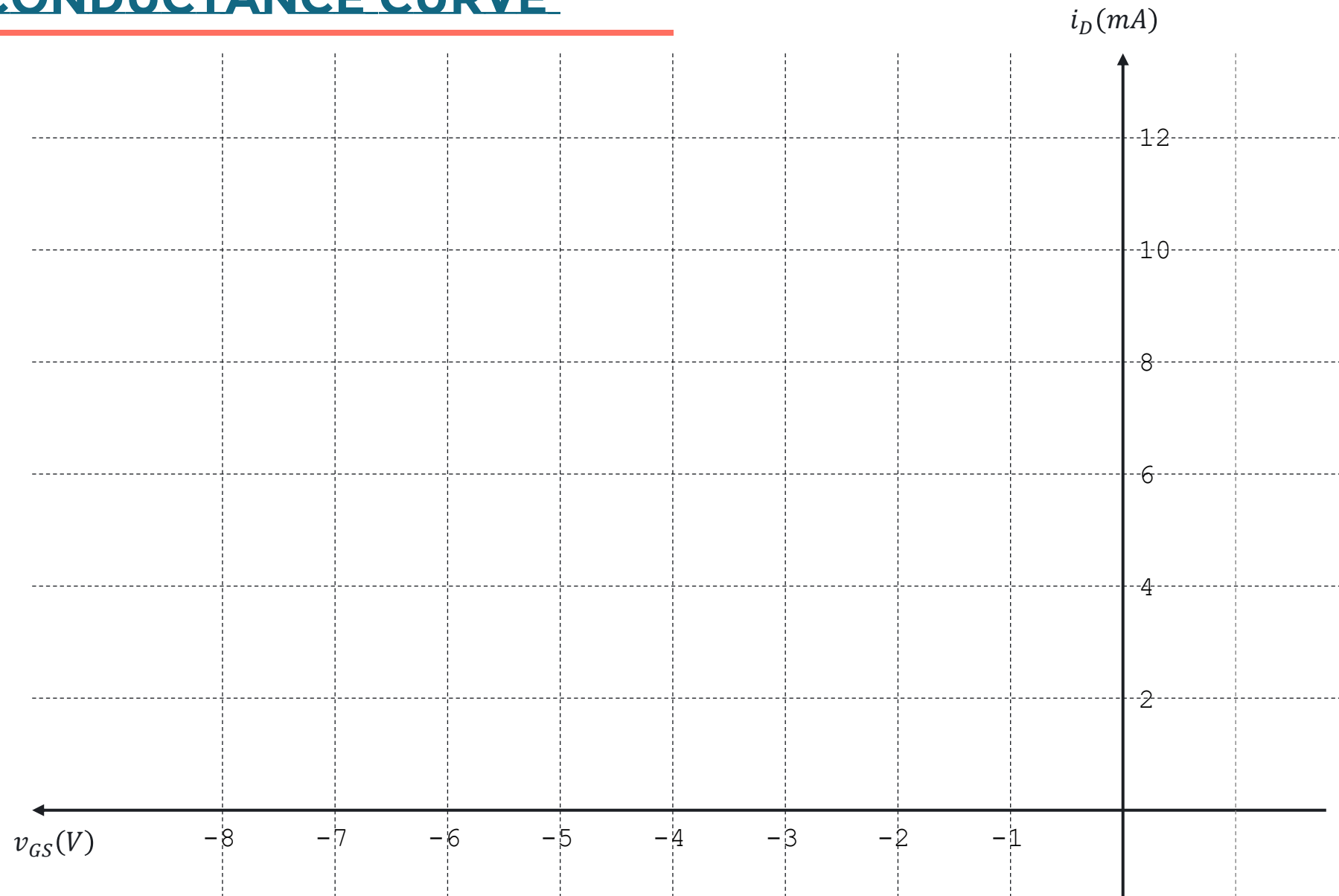

EXERCISE

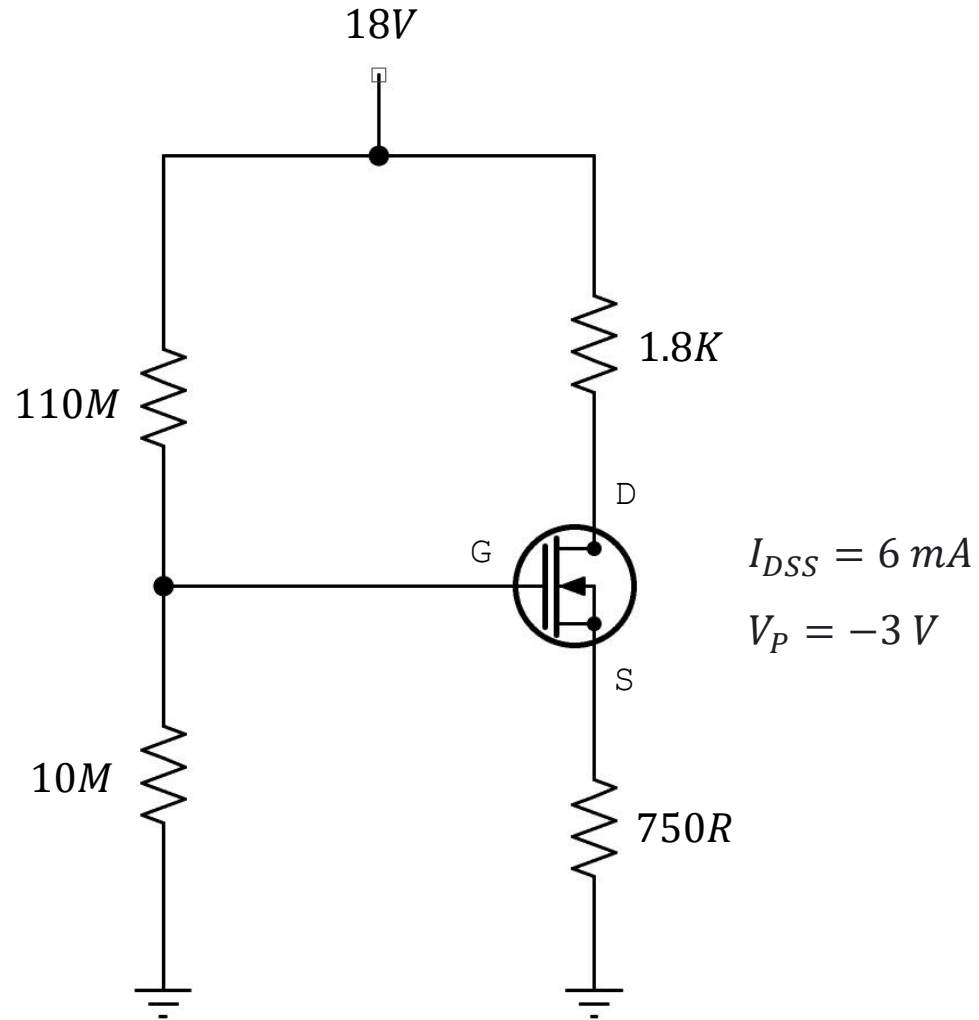


For the given network, determine the following:

- Gate-source voltage (v_{GSQ})
- Drain current (i_{DQ})
- Drain voltage (v_D)

and sketch the transconductance curve.



TRANSCONDUCTANCE CURVE

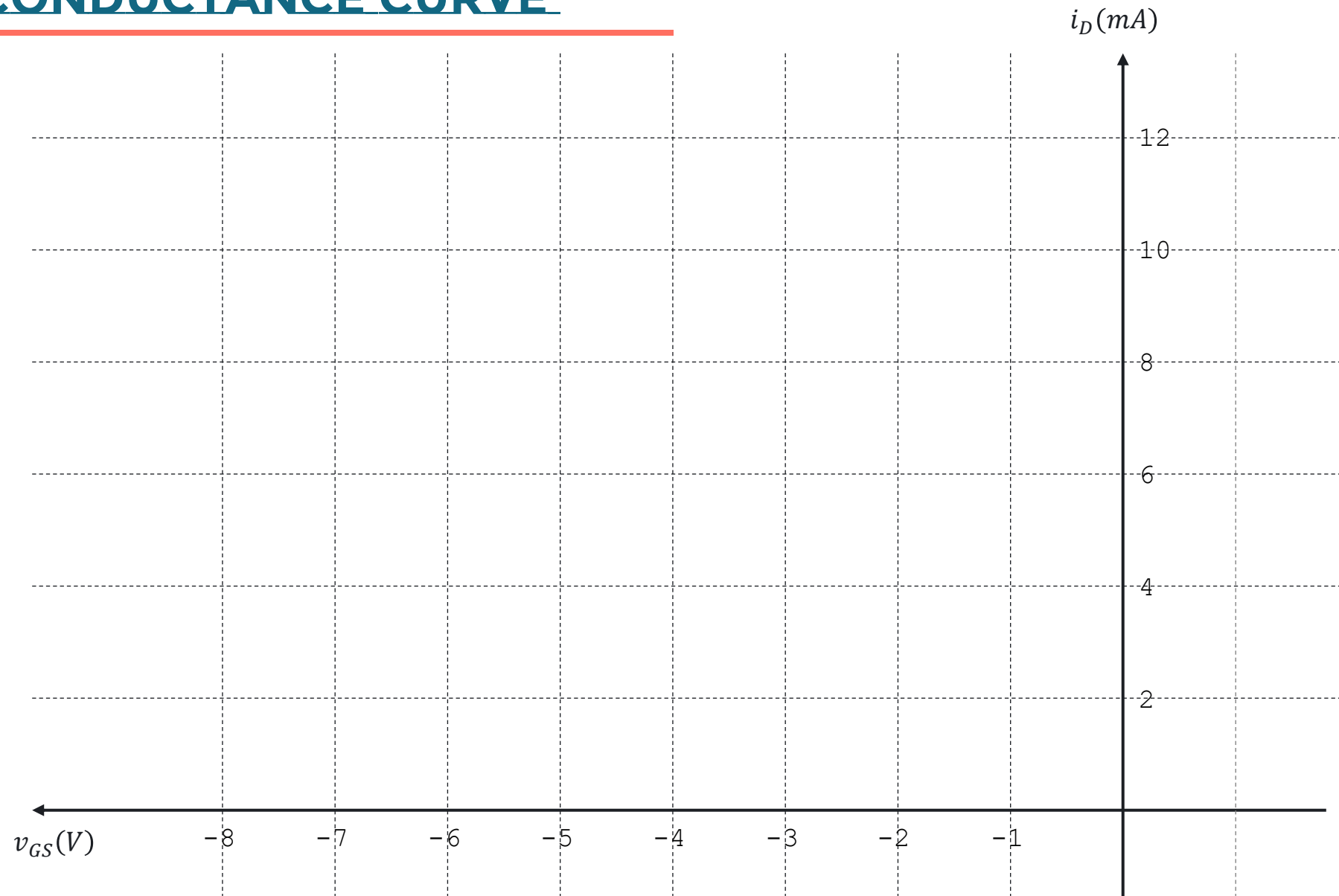

LABORATORY

