



FILTER CAPACITOR

POWER SUPPLY BUILDING BLOCKS

prepared by:

Gyro A. Madrona
Electronics Engineer

TOPIC OUTLINE

Filter Capacitor

Smoothing Pulsating DC




FILTER CAPACITOR




FILTER CAPACITOR

A filter capacitor charges up when the voltage rises and discharges when the voltage drops, filling in the gaps of the pulsating DC waveform. This results in a smoother DC output.


Power Supply Block Diagram

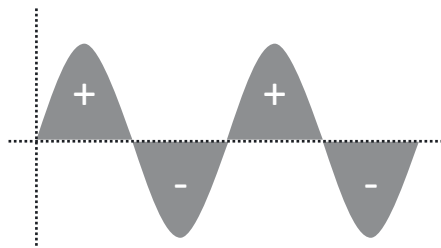

AC signal

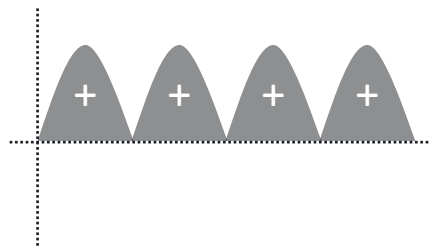

Pulsating DC

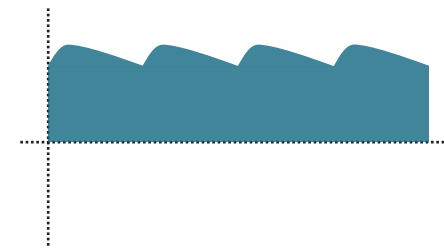

DC
with AC ripple



SMOOTHING PULSATING DC



SMOOTHING HALF-WAVE

Discharging equation

$$v_c(t) = v_o e^{-\frac{t}{\tau}}$$

where: $\tau = RC$


Let $\tau = 10\Delta t$

$$v_c(\Delta t) = v_o e^{-\frac{\Delta t}{10\Delta t}}$$

$$v_c(\Delta t) = 0.905v_o$$


For half-wave, if the discharge time constant for the capacitor is 10 times the pulse duration, the average DC output level is approximately **90% of v_p** .

DC with AC Ripple

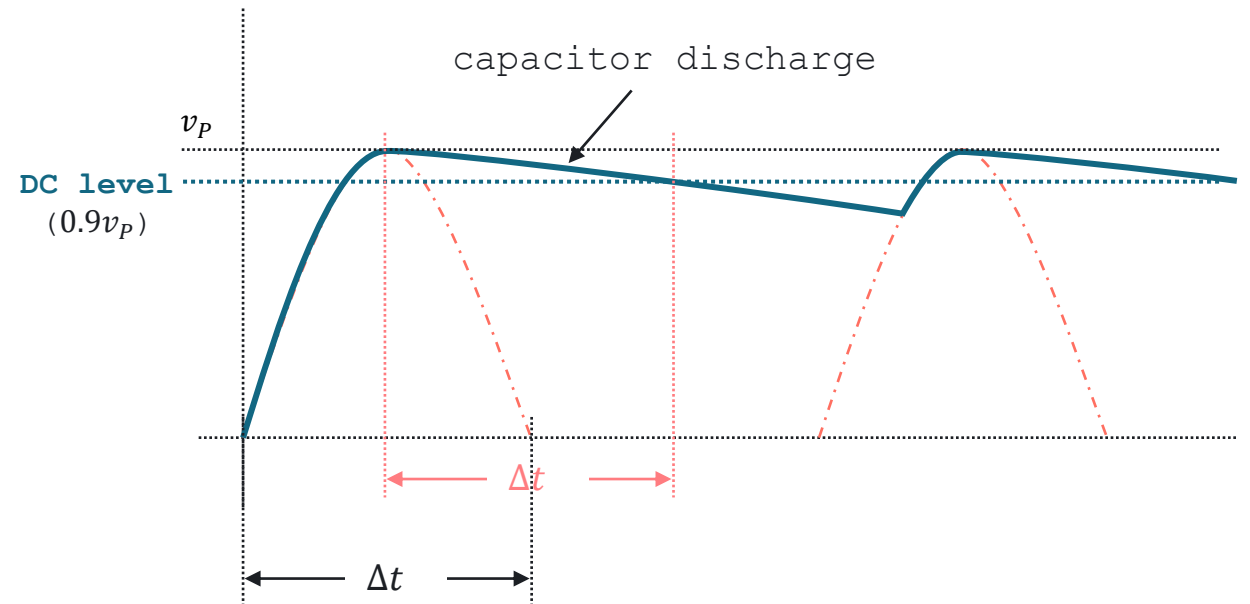

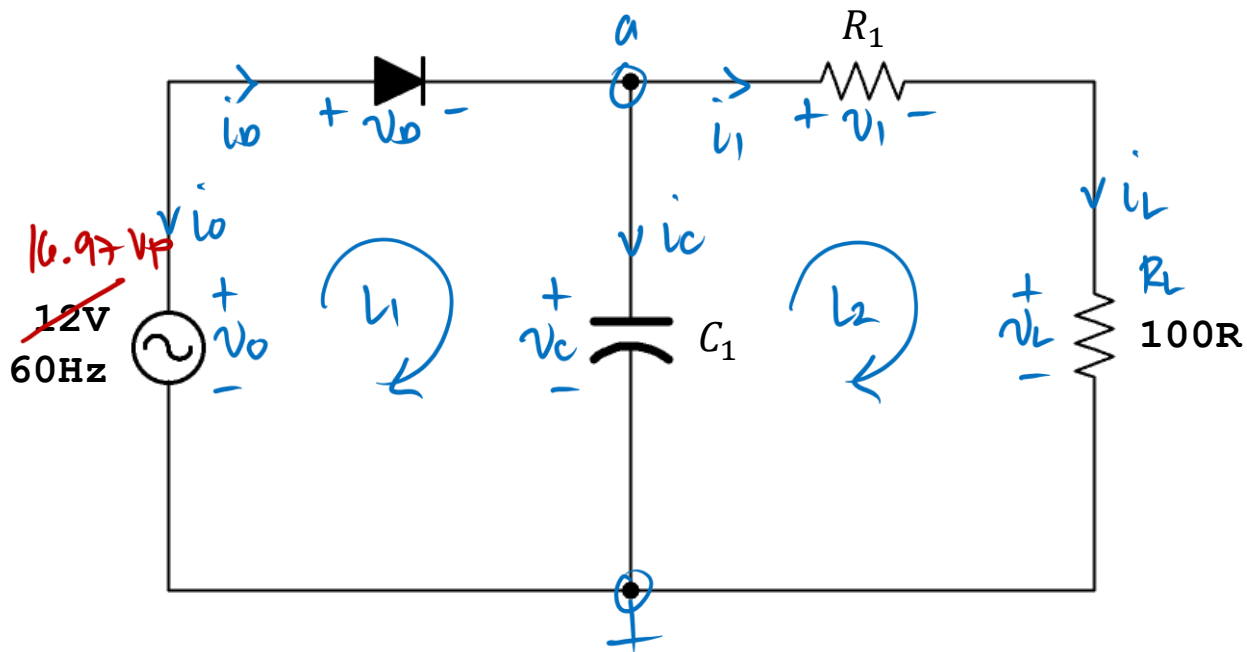EXERCISE

The AC input to the given rectifier circuit is a $12V_{RMS}$, 60Hz sine wave. For this circuit, you need $9V$ DC v_L across the 100Ω load resistor. Determine the value of R_1 and C_1 .



Solution

Peak voltage @ a

$$V_{RMS} = \frac{V_p}{\sqrt{2}}$$


$$V_p = V_{RMS} \sqrt{2}$$

$$V_0 = 12\sqrt{2}$$

$$\underline{V_0 = 16.97 V_p}$$

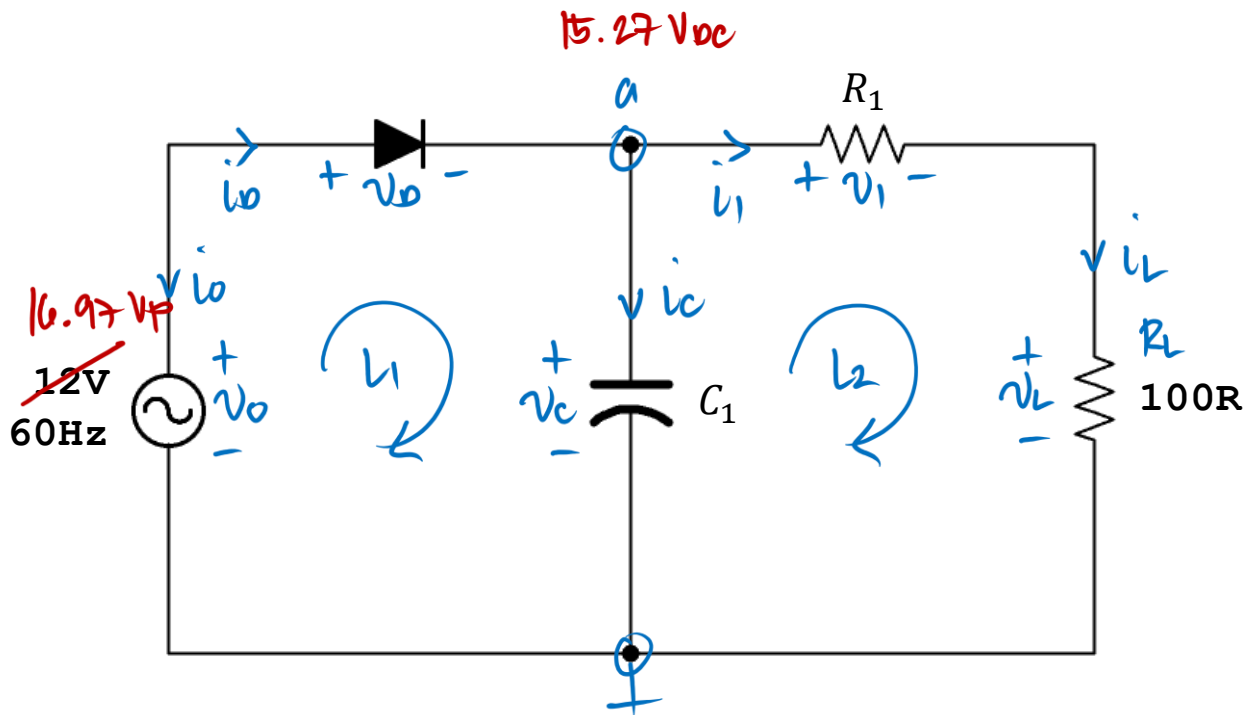EXERCISE

The AC input to the given rectifier circuit is a $12V_{RMS}$, 60Hz sine wave. For this circuit, you need $9V_{DC}$ across the 100Ω load resistor. Determine the value of R_1 and C_1 .



Solution

DC Level @ a

Let $\tau = 10 \text{ } \mu\text{s}$, then


$$V_{DC} = 0.9 V_P$$

$$V_a(DC) = 0.9 (16.97)$$

$$\underline{V_a(DC) = 15.27 \text{ V}}$$

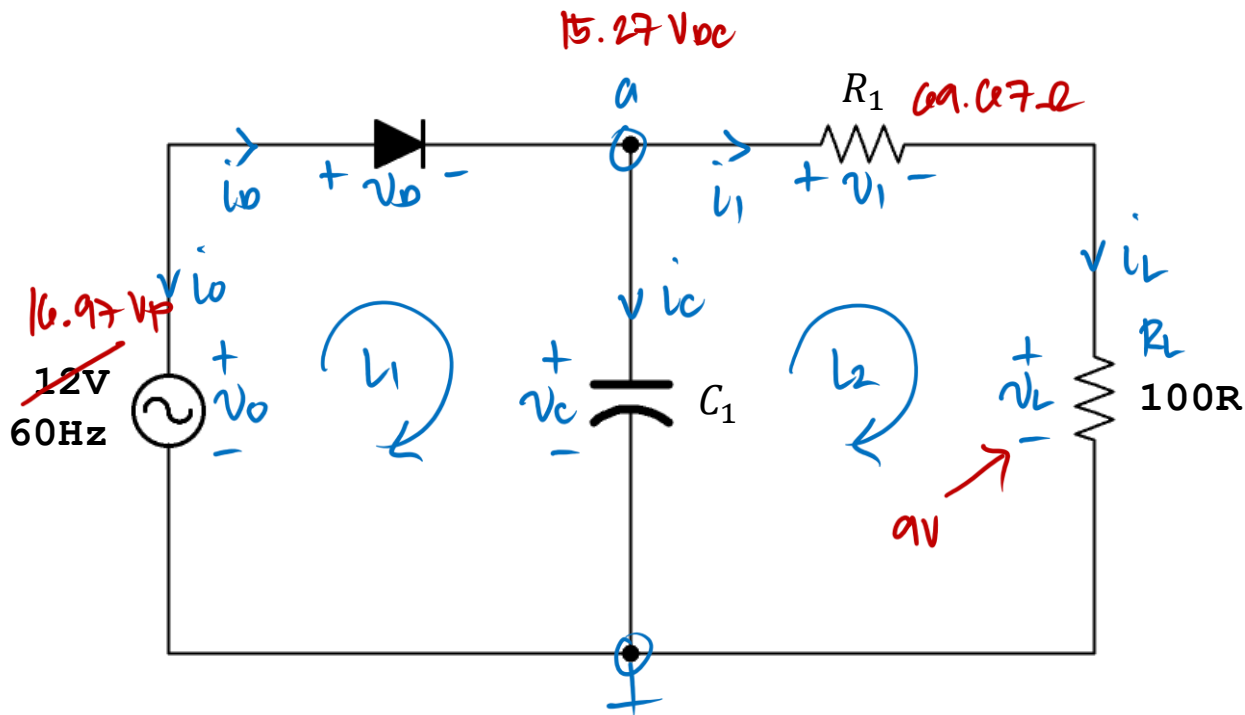EXERCISE

The AC input to the given rectifier circuit is a $12V_{RMS}$, 60Hz sine wave. For this circuit, you need $9V$ DC v_L across the 100Ω load resistor. Determine the value of R_1 and C_1 .



Solution

by VDT

$$v_L = v_a \frac{R_L}{R_1 + R_L}$$

$$R_1 + R_L = \frac{v_a R_L}{v_L}$$

$$R_1 = \frac{v_a R_L}{v_L} - R_L$$


$$R_1 = \frac{15.27(100)}{9} - 100$$

$$R_1 = 69.67\Omega$$

ans

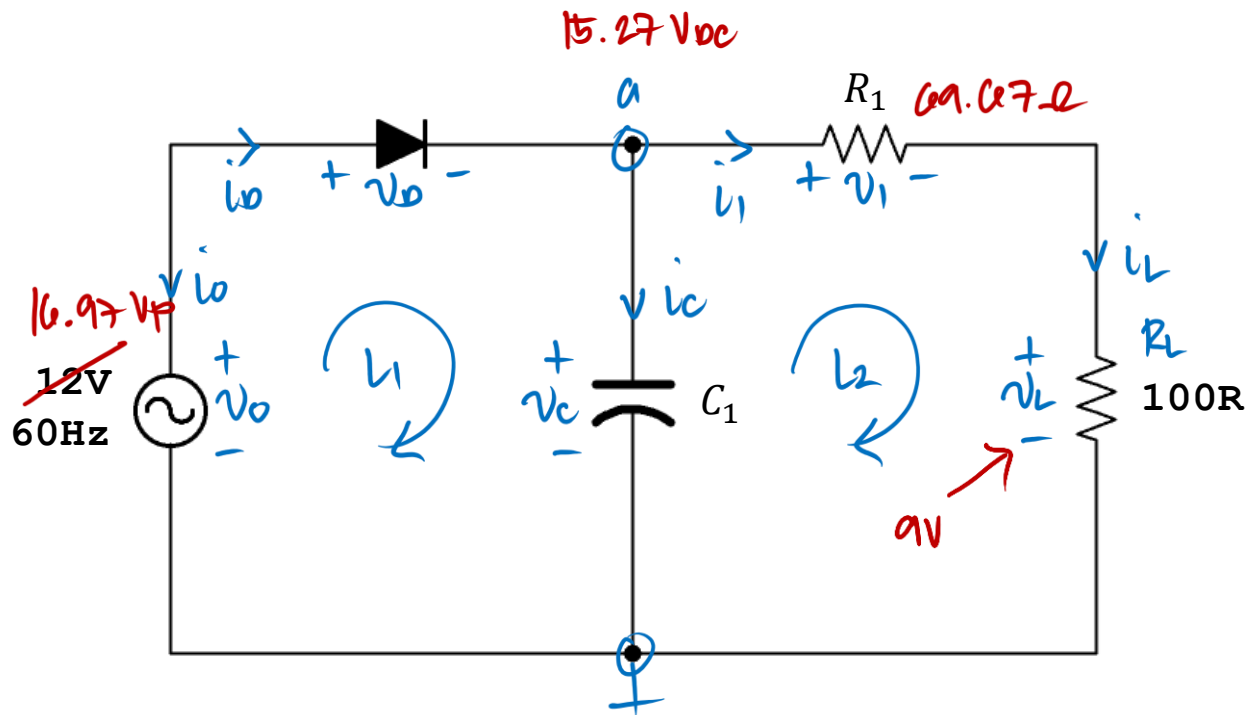
EXERCISE

The AC input to the given rectifier circuit is a $12V_{RMS}$, 60Hz sine wave. For this circuit, you need $9V$ DC across the 100Ω load resistor. Determine the value of R_1 and C_1 .



Solution

Pulse Duration

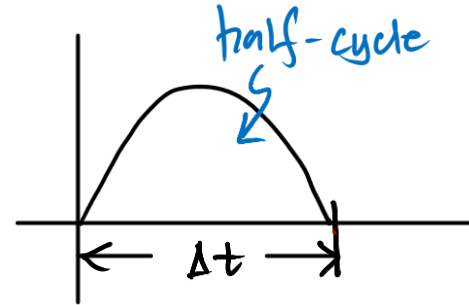

$$\Delta t = \frac{1}{2} \cdot \frac{1}{f}$$

$$\Delta t = \frac{1}{2(60)}$$

$$\Delta t = 8.33 \text{ ms}$$

$$\text{for } \tau = 10 \Delta t$$

$$\tau = RC$$

$$C_1 = \frac{10 \Delta t}{R_1 + R_L}$$

$$C_1 = \frac{10(8.33 \text{ ms})}{69.67 + 100}$$

$$C_1 = 498.95 \mu F$$

avg

SMOOTHING FULL-WAVE

Discharging equation

$$v_c(t) = v_o e^{-\frac{t}{\tau}}$$

where: $\tau = RC$


Let $\tau = 10\Delta t$

$$v_c(\Delta t/2) = v_o e^{-\frac{\Delta t/2}{10\Delta t}}$$

$$v_c(\Delta t/2) = 0.95v_o$$


For full-wave, if the discharge time constant for the capacitor is 10 times the pulse duration, the average DC output level is approximately **95% of v_p** .

DC with AC Ripple

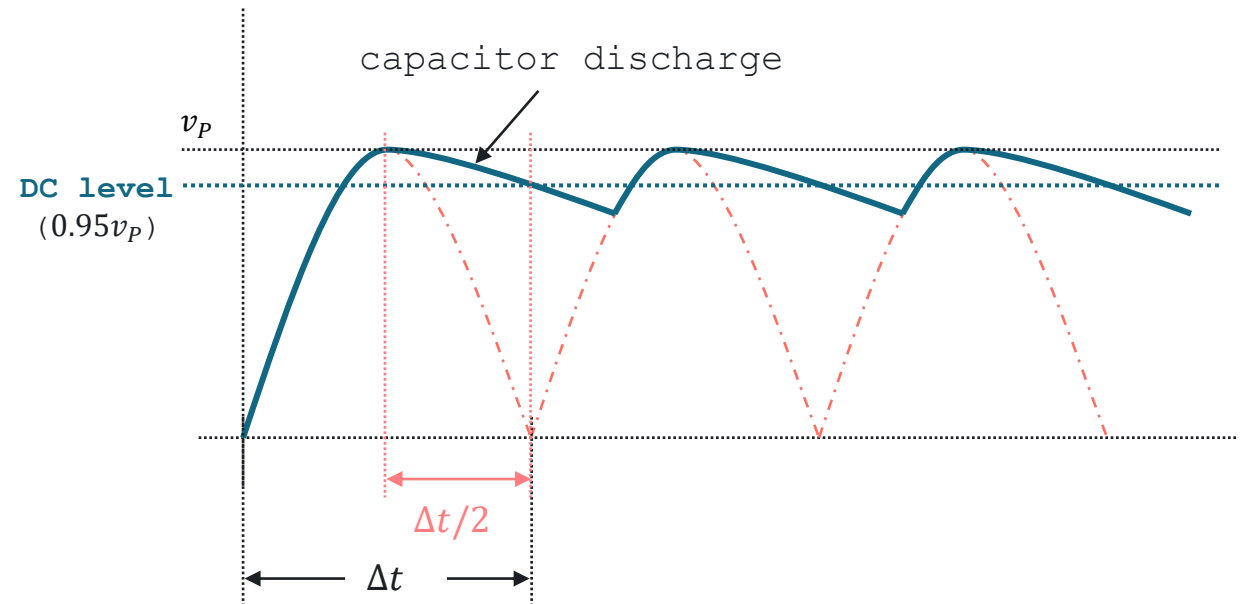

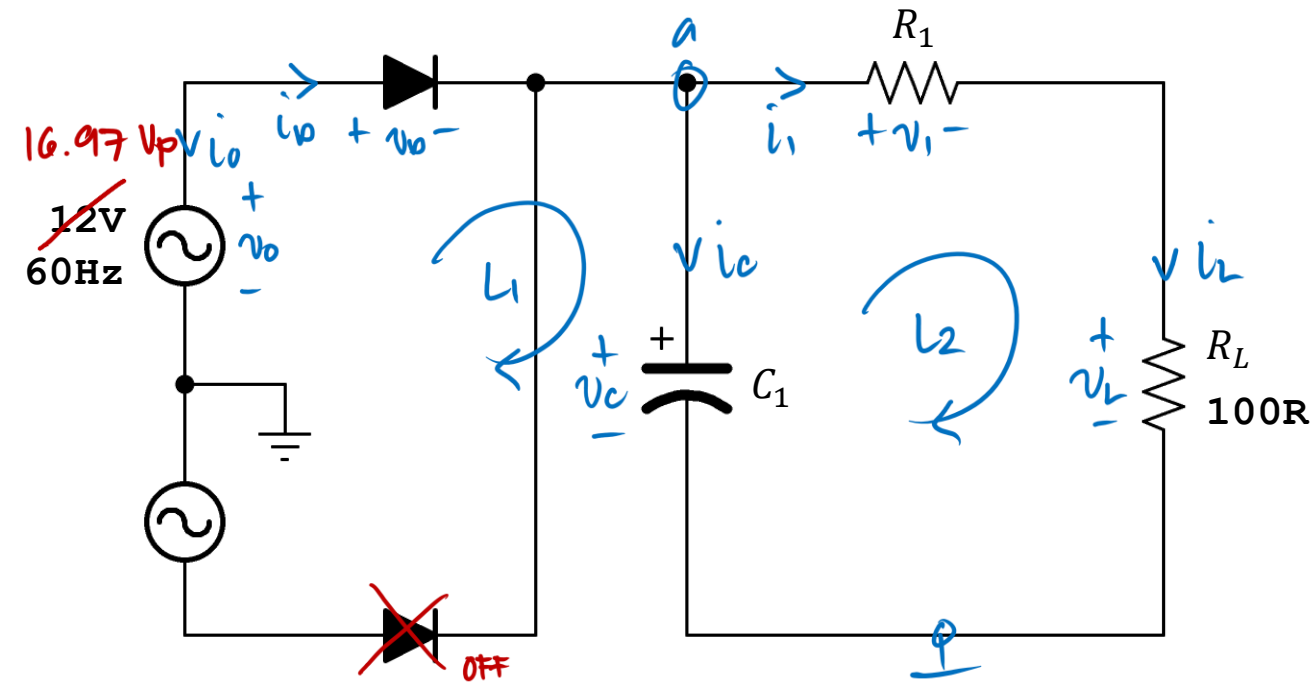EXERCISE

The AC input to the given rectifier circuit is a $12V_{RMS}$, 60Hz sine wave. For this circuit, you need 9V DC across the 100Ω load resistor. Determine the value of R_1 and C_1 .



Solution

Peak voltage @ a

$$V_{RMS} = \frac{V_p}{\sqrt{2}}$$


$$V_p = V_{RMS} \sqrt{2}$$

$$V_0 = 12\sqrt{2}$$

$$\underline{V_0 = 16.97 V_p}$$

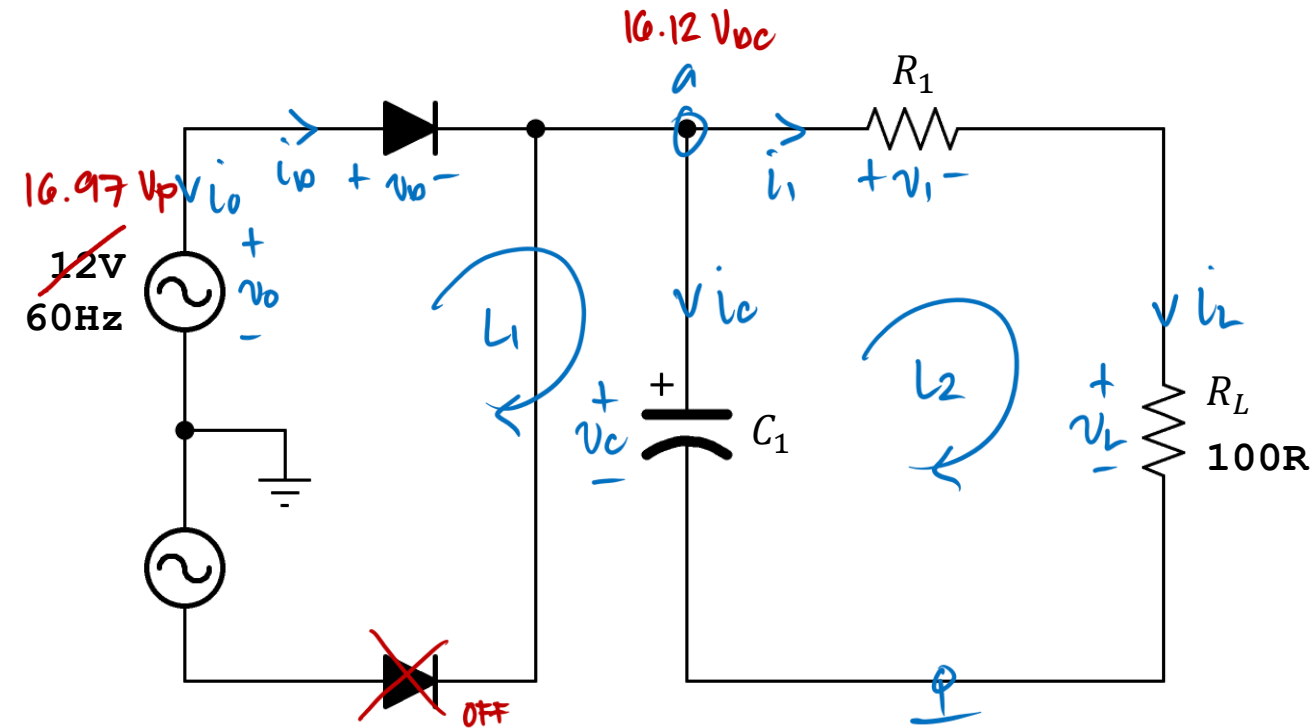EXERCISE

The AC input to the given rectifier circuit is a $12V_{RMS}$, 60Hz sine wave. For this circuit, you need 9V DC across the 100Ω load resistor. Determine the value of R_1 and C_1 .



Solution

DC Level @ a

Let $\tau = 10 \text{ At}$, then

$$V_{oc} = 0.95 V_p$$

$$V_a(v_c) = 0.95 (16.97)$$

$$\underline{V_a(v_c) = 16.12 \text{ V}}$$

The AC input to the given rectifier circuit is a $12V_{RMS}$, 60Hz sine wave. For this circuit, you need 9V DC across the 100Ω load resistor. Determine the value of R_1 and C_1 .



by VDT

$$V_L = V_a \frac{R_L}{R_1 + R_L}$$

$$R_1 + R_2 = \frac{V_a R_2}{V_L}$$

$$r_1 = \frac{v_a r_2}{v_L} - r_2$$


$$R_1 = \frac{16.12(100)}{9} - 100$$

$$R_1 = 79.11 \, \Omega$$

ans

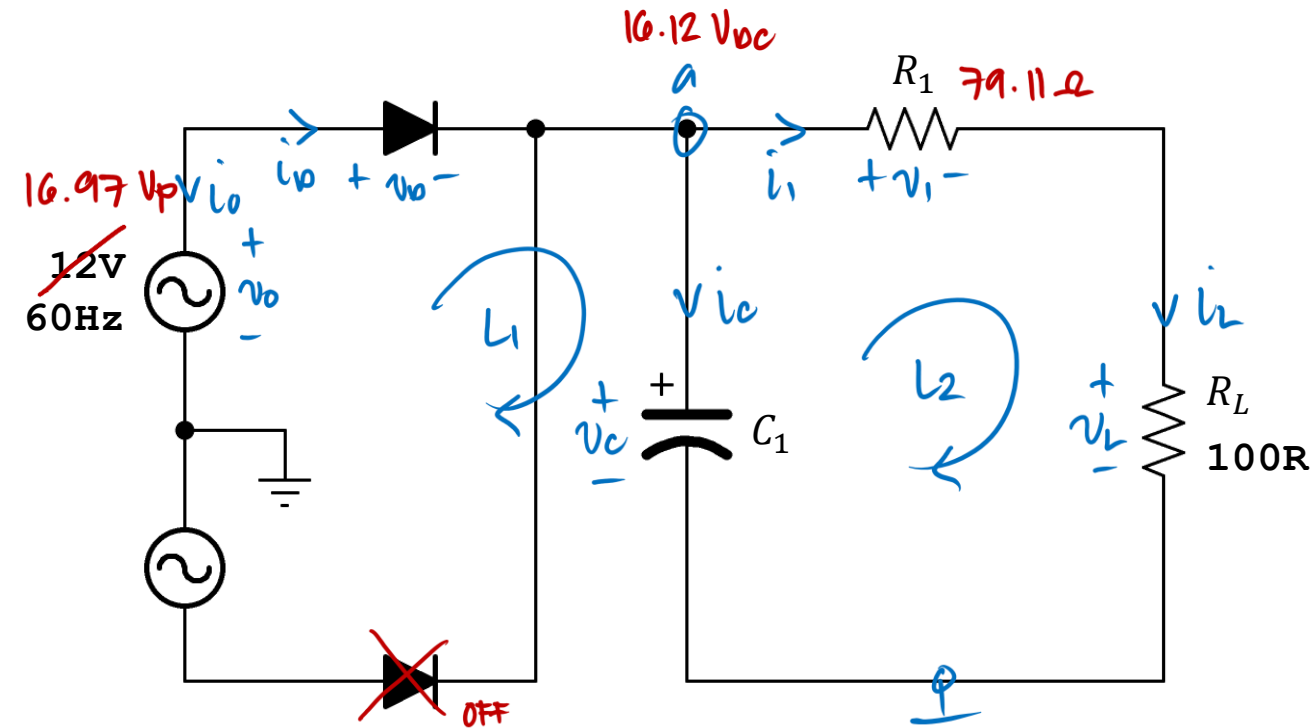
EXERCISE

The AC input to the given rectifier circuit is a $12V_{RMS}$, 60Hz sine wave. For this circuit, you need 9V DC across the 100Ω load resistor. Determine the value of R_1 and C_1 .



Solution

Pulse Duration

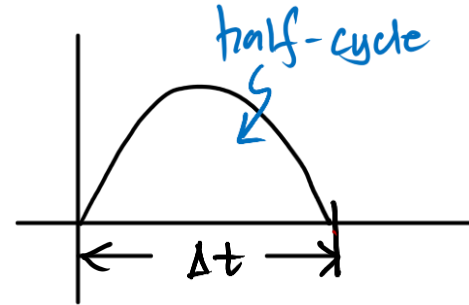

$$\Delta t = \frac{1}{2} \cdot \frac{1}{f}$$

$$\Delta t = \frac{1}{2(60)}$$

$$\Delta t = 8.33 ms$$

$$\text{For } \tau = 10 \Delta t$$

$$\tau = RC$$

$$C_1 = \frac{10 \Delta t}{R_1 + R_L}$$

$$C_1 = \frac{10(8.33 ms)}{79.11 + 100}$$

$$C_1 = 465.08 \mu F$$

avg

LABORATORY

