



# TRANSIENT RESPONSE OF CAPACITOR

## RC CIRCUITS

---

*prepared by:*

**Gyro A. Madrona**  
Electronics Engineer

## TOPIC OUTLINE

Charging a Capacitor


Discharging a Capacitor



# CHARGING A CAPACITOR



# RC CIRCUIT

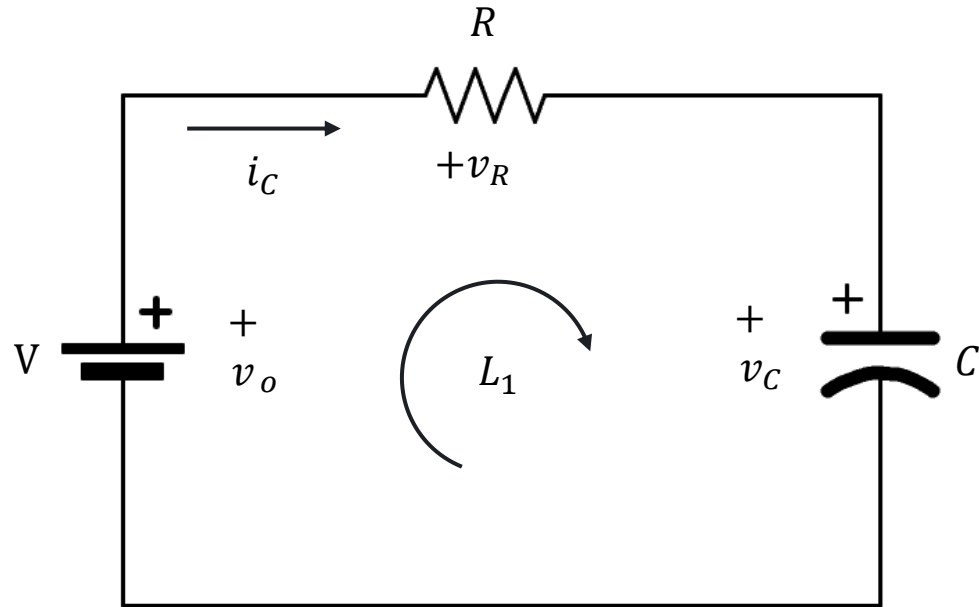

KVL @  $L_1$

$$-v_o + v_R + v_C = 0$$

$$v_R + v_C = v_o$$

$$i_C R + v_C = v_o \quad ; i_C = C \frac{d}{dt} v_C$$

$$RC \frac{d}{dt} v_C + v_C = v_o$$

$$\frac{d}{dt} v_C + \frac{1}{RC} v_C = \frac{v_o}{RC}$$

... first-order ODE

$$v_C(t) = v_o \left(1 - e^{-\frac{t}{RC}}\right)$$




# CAPACITOR VOLTAGE

## Charging Equation

$$v_c(t) = v_o(1 - e^{-\frac{t}{\tau}})$$

where:  $\tau = RC$

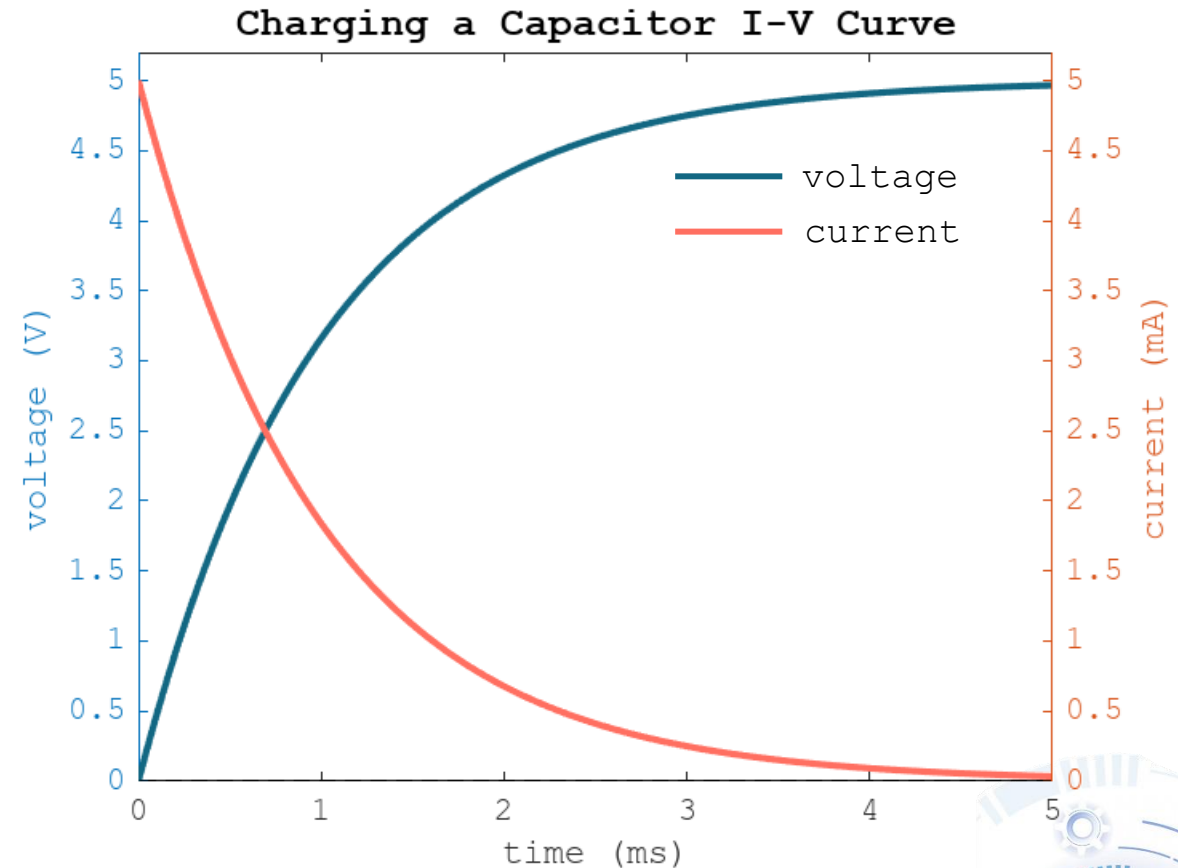The voltage across the capacitor starts at zero and exponentially increases to its maximum voltage ( $v_o$ ).




# CAPACITOR CURRENT

## Charging Equation

$$i_c(t) = \frac{v_o}{R} e^{-\frac{t}{\tau}}$$

where:  $\tau = RC$

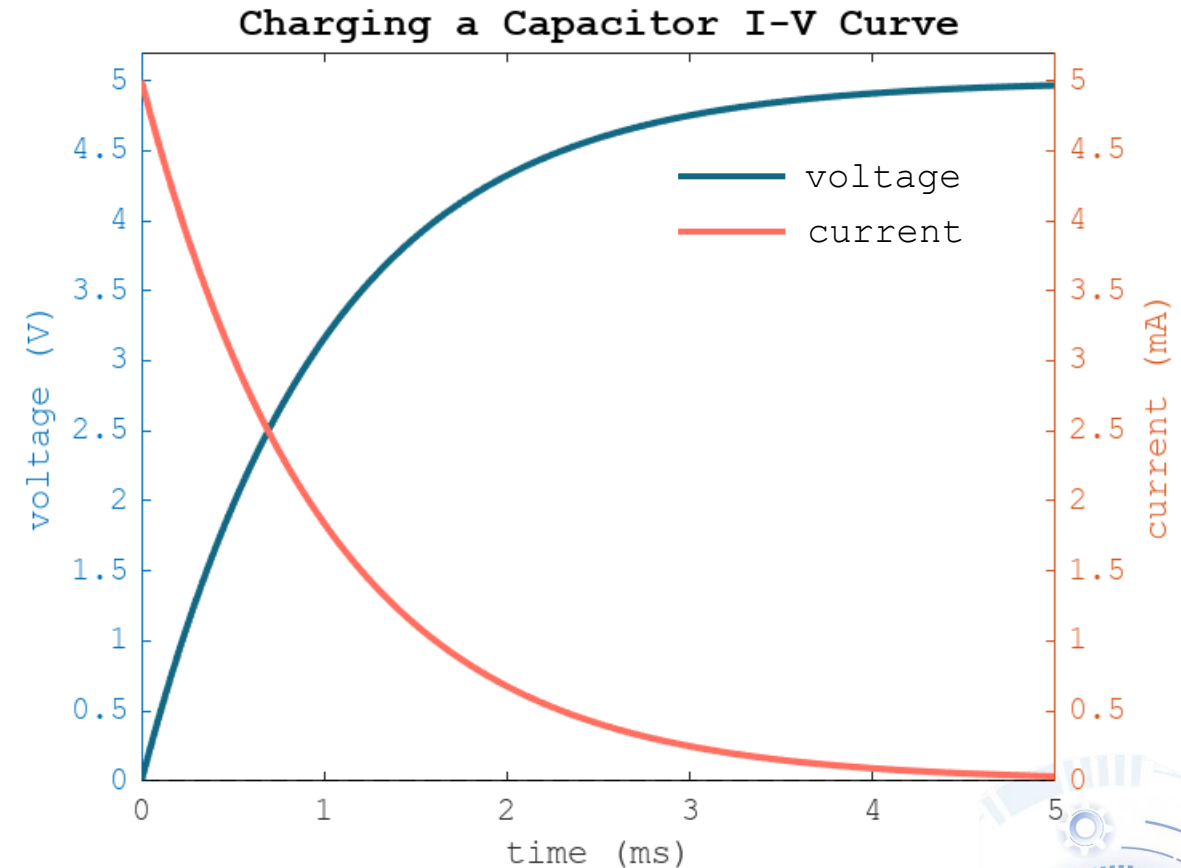The current through the capacitor instantly jumps to its maximum value ( $v_o/R$ ) amperes then decays exponentially to zero.




# TIME CONSTANT

The time constant ( $\tau$ ) is a measure of how quickly a capacitor charges or discharges in an RC circuit.

Formula

$$\tau = RC$$

unit: second

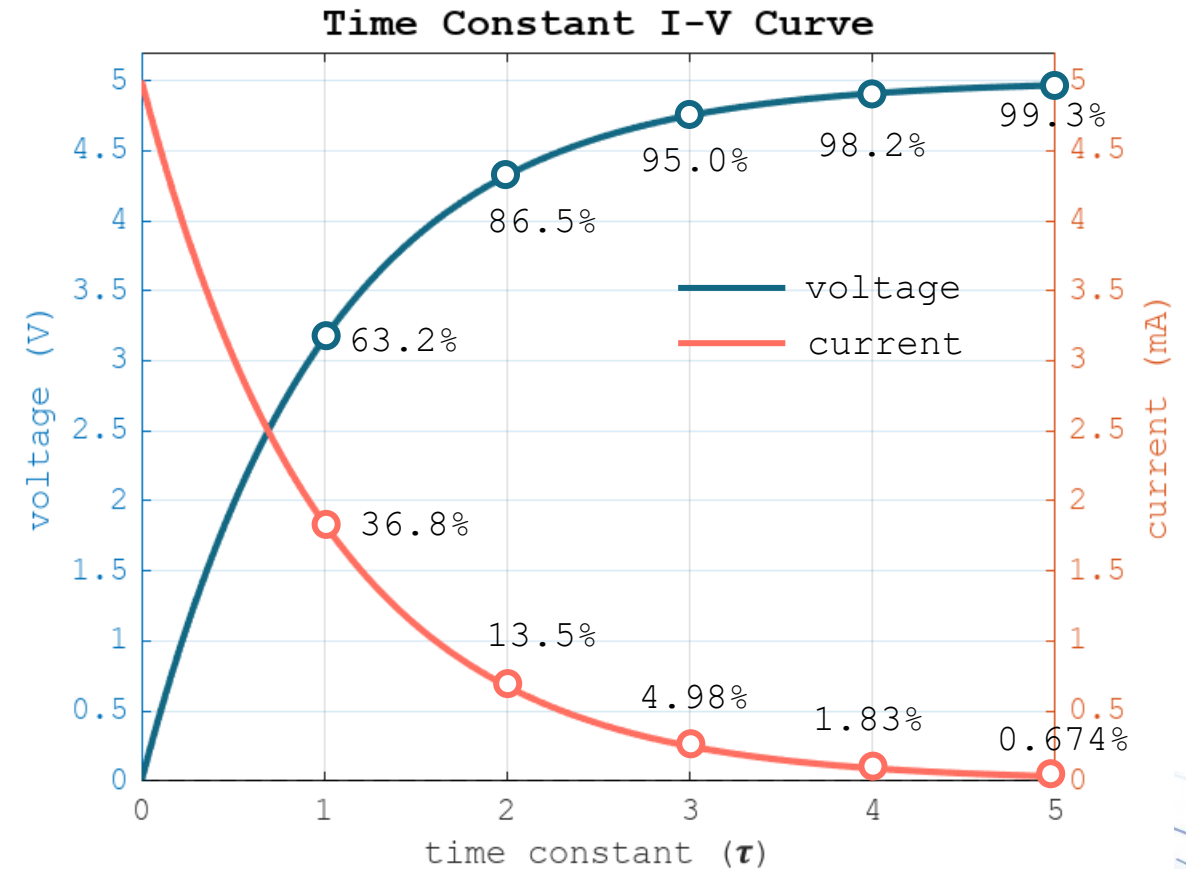

## EXERCISE

---

A  $100\mu\text{F}$  capacitor is connected to a 12V DC power supply through a resistor of  $1\text{K}\Omega$ . Determine the time it takes for the capacitor to charge to 86.5% of its maximum voltage.

Solution





## EXERCISE

---

A  $100\mu\text{F}$  capacitor is connected to a 12V DC power supply through a resistor of  $1\text{K}\Omega$ . Determine the voltage across the capacitor after 200 *ms* of charging.


Solution



# DISCHARGING A CAPACITOR



# RC CIRCUIT

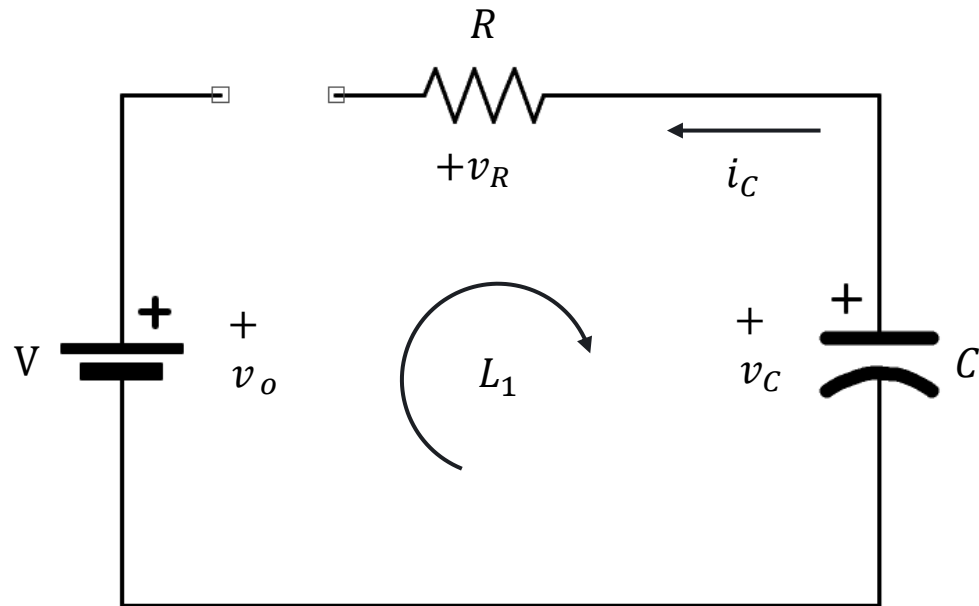

KVL @  $L_1$

$$v_R + v_C = 0$$

$$i_C R + v_C = 0 \quad ; i_C = C \frac{d}{dt} v_C$$

$$RC \frac{d}{dt} v_C + v_C = 0$$

$$\frac{d}{dt} v_C + \frac{1}{RC} v_C = 0$$

... first-order ODE

$$v_C(t) = v_o e^{-\frac{t}{RC}}$$




# CAPACITOR VOLTAGE

## Discharging Equation

$$v_c(t) = v_o e^{-\frac{t}{\tau}}$$

where:  $\tau = RC$

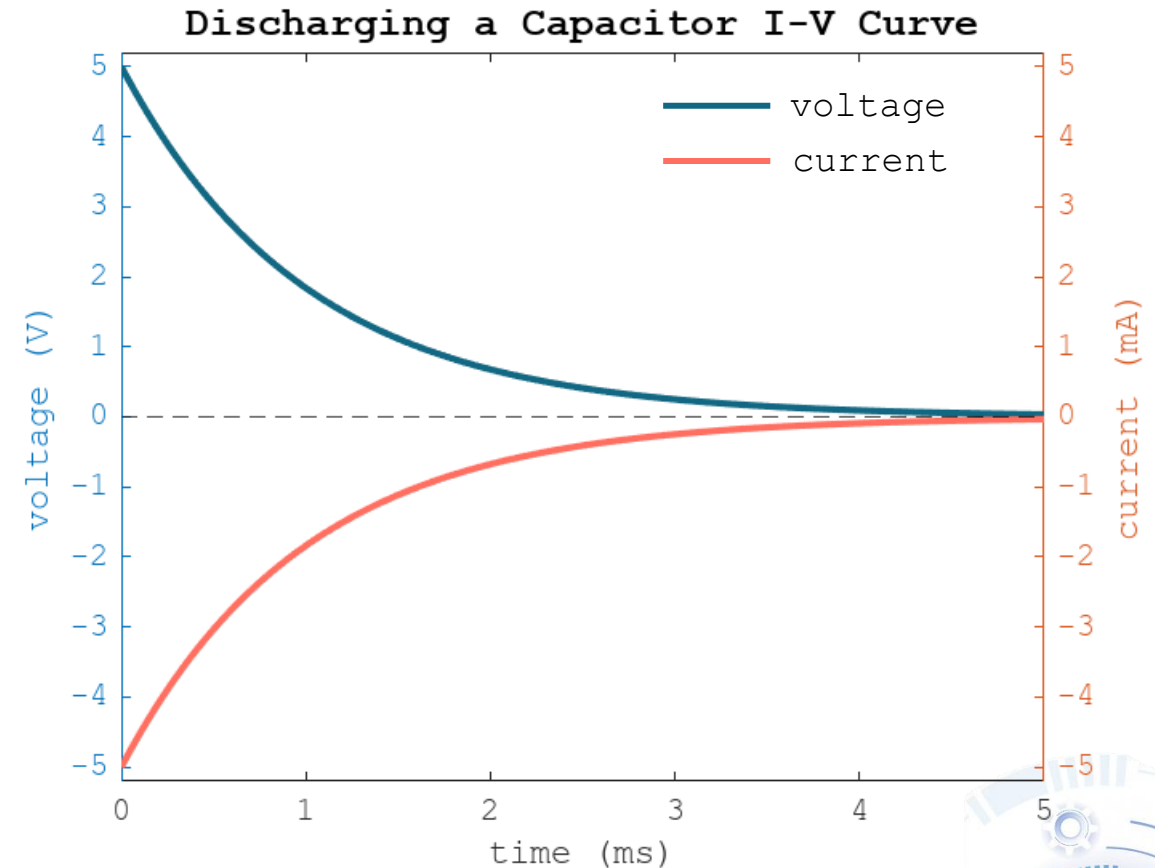The voltage across the capacitor starts at its maximum voltage ( $v_o$ ) then decays exponentially to zero.




# CAPACITOR CURRENT

## Discharging Equation

$$i_c(t) = -\frac{v_o}{R} \left( e^{-\frac{t}{\tau}} \right)$$

where:  $\tau = RC$

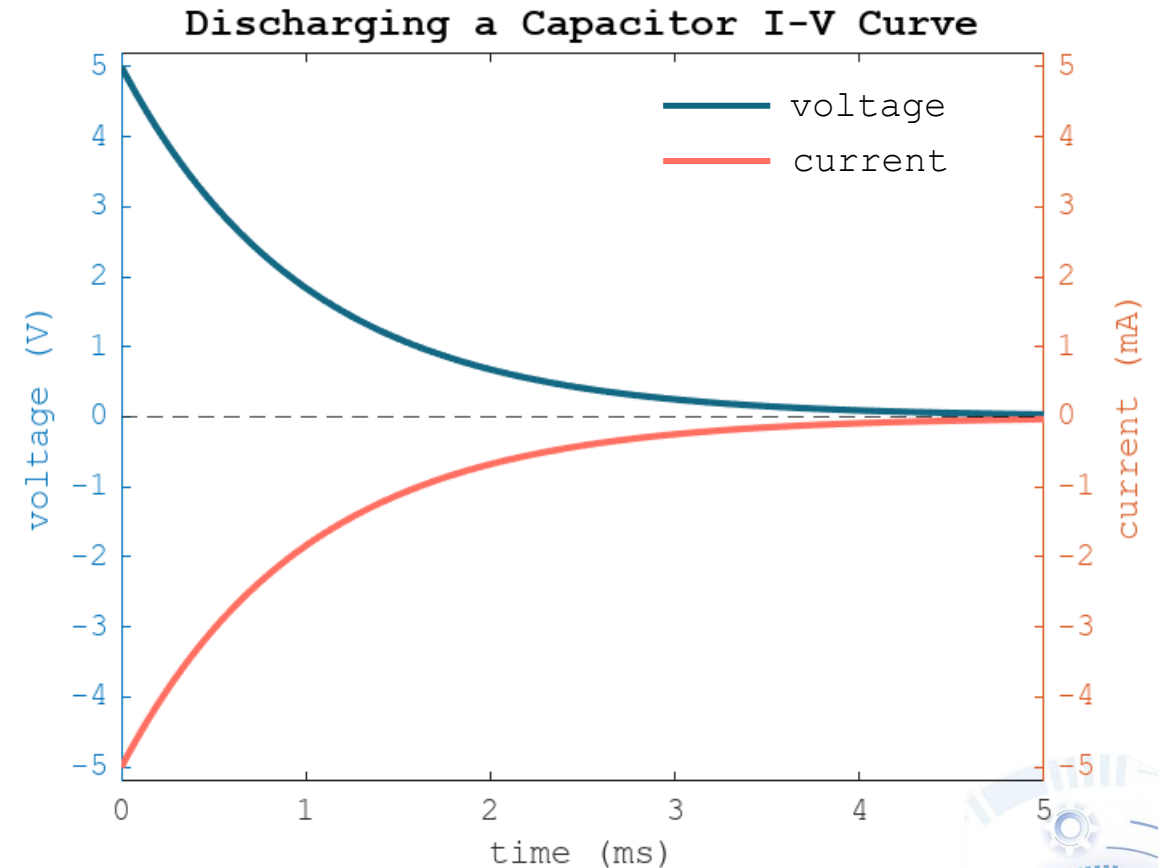The current through the capacitor instantly jumps to its maximum value, but in opposite direction ( $-v_o/R$ ) then decays exponentially to zero.



## EXERCISE

---


A  $200\mu\text{F}$  capacitor is initially charged to  $12\text{V}$ . It is then disconnected from the power supply and discharged through a resistor of  $1.5\text{K}\Omega$ . Determine the voltage across the capacitor after  $0.1\text{s}$  of discharging.

Solution



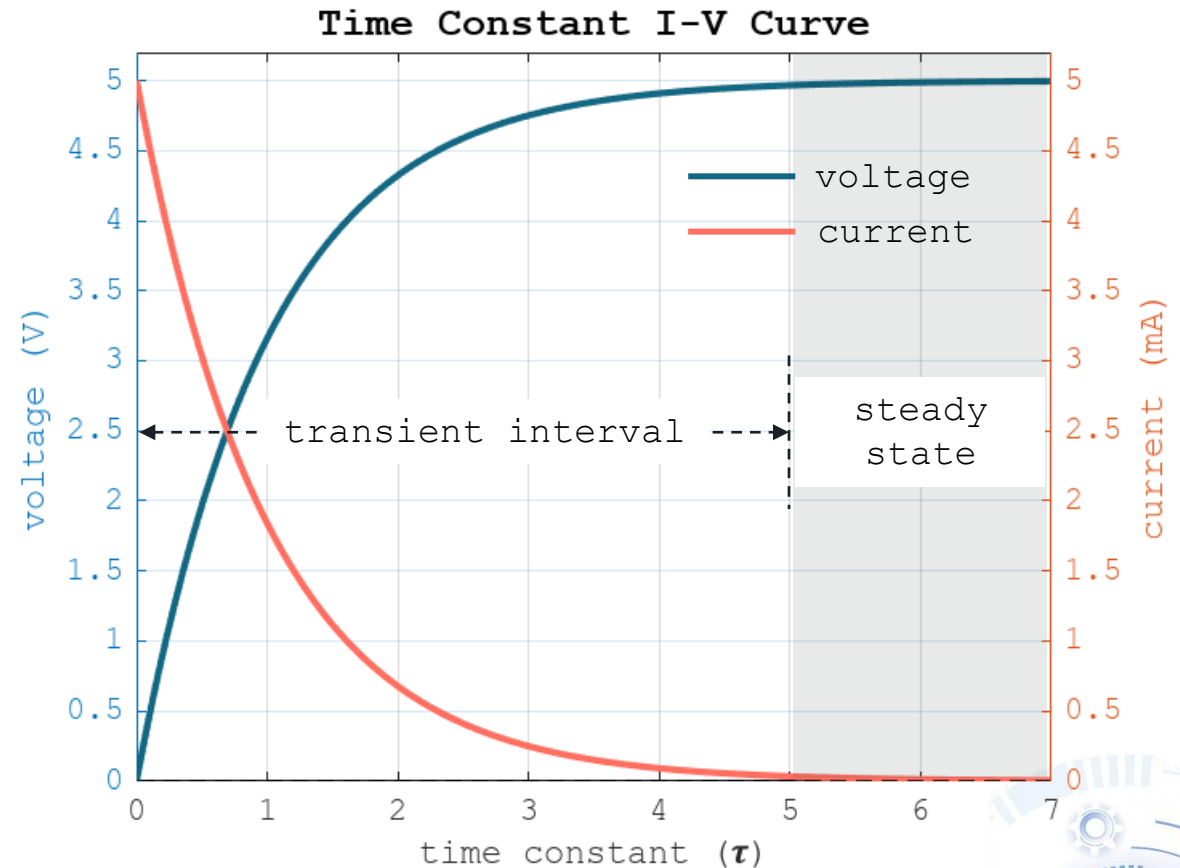
# TRANSIENT RESPONSE

The transient response of a capacitor describes the time-dependent changes in voltage across the capacitor and the current through it. The transient phase is typically considered to last for approximately five time constants ( $5\tau$ ) after which the system is assumed to have reached steady-state conditions.


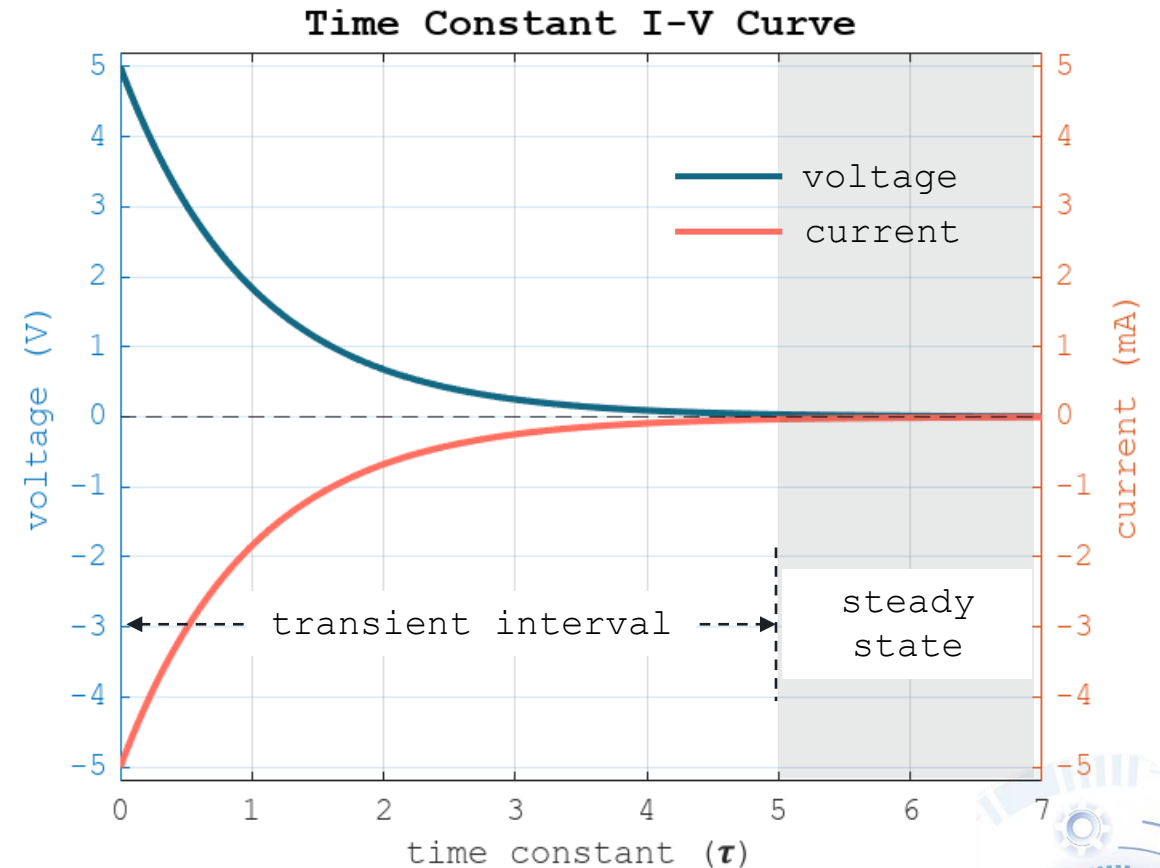
# TRANSIENT RESPONSE

The transient response of a capacitor describes the time-dependent changes in voltage across the capacitor and the current through it. The transient phase is typically considered to last for approximately five time constants ( $5\tau$ ) after which the system is assumed to have reached steady-state conditions.





# LABORATORY

