



# **CAPACITOR**

## **TRANSIENT RESPONSE**

---

*prepared by:*

**Gyro A. Madrona**  
Electronics Engineer

# TOPIC OUTLINE

RC Circuit

Charging a Capacitor

Discharging a Capacitor


Transient Response



# CHARGING A CAPACITOR



# RC CIRCUIT

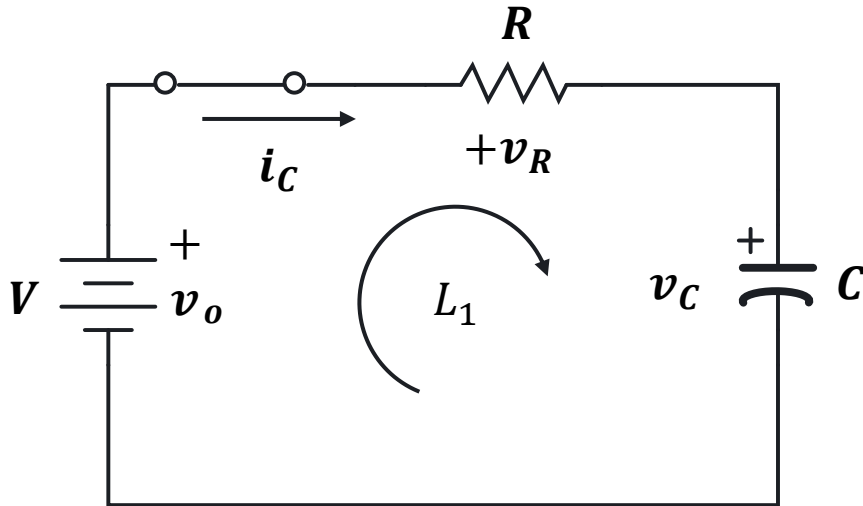

KVL @  $L_1$ :

$$-v_o + v_R + v_C = 0$$

$$v_R + v_C = v_o$$

$$i_C R + v_C = v_o \quad ; i_C = C \frac{d}{dt} v_C$$

$$RC \frac{d}{dt} v_C + v_C = v_o$$

$$\frac{d}{dt} v_C + \frac{1}{RC} v_C = \frac{v_o}{RC}$$

... first-order ODE

$$v_C(t) = v_o \left( 1 - e^{-\frac{t}{RC}} \right)$$




# CAPACITOR VOLTAGE

Charging equation:

$$v_c(t) = v_o \left(1 - e^{-\frac{t}{\tau}}\right)$$

where:  $\tau = RC$

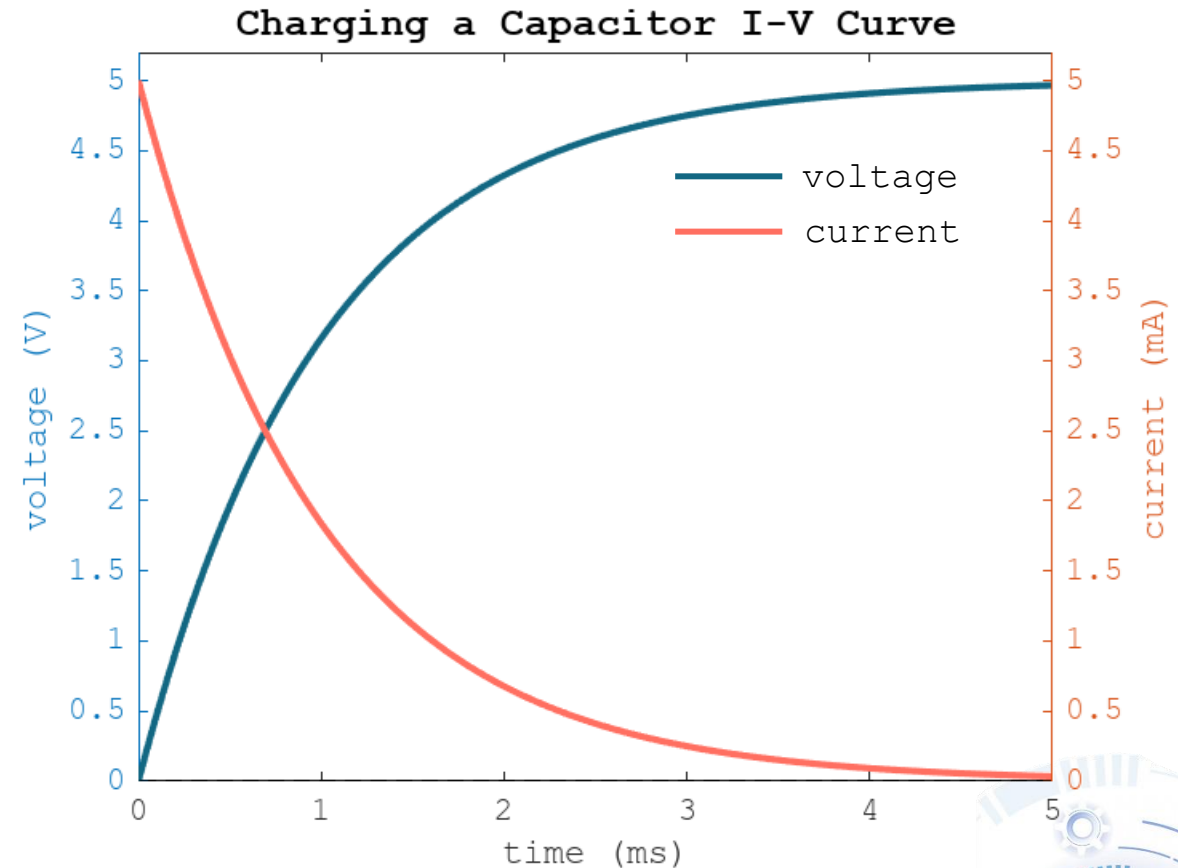The voltage across the capacitor starts at zero and exponentially increases to  $v_o$  volts (source voltage).




# CAPACITOR CURRENT

Charging equation:

$$i_c(t) = \frac{v_o}{R} e^{-\frac{t}{\tau}}$$

where:  $\tau = RC$

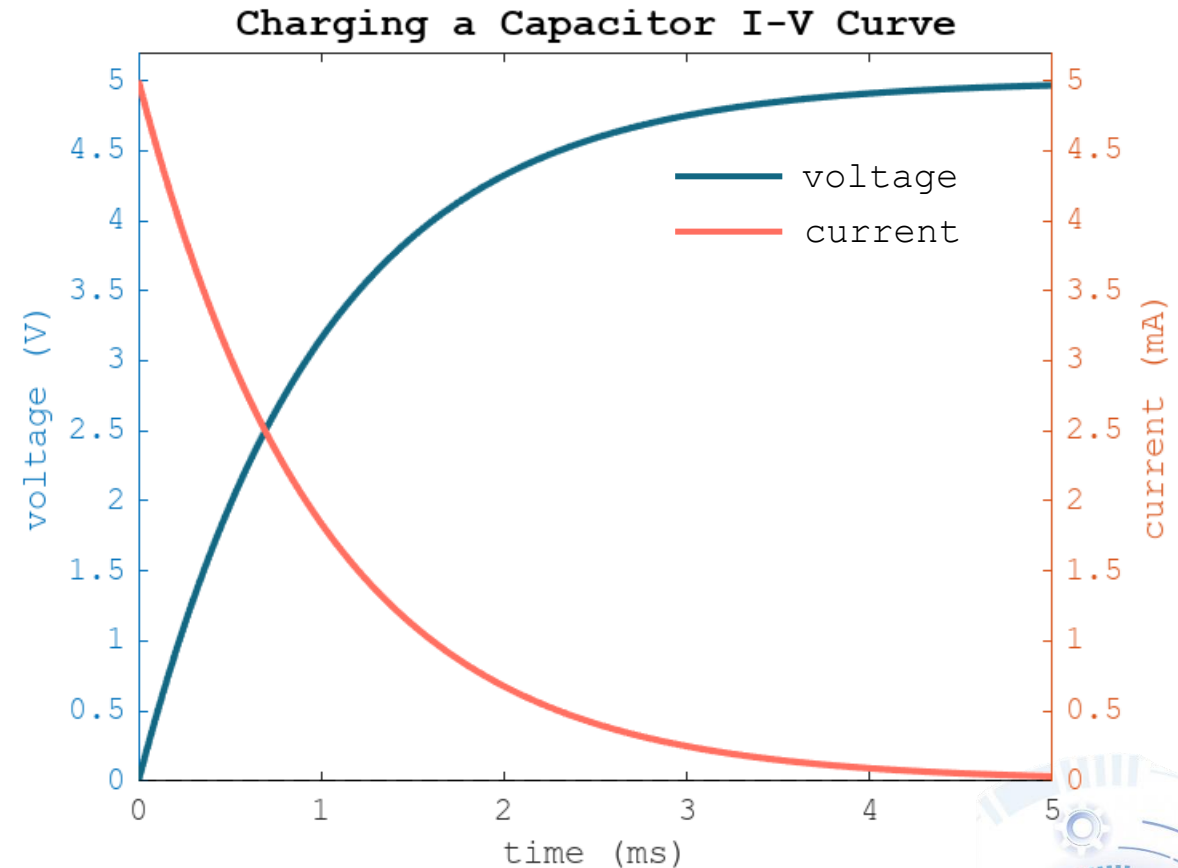The current through the capacitor instantly jumps to its maximum value of  $\frac{v_o}{R}$  amperes then decays exponentially to zero.




# TIME CONSTANT

The time constant  $\tau$  is a measure of how quickly a capacitor charges or discharges in an RC circuit.

Formula:

$$\tau = RC$$

unit: second

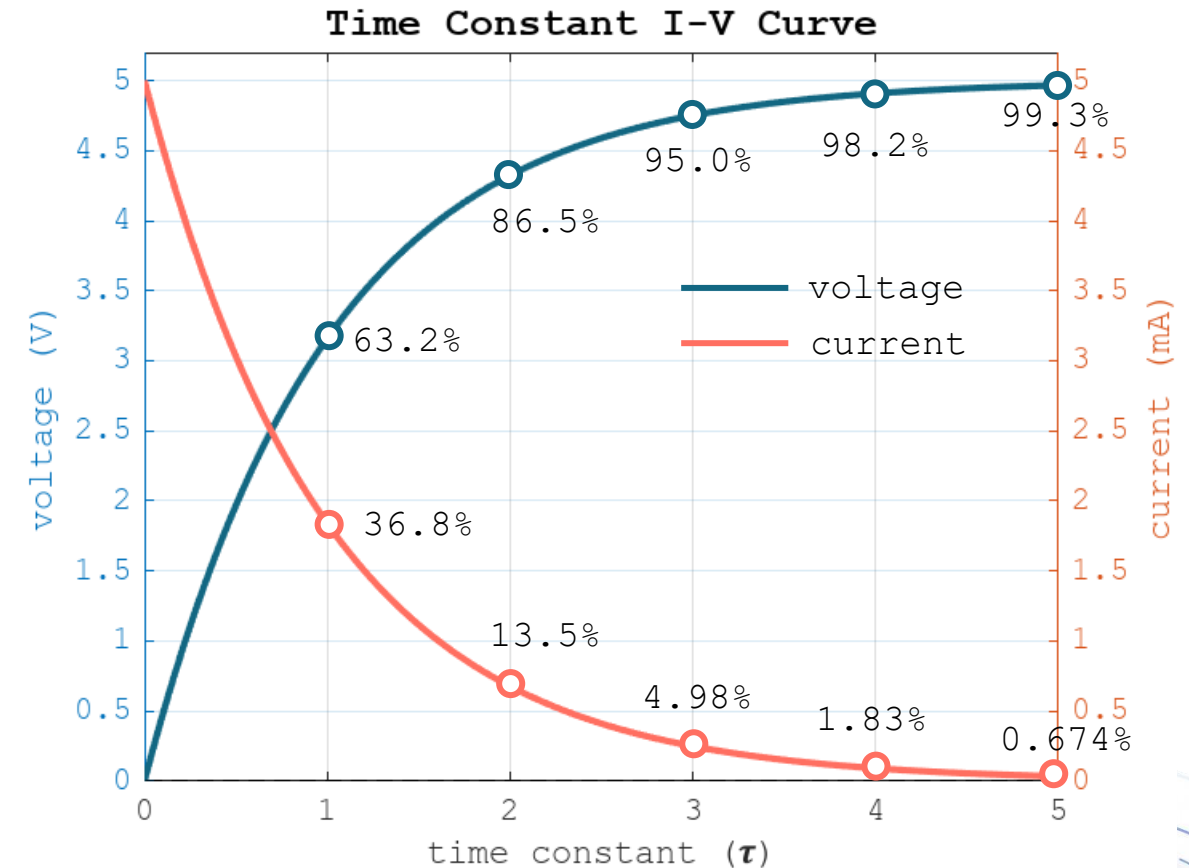

## EXERCISE

---

A  **$100\ \mu\text{F}$**  capacitor is connected to a  **$12\ \text{V}$**  DC power supply through a resistor of  **$1\ \text{k}\Omega$** . Determine the time it takes for the capacitor to charge to  **$86.5\%$**  of its maximum voltage.

Solution:





## EXERCISE

---

A **100  $\mu F$**  capacitor is connected to a **12 V** DC power supply through a resistor of **1  $K\Omega$** . Determine the voltage across the capacitor after **200 ms** of charging.


Solution:



# DISCHARGING A CAPACITOR



# RC CIRCUIT

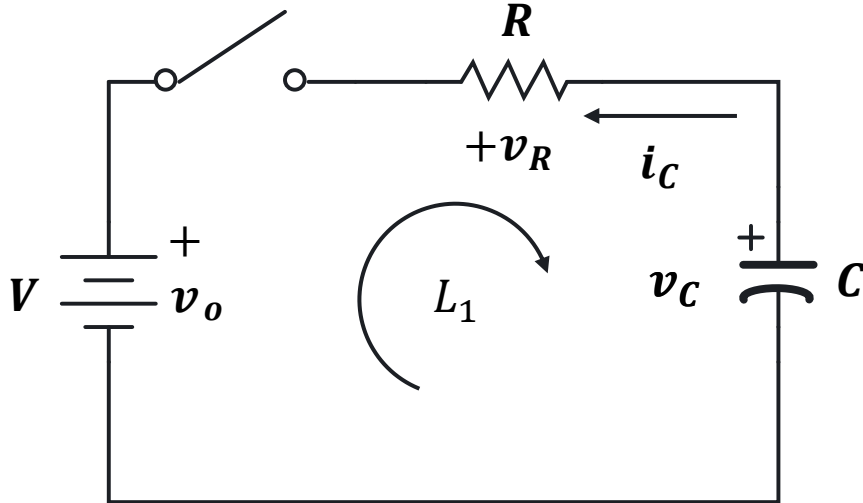

KVL @  $L_1$ :

$$v_R + v_C = 0$$

$$i_C R + v_C = 0 \quad ; i_C = C \frac{d}{dt} v_C$$

$$RC \frac{d}{dt} v_C + v_C = 0$$

$$\frac{d}{dt} v_C + \frac{1}{RC} v_C = 0$$

... first-order ODE

$$v_C(t) = v_o e^{-\frac{t}{RC}}$$




# CAPACITOR VOLTAGE

Discharging equation:

$$v_c(t) = v_o e^{-\frac{t}{\tau}}$$

where:  $\tau = RC$

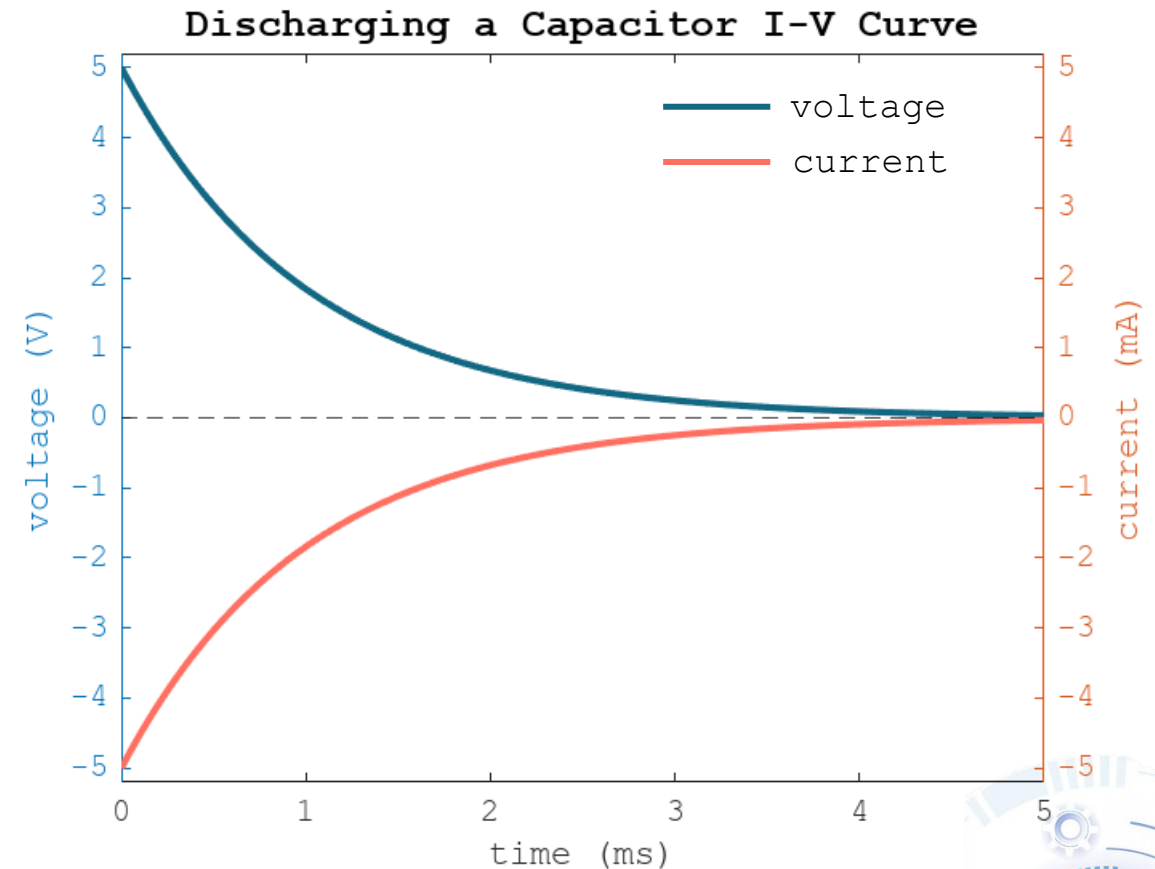The voltage across the capacitor starts at its maximum voltage  $v_o$  then decays exponentially to zero.




# CAPACITOR CURRENT

Discharging equation:

$$i_c(t) = -\frac{v_o}{R} \left( e^{-\frac{t}{\tau}} \right)$$

where:  $\tau = RC$

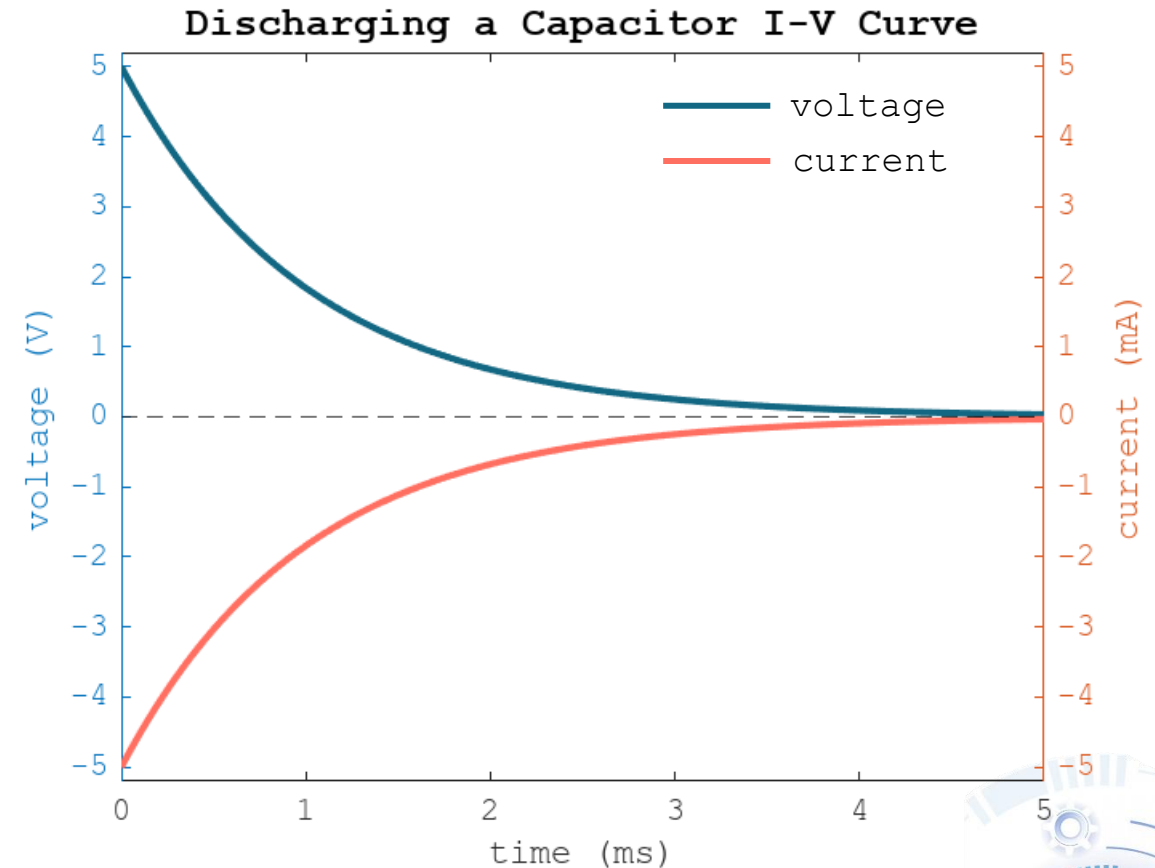The current through the capacitor instantly jumps to its maximum value, but in opposite direction of  $-\frac{v_o}{R}$  then decays exponentially to zero.



## EXERCISE


---

A  **$200\ \mu\text{F}$**  capacitor is initially charged to  **$12\ \text{V}$** . It is then disconnected from the power supply and discharged a resistor of  **$1.5\ \text{k}\Omega$** . Determine the voltage across the capacitor after  **$0.1\ \text{s}$**  of discharging.



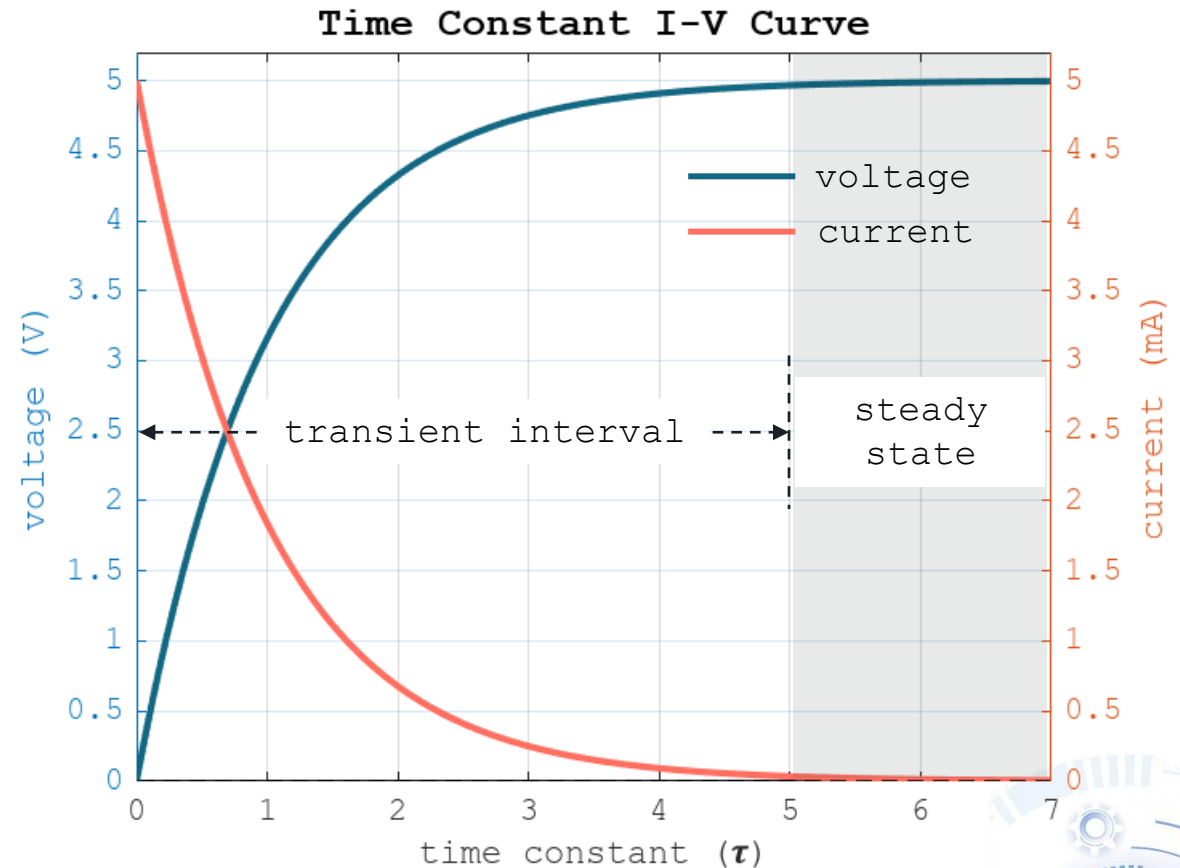
# TRANSIENT RESPONSE

The transient response of a capacitor describes the time-dependent changes in voltage across the capacitor and the current through it. The transient phase is typically considered to last for approximately five time constants  $5\tau$  after which the system is assumed to have reached steady-state conditions.


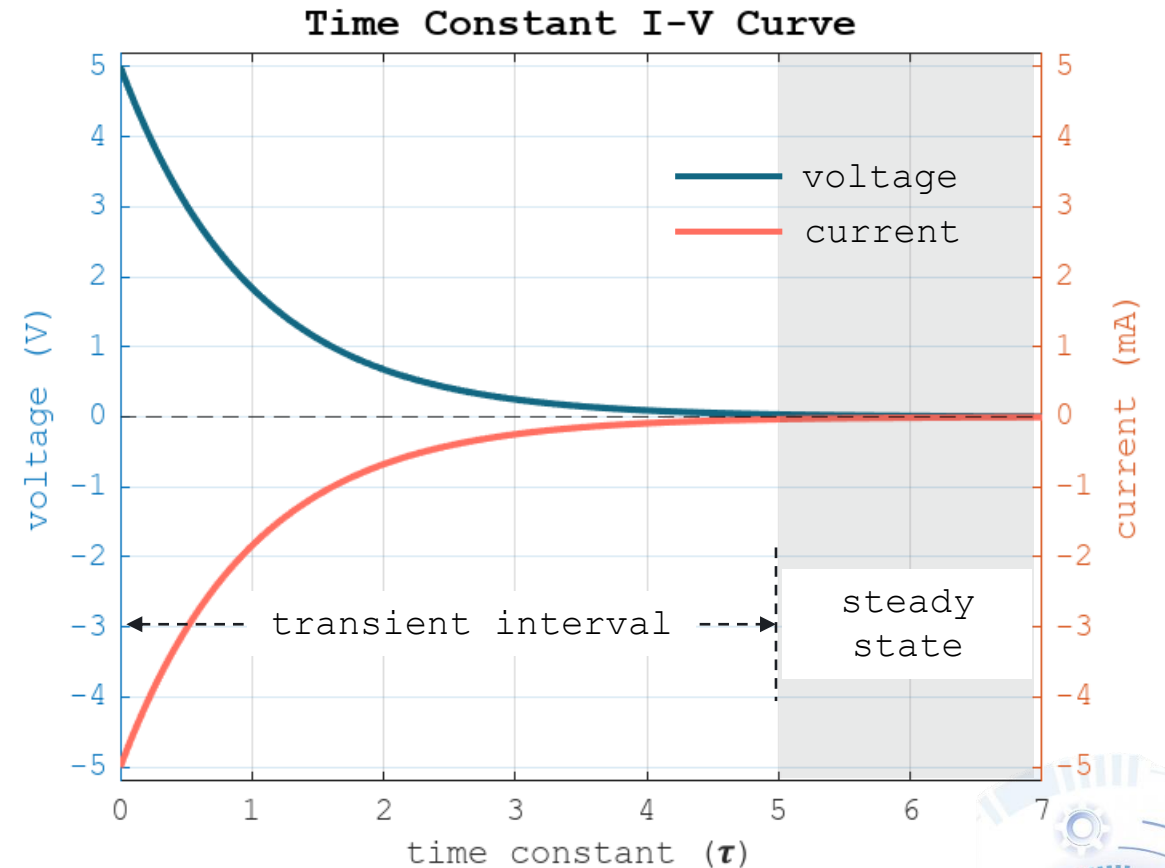
# TRANSIENT RESPONSE

The transient response of a capacitor describes the time-dependent changes in voltage across the capacitor and the current through it. The transient phase is typically considered to last for approximately five time constants  $5\tau$  after which the system is assumed to have reached steady-state conditions.





# LABORATORY

