



# **GATE-LEVEL MODELING**

## **VERILOG DESIGN STYLE**

---

*prepared by:*

**Gyro A. Madrona**  
Electronics Engineer

# **TOPIC OUTLINE**

**Logic Gate Primitives**

**Data Types**

**Bit and Bus**

**Gate-Level Modeling**



# LOGIC GATE PRIMITIVES



# NUMBER REPRESENTATION

---

## syntax

**size** **base** **number**

## Decimal

10' **d**8 → 00 0000 1000

## Binary

8' **b**1100 → 0000 1100

## Hexadecimal

9' **h**fe → 0 1111 1110

## Octal

7' **o**67 → 0 110 111

## Size matters

7' **h**fe → 0 1111 1110



# LOGIC GATE PRIMITIVES

## syntax

```
primitive instance_name(output,  
                           input1,input2,...) ;
```

```
not U1 (Y,A) ;
```

```
and U2 (Y,A,B) ;
```

```
or U3 (Y,A,B) ;
```








```
xor U4 (Y,A,B) ;
```

```
nand U5 (Y,A,B) ;
```

```
nor U6 (Y,A,B) ;
```

```
xnor U7 (Y,A,B) ;
```

## implementation

       


# DATA TYPES



# WIRE

module name

**xor\_gate**

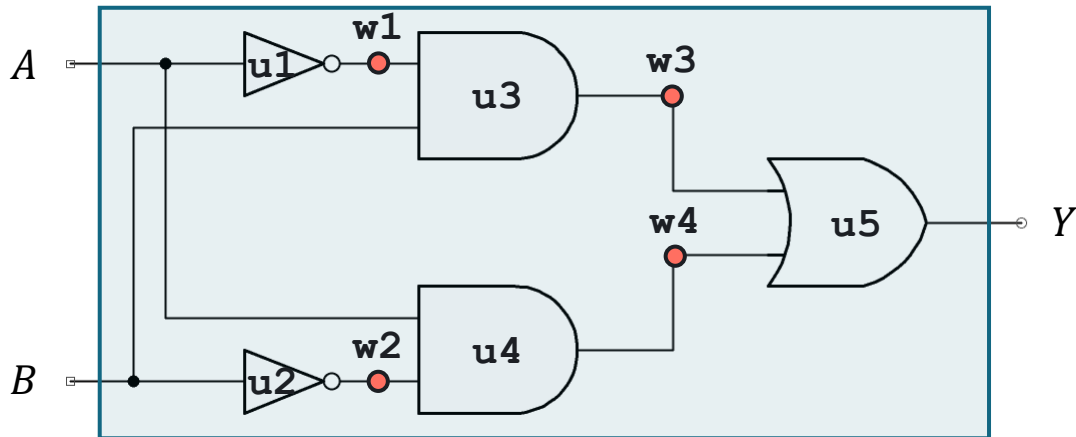

```
module xor_gate(Y,A,B) ;
```

```
    input A,B;
```

```
    output Y;
```

```
    wire w1,w2,w3,w4;
```

```
    or u5(Y,w3,w4) ;
```

```
    not u1(w1,A) ;
```

```
    not u2(w2,B) ;
```

```
    and u3(w3,w1,B) ;
```

```
    and u4(w4,A,w2) ;
```

```
endmodule
```


—it's all concurrent!

A wire represents a net (a logical connection) that reflects the value driven by its sources; but it **does not hold a value**.

# REG

module name

**testbench**

 

A **reg** represents a variable that can store a value assigned procedurally inside an **always** or **initial** block.

```
module testbench();
```

```
    reg a,b;
```

```
    wire y;
```

instantiate

```
    xor_gate dut(y,a,b);
```

```
    initial begin
```

```
        a = 0; b = 0; #10;
```

```
        a = 0; b = 1; #10;
```

```
        a = 1; b = 0; #10;
```

```
        a = 1; b = 1; #10;
```

sequential

```
    end
```

```
endmodule
```





# BIT AND BUS



# BIT AND BUS

Bit – a single binary signal

```
wire a; // 1-bit wire
```

```
reg b; // 1-bit reg
```

a \_\_\_\_\_

b \_\_\_\_\_

## 4-State Logic

1 – logic high

0 – logic low

x – unknown/don't care

z – high-impedance (not driven/open circuit)


Bus – a multi-bit vector

```
wire [3:0] w; // 4-bit bus
```

```
reg [7:0] r; // 8-bit bus
```

syntax


```
type [MSB:LSB] name;
```

 

# USING A WIRE BUS

module name

**xor\_gate**

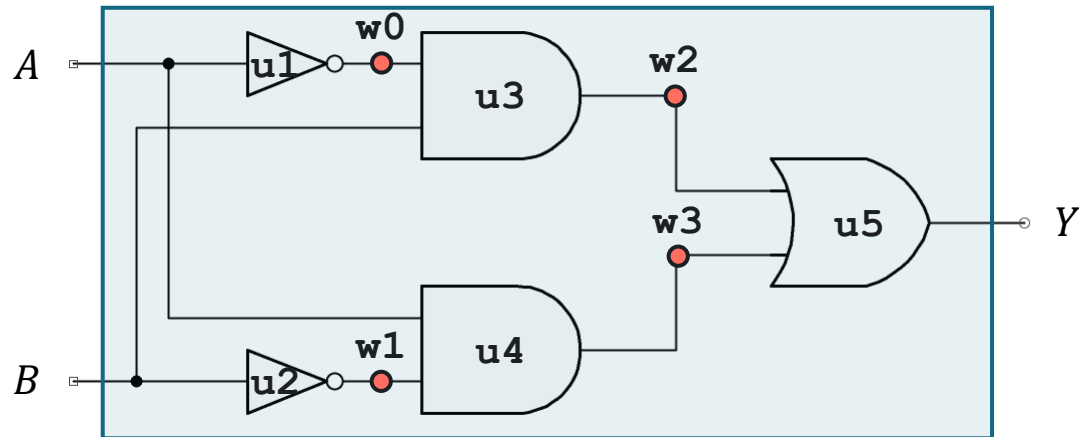


```
module xor_gate(Y,A,B);  
    input A,B;  
    output Y;  
    wire [3:0] w;  
  
    not u1(w[0],A);  
    not u2(w[1],B);  
    and u3(w[2],w[0],B);  
    and u4(w[3],A,w[1]);  
    or u5(Y,w[2],w[3]);  
endmodule
```



# TESTBENCH

module name

**testbench**

 

```
module testbench;
```

```
    reg a,b;
```

```
    wire y;
```

```
    xor_gate dut(.Y(y),.A(a),.B(b));
```

```
    initial begin
```

```
        a = 0; b = 0; #10;
```

```
        a = 0; b = 1; #10;
```

```
        a = 1; b = 0; #10;
```

```
        a = 1; b = 1; #10;
```

```
    end
```


```
endmodule
```



# TESTBENCH

module name

**testbench**

 

```
module testbench;
```

```
    reg A,B;
```

```
    wire Y;
```

```
    xor_gate dut(.Y(Y),.A(A),.B(B));
```

```
    initial begin
```

```
        a = 0; b = 0; #10;
```

```
        a = 0; b = 1; #10;
```

```
        a = 1; b = 0; #10;
```

```
        a = 1; b = 1; #10;
```

```
    end
```

```
endmodule
```




# GATE-LEVEL MODELING



# XNOR GATE MODULE

module name

**xnor\_gate**

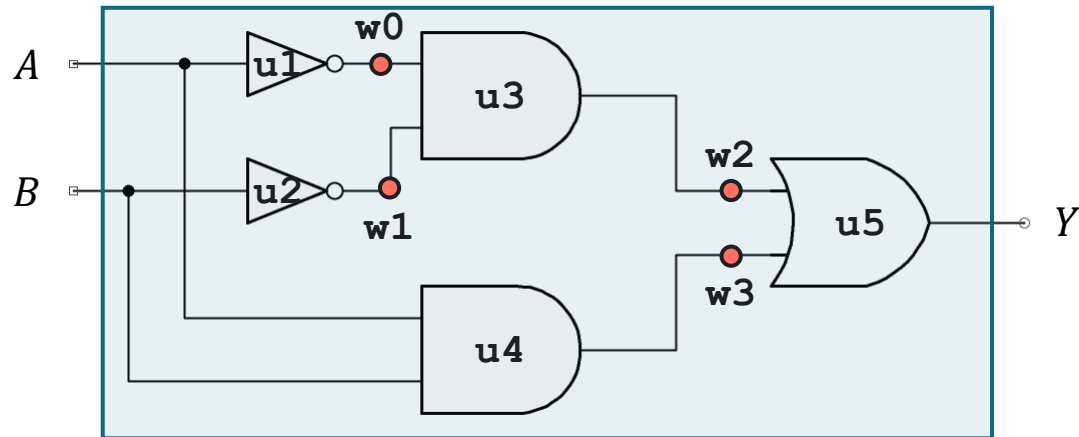

```
module xnor_gate(Y,A,B);
    input A,B;
    output Y;
    wire [3:0] w;

    not u1(w[0],A);
    not u2(w[1],B);
    and u3(w[0],w[1],w[2]);
    and u4(w[3],A,B);
    or u5(Y,w[2],w[3]);
endmodule
```


Gate-level modeling describes a circuit using built-in logic gate primitives (AND,OR,NOT,...etc.).



# HALF-ADDER MODULE

```
module half_adder(sum,cout,A,B) ;
```

implementation

 

```
endmodule
```






# FULL-ADDER MODULE

```
module full_adder(sum,cout,A,B,cin) ;
```

implementation

 

```
endmodule
```



# LABORATORY

