

KIRCHHOFF'S CURRENT AND VOLTAGE LAW

BASIC CIRCUIT ANALYSIS METHOD

prepared by:

Gyro A. Madrona

Electronics Engineer

TOPIC OUTLINE

Circuit Convention

Kirchhoff's Current Law (KCL)

Kirchhoff's Voltage Law (KVL)



CIRCUIT CONVENTION



CONVENTION

A convention is a widely accepted practice, method, or behavior that is followed by common agreement or tradition, rather than by formal rules.

example

Color coding in Offices

red – urgent documents

blue – general files

green – financial records

This is a common practice but not formally regulated.



STANDARD

A standard is a formal, established guideline, rule, or specification that is often mandatory and enforced by an authoritative body or organization.

example

IEC 60062 Resistor Color Code

black – 0

brown – 1

red – 2

.

.

.

white – 9

Resistors have colored bands that represent specific digits, multipliers, and tolerance values.



LABELING VARIABLES

Steps in Labeling Variables

1. Label the Reference Node (ground)

Select a reference node with the most connections or the negative (-) terminal of a voltage source.

2. Label Node Voltages


Mark higher potentials as positive (+) relative to the reference node.

3. Label Currents

Entering the positive (+) terminal of a component.

4. Create a voltage loop

Follow the defined current directions.

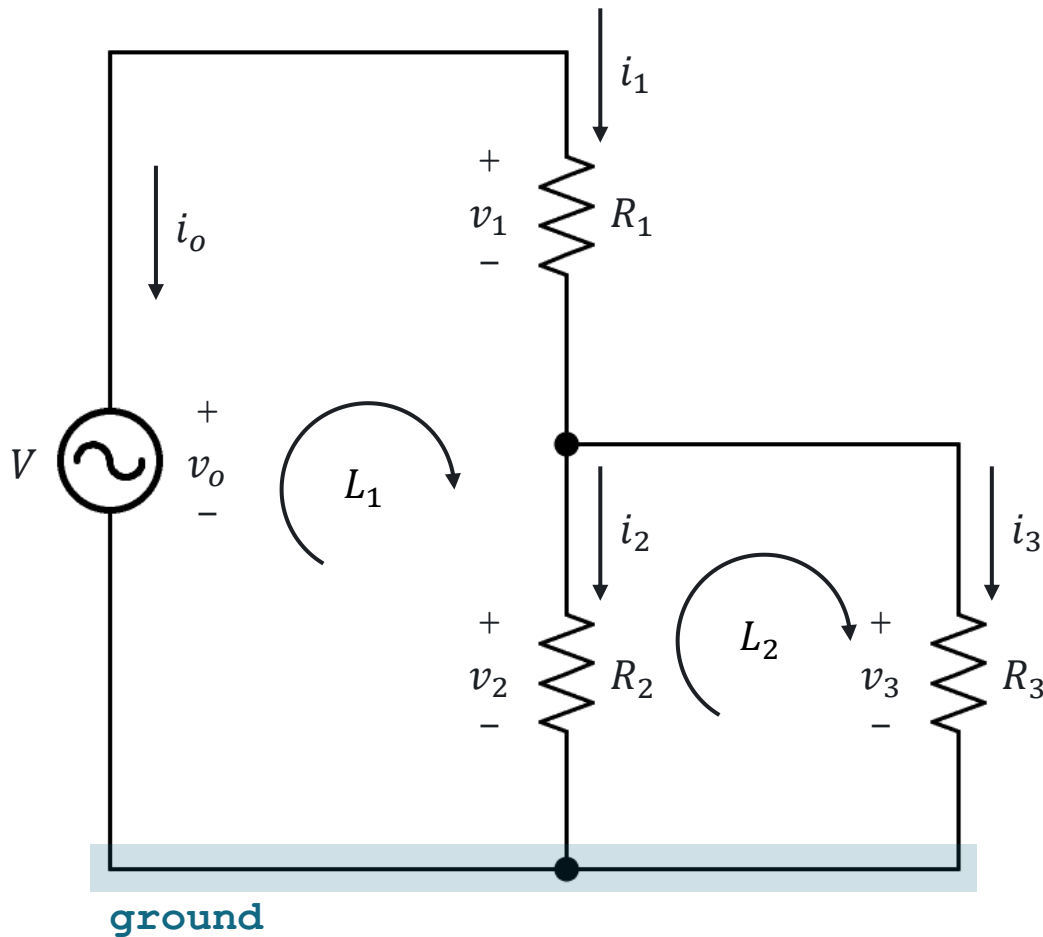

CIRCUIT CONVENTION

Current Flow Convention

- Current entering a node is negative $(-)$
- Current leaving a node is positive $(+)$

@a

$-i_1$


$+i_2$

$+i_3$

@b

$+i_o$


$+i_1$

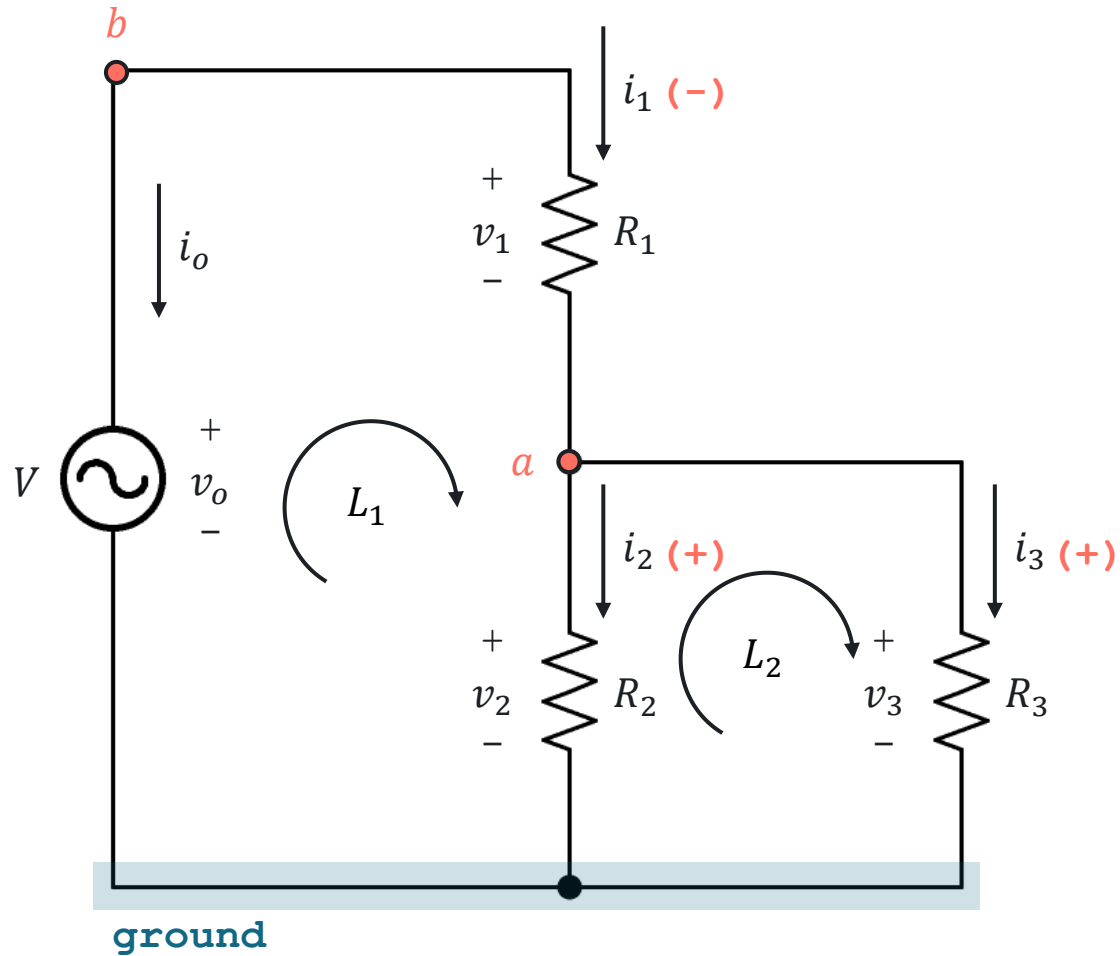

CIRCUIT CONVENTION

Voltage Loop Convention

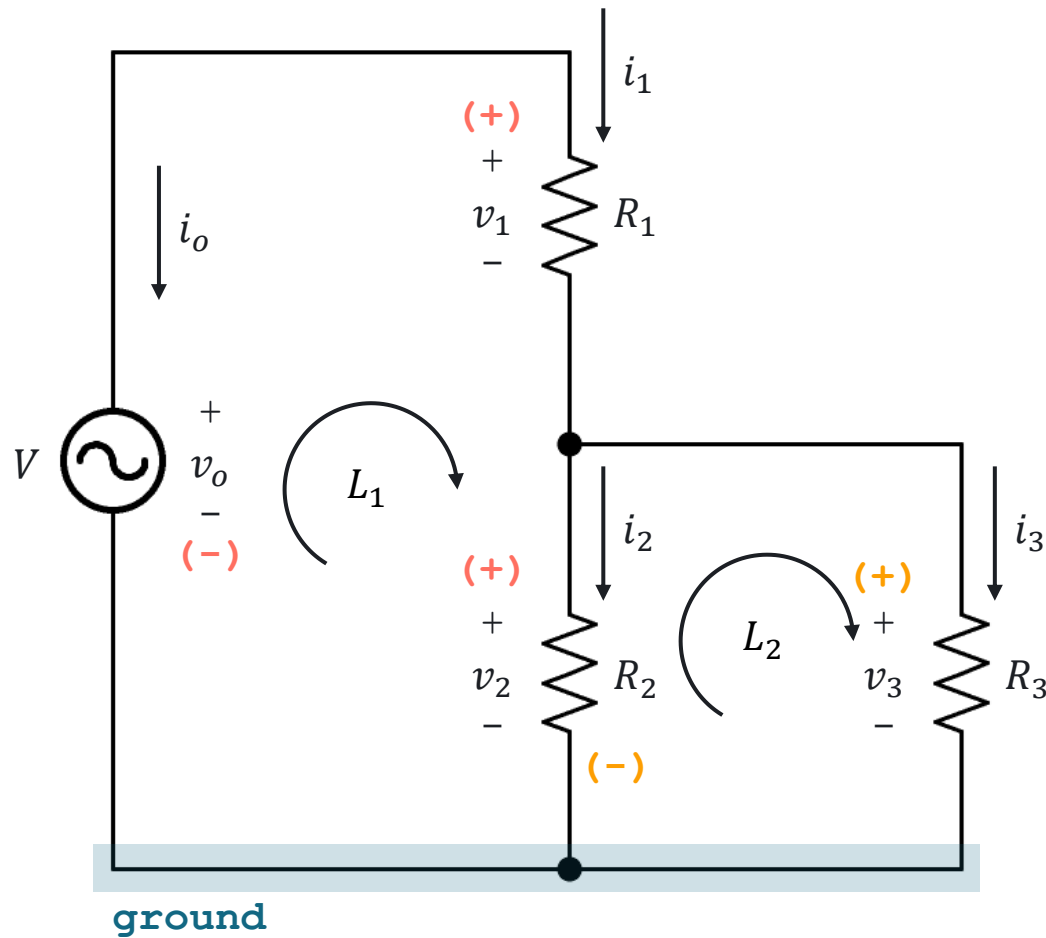The “sign” of voltage of the element is the first sign the loop encounters.



@ L_1

$-v_o$

$+v_1$

$+v_2$

@ L_2

$-v_2$

$+v_3$



KIRCHHOFF'S CURRENT AND VOLTAGE LAW



KIRCHHOFF'S CURRENT LAW

Kirchhoff's current law states that summation of currents going-in and going-out a node is zero.


$$\sum i_j = 0$$

KCL @a

$$-i_1 + i_2 + i_3 = 0$$

KCL @b

$$i_o + i_1 = 0$$

 

KIRCHHOFF'S VOLTAGE LAW

Kirchhoff's voltage law states that the summation of voltages in a closed-loop is zero.


$$\sum v_j = 0$$

KVL @ L_1

$$-v_o + v_1 + v_2 = 0$$

KVL @ L_2


$$-v_2 + v_3 = 0$$

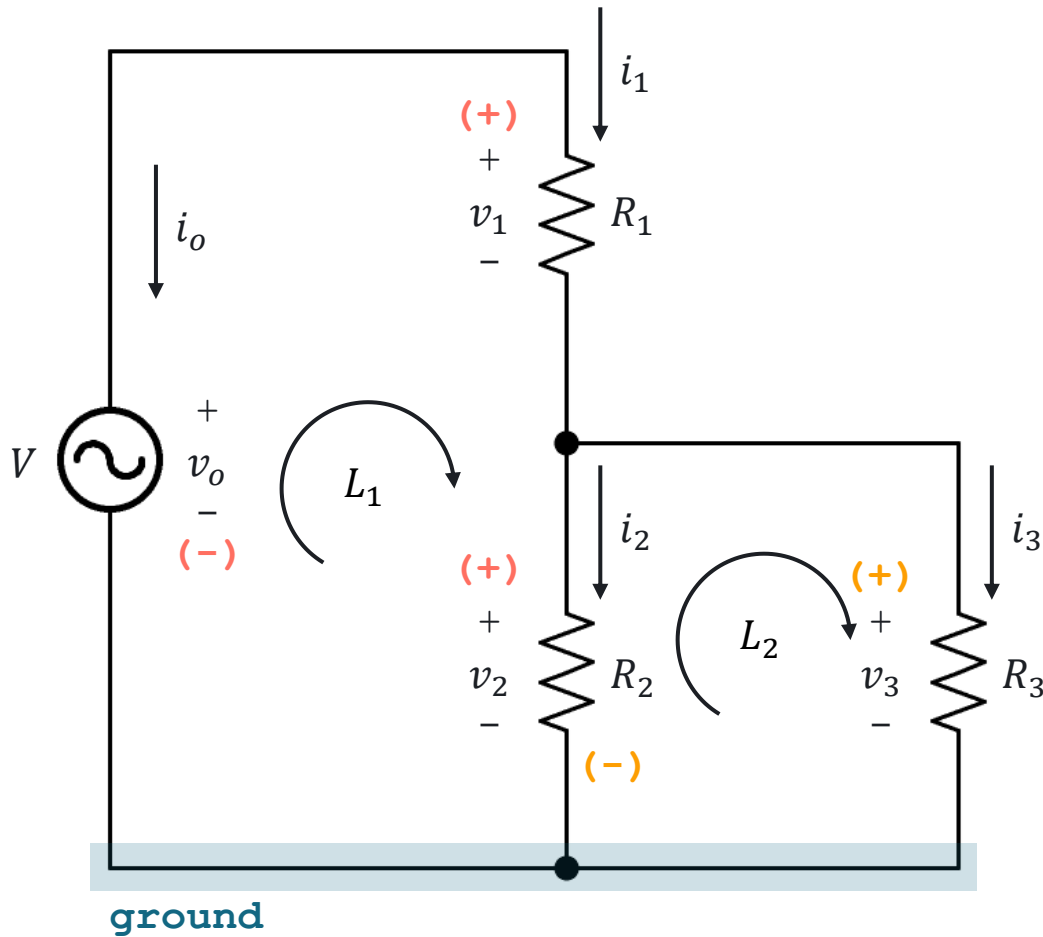

EXERCISE

Analyze the given circuit to determine both the current through and the voltage drop across each resistor.


Solution

 

EXERCISE

Determine the voltage drop across the load resistor and the current flowing through it.

Solution

 

LABORATORY

