

# SYNTHESIS OF LOGIC FUNCTIONS

## COMBINATIONAL LOGIC CIRCUITS

---

*prepared by:*

**Gyro A. Madrona**

Electronics Engineer

## TOPIC OUTLINE

Synthesis of XOR/XNOR Gate

Synthesis of BCD-to-7-Segment Decoder




# SYNTHESIS OF XOR/XNOR GATE



# EXCLUSIVE-OR GATE


## Logic Symbol

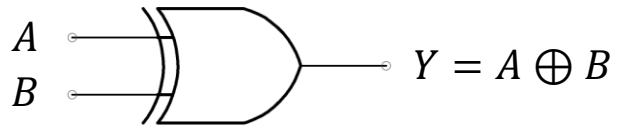

## Truth Table

$A$	$B$	$Y$	Minterm
0	0	0	
0	1	1	
1	0	1	
1	1	0	

## Equivalent Logic Circuit

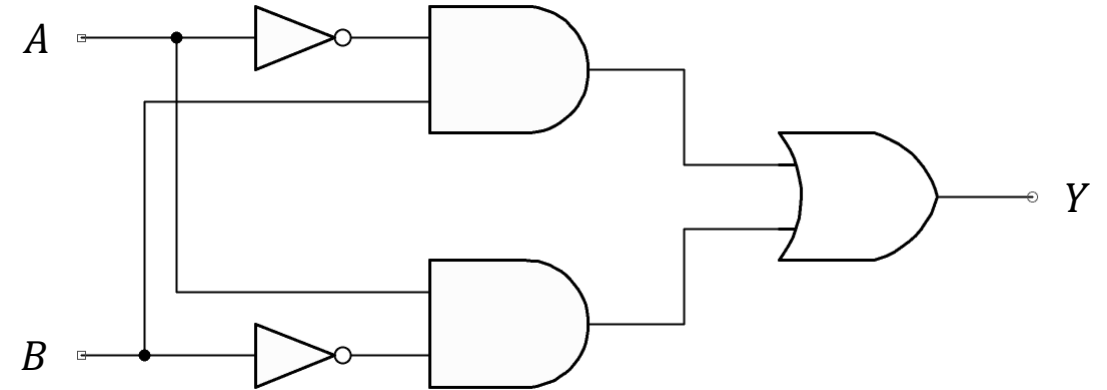


$$Y = \bar{A}B + A\bar{B}$$



# EXCLUSIVE-NOR GATE


## Logic Symbol

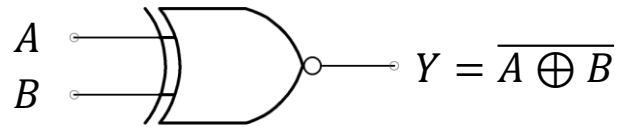

## Truth Table

A	B	Y	Minterm
0	0	1	
0	1	0	
1	0	0	
1	1	1	

## Equivalent Logic Circuit

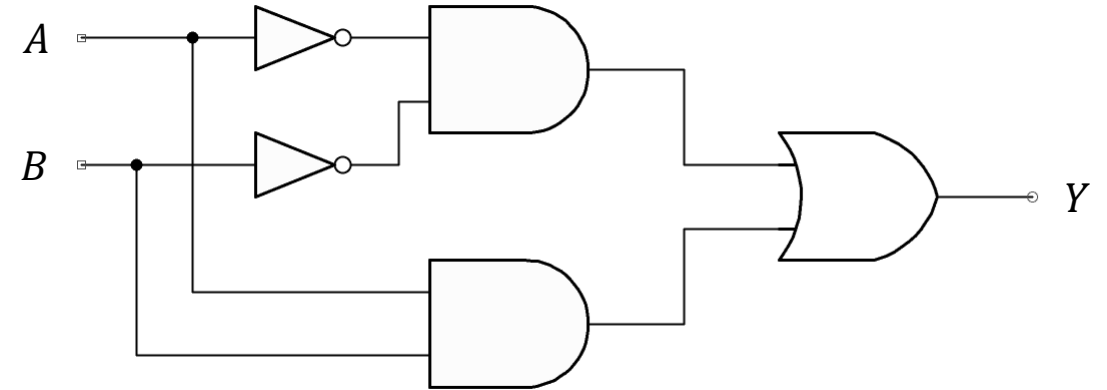

$$Y = \bar{A}\bar{B} + AB$$



## EXERCISE

---

Develop a logic circuit with four input variables that will only produce a 1 output when exactly three input variables are 1s.


Solution



## EXERCISE

Reduce the combinational logic circuit to a minimum form.

Solution

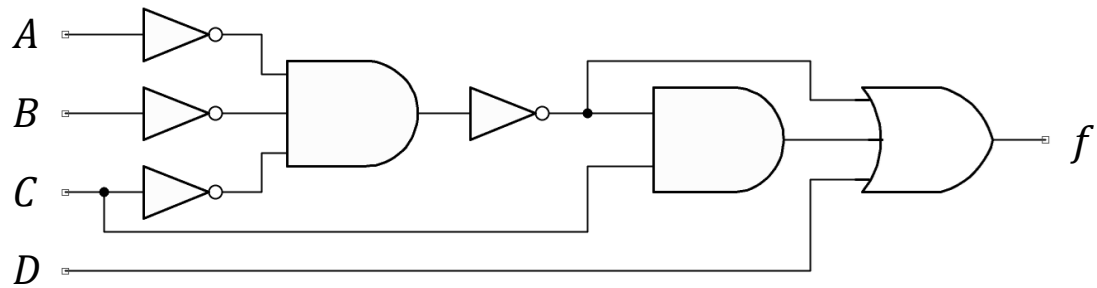

# SYNTHESIS OF BCD-TO- 7-SEGMENT DECODER






# THE 7-SEGMENT DISPLAY

---

A standard 7-segment display consists of seven LEDs (segments) arranged in a rectangular layout to form the number 8. Each segment is labeled from *a* to *g*, and an optional eighth segment (DP) is used for the decimal point.

Segment Arrangement

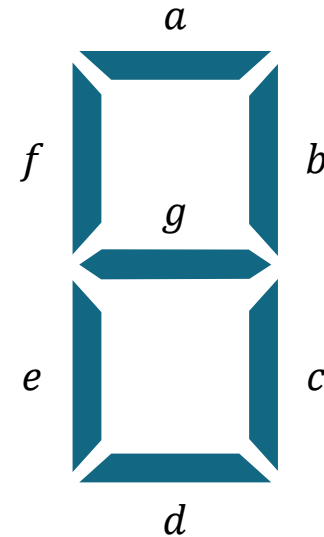


# EXPRESSION FOR SEGMENT A

Truth Table

$N$	$DCBA$	$f_a$
0	0000	
1	0001	
2	0010	
3	0011	
4	0100	
5	0101	
6	0110	
7	0111	
8	1000	

$N$	$DCBA$	$f_a$
9	1001	
10	1010	
11	1011	
12	1100	
13	1101	
14	1110	
15	1111	

Segment Arrangement

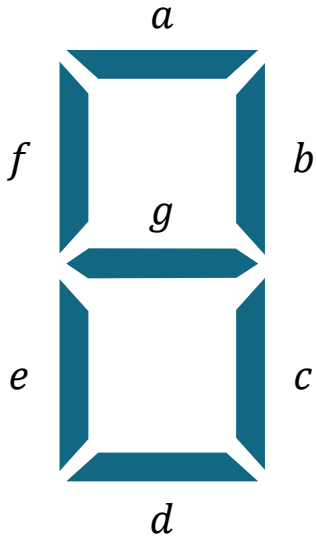

# EXPRESSION FOR SEGMENT A

Truth Table

$N$	$DCBA$	$f_a$
0	0000	
1	0001	
2	0010	
3	0011	
4	0100	
5	0101	
6	0110	
7	0111	
8	1000	

K-Map

$N$	$DCBA$	$f_a$
9	1001	
10	1010	
11	1011	
12	1100	
13	1101	
14	1110	
15	1111	



# EXPRESSION FOR SEGMENT A

Truth Table

$N$	$DCBA$	$f_a$
0	0000	
1	0001	
2	0010	
3	0011	
4	0100	
5	0101	
6	0110	
7	0111	
8	1000	

QM Method

$N$	$DCBA$	$f_a$
9	1001	
10	1010	
11	1011	
12	1100	
13	1101	
14	1110	
15	1111	




## EXERCISE

---

Using Karnaugh Map and the Quine-McCluskey method, synthesize the minimized Boolean expressions for each segment ( $a-g$ ) of a 7-segment display decoder.

Segment Arrangement

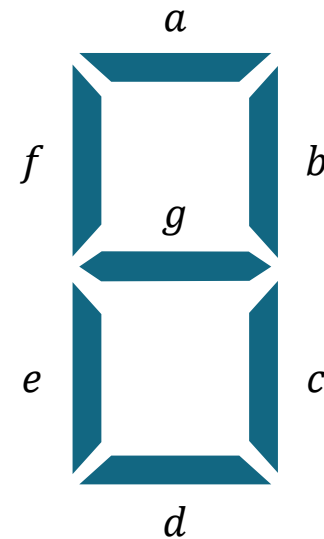

# LABORATORY

