



# **BOOLEAN ALGEBRA**

## **LOGIC MINIMIZATION**

---

*prepared by:*

**Gyro A. Madrona**  
Electronics Engineer

# TOPIC OUTLINE

Laws of Boolean Algebra

Rules of Boolean Algebra

DeMorgan's Theorem



# **LAWS OF BOOLEAN** **ALGEBRA**



# BOOLEAN ALGEBRA

---

Boolean algebra is the mathematics of digital logic. It was formulated by 1874 by George Boole.



George Boole





# COMMUTATIVE LAWS

---


## Commutative law of addition

$$A + B = B + A$$

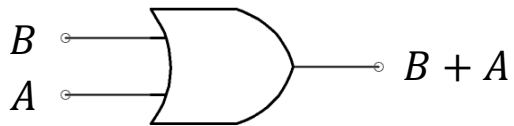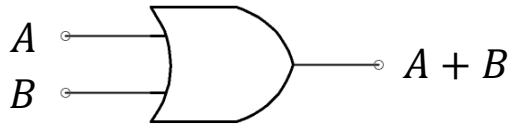

## Commutative law of multiplication



$$AB = BA$$

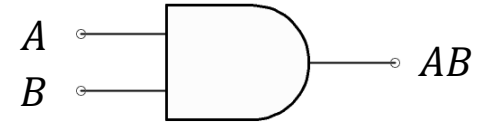

# ASSOCIATIVE LAWS



## Associative law of addition

$$A + (B + C) = (A + B) + C$$

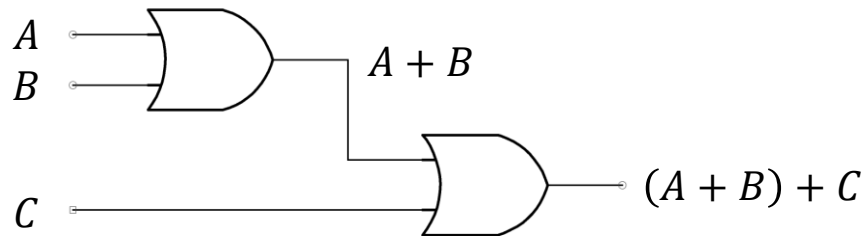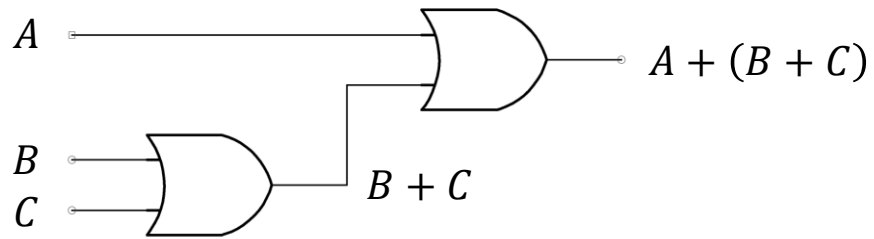

## Associative law of multiplication



$$A(BC) = (AB)C$$

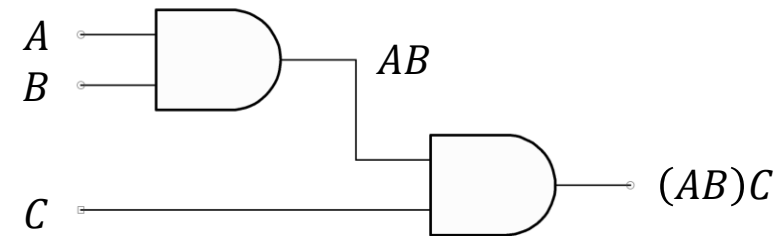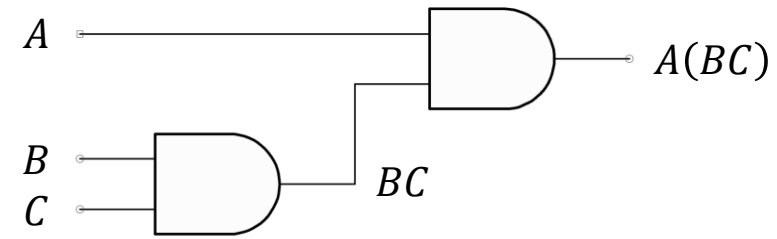

# DISTRIBUTIVE LAW

Distributive law

$$A(B + C) = AB + AC$$

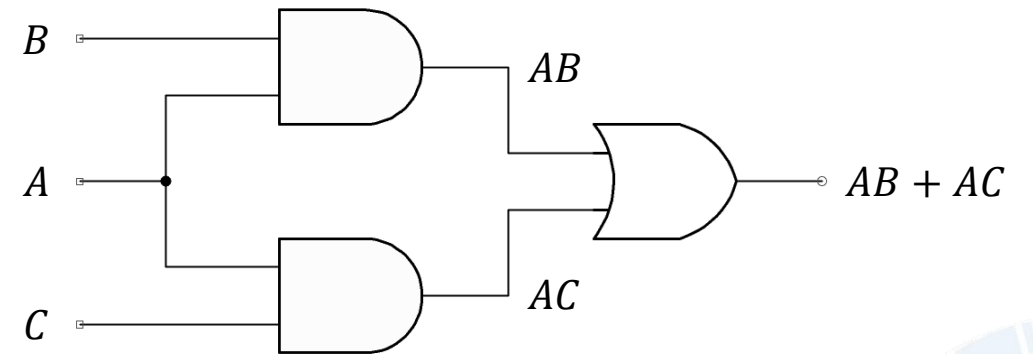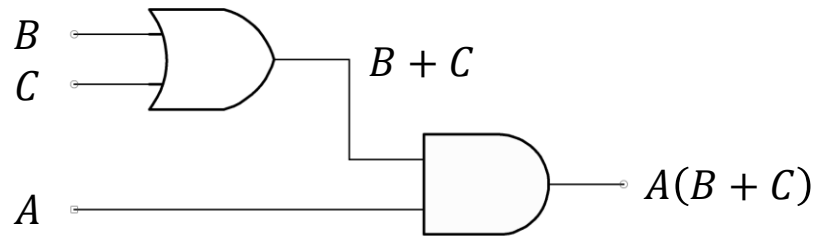

# RULES OF BOOLEAN ALGEBRA





# BASIC RULES OF BOOLEAN ALGEBRA

---

Basic rules of Boolean algebra are useful in manipulating and simplifying Boolean expressions.

## Basic rules of Boolean algebra

1.  $A + 0 = A$

2.  $A + 1 = 1$

3.  $A \cdot 0 = 0$

4.  $A \cdot 1 = A$

5.  $A + A = A$

6.  $A + \bar{A} = 1$

7.  $A \cdot A = A$

8.  $A \cdot \bar{A} = 0$

9.  $\bar{\bar{A}} = A$

10.  $A + AB = A$

11.  $A + \bar{A}B = A + B$

12.  $(A + B)(A + C) = A + BC$




## RULE 1 AND 2

---


Rule 1:  $A + 0 = A$

A variable Ored with 0 is always equal to the variable.

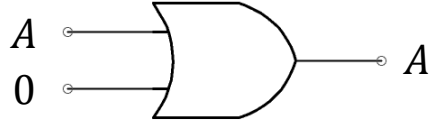

Rule 2:  $A + 1 = 1$

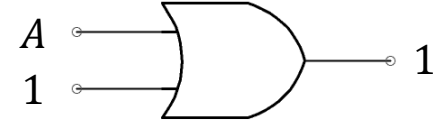A variable Ored with 1 is always equal to 1.




## RULE 3 AND 4

---


Rule 3:  $A \cdot 0 = 0$

A variable ANDed with 0 is always equal to 0

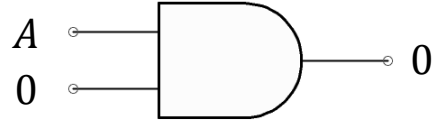

Rule 4:  $A \cdot 1 = A$

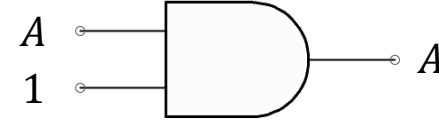A variable ANDed with 1 is always equal to the variable.




## RULE 5 AND 6

---


Rule 5:  $A + A = A$

A variable ORed with itself is always equal to the variable.

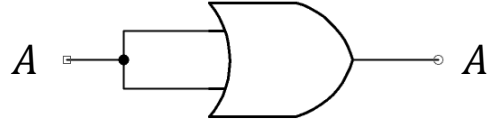

Rule 6:  $A + \bar{A} = 1$

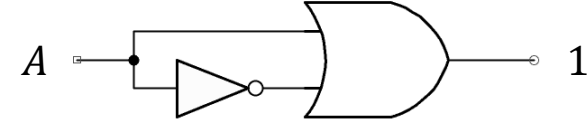A variable ORed with its complement is always equal to 1.




## RULE 7 AND 8

---


Rule 7:  $A \cdot A = A$

A variable ANDed with itself is always equal to the variable.

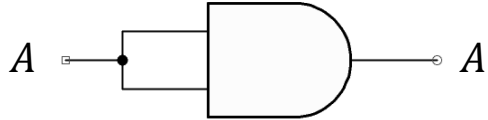

Rule 8:  $A \cdot \bar{A} = 0$

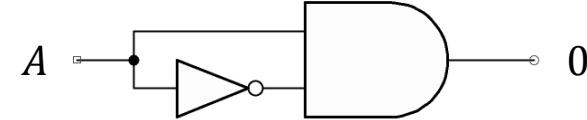
A variable ANDed with its complement is always equal to 0.



## RULE 9 AND 10

Rule 9:  $\overline{\overline{A}} = A$

A double complement of a variable is always equal to the variable.

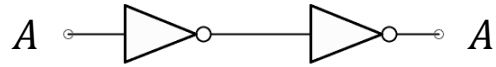


Rule 10:  $A + AB = A$

$$A + AB = A \cdot 1 + AB$$

$$= A + (1 + B)$$

$$= A + 1$$

$$= A$$


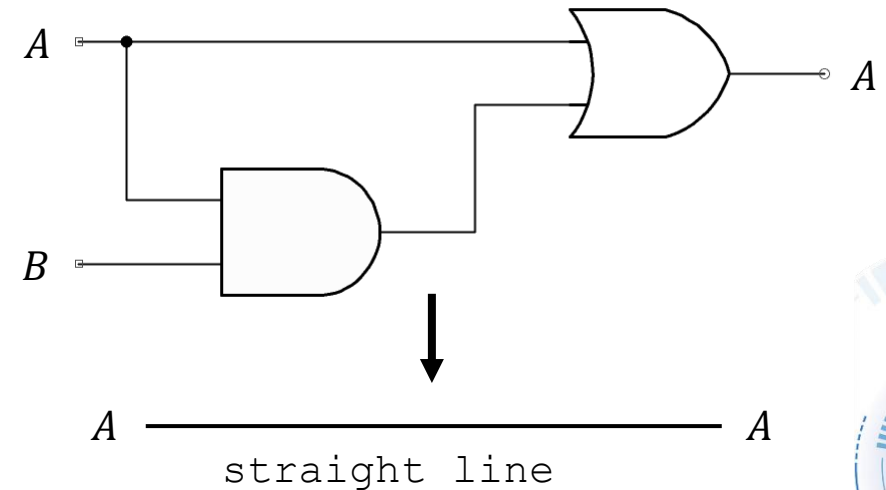


## RULE 11

---

Rule 11:  $A + \bar{A}B = A + B$
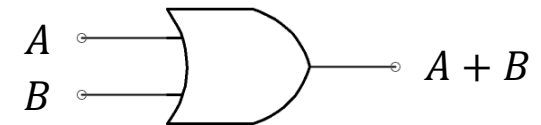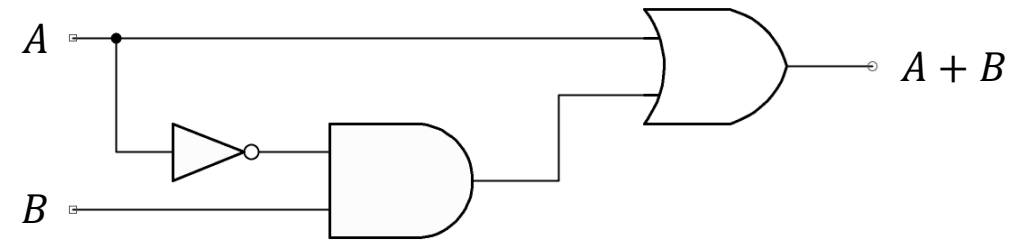
$$\begin{aligned} A + \bar{A}B &= (A + AB) + \bar{A}B \\ &= (AA + AB) + \bar{A}B \\ &= AA + AB + A\bar{A} + \bar{A}B \\ &= (A + \bar{A})(A + B) \\ &= 1 \cdot (A + B) \\ &= A + B \end{aligned}$$



## RULE 12


Rule 12:  $(A + B)(A + C) = A + BC$

$$(A + B)(A + C) = AA + AC + AB + BC$$

$$= A + AC + AB + BC$$

$$= A + AB + BC$$

$$= A + BC$$

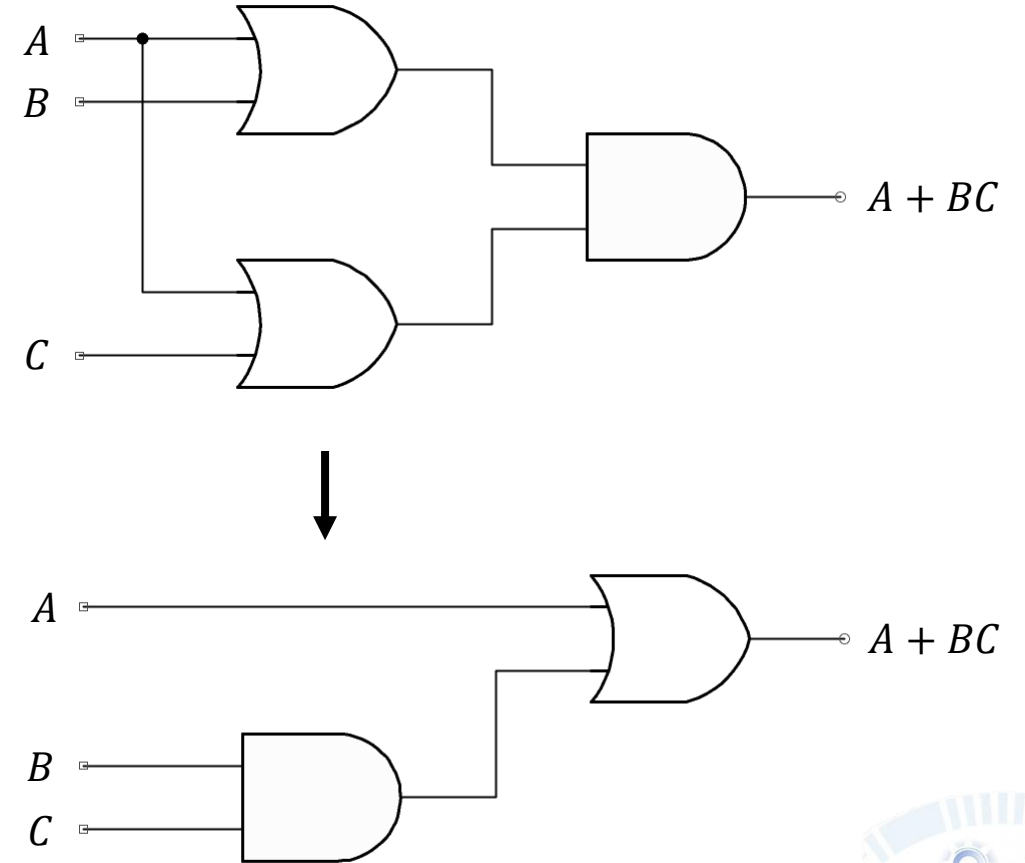



# DEMORGAN'S THEOREMS



# FIRST THEOREM

DeMorgan's first theorem states that the complement of a product of variables is equal to the sum of the complements of the variables.

Logic Expression

$$\overline{XY} = \bar{X} + \bar{Y}$$


Truth Table

$X$	$Y$	$\overline{XY}$	$\bar{X} + \bar{Y}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

NAND



Negative-OR

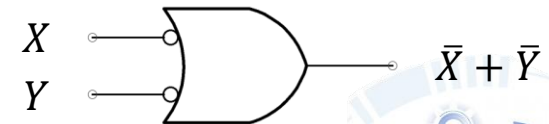

## SECOND THEOREM

DeMorgan's second theorem states that the complement of a sum of variables is equal to the product of the complements of the variables.


Logic expression

$$\overline{X + Y} = \bar{X} \cdot \bar{Y}$$


Truth Table

$X$	$Y$	$\overline{X + Y}$	$\bar{X} \cdot \bar{Y}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

NOR

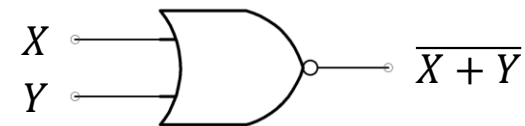

Negative-AND

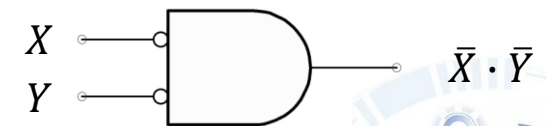

## EXERCISE

---

Apply DeMorgan's theorems to the expression:

$$f = \overline{(A + B)C}$$

Solution



## EXERCISE

---

Simplify the Boolean expression:

$$f = AB + A(B + C) + B(B + C)$$

Solution



## EXERCISE

---

Simplify the Boolean expression:

$$f = [A\bar{B}(C + BD) + \bar{A}\bar{B}]C$$

Solution



## EXERCISE

---

Apply DeMorgan's theorems to the expression:

$$f = \overline{(\bar{A} + B) + CD}$$

Solution



## EXERCISE

---

Simplify the Boolean expression:

$$f = A\bar{B} + A(\overline{B + C}) + B(\overline{B + C})$$

Solution





# LABORATORY

