



NODE ANALYSIS METHOD

BASIC CIRCUIT ANALYSIS METHOD

prepared by:

Gyro A. Madrona
Electronics Engineer

TOPIC OUTLINE

Node Voltage


Node Analysis Method



NODE ANALYSIS METHOD



NODE VOLTAGE

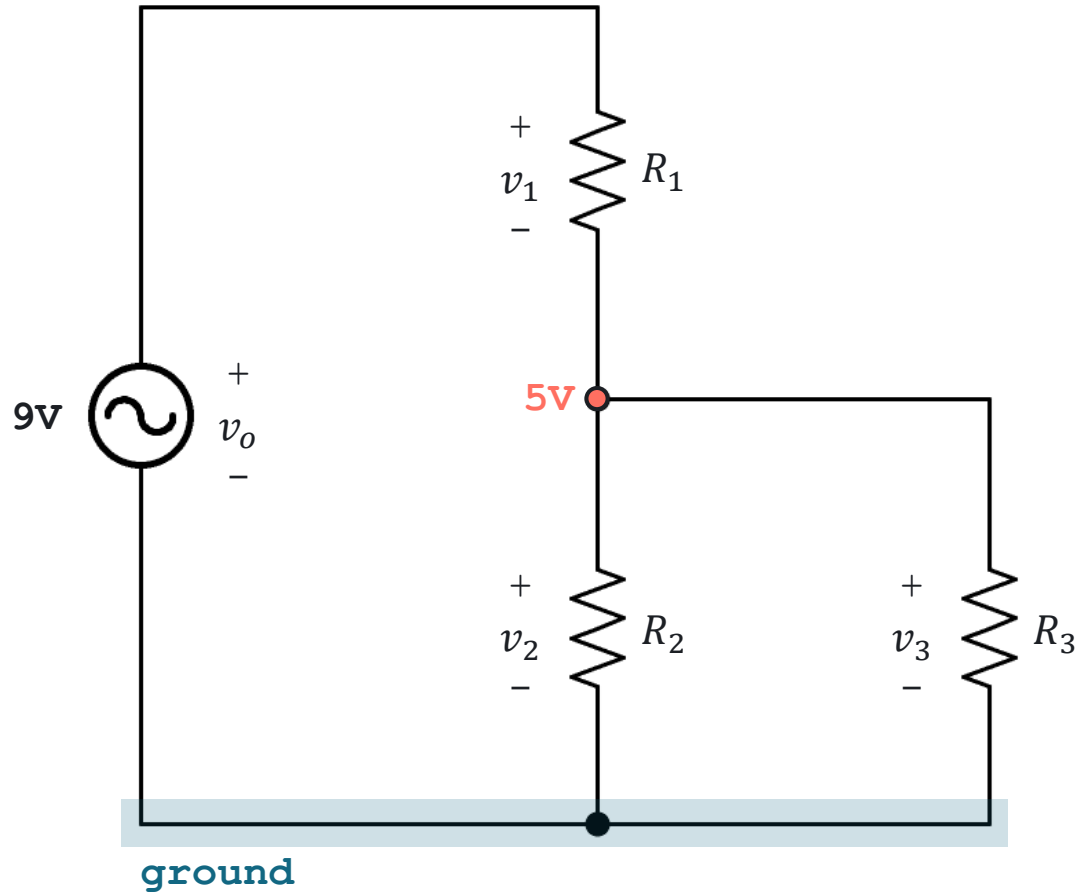

Node Voltage is the electrical potential difference at a specific node in a circuit relative to a reference node.

example


$$v_1 = 9V - 5V$$

$$v_2 = 5V - 0$$

$$v_3 = 5V - 0$$




NODE ANALYSIS METHOD

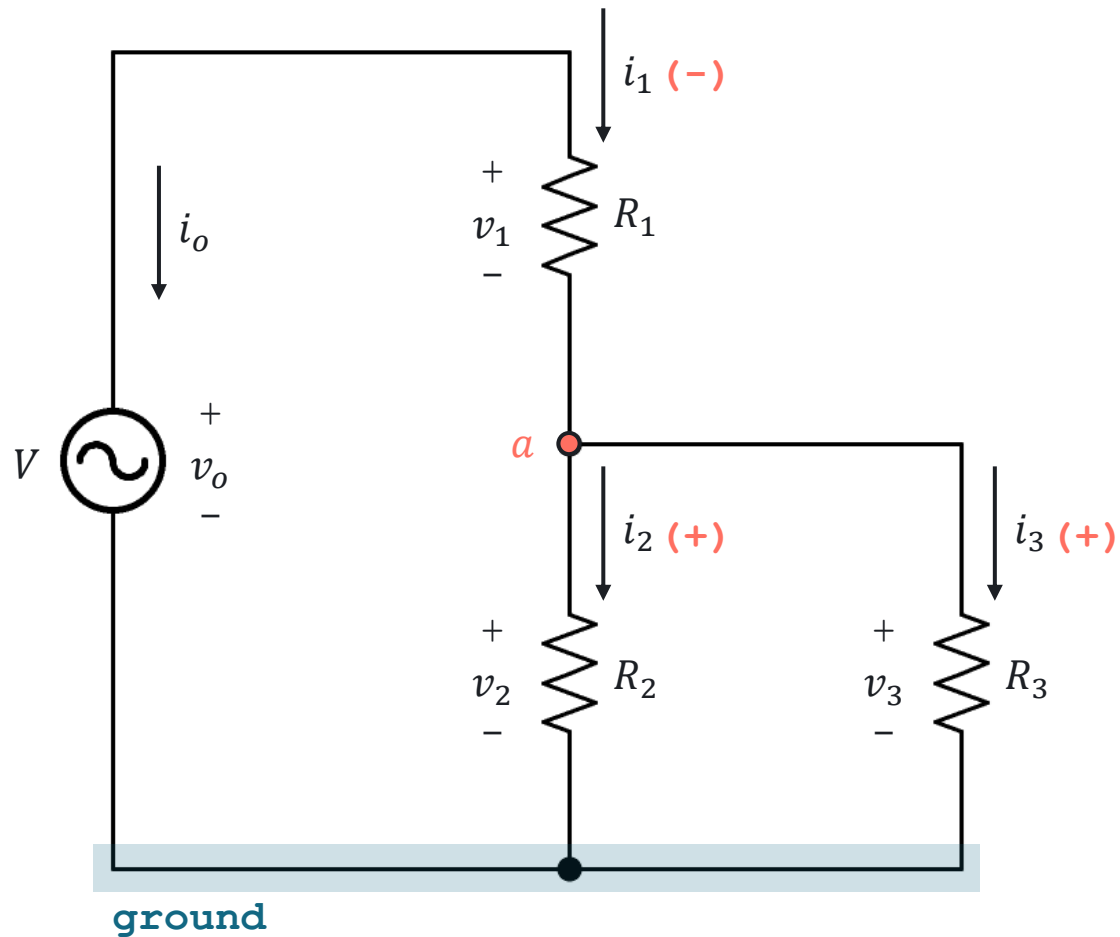

The node analysis method is based on Kirchhoff's current law (KCL), which is implicitly applied to establish voltage-current relationships forming a system of equations to be solved for the unknown node voltages.



NODE ANALYSIS METHOD

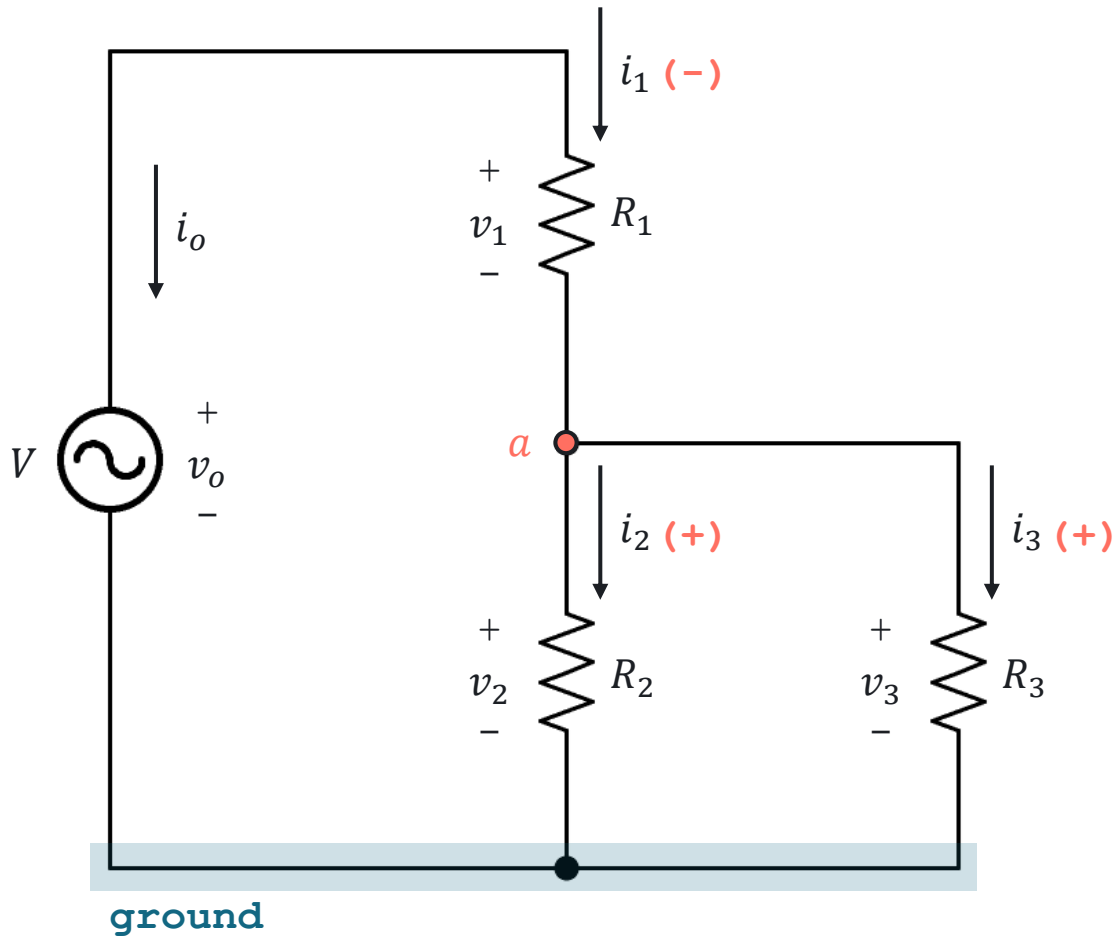

KCL @a

$$-i_1 + i_2 + i_3 = 0$$

$$-\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} = 0$$

$$-\frac{v_o - v_a}{R_1} + \frac{v_a - 0}{R_2} + \frac{v_a - 0}{R_3} = 0$$

$$-v_o G_1 + v_a G_1 + v_a G_2 + v_a G_3 = 0$$

$$v_a (G_1 + G_2 + G_3) = v_o G_1$$

$$v_a = \frac{v_o G_1}{G_1 + G_2 + G_3}$$



ELECTRICAL POWER

Electrical power refers to the rate at which electrical energy is converted per unit time (joules/second).

Formulas


$$P = vi$$

$$P = i^2 R$$

$$P = \frac{v^2}{R}$$


$$P_o = P_1 + P_2 + P_3 + \cdots P_n$$

unit: Watt (W)

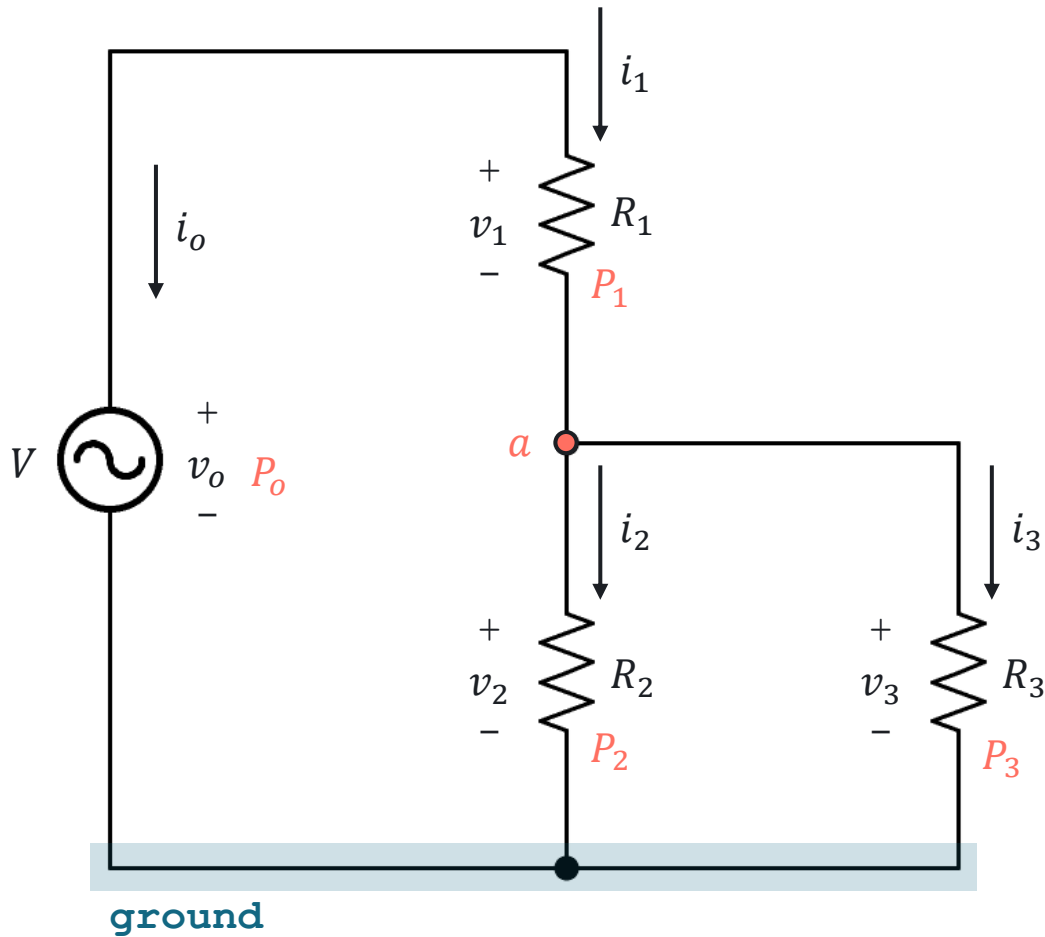

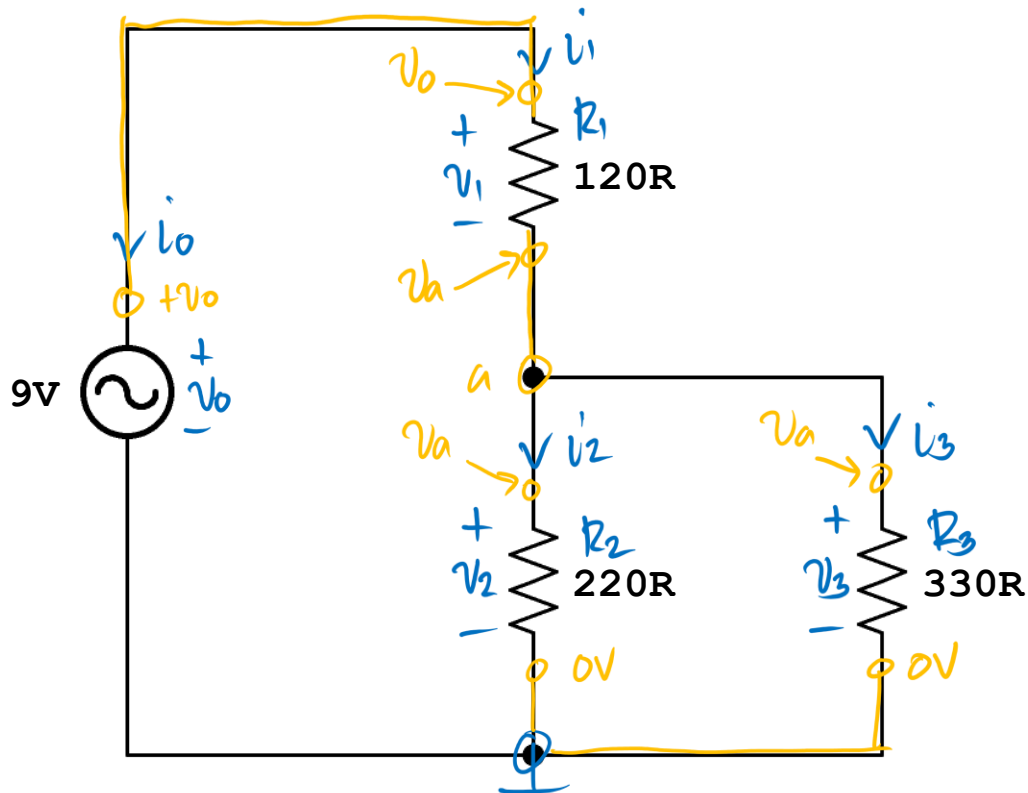EXERCISE

Determine the current through and voltage across each resistor, as well as the total power of the given circuit.



Solution

KCL @ a

$$-i_1 + i_2 + i_3 = 0$$

$$-\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} = 0$$

$$-v_1 G_1 + v_2 G_2 + v_3 G_3 = 0$$

$$-(v_0 - v_a) G_1 + (v_a - 0) G_2 + (v_a - 0) G_3 = 0$$

$$-v_0 G_1 + v_a G_1 + v_a G_2 + v_a G_3 = 0$$


factor out v_a

$$\frac{v_a (G_1 + G_2 + G_3)}{G_1 + G_2 + G_3} = \frac{v_0 G_1}{G_1 + G_2 + G_3}$$

$$v_a = \frac{v_0 G_1}{G_1 + G_2 + G_3}$$

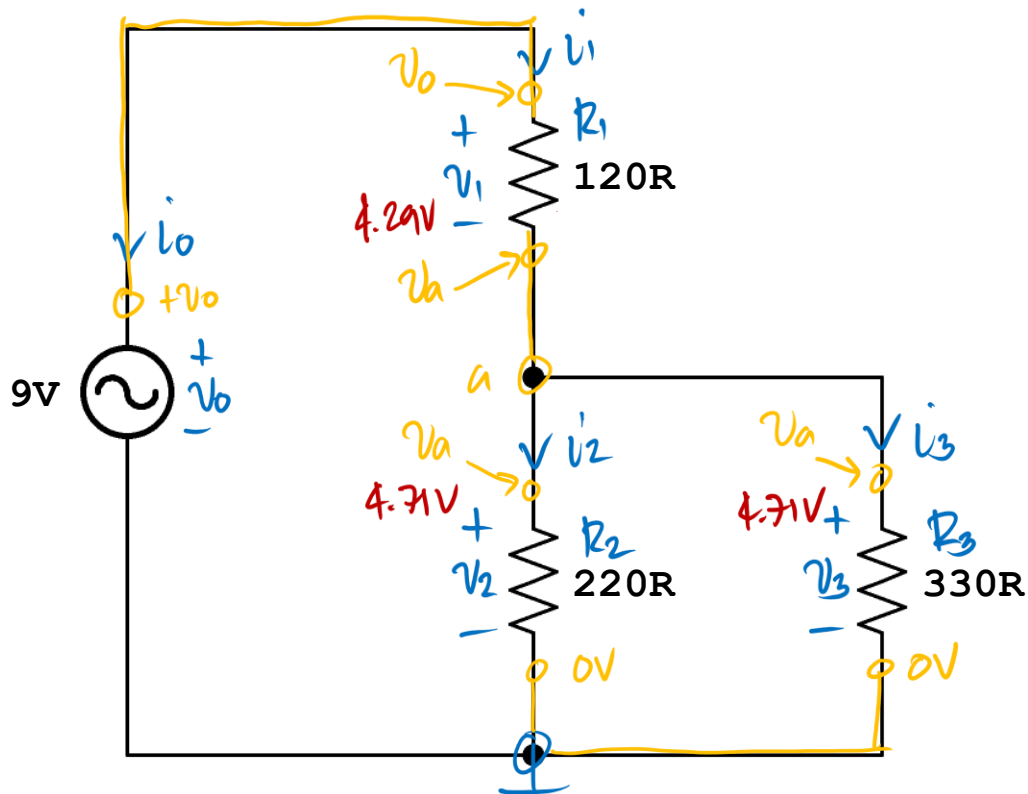EXERCISE

Determine the current through and voltage across each resistor, as well as the total power of the given circuit.



Solution

$$V_a = \frac{V_0 G_1}{G_1 + G_2 + G_3}$$
$$V_a = \frac{9 \left(\frac{1}{120} \right)}{\frac{1}{120} + \frac{1}{220} + \frac{1}{330}}$$

$$\underline{V_a = 4.71 \text{ V}}$$

$$V_1 = V_0 - V_a$$

$$V_1 = 9 - 4.71$$

$$\boxed{V_1 = 4.29 \text{ V}}$$

ans

$$V_2 = V_a - 0$$

$$\boxed{V_2 = 4.71 \text{ V}}$$

ans


$$V_3 = V_a - 0$$

$$\boxed{V_3 = 4.71 \text{ V}}$$

ans

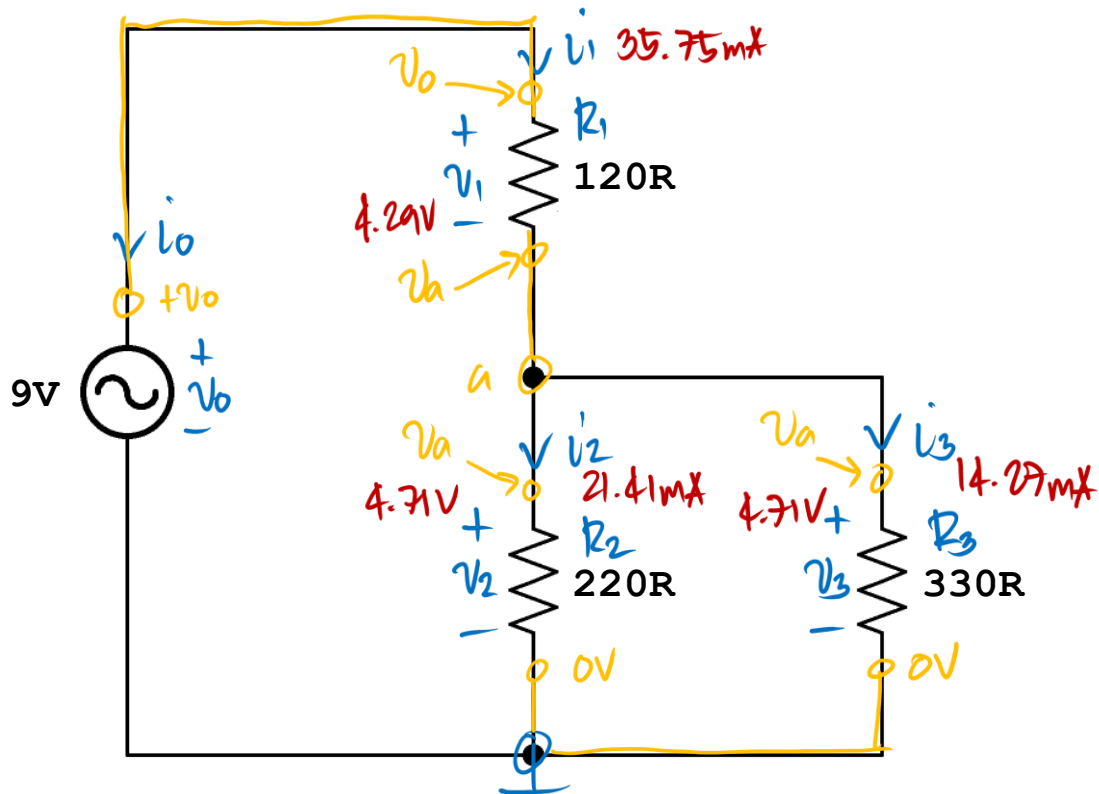EXERCISE

Determine the current through and voltage across each resistor, as well as the total power of the given circuit.



Solution

$$i_1 = \frac{v_1}{R_1}$$

$$i_1 = \frac{4.29}{120}$$

$$i_1 = 35.75 \text{ mA}$$

ans

$$i_2 = \frac{v_2}{R_2}$$

$$i_2 = \frac{4.71}{220}$$

$$i_2 = 21.41 \text{ mA}$$

ans

$$i_3 = \frac{v_3}{R_3}$$

$$i_3 = \frac{4.71}{330}$$


$$i_3 = 14.27 \text{ mA}$$

ans



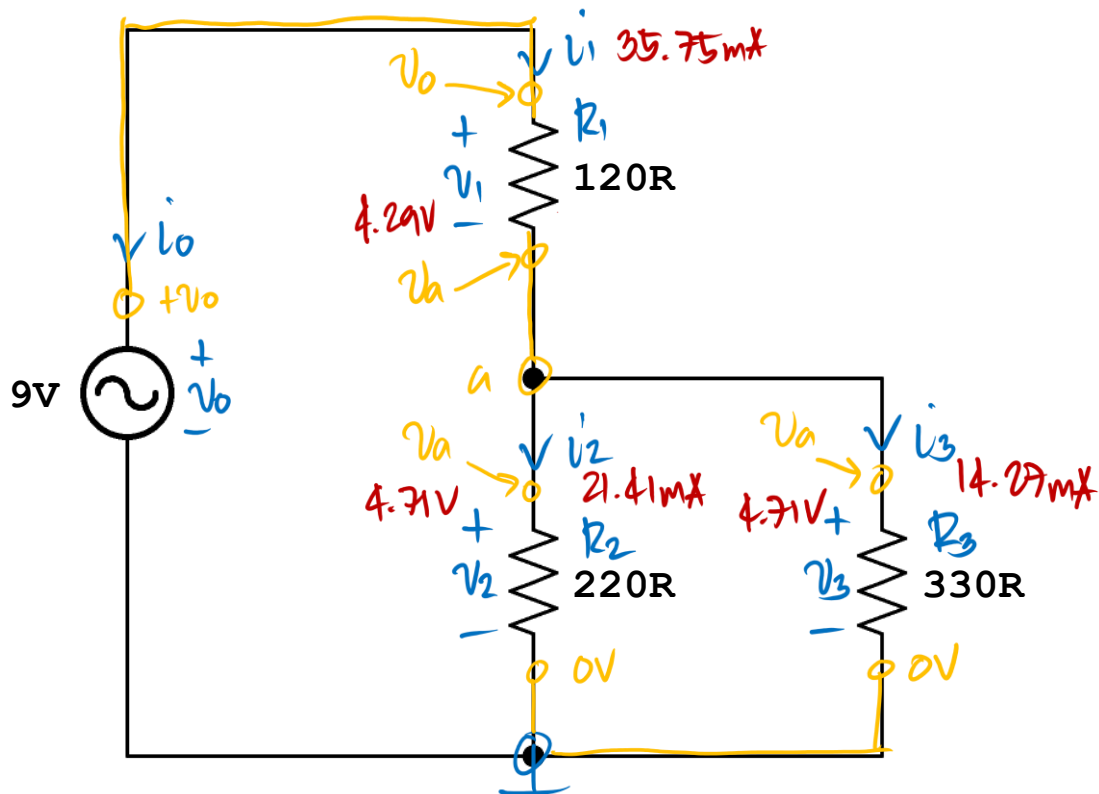EXERCISE

Determine the current through and voltage across each resistor, as well as the total power of the given circuit.



Solution

$$P_1 = i_1 v_1$$

$$P_1 = 35.75\text{m} (4.29)$$

$$P_1 = 153.37\text{mW}$$

$$P_2 = i_2 v_2$$

$$P_2 = 21.41\text{m} (4.71)$$

$$P_2 = 100.84\text{mW}$$

Total Power

$$P_0 = P_1 + P_2 + P_3$$

$$P_0 = 153.37 + 100.84 + 67.21$$

$$P_0 = 321.42\text{mW}$$

ans


$$P_3 = i_3 v_3$$

$$P_3 = 14.27\text{m} (4.71)$$

$$P_3 = 67.21\text{mW}$$

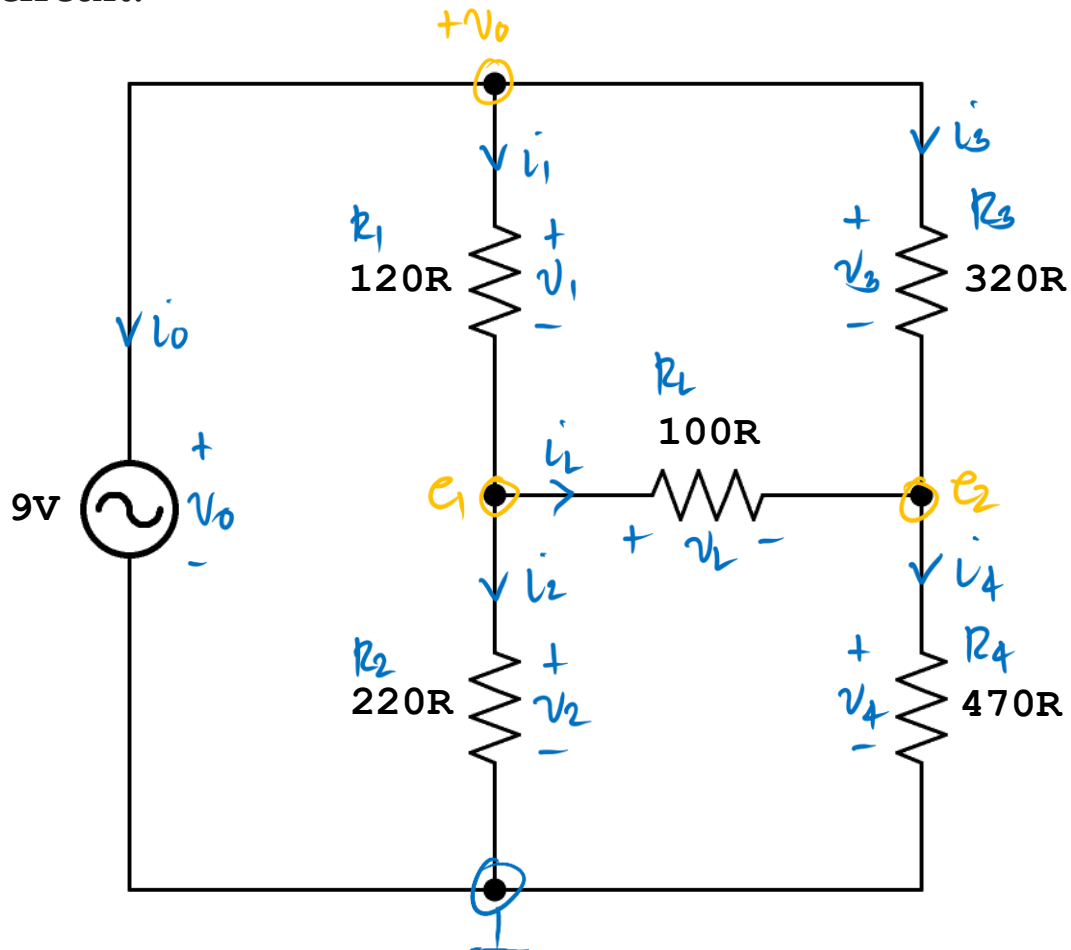EXERCISE

Determine the current through and voltage across each resistor, as well as the total power of the given circuit.



Solution

KCL @ e_1

$$-i_1 + i_2 + i_L = 0$$

$$-\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_L}{R_L} = 0$$

$$-\frac{v_0 - e_1}{R_1} + \frac{e_1}{R_2} + \frac{e_1 - e_2}{R_L} = 0$$


$$-\frac{v_0}{R_1} + \frac{e_1}{R_1} + \frac{e_1}{R_2} + \frac{e_1}{R_L} - \frac{e_2}{R_L} = 0$$

$$-v_0 G_1 + e_1 G_1 + e_1 G_2 + e_1 G_L - e_2 G_L = 0$$

$$e_1(G_1 + G_2 + G_L) - e_2 G_L = v_0 G_1 \quad (\text{eq. 1})$$

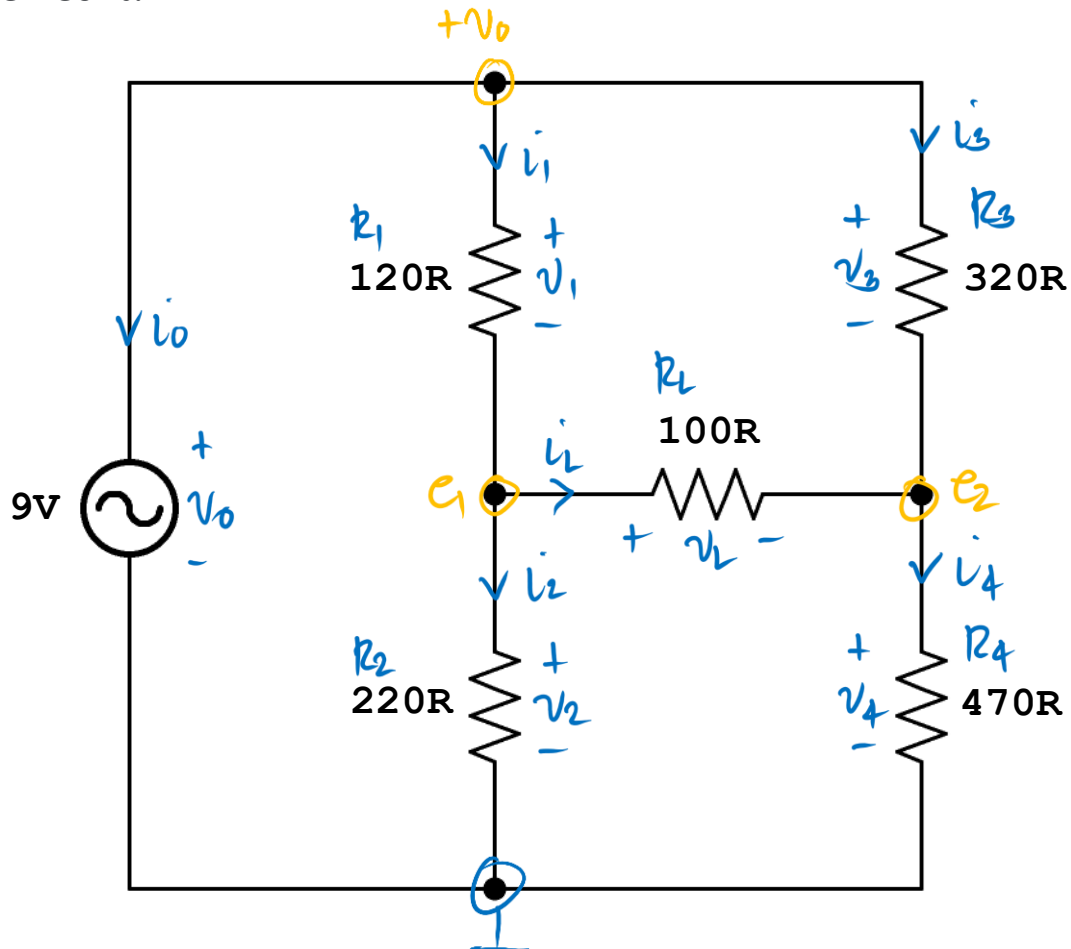EXERCISE

Determine the current through and voltage across each resistor, as well as the total power of the given circuit.



Solution

KCL @ e_2

$$-i_3 + i_4 - i_L = 0$$

$$-\frac{v_3}{R_3} + \frac{v_4}{R_4} - \frac{v_L}{R_L} = 0$$

$$-\frac{v_0 - e_2}{R_3} + \frac{e_2}{R_4} - \frac{e_1 - e_2}{R_L} = 0$$

$$-\frac{v_0}{R_3} + \frac{e_2}{R_3} + \frac{e_2}{R_4} - \frac{e_1}{R_L} + \frac{e_2}{R_L} = 0$$

$$-v_0 G_3 + e_2 G_3 + e_2 G_4 - e_1 G_L + e_2 G_L = 0$$

$$-e_1 G_L + e_2 (G_3 + G_4 + G_L) = v_0 G_3 \quad (\text{eq. 2})$$

EXERCISE

Gaussian Elimination Method

e_1	e_2		
$\frac{151}{66}$	-1	7.5	r_1
-1	$\frac{1147}{752}$	$\frac{45}{16}$	$r_2 \leftarrow \frac{66}{151} r_1 + r_2$

e_1	e_2		
$\frac{151}{66}$	-1	7.5	r_1
0	1.0882	6.091	r_2

System of Linear Equations

$$e_1(\cancel{\frac{1}{120}} + \cancel{\frac{1}{200}} + \cancel{\frac{1}{10}}) - e_2\cancel{\frac{1}{100}} = \cancel{20} \cancel{61} \quad (\text{eq. 1})$$

$$-e_1\cancel{\frac{1}{100}} + e_2(\cancel{\frac{1}{320}} + \cancel{\frac{1}{470}} + \cancel{\frac{1}{100}}) = \cancel{20} \cancel{63} \quad (\text{eq. 2})$$

$$100 \left[\frac{151}{6600} e_1 - \frac{1}{100} e_2 = \frac{3}{40} \right] \quad (\text{eq. 1})$$

$$\frac{151}{66} e_1 - e_2 = 7.5$$

$$100 \left[-\frac{1}{100} e_1 + \frac{1147}{75200} e_2 = \frac{9}{320} \right] \quad (\text{eq. 2})$$

$$-e_1 + \frac{1147}{752} e_2 = \frac{45}{16}$$



EXERCISE

Gaussian Elimination Method

e_1	e_2		
$\frac{151}{66}$	-1	7.5	r_1
-1	$\frac{1147}{752}$	$\frac{45}{16}$	$r_2 \leftarrow \frac{66}{151} r_1 + r_2$

e_1	e_2		
$\frac{151}{66}$	-1	7.5	r_1
0	1.0882	6.091	r_2

System of Linear Equations

from r_2

$$\frac{1.0882 e_2 = 6.091}{1.0882}$$

$$e_2 = 5.597 \text{ V}$$

from r_1

$$\frac{151}{66} e_1 - \cancel{e_2} = 7.5$$


$$e_1 = (7.5 + 5.597) \frac{66}{151}$$

$$e_1 = 5.725 \text{ V}$$



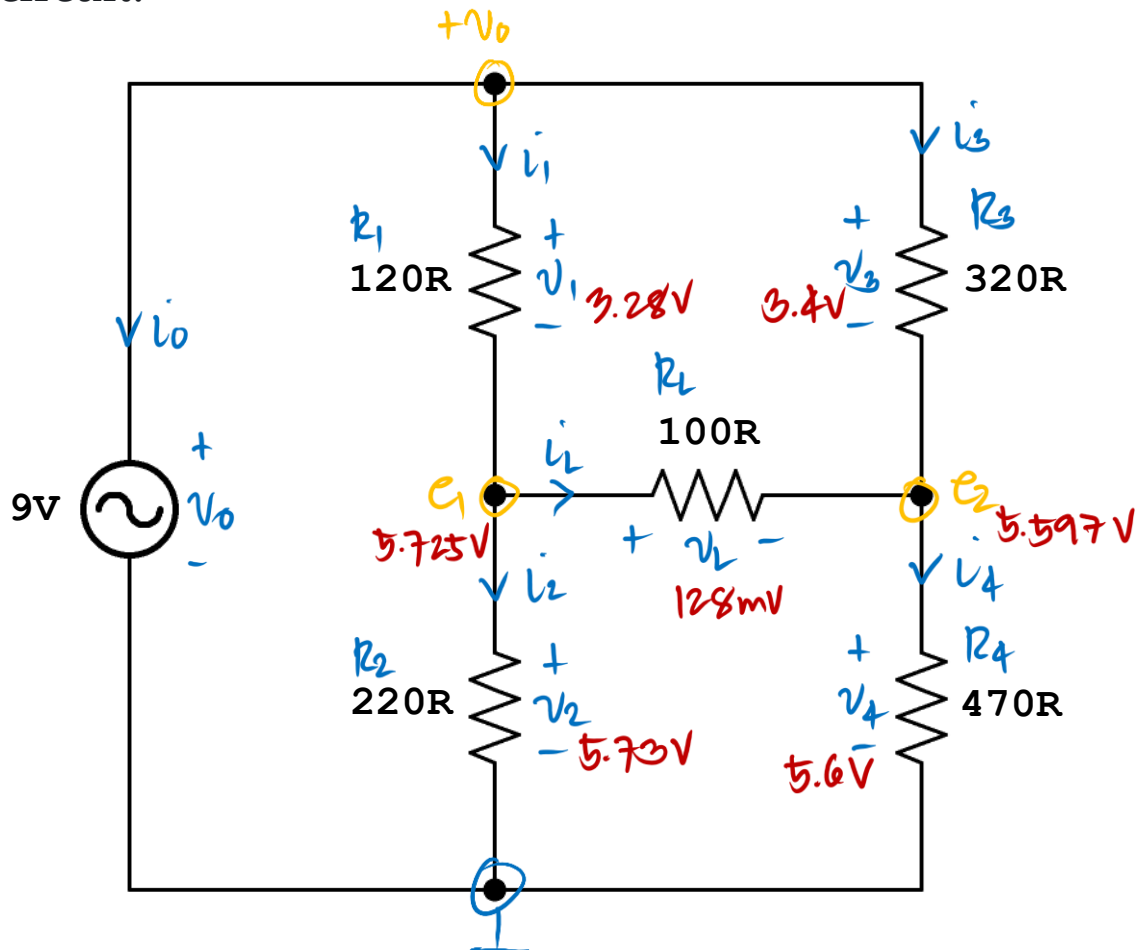EXERCISE

Determine the current through and voltage across each resistor, as well as the total power of the given circuit.



Solution

$$v_L = e_1 - e_2$$

$$v_L = 5.725 - 5.597$$

$$v_L = 128 \text{ mV}$$

ans

$$v_1 = v_0 - e_1$$

$$v_1 = 9 - 5.725$$

$$v_1 = 3.28 \text{ V}$$

ans

$$v_2 = e_1 - 0$$

$$v_2 = 5.73 \text{ V}$$

ans

$$v_3 = v_0 - e_2$$

$$v_3 = 9 - 5.597$$

$$v_3 = 3.4 \text{ V}$$

ans

$$v_4 = e_2 - 0$$


$$v_4 = 5.6 \text{ V}$$

ans



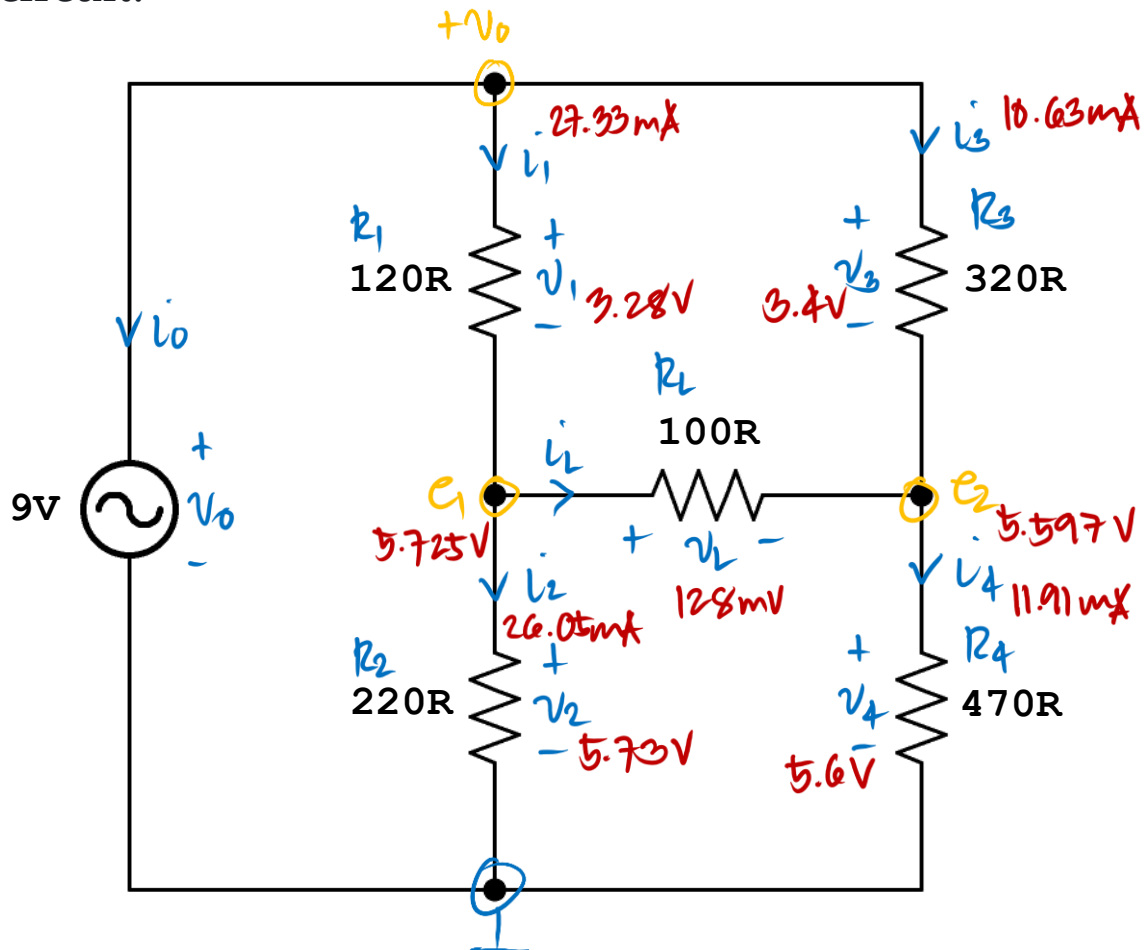EXERCISE

Determine the current through and voltage across each resistor, as well as the total power of the given circuit.



Solution

$$i_1 = \frac{v_1}{R_1}$$

$$i_1 = \frac{3.28}{120}$$

$$i_1 = 27.33 \text{ mA}$$

ans

$$i_2 = \frac{v_2}{R_2}$$

$$i_2 = \frac{5.73}{220}$$

$$i_2 = 26.05 \text{ mA}$$

ans

$$i_3 = \frac{v_3}{R_3}$$

$$i_3 = \frac{3.4}{320}$$

$$i_3 = 10.63 \text{ mA}$$

ans

$$i_4 = \frac{v_4}{R_4}$$


$$i_4 = \frac{5.6}{470}$$

$$i_4 = 11.91 \text{ mA}$$

ans

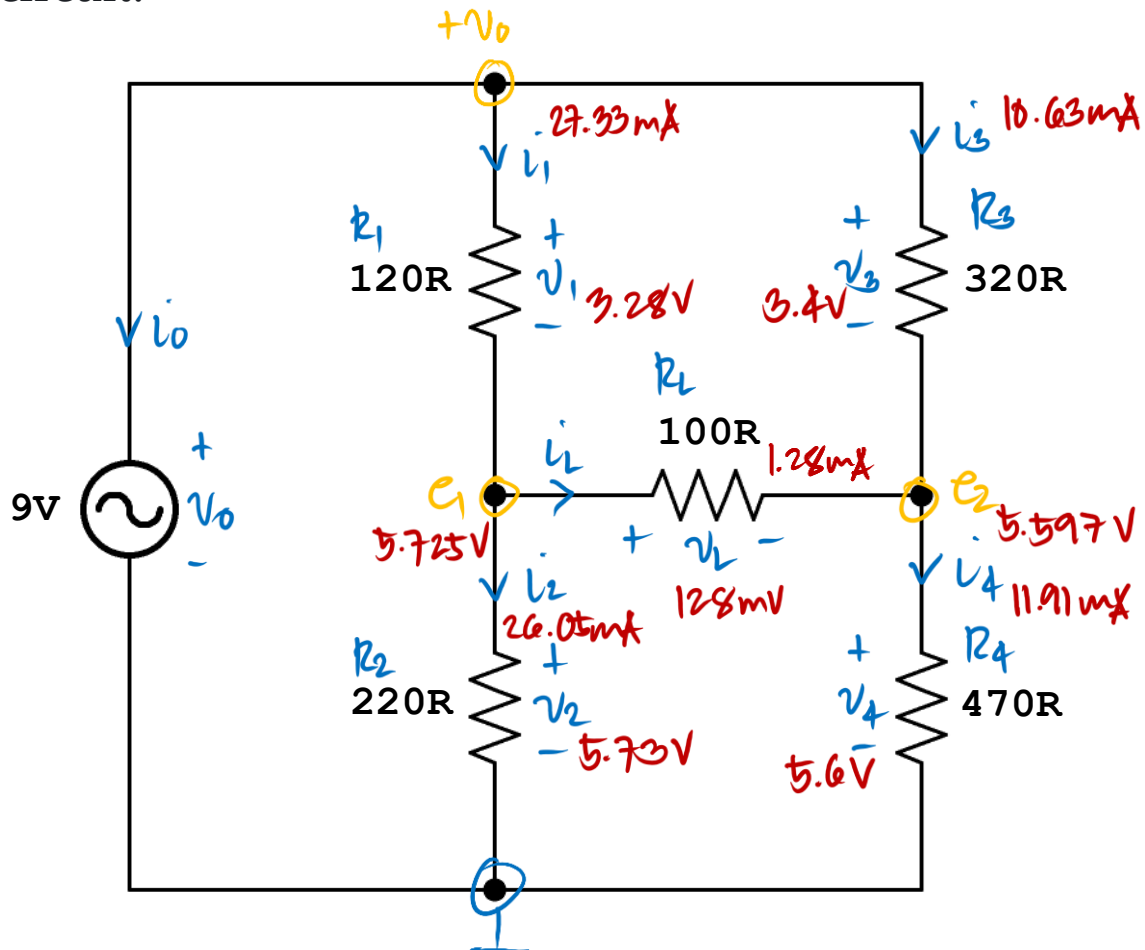EXERCISE

Determine the current through and voltage across each resistor, as well as the total power of the given circuit.



Solution

$$i_L = \frac{v_L}{R_L}$$

$$i_L = \frac{128 \text{ m}}{100}$$


$$i_L = 1.28 \text{ mA}$$

ans



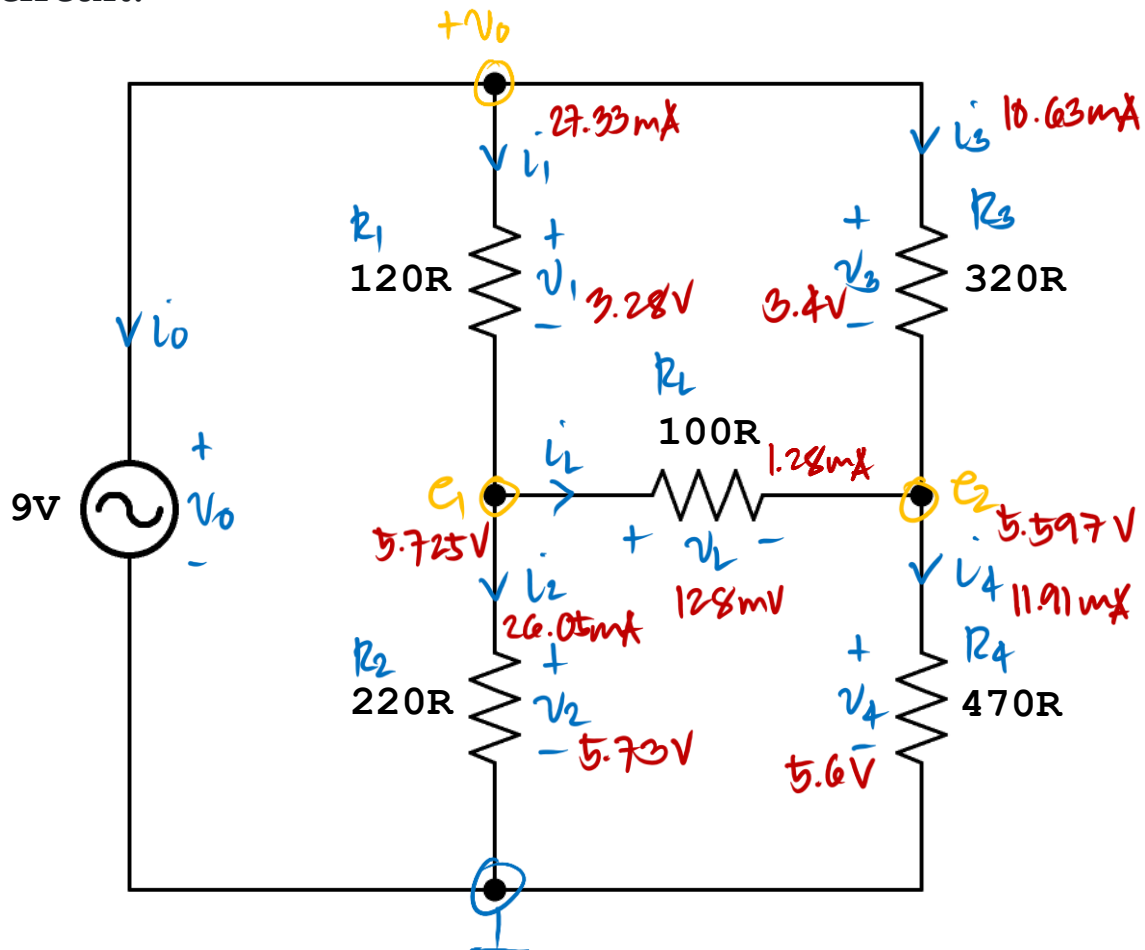EXERCISE

Determine the current through and voltage across each resistor, as well as the total power of the given circuit.



Solution

$$P_0 = P_1 + P_2 + P_3 + P_4 + P_L$$

$$P_0 = i_1 v_1 + i_2 v_2 + i_3 v_3 + i_4 v_4 + i_L v_L$$

$$P_0 = 27.33\text{m}(3.28) + 26.05\text{m}(5.73) + 10.63\text{m}(3.4) + 11.91\text{m}(5.6) + 1.28\text{m}(128\text{m})$$

$$P_0 = 341.91\text{mW}$$

ans

LABORATORY

