



EMITTER-STABILIZED BIAS

BJT DC BIASING

prepared by:

Gyro A. Madrona

Electronics Engineer

TOPIC OUTLINE

Emitter-Stabilized Bias Circuit

- Base-Emitter Loop
- Collector-Emitter Loop
- Load Line Analysis



EMITTER-STABILIZED BIAS CIRCUIT



CURRENT GAIN

The current gain parameters alpha (α) and beta (β) describe the relationship between currents in the transistor's three terminals (emitter, base, and collector).

Alpha (α) is the ratio of the collector current to the emitter current.

Formula

$$\alpha = \frac{i_C}{i_E}$$

α is always less than 1 (typically 0.95 to 0.995)


Beta (β) is the ratio of the collector current to the base current.

Formula

$$\beta = \frac{i_C}{i_B}$$




EMITTER-STABILIZED BIAS CIRCUIT

 

The emitter-stabilized bias is an improved biasing method by adding resistor in the emitter (R_E). This resistor introduces negative feedback, which helps stabilize the operating point against variations in temperature and transistor beta (β).



BASE-EMITTER LOOP

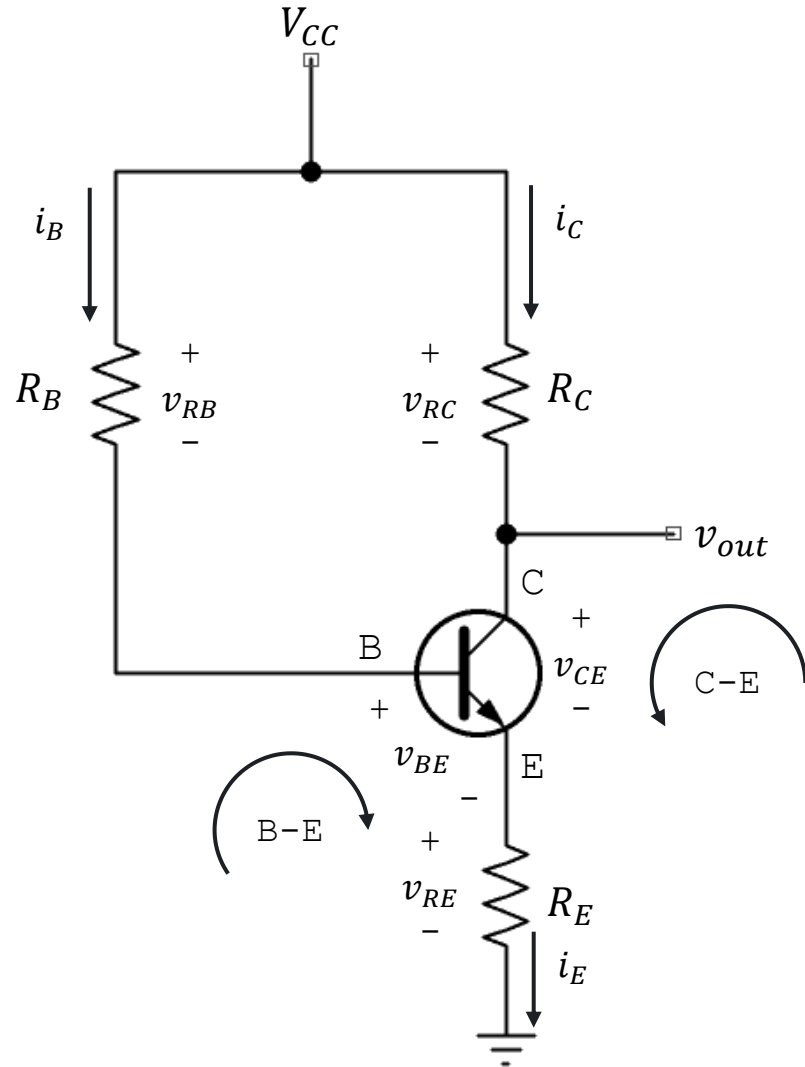

KVL @B-E

$$-v_{CC} + v_{RB} + v_{BE} + v_{RE} = 0$$

$$v_{RB} + v_{RE} = v_{CC} - v_{BE}$$

$$i_B R_B + i_E R_E = v_{CC} - v_{BE}$$


$$i_E = i_B + i_C$$

$$i_E = i_B + \beta i_B$$

$$i_E = i_B(\beta + 1)$$



BASE-EMITTER LOOP

 

KVL @B-E

$$-v_{CC} + v_{RB} + v_{BE} + v_{RE} = 0$$

$$v_{RB} + v_{RE} = v_{CC} - v_{BE}$$

$$i_B R_B + i_E R_E = v_{CC} - v_{BE}$$


$$i_B R_B + i_B (\beta + 1) R_E = v_{CC} - v_{BE}$$

$$i_B (R_B + (\beta + 1) R_E) = v_{CC} - v_{BE}$$

$$i_B = \frac{v_{CC} - v_{BE}}{R_B + (\beta + 1) R_E}$$



COLLECTOR-EMITTER LOOP

 

KVL @C-E

$$-v_{CC} + v_{RC} + v_{CE} + v_{RE} = 0$$

$$v_{CE} = v_{CC} - v_{RC} - v_{RE}$$


$$v_{CE} = v_{CC} - i_C R_C - i_E R_E$$

$$i_E \approx i_C$$

$$v_{CE} = v_{CC} - i_C (R_C + R_E)$$



EXERCISE

 


For the given emitter-stabilized bias network, determine:

- Base current (i_{BQ})
- Collector current (i_{CQ})
- Collector-Emitter voltage (v_{CEQ})
- Collector voltage (v_C)



EXERCISE

Solution

 

LOAD LINE ANALYSIS




SATURATION POINT

The saturation point is the operating state where BJT conducts the maximum collector current ($i_{C(sat)}$) with zero collector-emitter voltage ($v_{CE} = 0$).


In this region the transistor acts like a closed switch (zero resistance between collector-emitter).

Collector Characteristic Curve

 


SATURATION POINT

Mentally Short

 

Collector Characteristic Curve

 


CUTOFF POINT

The cutoff point is the operating state where BJT conducts zero collector current ($i_C = 0$) with v_{CE} at its maximum ($v_{CE} = V_{CC}$).


In this region the transistor acts like an open switch (infinite resistance between collector-emitter).

Collector Characteristic Curve

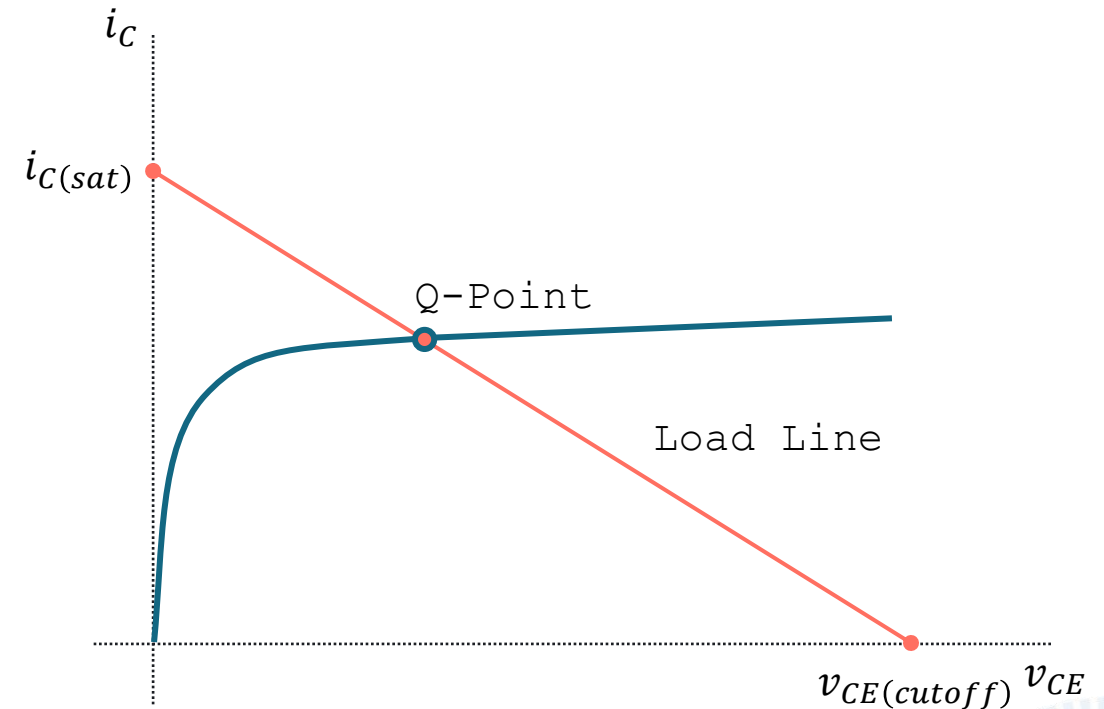


CUTOFF POINT

Mentally Open

 


Collector Characteristic Curve

 


QUIESCENT POINT

The Q-point is the stable DC operating condition characterized by specific value of collector current (i_C) and collector-emitter voltage (v_{CE}).

Collector Characteristic Curve

 

EXERCISE

 


Plot the DC load line analysis for the emitter-stabilized bias network, indicating:

- Saturation current ($i_{C(sat)}$)
- Cutoff voltage ($v_{CE(cutoff)}$)
- Operating Point (Q-Point)




EXERCISE

Solution

 


EXERCISE

Load Line Analysis

 

EXERCISE

 

For the given emitter-stabilized bias network, determine:

- Base current (i_{BQ})
- Collector current (i_{CQ})
- Collector-Emitter voltage (v_{CEQ})
- Emitter voltage (v_E)


and plot the DC load line analysis indicating:

- Saturation current ($i_{C(sat)}$)
- Cutoff voltage ($v_{CE(cutoff)}$)
- Operating Point (Q-Point)




EXERCISE

Solution

 

EXERCISE

Load Line Analysis

 

IMPROVE STABILITY

Bias	β	$i_B (\mu A)$	$i_C (mA)$	$v_{CE} (V)$	$\% \Delta v_{CE}$
Fixed-Bias	50	47.08	2.35	6.83	-76%
	100	47.08	4.71	1.64	
Emitter-Stabilized					
Voltage-Divider Bias					



LABORATORY

