



# **INDUCTOR**

## **TRANSIENT RESPONSE**

---

*prepared by:*

**Gyro A. Madrona**  
Electronics Engineer

# TOPIC OUTLINE

RL Circuit

Energizing an Inductor

De-energizing an Inductor


Transient Response



# ENERGIZING AN INDUCTOR



# RL CIRCUIT

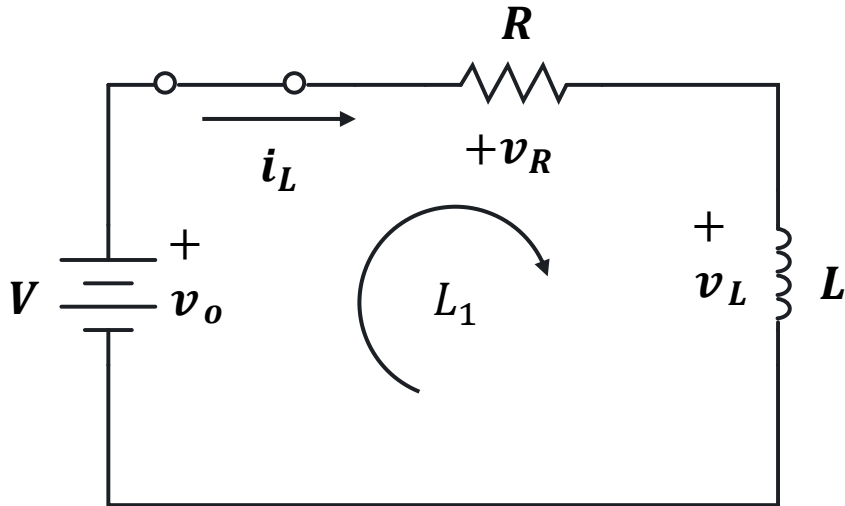

KVL @  $L_1$ :

$$-v_o + v_R + v_L = 0$$

$$v_R + v_L = v_o$$

$$i_L R + v_L = v_o \quad ; v_L = L \frac{d}{dt} i_L$$

$$i_L R + L \frac{d}{dt} i_L = v_o$$

$$\frac{d}{dt} i_L + \frac{R}{L} i_L = \frac{v_o}{L}$$

... first-order ODE

$$i_L = \frac{v_o}{R} (1 - e^{-\frac{R}{L}t})$$




# INDUCTOR CURRENT

Energizing equation:

$$i_L(t) = \frac{v_o}{R} (1 - e^{-\frac{t}{\tau}})$$

where:  $\tau = \frac{L}{R}$

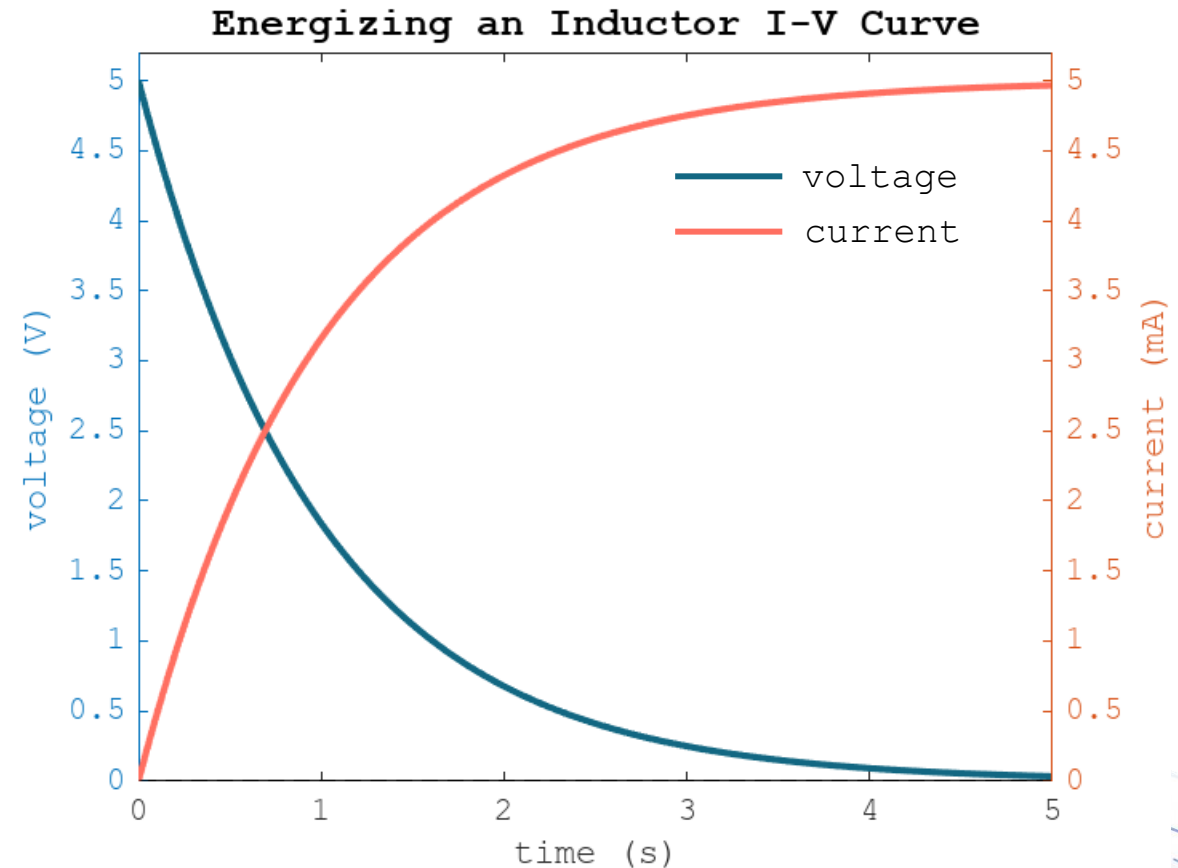The current through the inductor starts at zero and exponentially increases to  $\frac{v_o}{R}$  amperes (maximum current).




# INDUCTOR VOLTAGE

Energizing equation:

$$v_L(t) = v_o e^{-\frac{t}{\tau}}$$

$$\text{where: } \tau = \frac{L}{R}$$

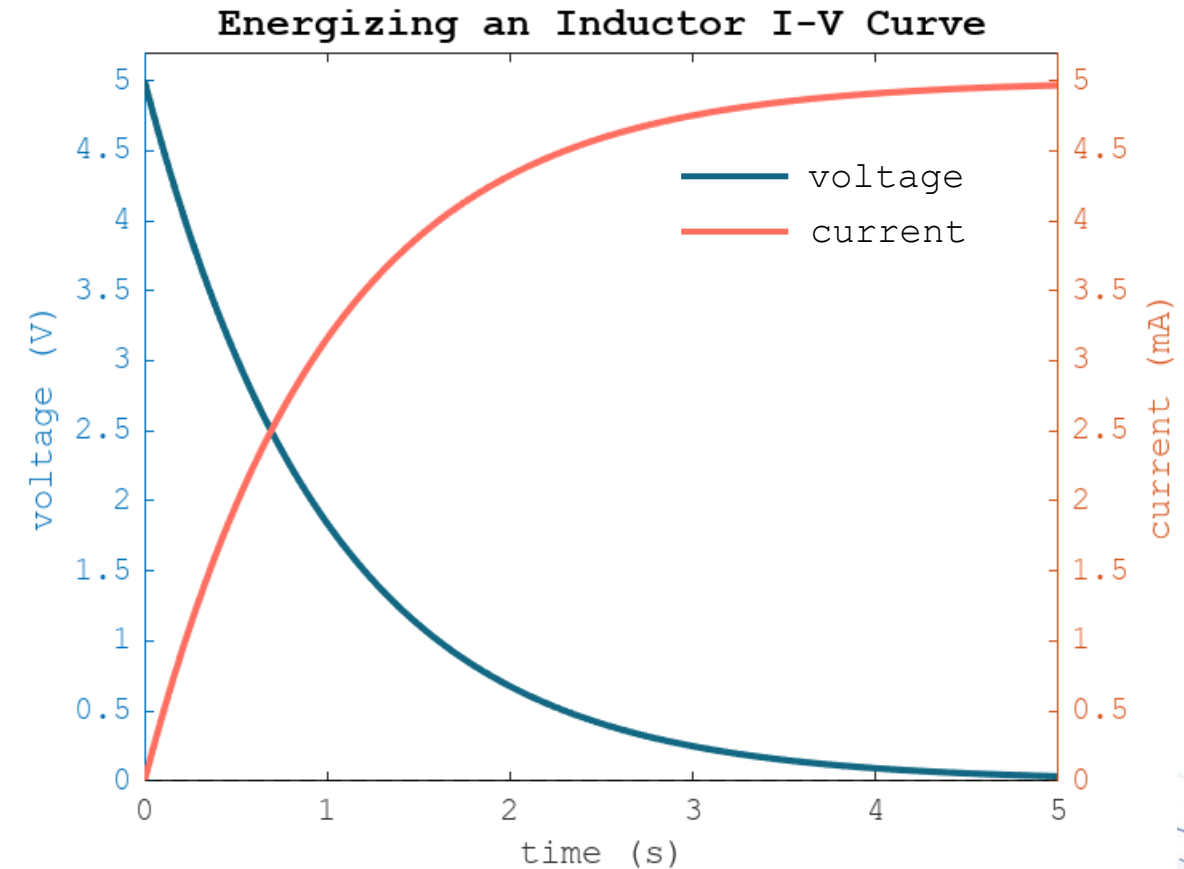The voltage across the inductor instantly jumps to its maximum value of  $v_o$  volts then decays exponentially to zero.




# TIME CONSTANT

The time constant  $\tau$  is a measure of how quickly an inductor energizes or de-energizes in an RL circuit.

Formula:

$$\tau = \frac{L}{R}$$

unit: second

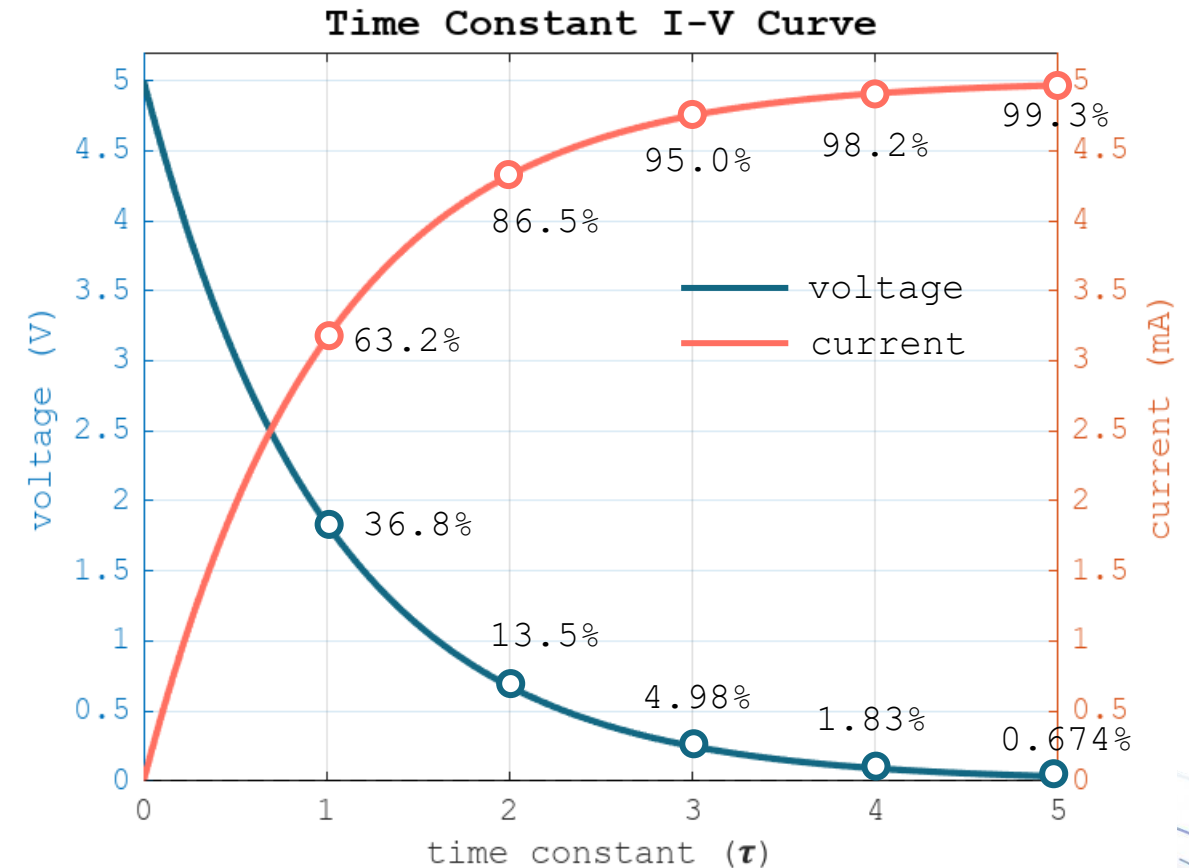

## EXERCISE

---

A **50 mH** inductor is connected to a **12 V** DC power supply through a resistor of **500  $\Omega$** . Determine the time it takes for the inductor to charge to **95%** of its maximum current.

Solution:





## EXERCISE

---

A **50 mH** inductor is connected to a **12 V** DC power supply through a resistor of **500  $\Omega$** . Determine the **current** through the inductor after **300  $\mu$ s** of charging.


Solution:



# DE-ENERGIZING AN INDUCTOR



# RL CIRCUIT

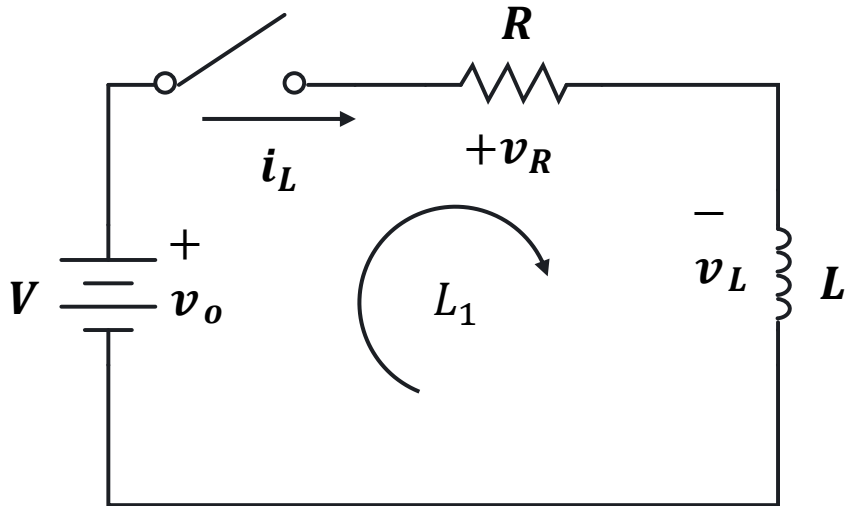

KVL @  $L_1$ :

$$v_R - v_L = 0$$

$$i_L R - v_L = 0 \quad ; v_L = L \frac{d}{dt} i_L$$

$$i_L R - L \frac{d}{dt} i_L = 0$$

$$\frac{d}{dt} i_L - \frac{R}{L} i_L = 0$$

... first-order ODE

$$i_L = \frac{v_o}{R} e^{-\frac{R}{L}t}$$




# INDUCTOR CURRENT

De-energizing equation:

$$i_L(t) = \frac{v_o}{R} e^{-\frac{t}{\tau}}$$

where:  $\tau = \frac{L}{R}$

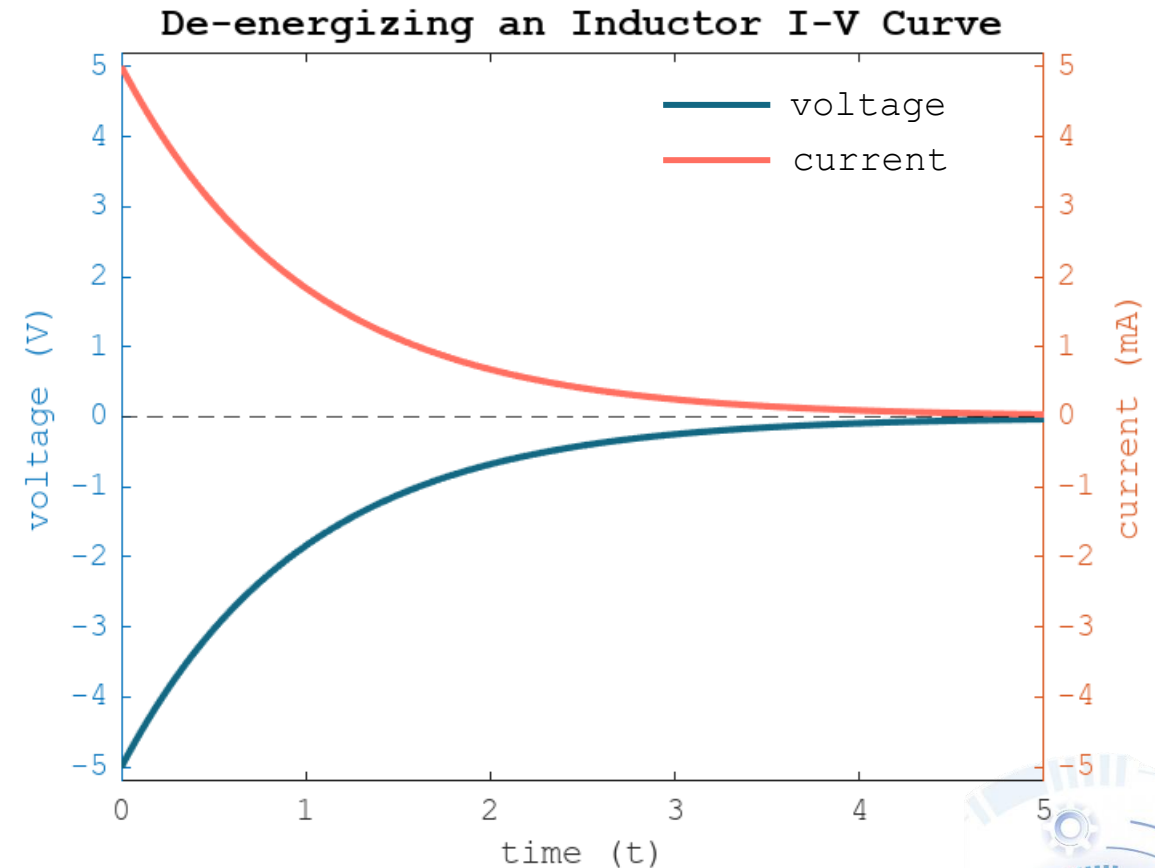The current through the inductor starts at its maximum value  $\frac{v_o}{R}$  amperes then decays exponentially to zero.




# INDUCTOR VOLTAGE

De-energizing equation:

$$v_L(t) = -v_o e^{-\frac{t}{\tau}}$$

where:  $\tau = \frac{L}{R}$

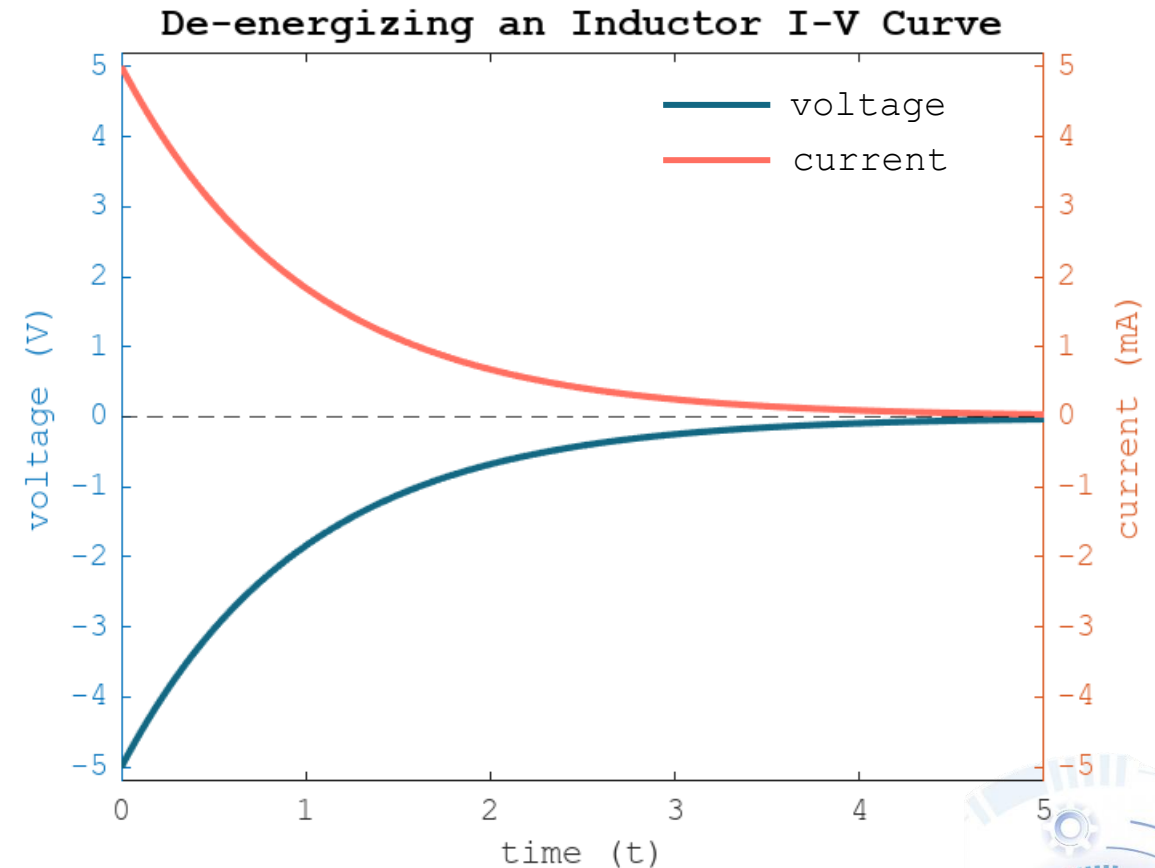The voltage across the inductor instantly jumps to its maximum value, but in opposite direction of  $-v_o$  volts then decays exponentially to zero.



## EXERCISE

---


A **100 mH** inductor is initially charged to **6 V**. It is then disconnected from the power supply and discharged through a resistor of **500  $\Omega$** . Determine the current through the inductor after **0.02 s** of discharging.

Solution:



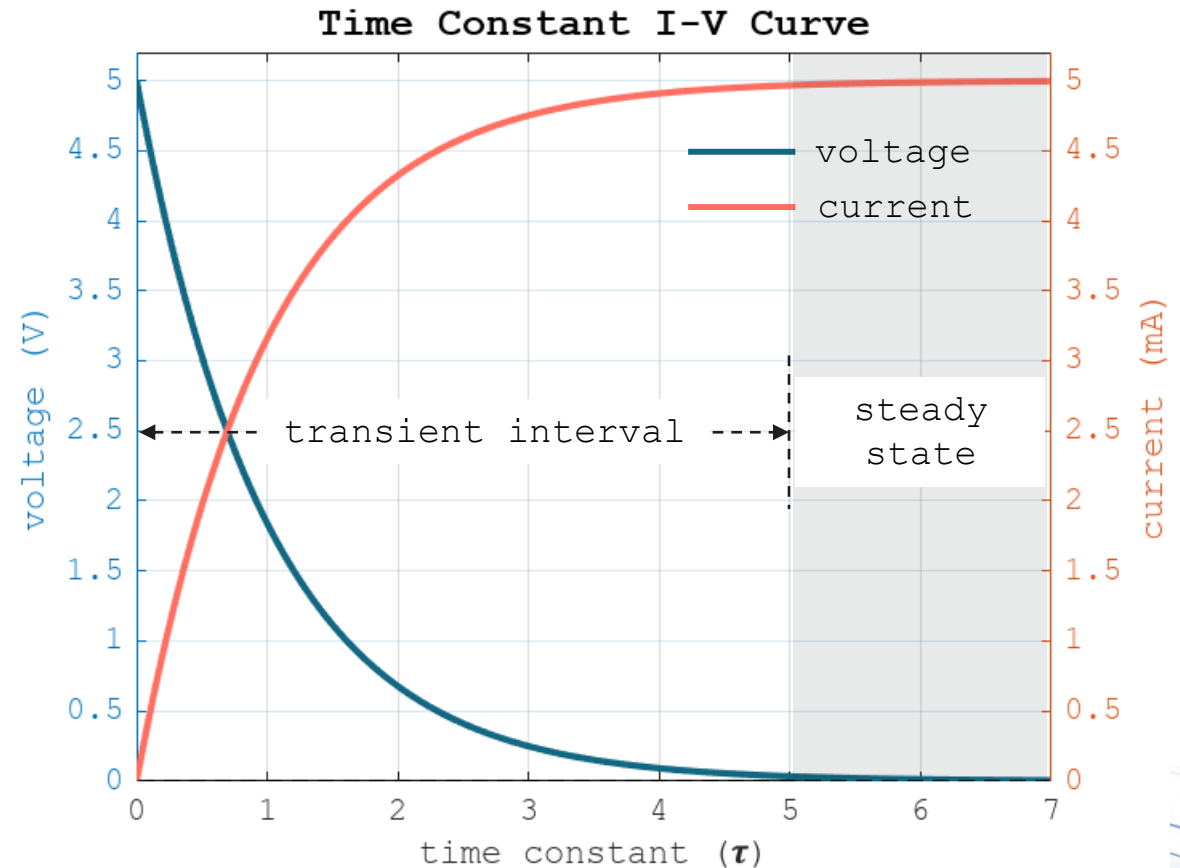
# TRANSIENT RESPONSE

The transient response of an inductor describes the time-dependent changes in current through the inductor and the voltage across it. The transient phase is typically considered to last for approximately five time constants  $5\tau$  after which the system is assumed to have reached steady-state conditions.


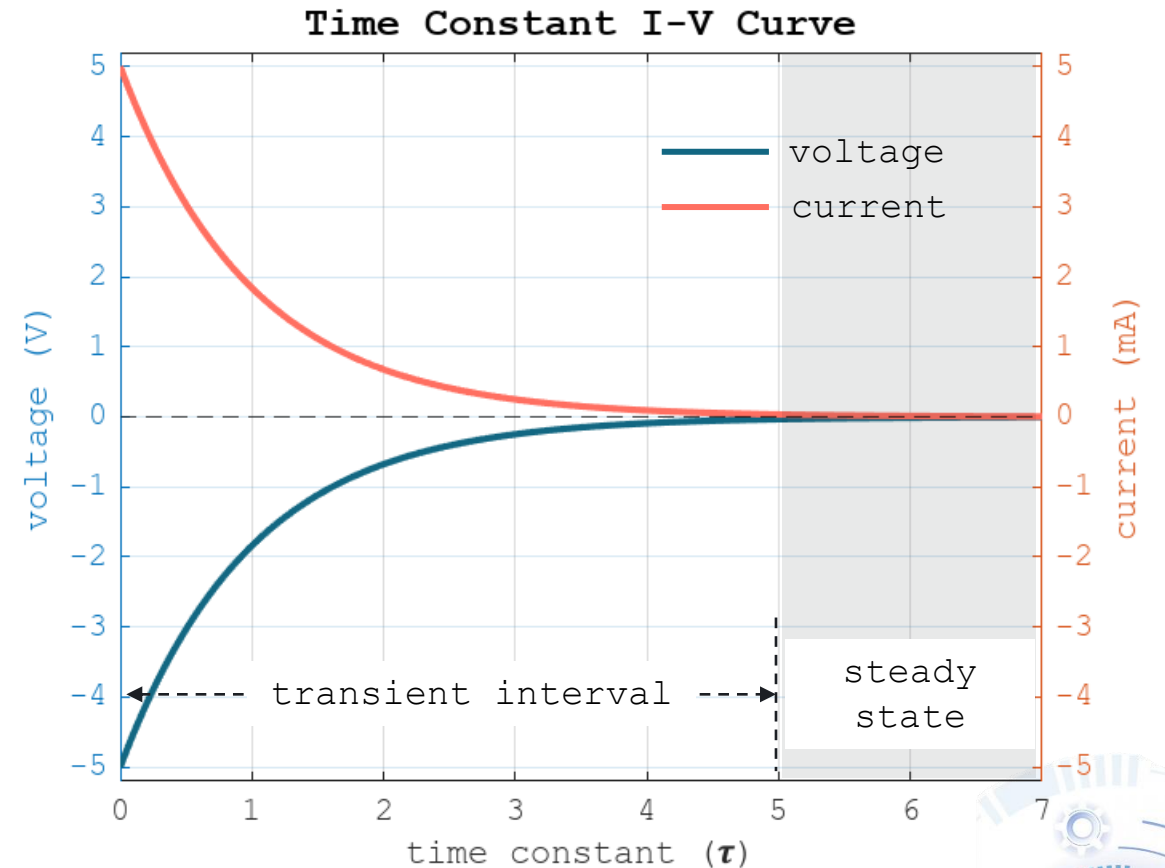
# TRANSIENT RESPONSE

The transient response of an inductor describes the time-dependent changes in current through the inductor and the voltage across it. The transient phase is typically considered to last for approximately five time constants  $5\tau$  after which the system is assumed to have reached steady-state conditions.





# LABORATORY

