



KCL AND KVL

CIRCUIT ANALYSIS METHOD

prepared by:

Gyro A. Madrona
Electronics Engineer

TOPIC OUTLINE

Circuit Convention

Kirchhoff's Current Law (KCL)

Kirchhoff's Voltage Law (KVL)



CIRCUIT CONVENTION



CONVENTION

A convention is a widely accepted practice, method, or behavior that is followed by common agreement or tradition, rather than by formal rules.

Example:

Color coding in Offices:

red – urgent documents

blue – general files

green – financial records

This is a common practice but not formally regulated.



STANDARD

A standard is a formal, established guideline, rule, or specification that is often mandatory and enforced by an authoritative body or organization.

Example:

IEC 60062 Resistor Color Code:

black – 0

brown – 1

red – 2

.

.


.

white – 9

Resistors have colored bands that represent specific digits, multipliers, and tolerance values.



LABELING VARIABLES

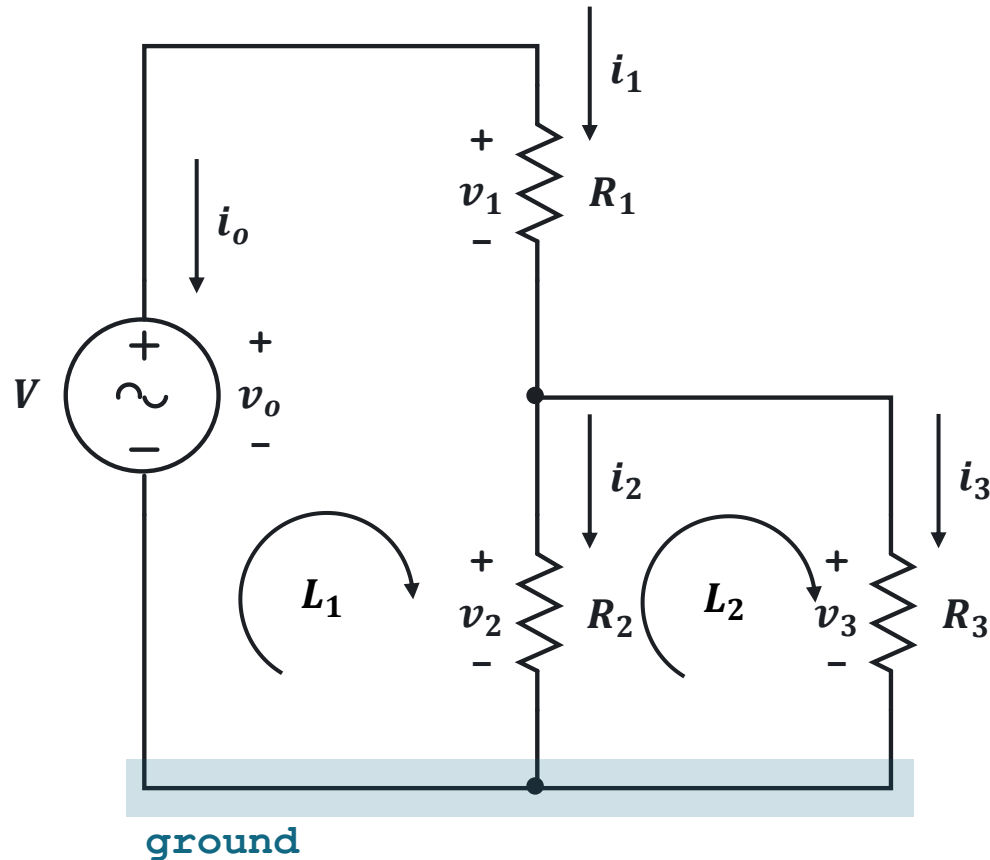

Steps in Labeling Variables:

1. Label the Reference Node (ground):

Select a reference node with the most connections or the negative (-) terminal of a voltage source.

2. Label Node Voltages:

Mark higher potentials as positive (+) relative to the reference node.

3. Label Currents:


Entering the positive (+) terminal of a component.

4. Create a voltage loop:

Follow the defined current directions.



CURRENT FLOW CONVENTION

 

Current Flow Convention:

- Current entering a node is negative $(-)$
- Current leaving a node is positive $(+)$

@ a :


$$-i_1$$

$$+i_2$$

$$+i_3$$



VOLTAGE LOOP CONVENTION

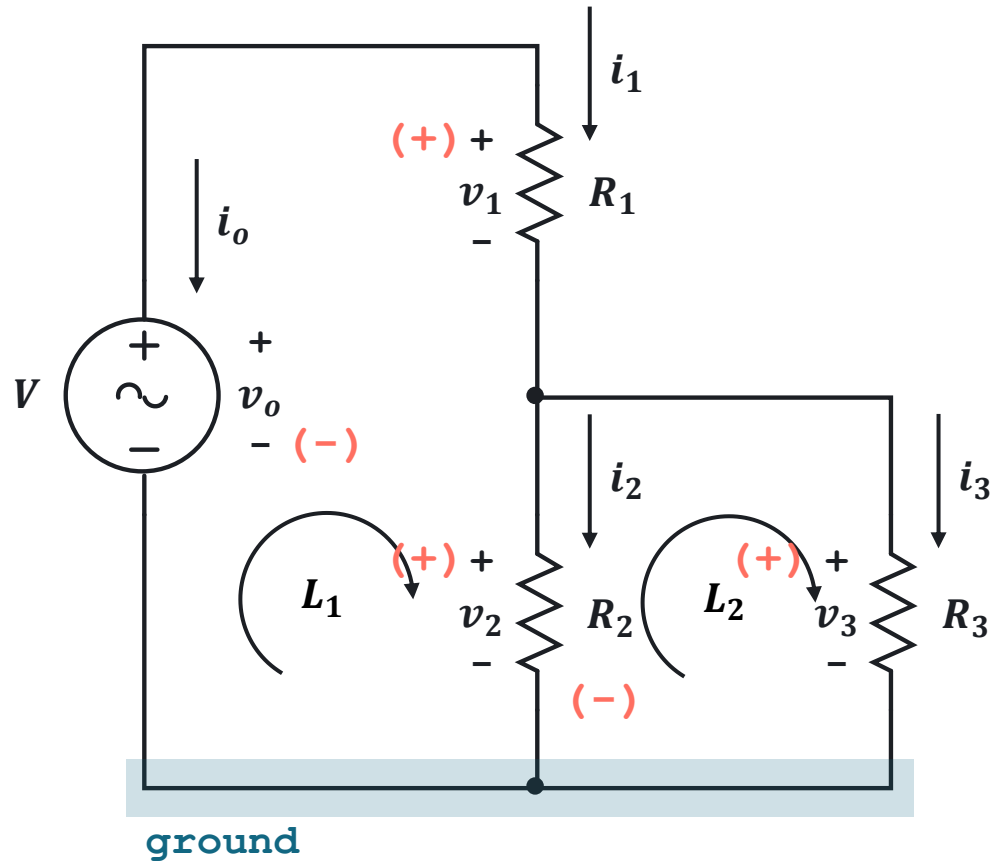

Voltage Loop Convention:

The “sign” of voltage of the element is the first sign the loop encounters.

@ L_1 :

$-v_0$

$+v_1$

$+v_2$

@ L_2 :

$-v_2$


$+v_3$



KIRCHHOFF'S CURRENT LAW AND VOLTAGE LAW



KCL

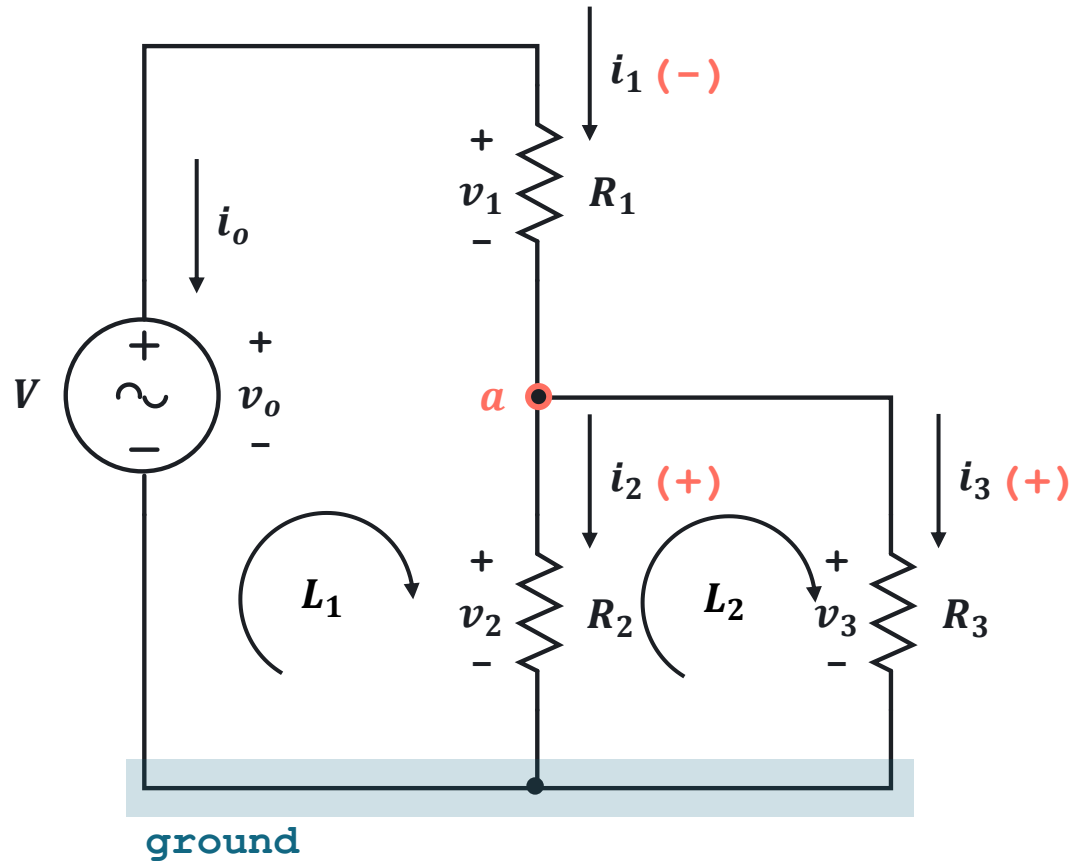

Kirchhoff's Current Law:


The summation of currents going-in and going-out a node is zero.

$$\sum i_j = 0$$

KCL @ a :

$$-i_1 + i_2 + i_3 = 0$$



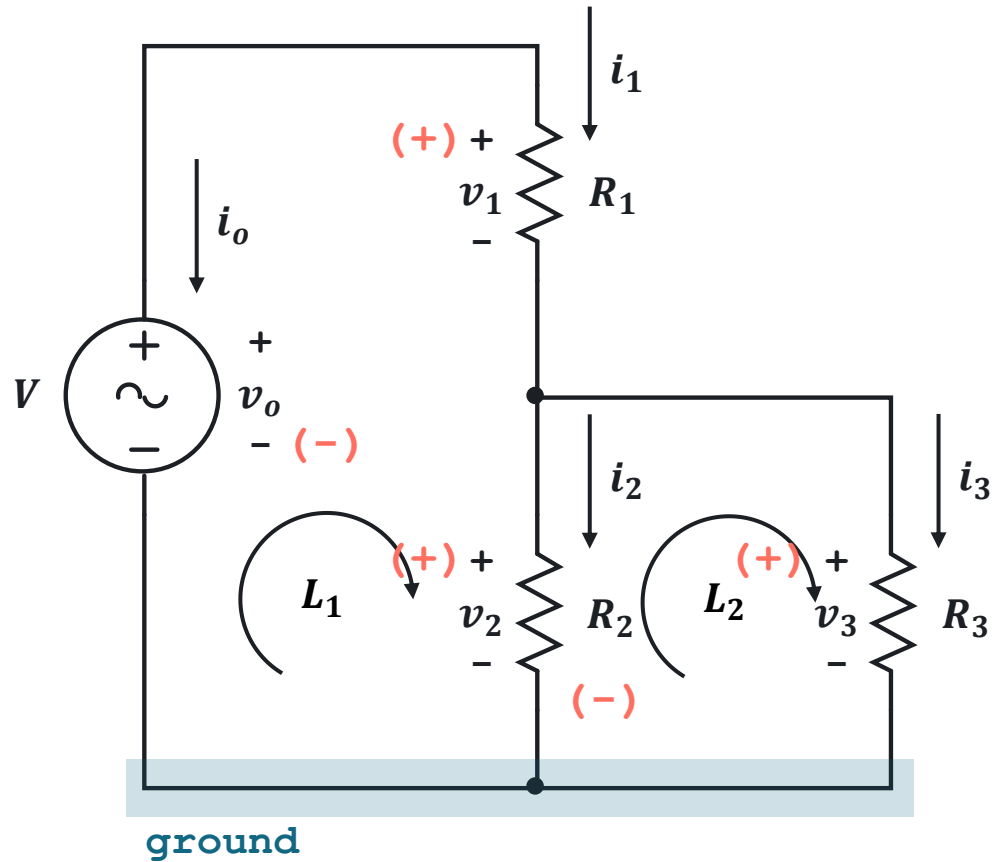

Kirchhoff's Voltage Law:


The summation of voltages in a closed-loop is zero.

$$\sum v_j = 0$$

KVL @ L_1 :

$$-v_o + v_1 + v_2 = 0$$



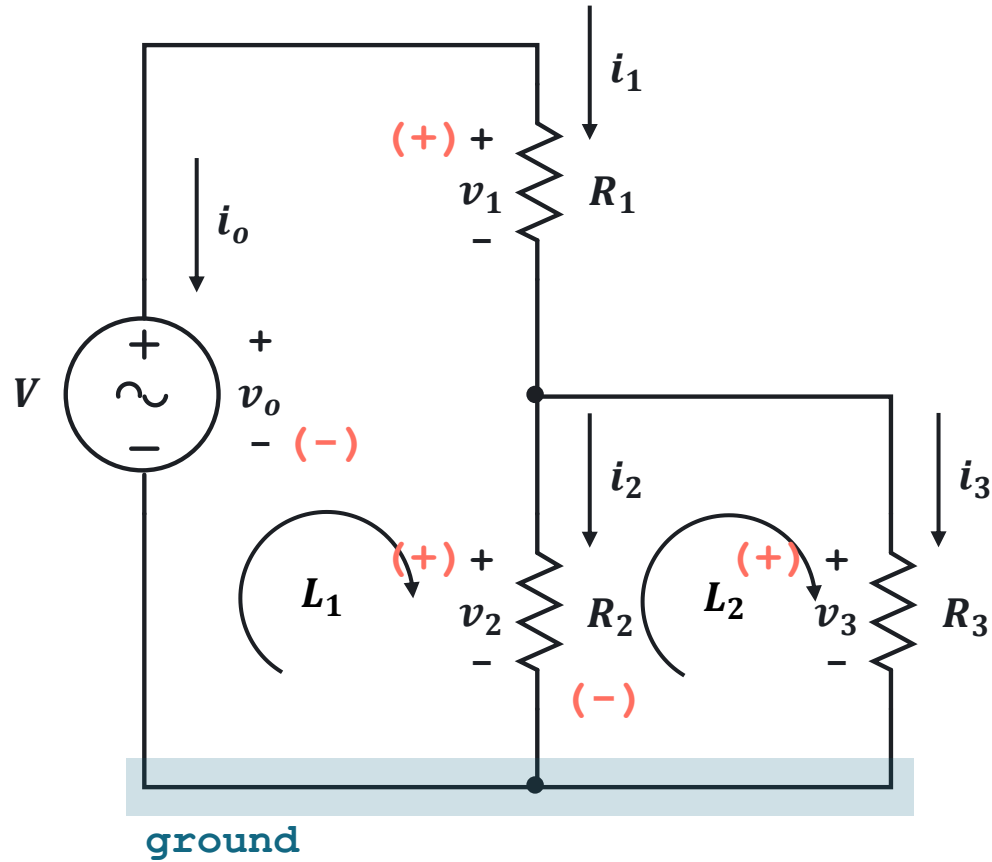

Kirchhoff's Voltage Law:

The summation of voltages in a closed-loop is zero.

$$\sum v_j = 0$$

KVL @ L_2 :


$$-v_2 + v_3 = 0$$



EXERCISE

Determine the current flowing through each resistor and the voltage drop across each resistor in the given circuit.


Solution:

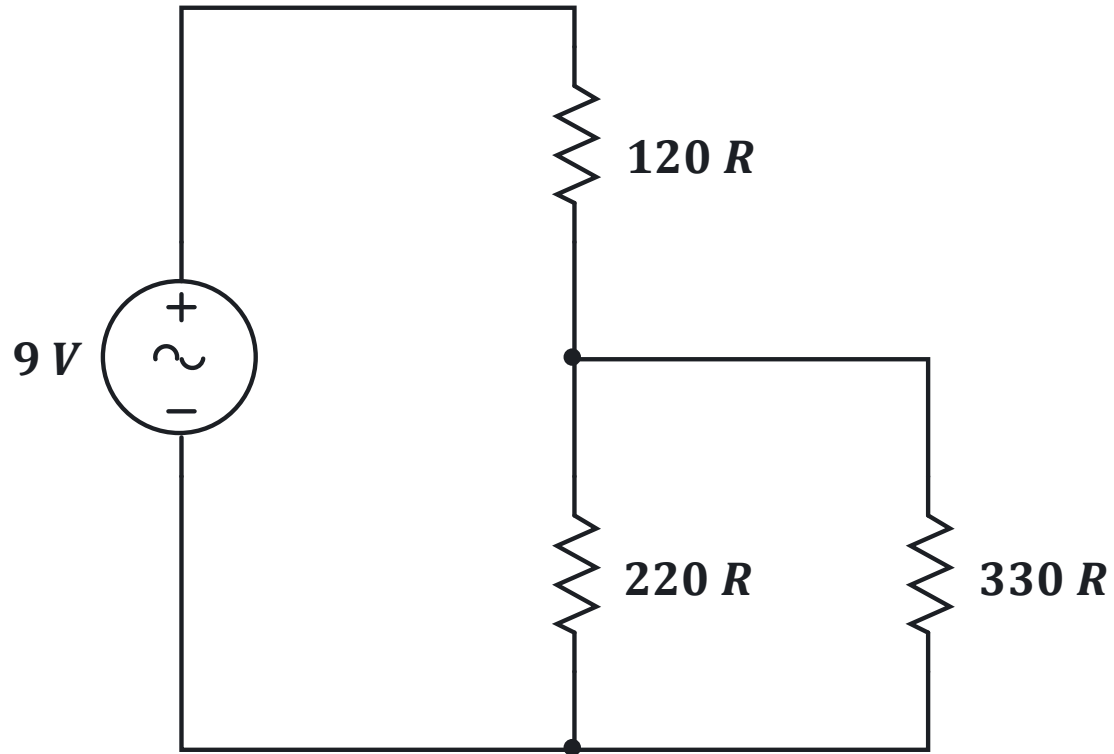

EXERCISE

Determine the **load R_L voltage** and **current** of the given circuit.

Solution:

 

LABORATORY

