

DC ANALYSIS OF DIODE CIRCUITS

SEMICONDUCTOR DIODE

prepared by:

Gyro A. Madrona

Electronics Engineer

TOPIC OUTLINE

Diode Logic

- OR Gate
- AND Gate


Analyzing Diode Behavior in DC Circuits



DIODE LOGIC




POSITIVE LOGIC OR GATE

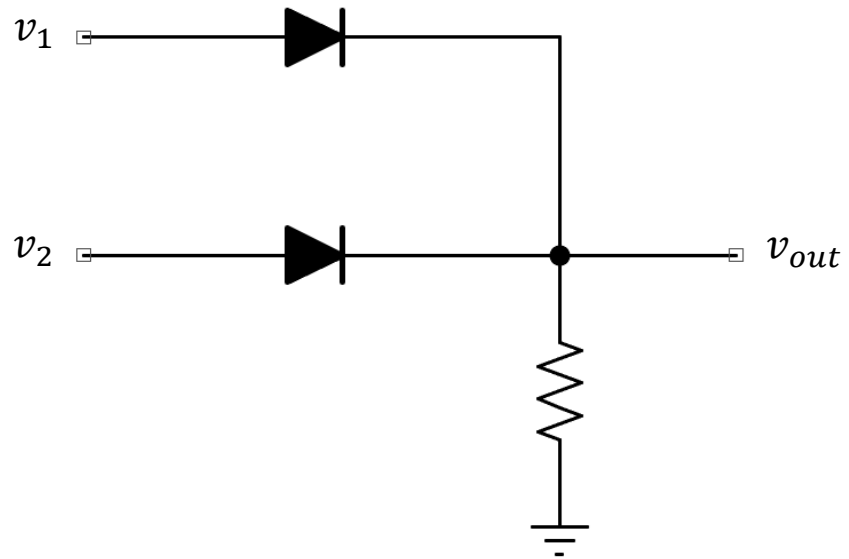

v_1	v_2	v_{out}
0	0	
0	5	
5	0	
5	5	



POSITIVE LOGIC AND GATE

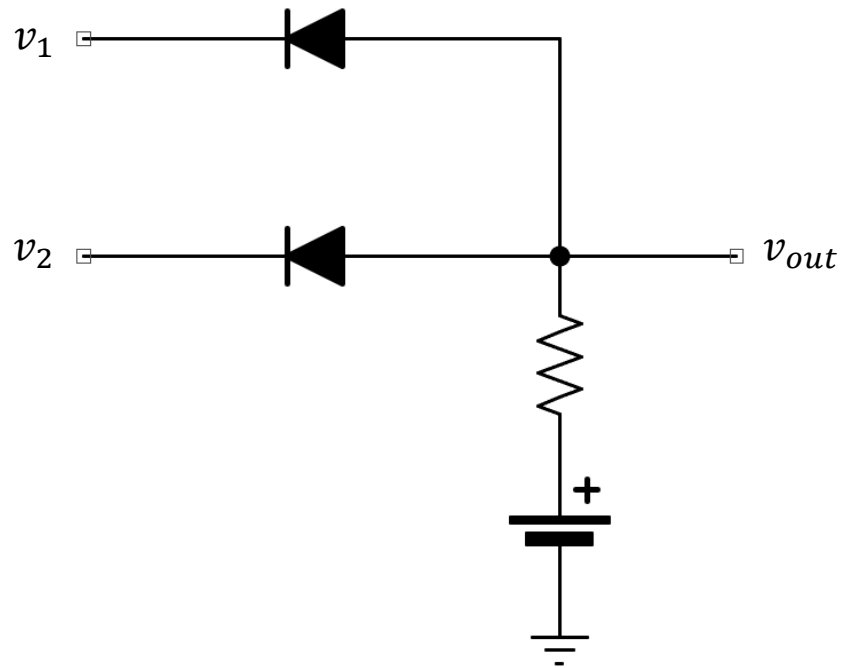

v_1	v_2	v_{out}
0	0	
0	5	
5	0	
5	5	




ANALYZING DIODE BEHAVIOR IN DC CIRCUITS



EXERCISE

Determine the voltage across the load (v_L), the current flowing through the load (i_L), and the power dissipated by the load resistor (P_L) in the given circuit.


Solution

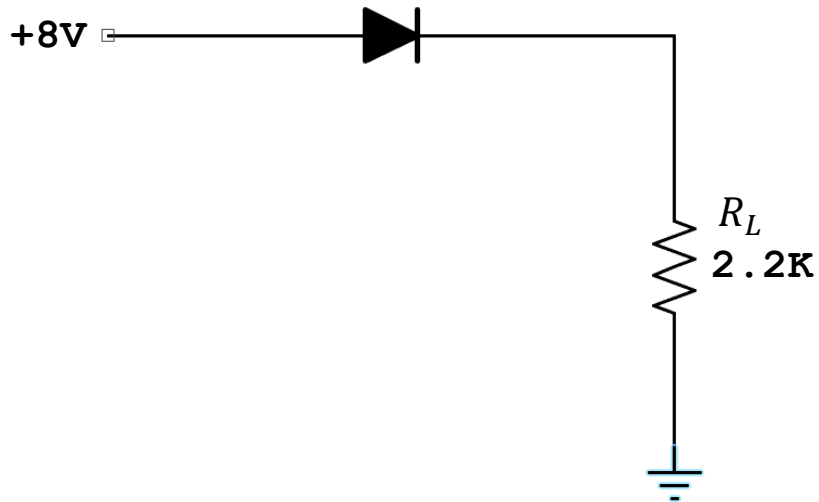

EXERCISE

Determine the voltage across the load (v_L), the current flowing through the load (i_L), and the power dissipated by the load resistor (P_L) in the given circuit.


Solution

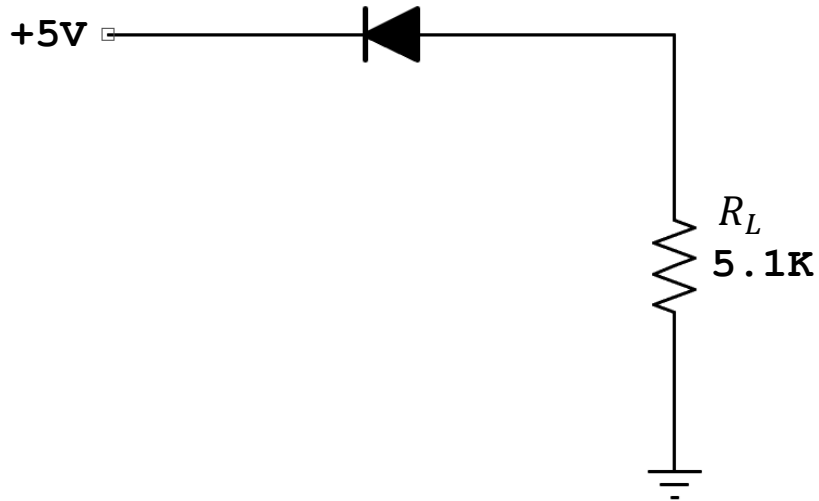

EXERCISE

Determine the voltage across the load (v_L), the current flowing through the load (i_L), and the power dissipated by the load resistor (P_L) in the given circuit.


Solution

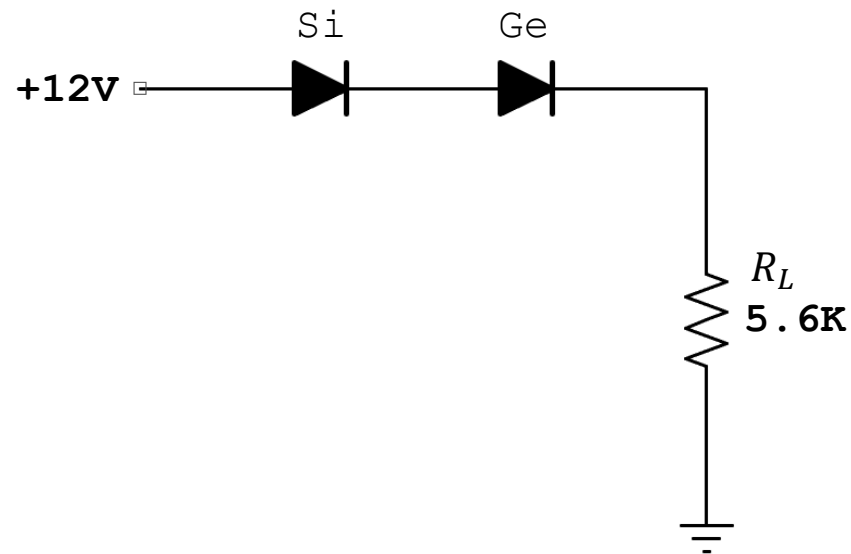

EXERCISE

Determine the output voltage (v_{out}), the current flowing through the resistor (i_R), and the currents flowing through diodes D_1 and D_2 (i_{D1} and i_{D2}) in the circuit.

Solution

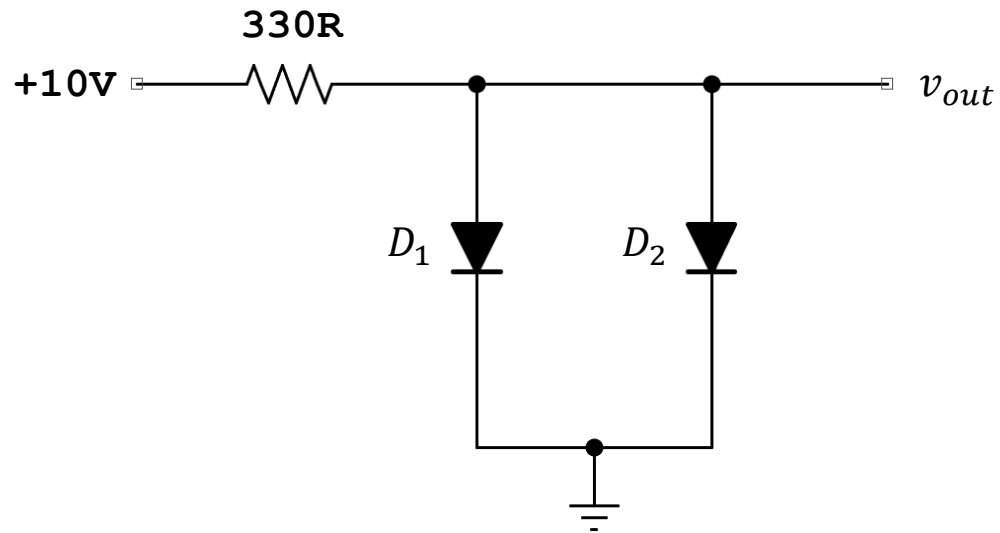

LABORATORY

