



LOGIC GATES

INTRODUCTION

prepared by:

Gyro A. Madrona
Electronics Engineer

TOPIC OUTLINE

Logic Gates

- Logic Symbol
- Truth Table
- Timing Diagram




LOGIC GATES



INVERTER

The inverter (NOT gate) performs the operation called inversion or complementation.


Logic Symbol

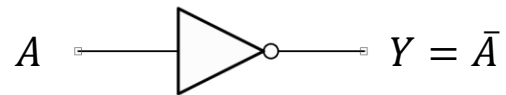

Truth Table

A	Y
0	1
1	0


Timing Diagram

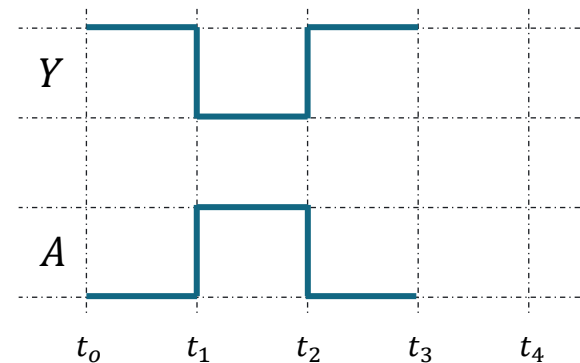

EXERCISE

Given the inverter network, determine the logic levels at points E and F when a LOW signal is applied at point A.


Solution

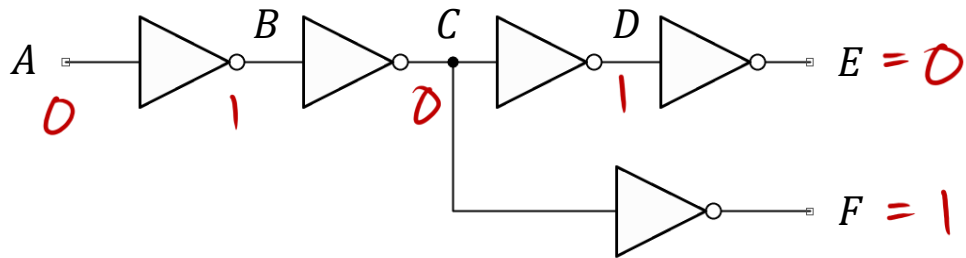

AND GATE

The AND gate is one of the basic gates that can be combined to form any logic function. It performs logical multiplication.


Logic Symbol

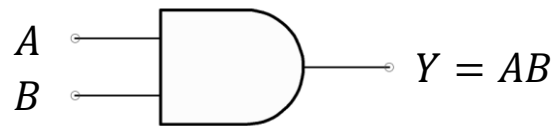

Truth Table


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Timing Diagram

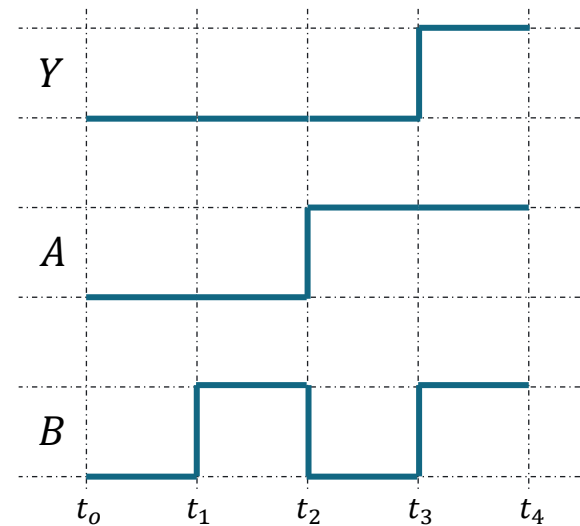


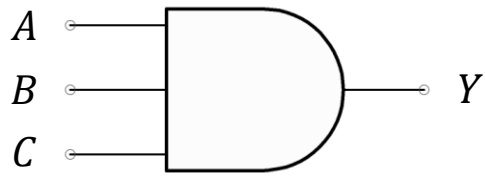EXERCISE

For the 3-input AND gate, determine the output waveform in relation to the inputs.




Solution

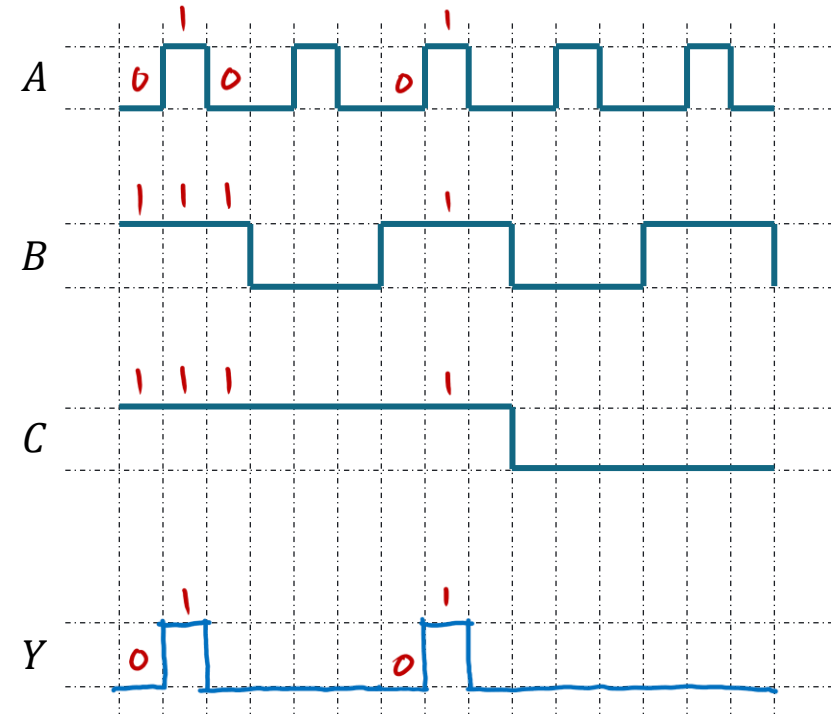

OR GATE

The OR gate is another basic gates from which all logic functions are constructed. It performs logical addition.


Logic Symbol

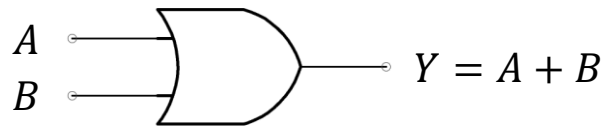

Truth Table


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Timing Diagram

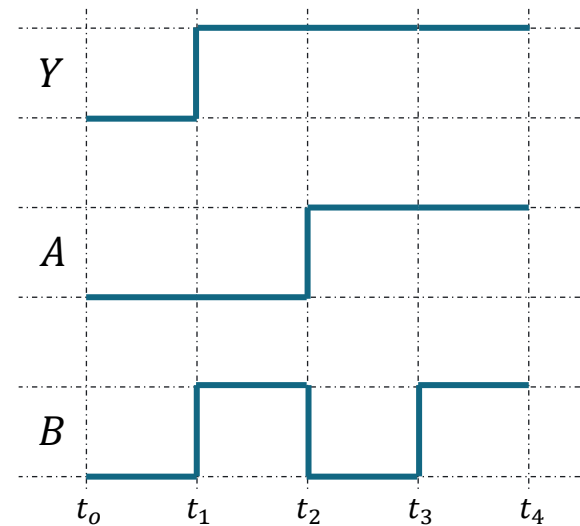


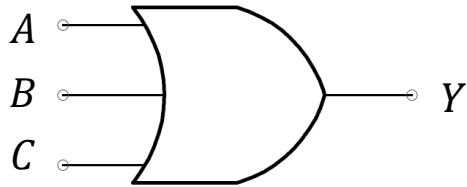EXERCISE

For the 3-input OR gate, determine the output waveform in relation to the inputs.




Solution

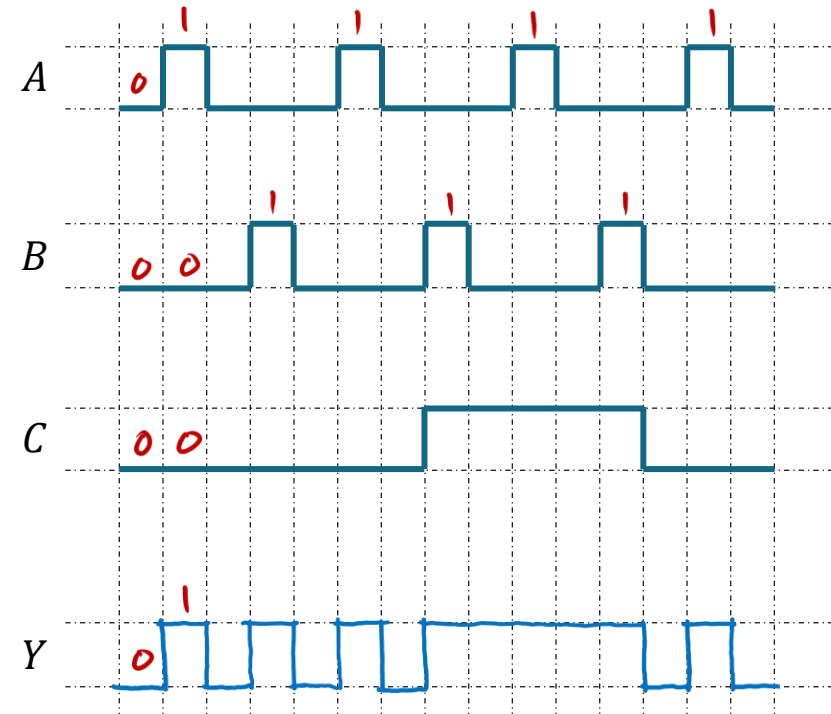

NAND_GATE

The NAND gate is a logical complement of the AND gate. It is considered a universal gate, meaning it can be used in combination to perform AND, OR, and inverter operations.


Logic Symbol

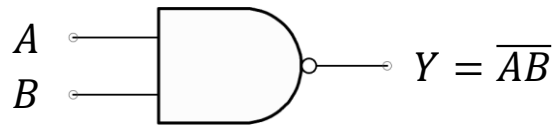

Truth Table


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Timing Diagram

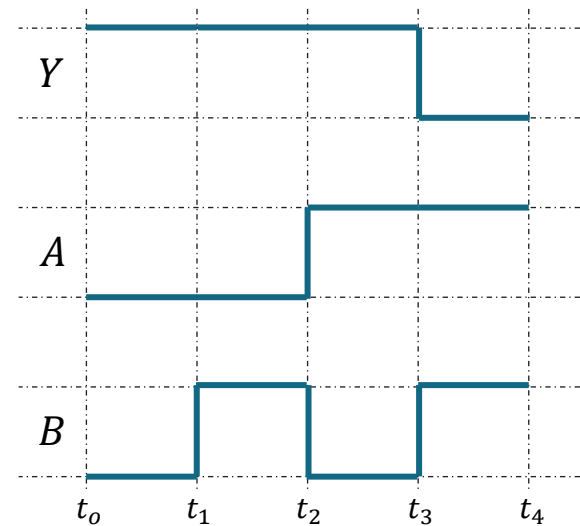

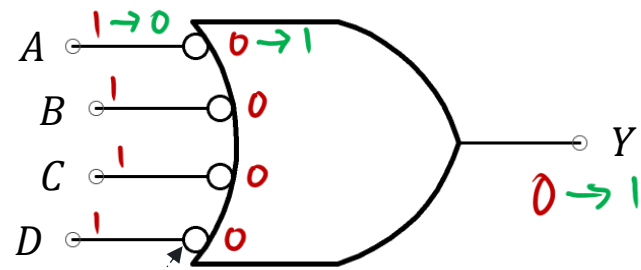
EXERCISE

For the 4-input NAND gate, operating as negative-OR gate, determine the output with respect to the inputs.



Bubble indicates
active-LOW input


Solution

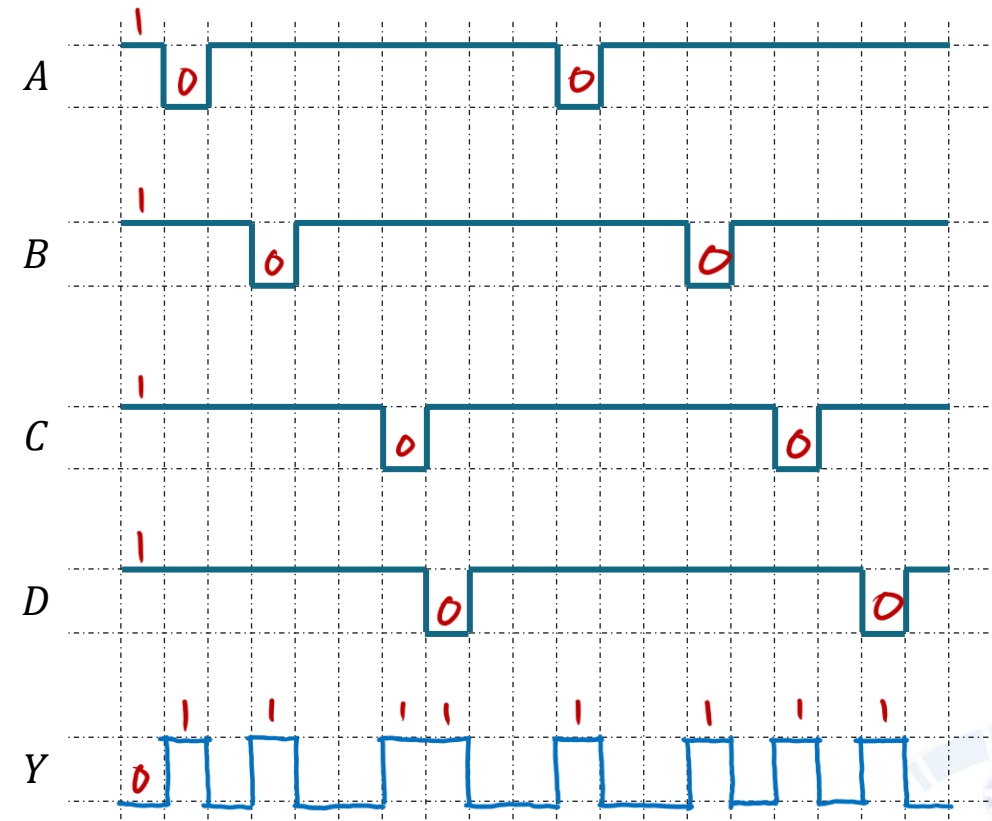

NOR GATE

NOR gate is also a universal gate, and it is the logical complement of the OR gate.


Logic Symbol

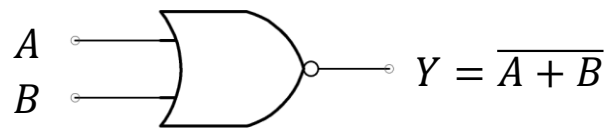

Truth Table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


Timing Diagram

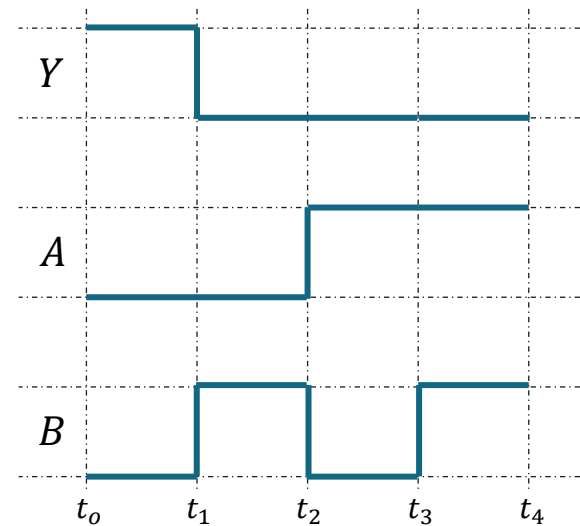

EXERCISE

As part of an aircraft's functional monitoring system, a circuit is required to indicate the status of the landing gears prior to landing. $S_1 = 0$ $S_2 = 0$ $S_3 = 0$ A green LED display turns on if all three gears are properly extended when the "gear down" switch has been activated in preparation for landing. A red LED display turns on if any of the gears fail to extend properly prior to landing. When a landing gear is extended, its sensor produces a LOW voltage. When a landing gear is retracted, its sensor produces a HIGH voltage. Implement a circuit to meet this requirement.


Solution

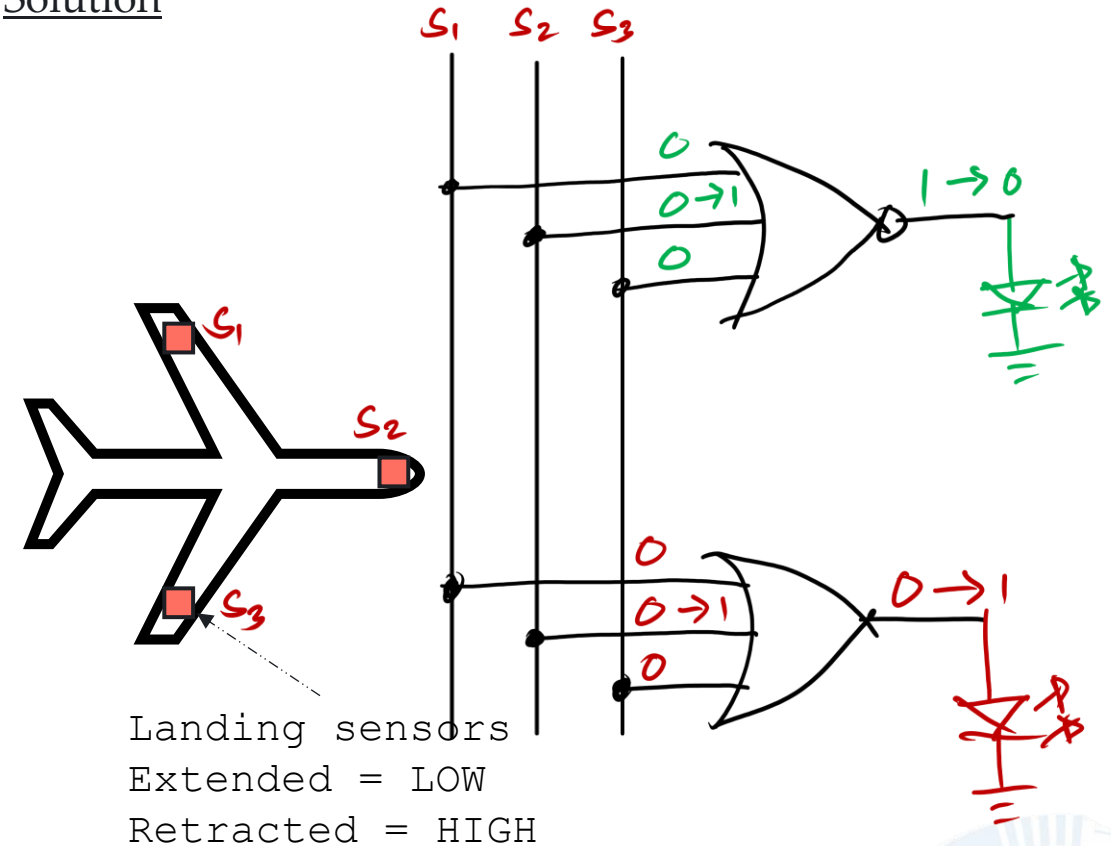

EXERCISE

As part of an aircraft's functional monitoring system, a circuit is required to indicate the status of the landing gears prior to landing. $S_1 = 0$ $S_2 = 0$ $S_3 = 0$ A green LED display turns on if all three gears are properly extended when the "gear down" switch has been activated in preparation for landing. A red LED display turns on if any of the gears fail to extend properly prior to landing. When a landing gear is extended, its sensor produces a LOW voltage. When a landing gear is retracted, its sensor produces a HIGH voltage. Implement a circuit to meet this requirement.


Solution

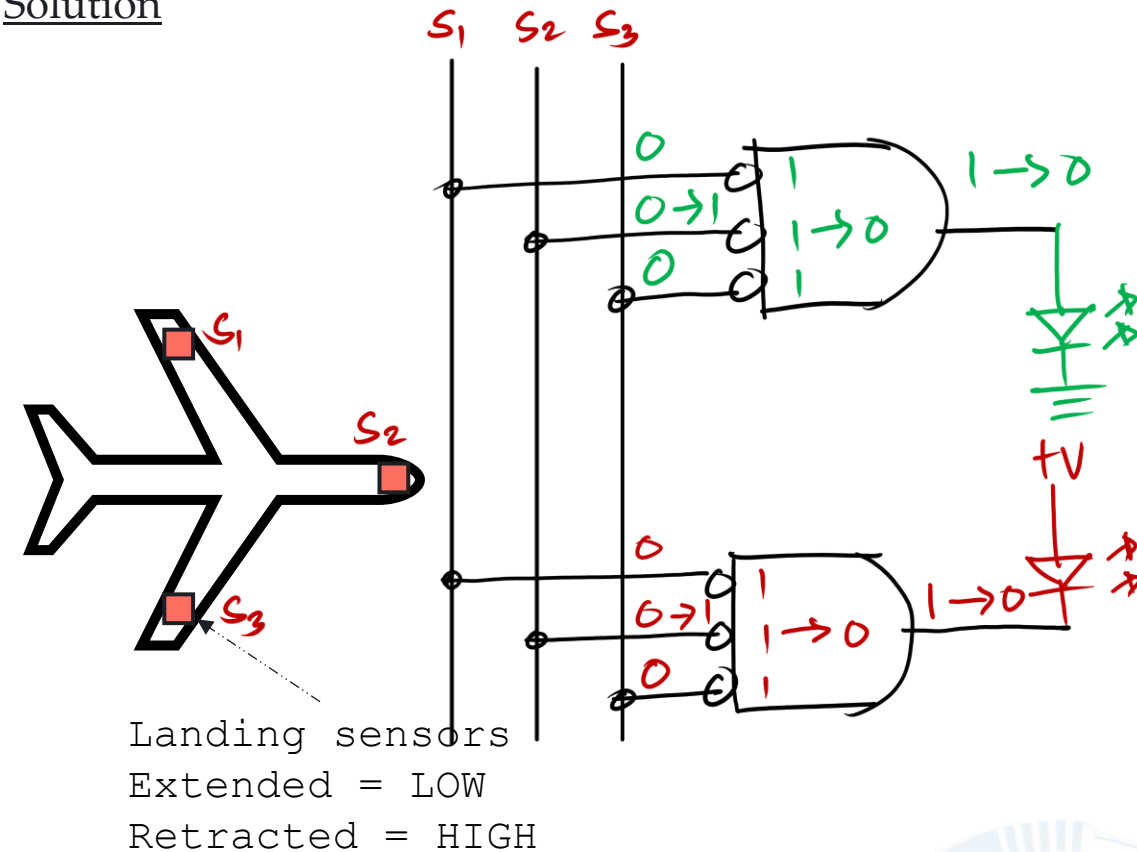

EXCLUSIVE-OR GATE

The exclusive-OR (XOR) gate performs modulo-2 addition.


Logic Symbol

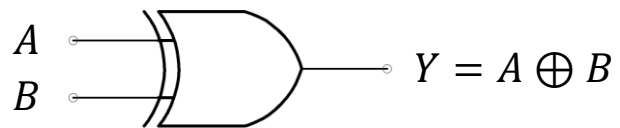

Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


Timing Diagram

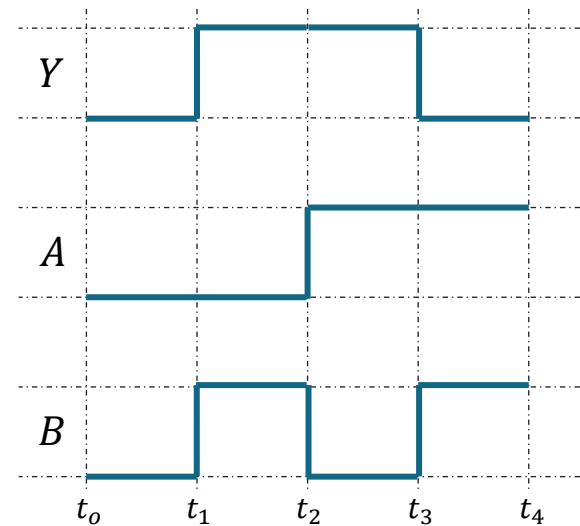

EXCLUSIVE-NOR GATE

The exclusive-NOR (XNOR) gate is the logical complement of the XOR gate.


Logic Symbol

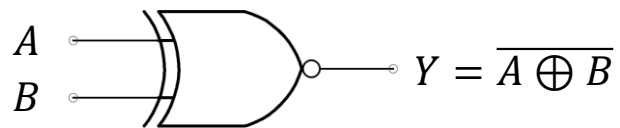

Truth Table


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

Timing Diagram

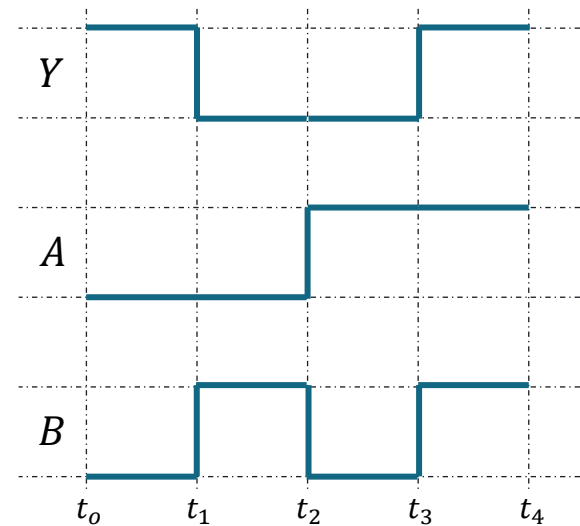


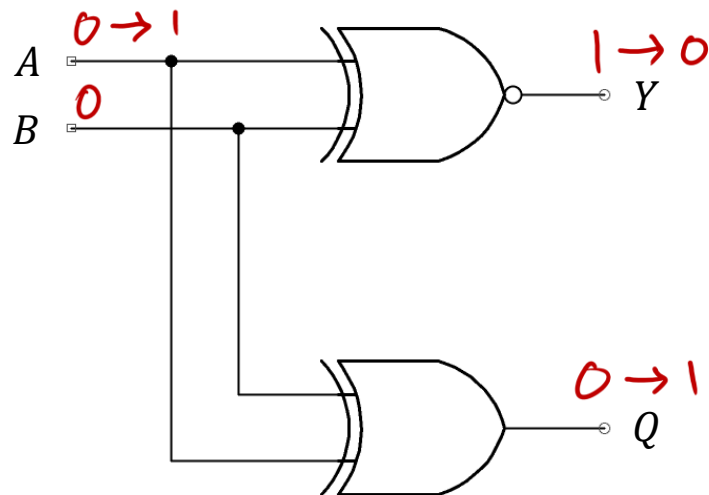EXERCISE

Determine the output waveforms for the XOR gate and for the XNOR gate, given the input waveforms, A and B.




Solution

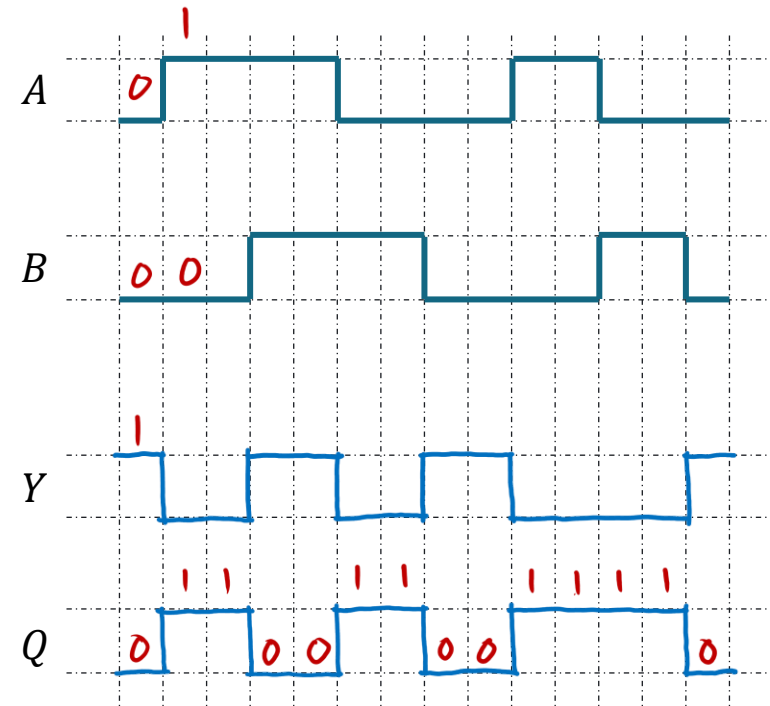

EXERCISE


In the simple programmed AND array with programmable links, determine the Boolean output expressions.

Solution

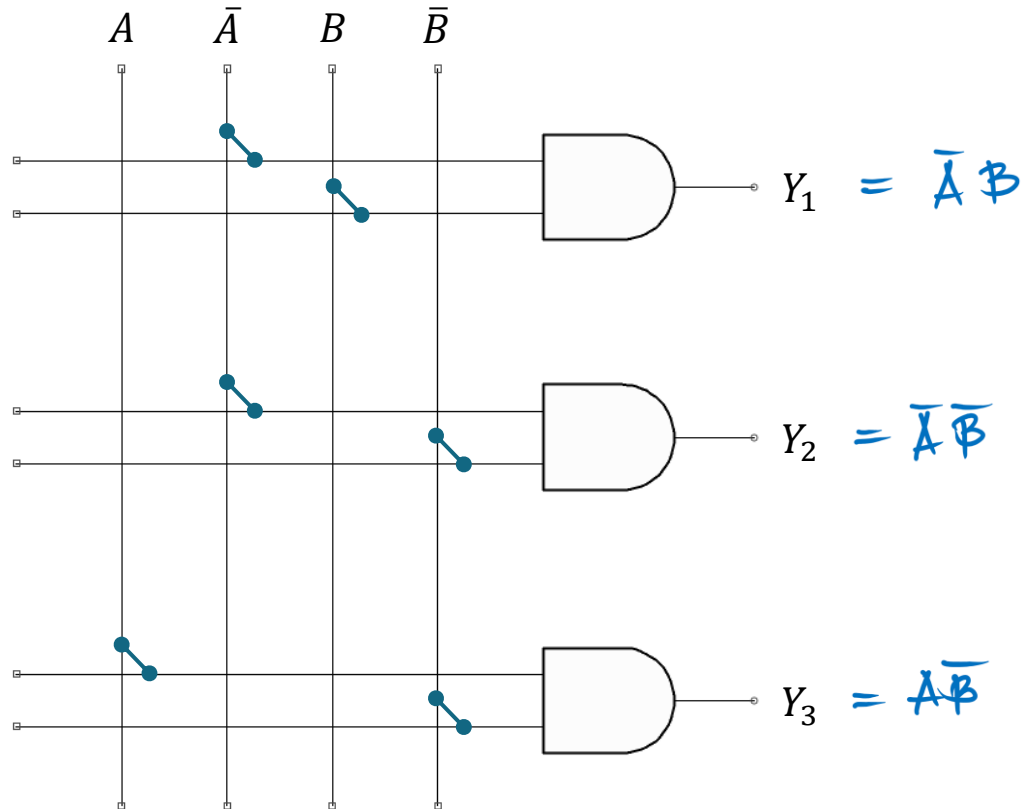


IC PACKAGES

DIP (Dual In-line Package)

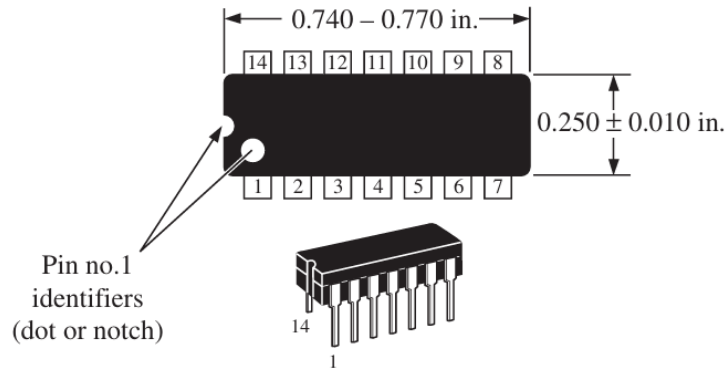

SOIC (Small-Outline IC)

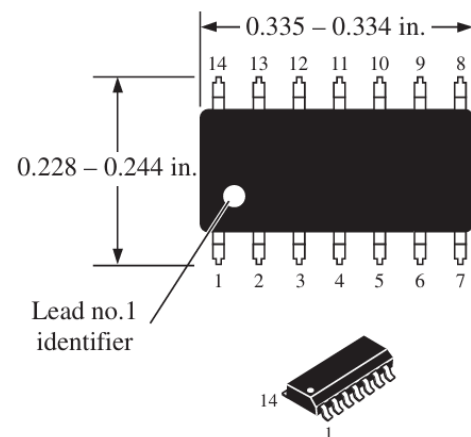

Datasheet links

[7404-Inverter Gate datasheet](#)

[7408-AND Gate datasheet](#)

[7432-OR Gate datasheet](#)

[7403-NAND Gate datasheet](#)

[7402-NOR Gate datasheet](#)


[74136-XOR Gate datasheet](#)

[74266-XNOR Gate datasheet](#)




PIN CONFIGURATION


Hex inverter

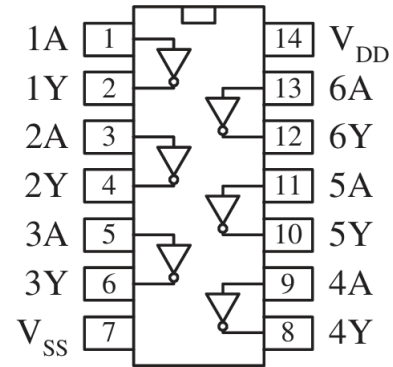


Quad 2-input OR

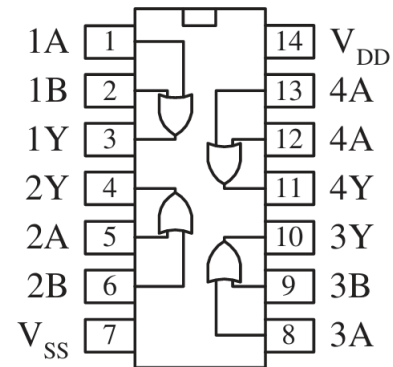


Quad 2-input NOR

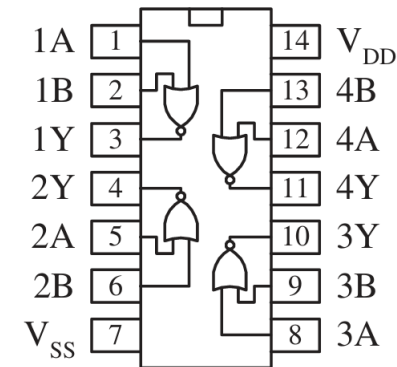


Quad 2-input AND

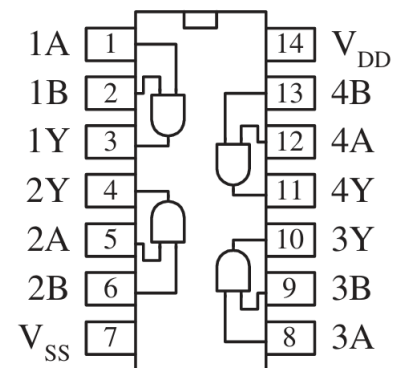


Quad 2-input NAND

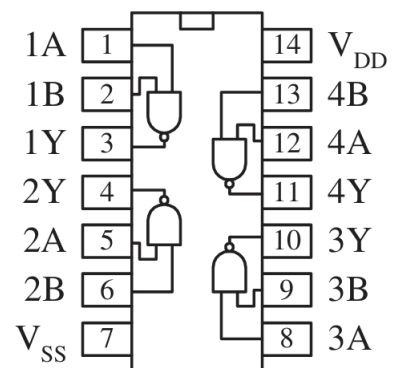

Quad 2-input XNOR

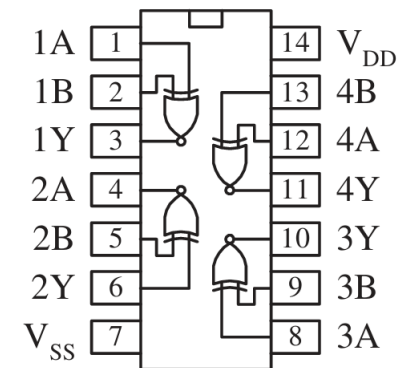

Quad 2-input XOR

 

LABORATORY

