



# THEVENIN'S THEOREM

## BASIC CIRCUIT ANALYSIS METHOD

---

*prepared by:*

**Gyro A. Madrona**  
Electronics Engineer

# TOPIC OUTLINE

## Thevenin's Theorem



# THEVENIN'S THEOREM




# THEVENIN'S THEOREM

---


Thevenin's theorem states that it is possible to simplify any linear circuit, irrespective of how complex it is, to an equivalent circuit with a single voltage source ( $v_{TH}$ ) and a series resistance ( $R_{TH}$ ).

Arbitrary Network

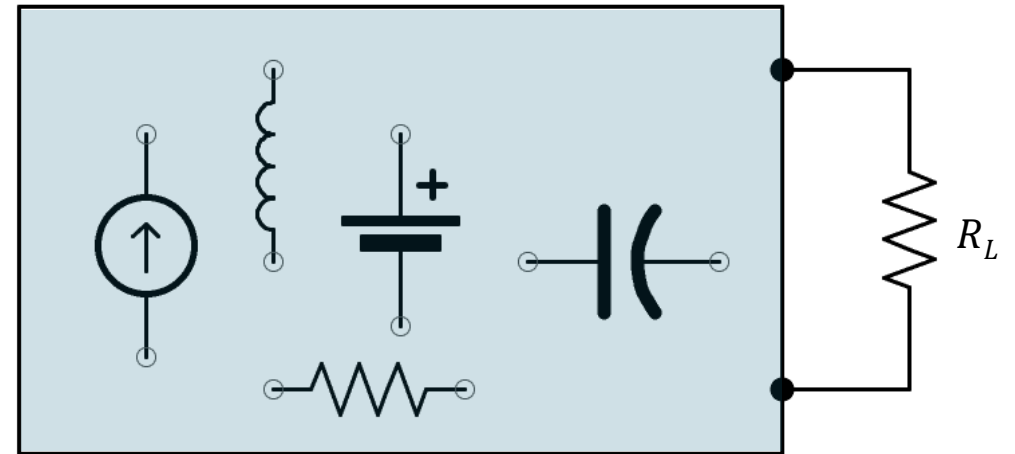


# THEVENIN'S THEOREM

## Thevenin's Equivalent Circuit

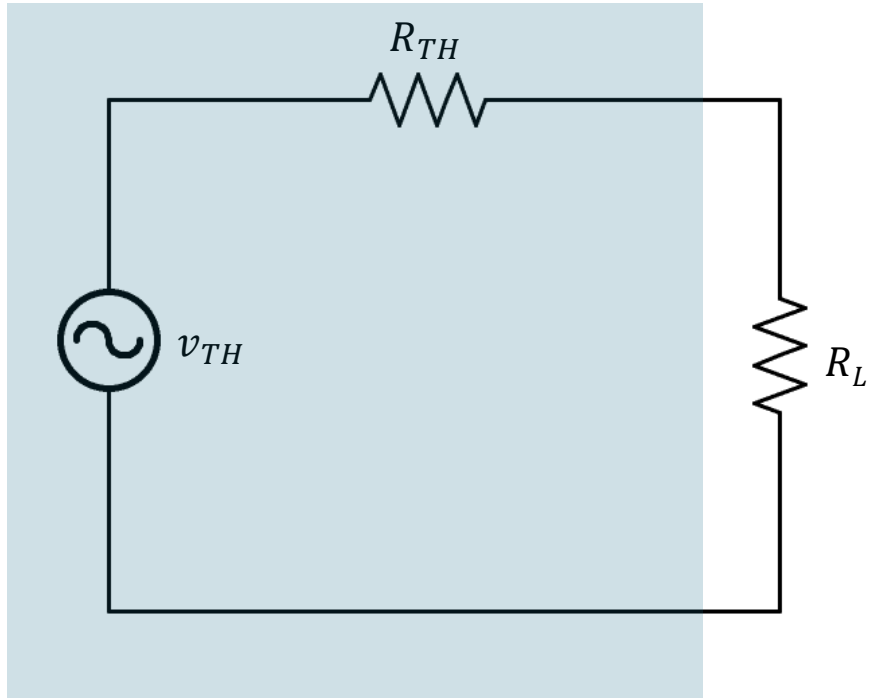


## Arbitrary Network

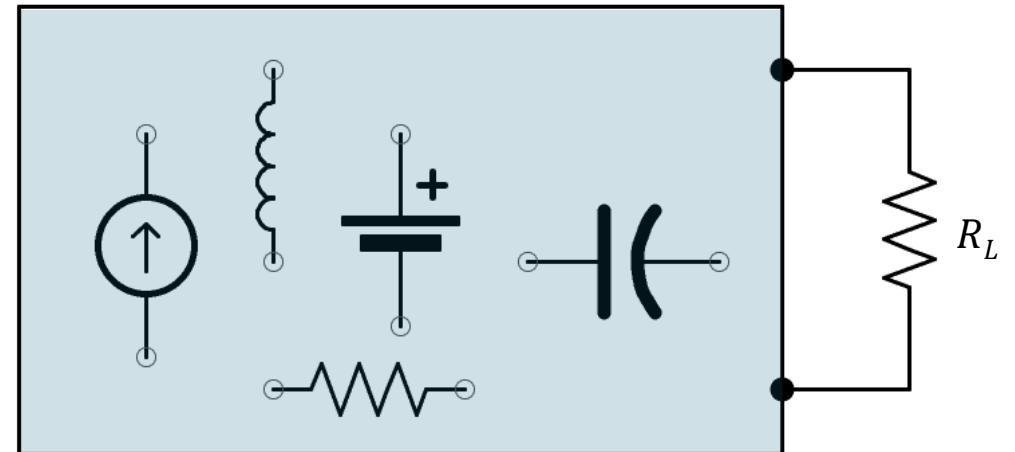

# STEPS TO APPLY THEVENIN'S THEOREM


---

1. Identify the load.

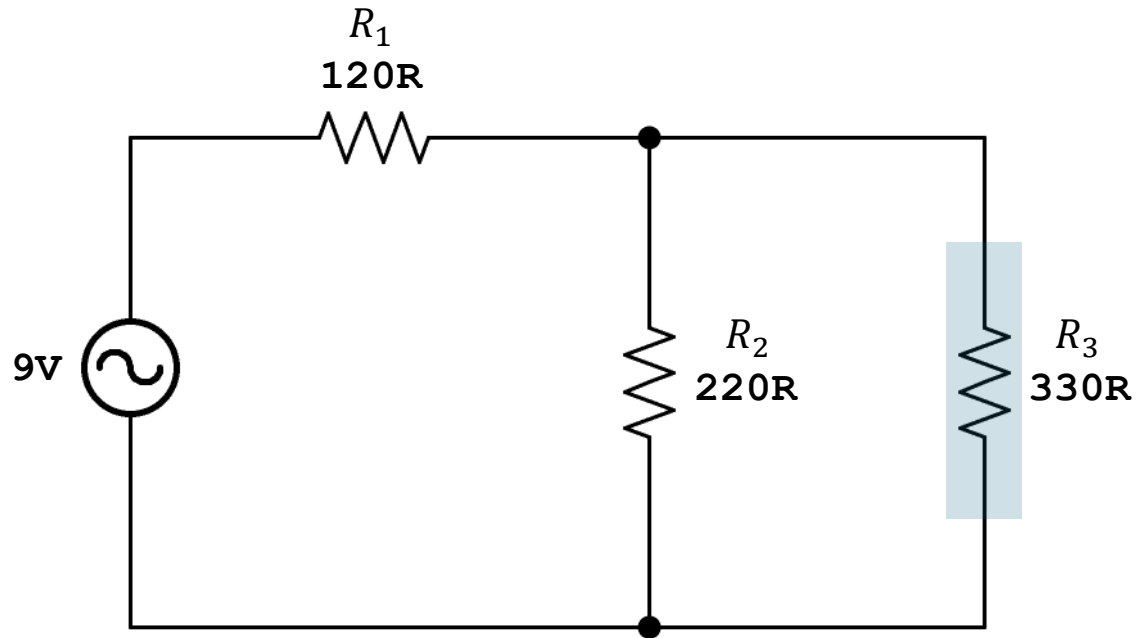

# STEPS TO APPLY THEVENIN'S THEOREM


---

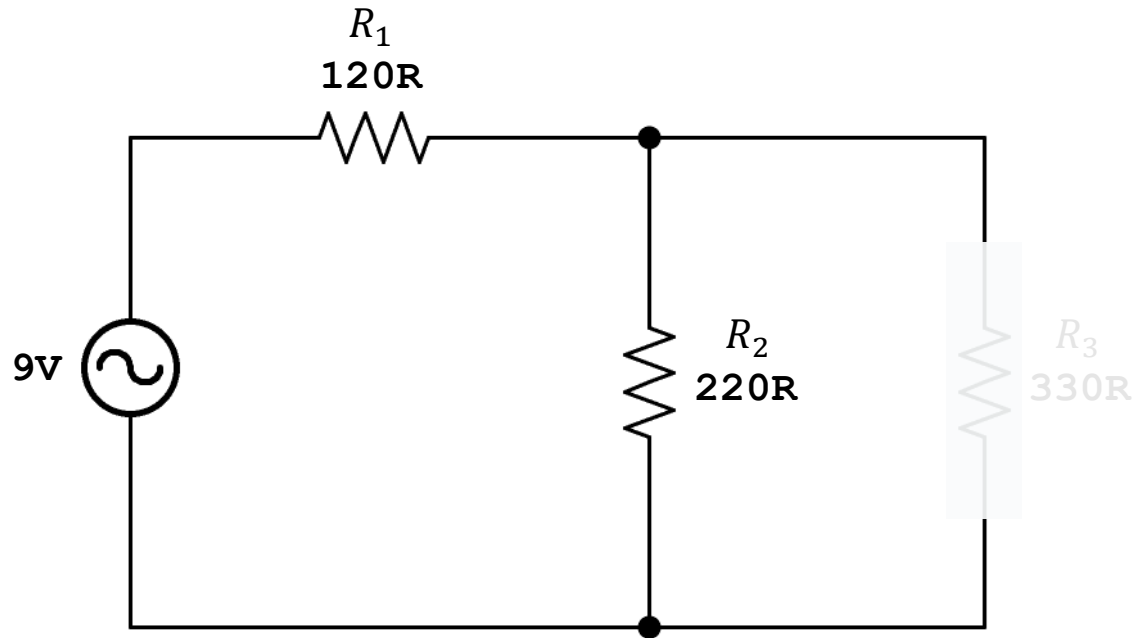

1. Identify the load.
2. Remove the load.



# STEPS TO APPLY THEVENIN'S THEOREM

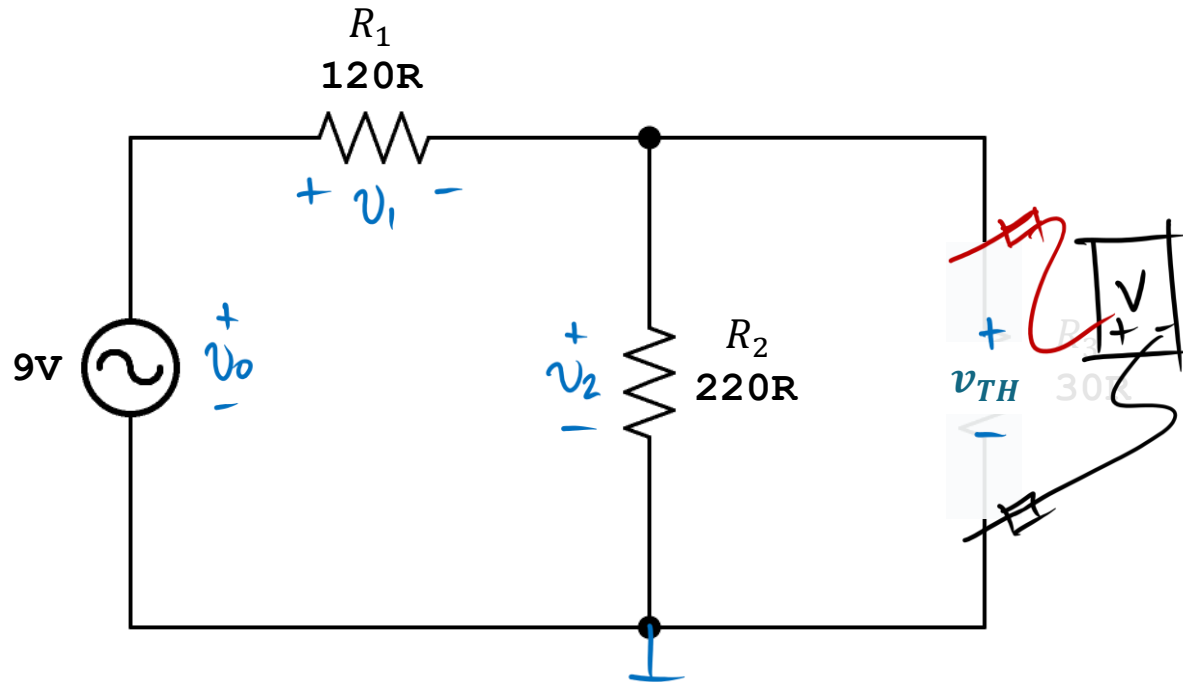

1. Identify the load.

2. Remove the load.

3. Determine the Thevenin voltage ( $v_{th}$ ):

Calculate the open-circuit voltage across the terminals where the load was connected.

by VOT


$$v_{th} = v_o \frac{R_2}{R_1 + R_2}$$

$$v_{th} = 9 \frac{220}{120 + 220}$$

$$\underline{v_{th} = 5.82 \text{ V}}$$



# STEPS TO APPLY THEVENIN'S THEOREM

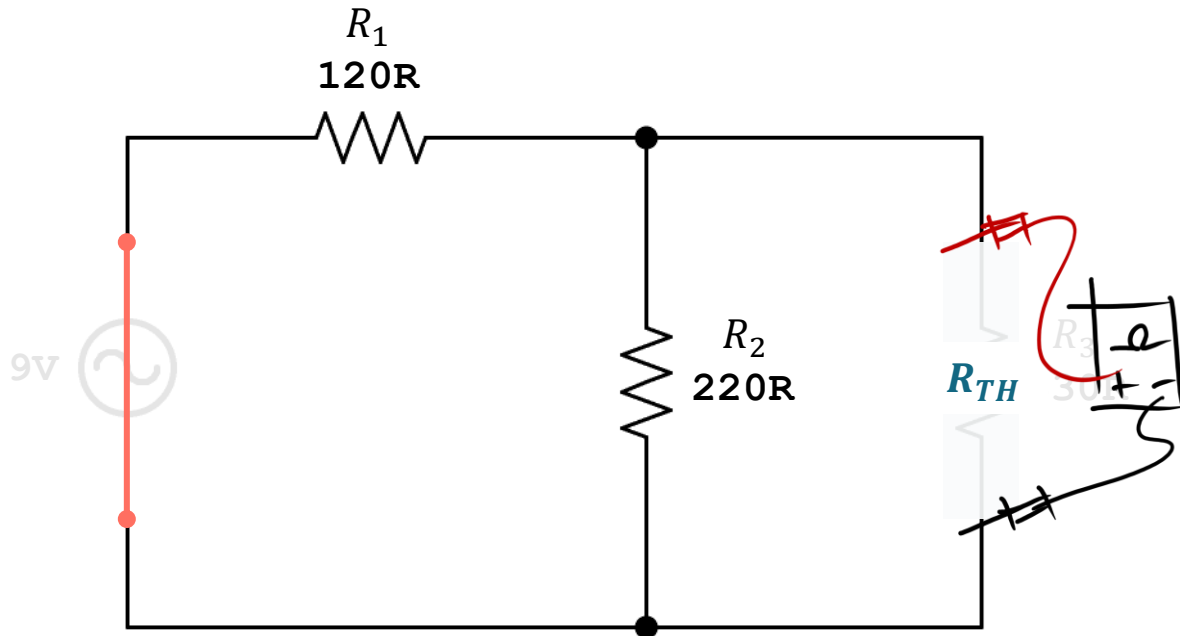


1. Identify the load.
2. Remove the load.
3. Determine the Thevenin voltage ( $v_{th}$ ):  
Calculate the open-circuit voltage across the terminals where the load was connected.
4. Determine the Thevenin Resistance ( $R_{TH}$ ):  
Set all independent sources to zero and calculate the equivalent resistance looking into the terminals where the load was connected.

$$\frac{1}{R_{TH}} = \frac{1}{R_1} + \frac{1}{R_2} \quad \frac{1}{R_{TH}} = \frac{17}{1320}$$

$$\frac{1}{R_{TH}} = \frac{1}{120} + \frac{1}{220} \quad \underline{R_{TH} = 77.65\Omega}$$

# STEPS TO APPLY THEVENIN'S THEOREM

## Thevenin Equivalent Circuit

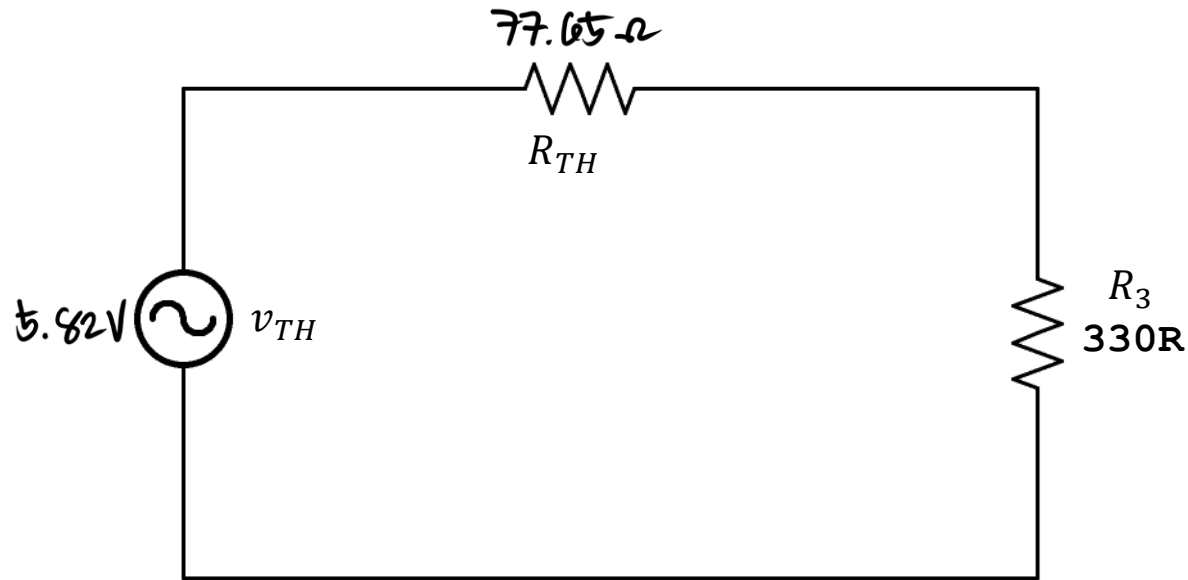


1. Identify the load.
2. Remove the load.
3. Determine the Thevenin voltage ( $v_{th}$ ):  
Calculate the open-circuit voltage across the terminals where the load was connected.
4. Determine the Thevenin Resistance ( $R_{TH}$ ):  
Set all independent sources to zero and calculate the equivalent resistance looking into the terminals where the load was connected.
5. Replace the original circuit with Thevenin equivalent and reconnect the load.



# STEPS TO APPLY THEVENIN'S THEOREM

## Thevenin Equivalent Circuit

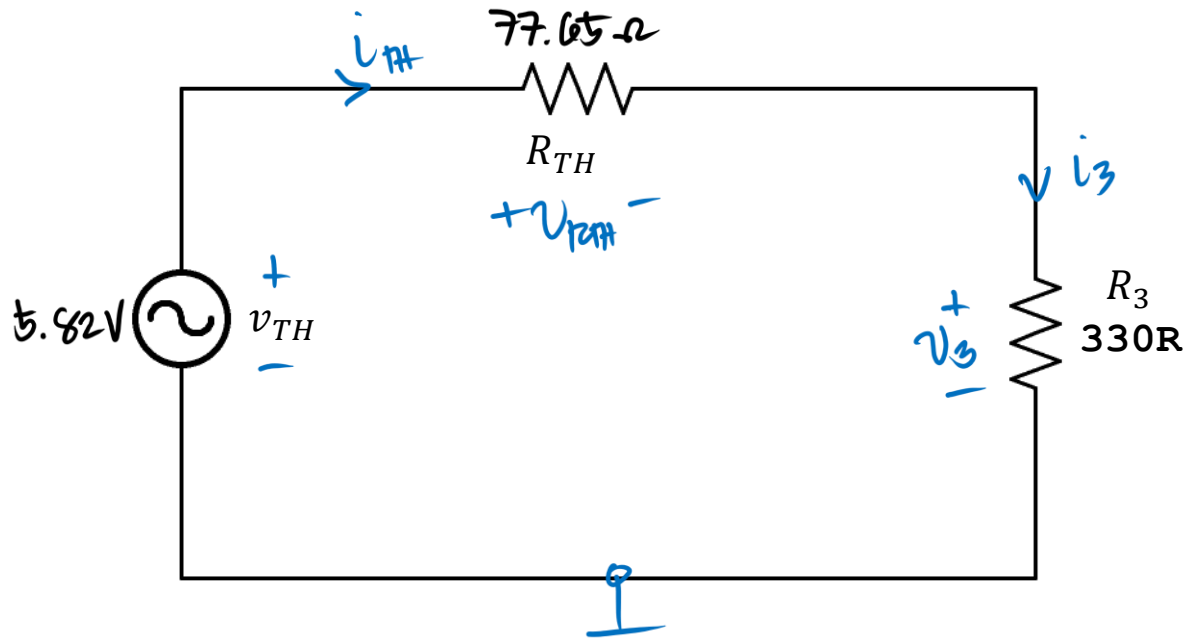

by VPT

$$v_3 = v_{TH} \frac{R_3}{R_{TH} + R_3}$$

$$v_3 = 5.82 \frac{330}{77.65 + 330}$$

$$v_3 = 4.71 V$$

*ans*

$$i_3 = \frac{v_3}{R_3}$$

$$i_3 = \frac{4.71}{330}$$


$$i_3 = 14.27 \mu A$$

*ans*


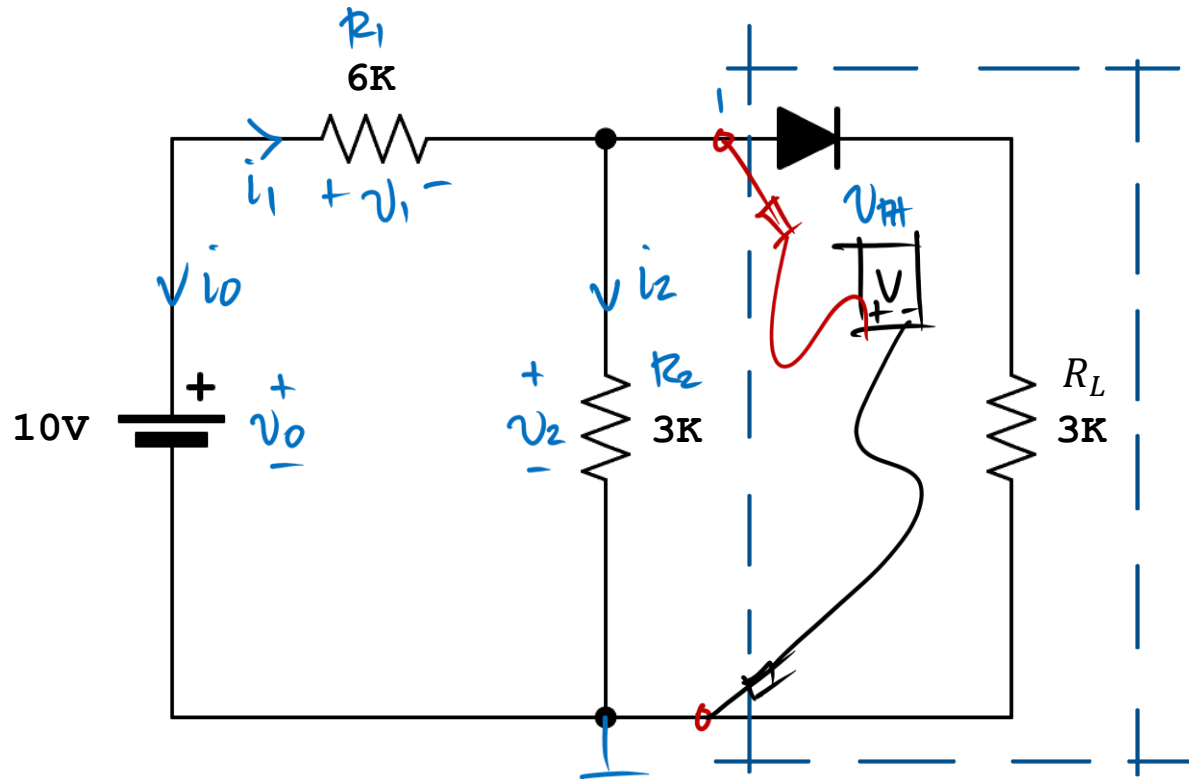
## EXERCISE

Use the 2<sup>nd</sup> approximation diode to calculate the load voltage and load current of the given network.



Solution

Thevenin Voltage

$$V_{TH} = V_0 \frac{r_2}{r_1 + r_2}$$


$$V_{TH} = 10 \frac{3\text{K}}{6\text{K} + 3\text{K}}$$

$$\underline{V_{TH} = 3.33\text{V}}$$


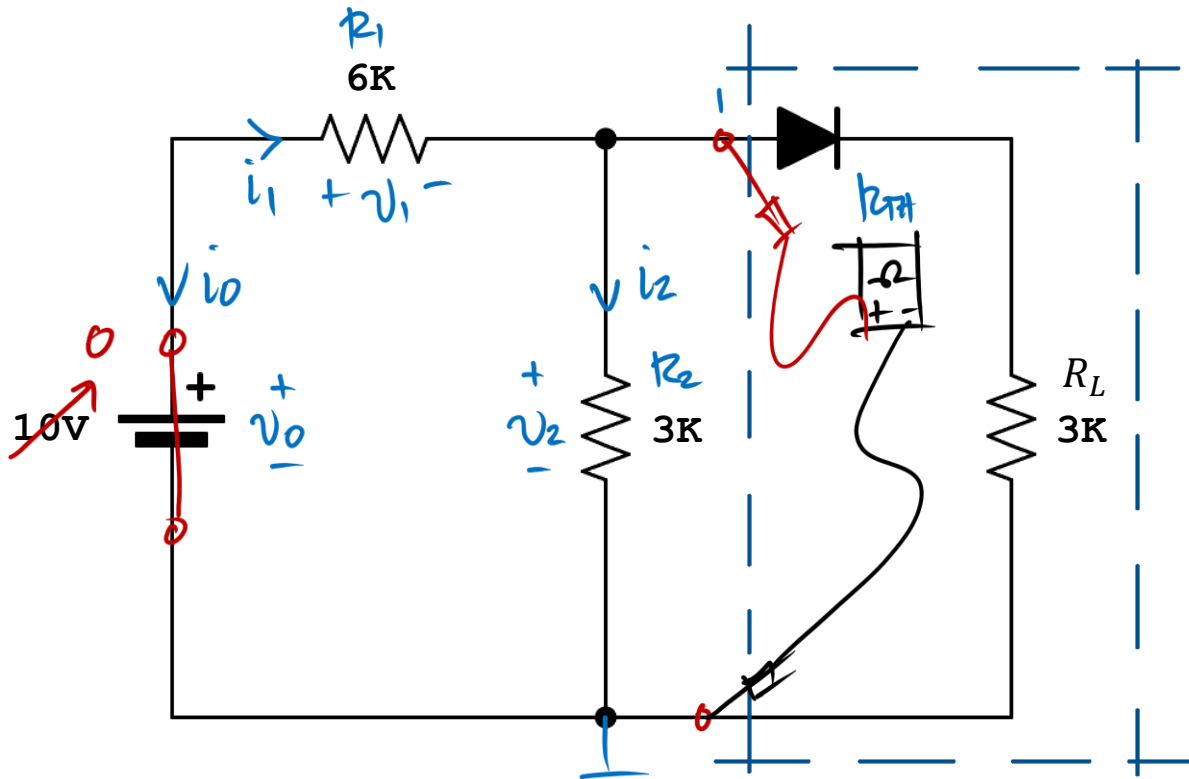
## EXERCISE

Use the 2<sup>nd</sup> approximation diode to calculate the load voltage and load current of the given network.



Solution

Thevenin Resistance

$$\frac{1}{R_{TH}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{TH}} = \frac{1}{6K} + \frac{1}{3K}$$


$$\frac{1}{R_{TH}} = \frac{1}{2K}$$

$$\underline{R_{TH} = 2K}$$


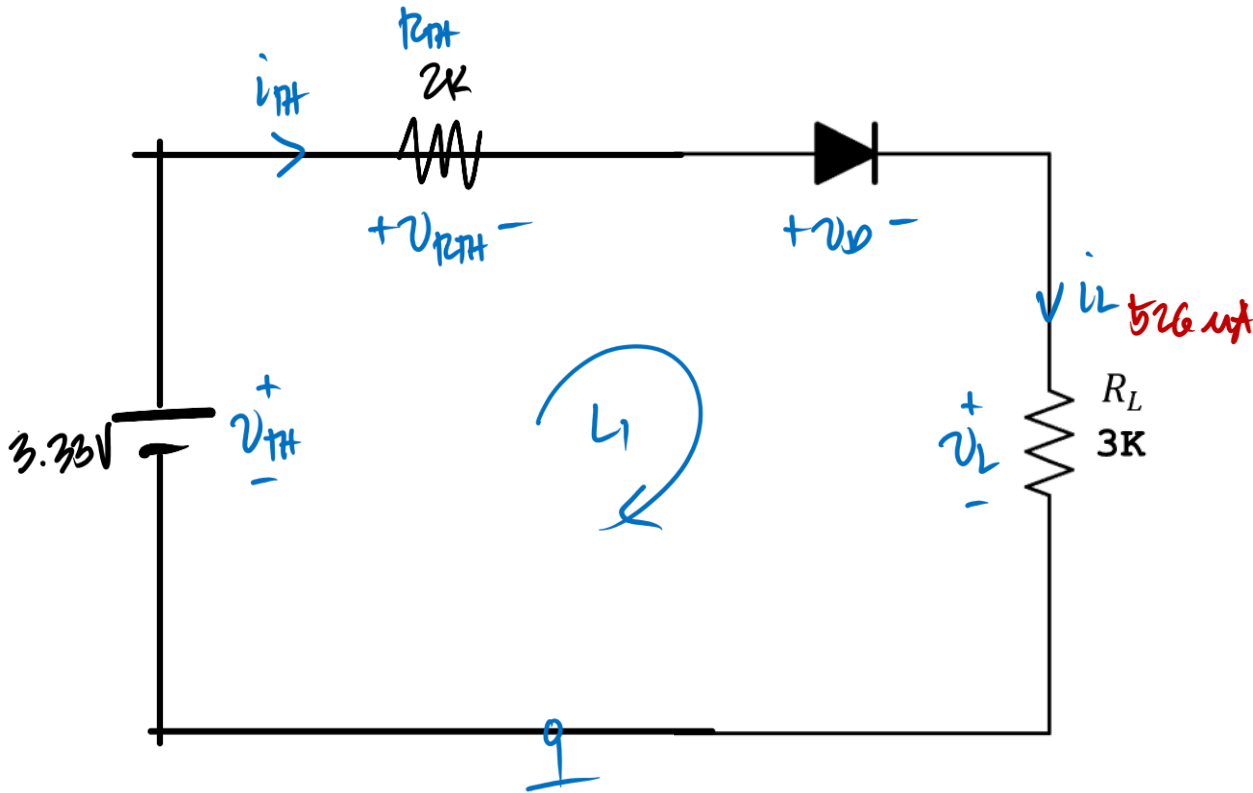
## EXERCISE

Use the 2<sup>nd</sup> approximation diode to calculate the load voltage and load current of the given network.



Solution

KVL @  $L_1$

$$-v_{TH} + v_{RTH} + v_D + v_L = 0$$

$$v_{RTH} + v_L = v_{TH} - v_D$$

$$\cancel{i_{TH}} R_{TH} + i_L R_L = v_{TH} - v_D$$

$$i_L (R_{TH} + R_L) = \frac{v_{TH} - \cancel{v_D}}{\dots} \rightarrow 0.7$$


$$i_L = \frac{3.33 - 0.7}{2k + 3k}$$

$$i_L = 526 \mu A$$

ans
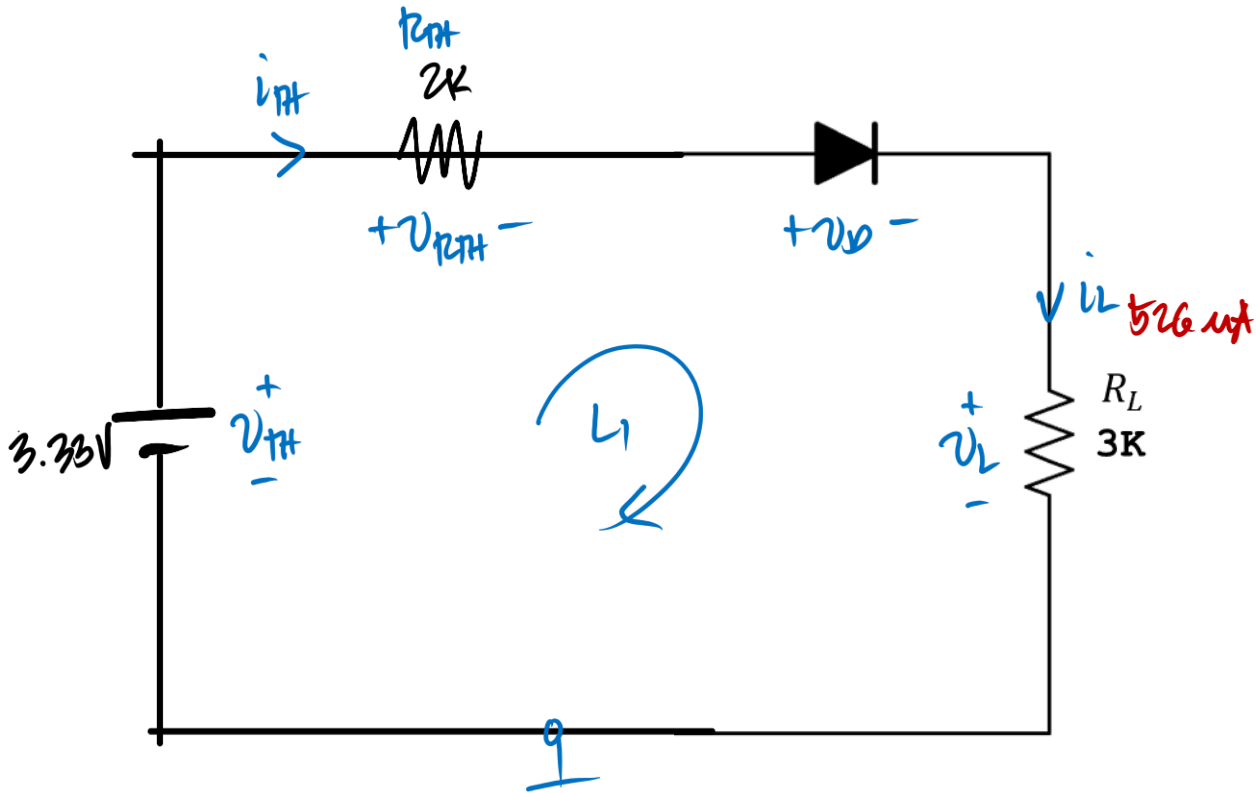
## EXERCISE

Use the 2<sup>nd</sup> approximation diode to calculate the load voltage and load current of the given network.



Solution

$$v_L = i_L R_L$$

$$v_L = 526 \mu A (3k)$$

$$v_L = 1.58 V$$

ans



# LABORATORY

