



# **ELEMENT COMBINATION** **RULE**

## **BASIC CIRCUIT ANALYSIS METHOD**

---

*prepared by:*

**Gyro A. Madrona**

Electronics Engineer

# TOPIC OUTLINE

Ohm's Law

Series Network

Parallel Network

Series-Parallel Network



# OHM'S LAW



# OHM'S LAW

---

Ohm's Law states that the ratio of voltage ( $V$ ) to current ( $I$ ) is constant ( $R$ ).

Mathematical representation

$$R = \frac{V}{I}$$

Basic Electrical Quantities

## 1. Voltage ( V )

The measure of electrical potential energy per unit charge. It is the "push" or "force" that drives electric current through a circuit.

Formula

$$V = IR$$

unit: Volt ( V )



# OHM'S LAW

---

Ohm's Law states that the ratio of voltage ( $V$ ) to current ( $I$ ) is constant ( $R$ ).

Mathematical representation

$$R = \frac{V}{I}$$

Basic Electrical Quantities

## 2. Current ( I )

The flow of electric charge, typically carried by electrons in a conductor. It represents the rate at which charge flows through a point in a circuit.

Formula

$$I = \frac{V}{R}$$

unit: Ampere ( A )



# OHM'S LAW

---

Ohm's Law states that the ratio of voltage ( $V$ ) to current ( $I$ ) is constant ( $R$ ).

Mathematical representation

$$R = \frac{V}{I}$$

Basic Electrical Quantities

### 3. Resistance ( $R$ )

The opposition to the flow of electric current in a material or component. It determines how much current will flow for a given voltage.

Formula


$$R = \frac{V}{I}$$

unit: Ohm (  $\Omega$  )


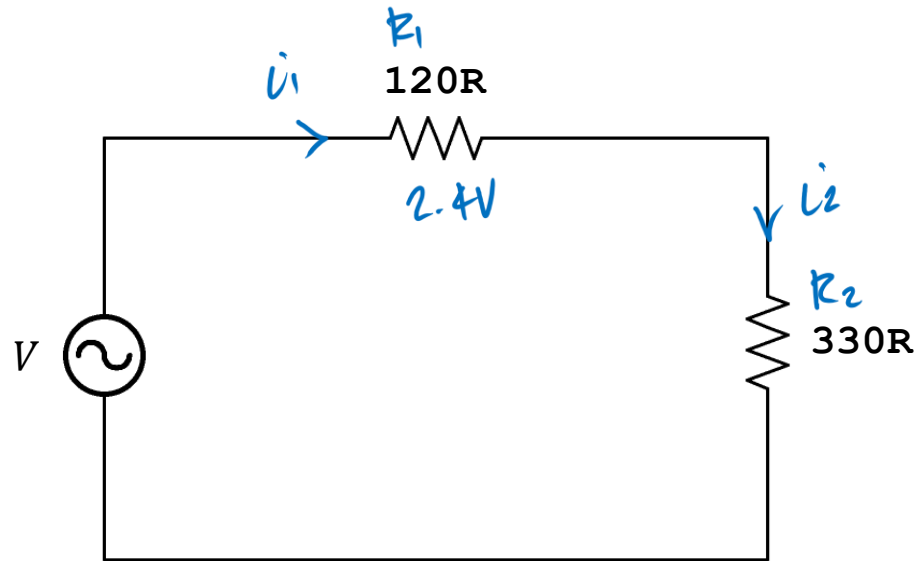
## EXERCISE

In the given circuit, the voltage drop across a  $120\Omega$  resistor is measured as 2.4V. Determine the current flowing through the resistors.



Solution

$$i_1 = \frac{V_1}{R_1}$$
$$= \frac{2.4}{120}$$

$$i_1 = 20\text{mA}$$

ans

$$i_2 = 20\text{mA}$$


ans

Series network :  $i_1 = i_2$


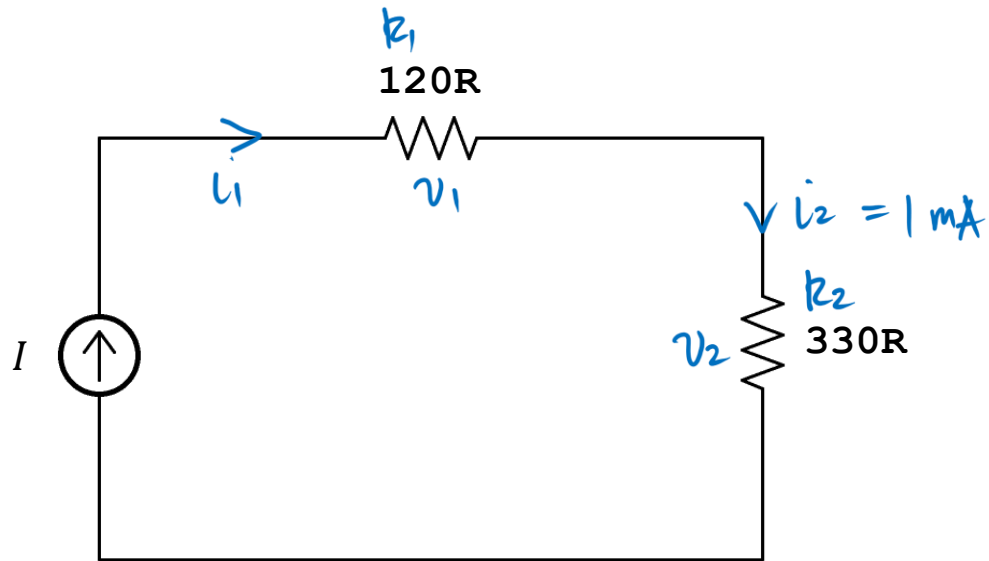
## EXERCISE

A  $330\ \Omega$  resistor in the given circuit carries a current of  $1\text{mA}$ . Calculate the voltage drop across the resistors.



Solution

$$v_2 = i_2 R_2$$

$$v_2 = (1\text{m})(330)$$

$$v_2 = 330\text{mV}$$

ans

$$v_1 = i_1 R_1$$

$$v_1 = (1\text{m})(120)$$

$$v_1 = 120\text{mV}$$


ans




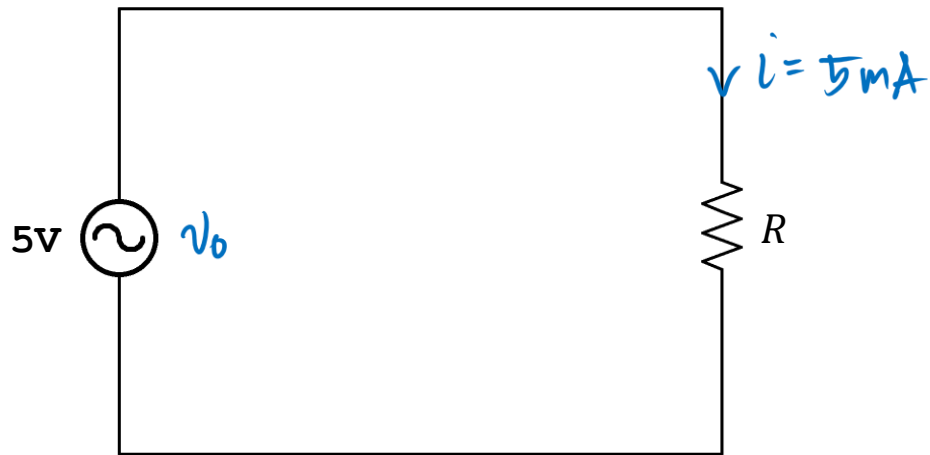
## EXERCISE

The given circuit has an applied voltage of 5V, resulting in a current flow of 5mA. Determine the resistance of the circuit.



Solution

$$R = \frac{v_0}{i}$$
$$= \frac{5}{5m}$$

$$R = 1k\Omega$$

ans




# SERIES NETWORK



# SERIES NETWORK

A series network refers to a configuration where components are connected end-to-end, forming a single path for current to flow.

Series Network

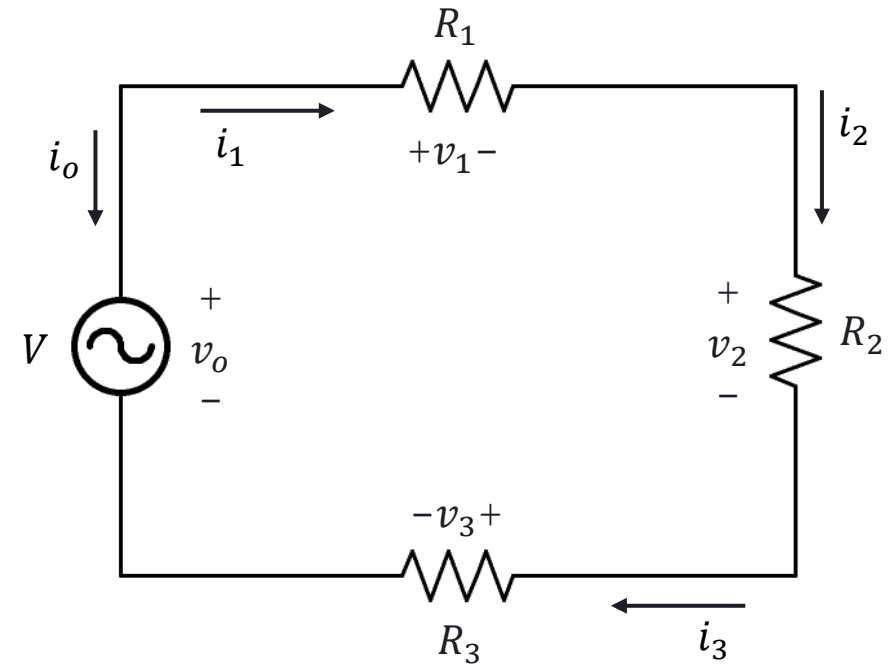


# CURRENT

In a series network, the same current flows through all components.

Mathematical representation

$$i_o = i_1 = i_2 = i_3 = \cdots i_n$$

Series Network

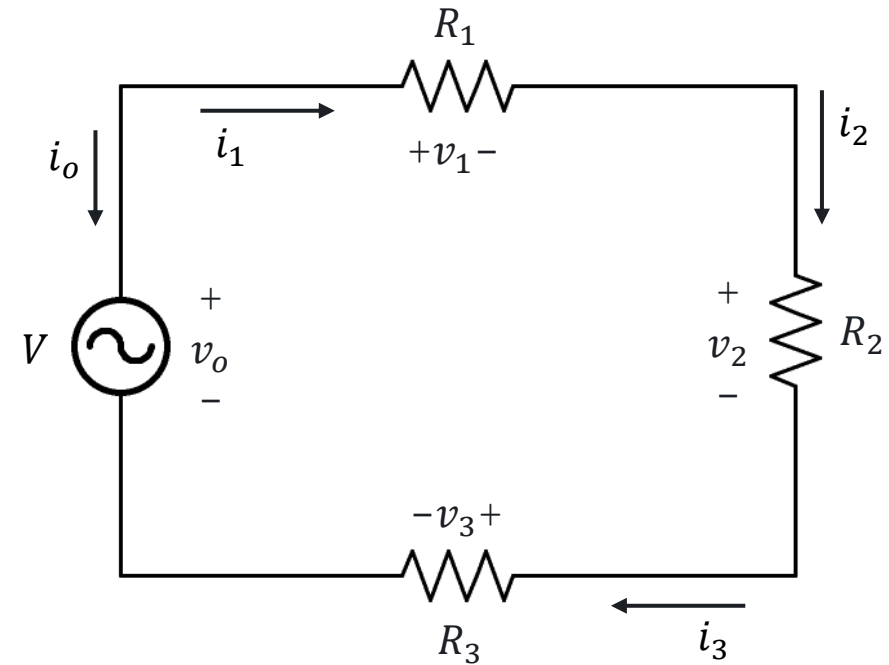


# RESISTANCE

In a series network, the total resistance is the sum of the individual resistances.

Mathematical representation

$$R_o = R_1 + R_2 + R_3 + \cdots R_n$$

## Series Network

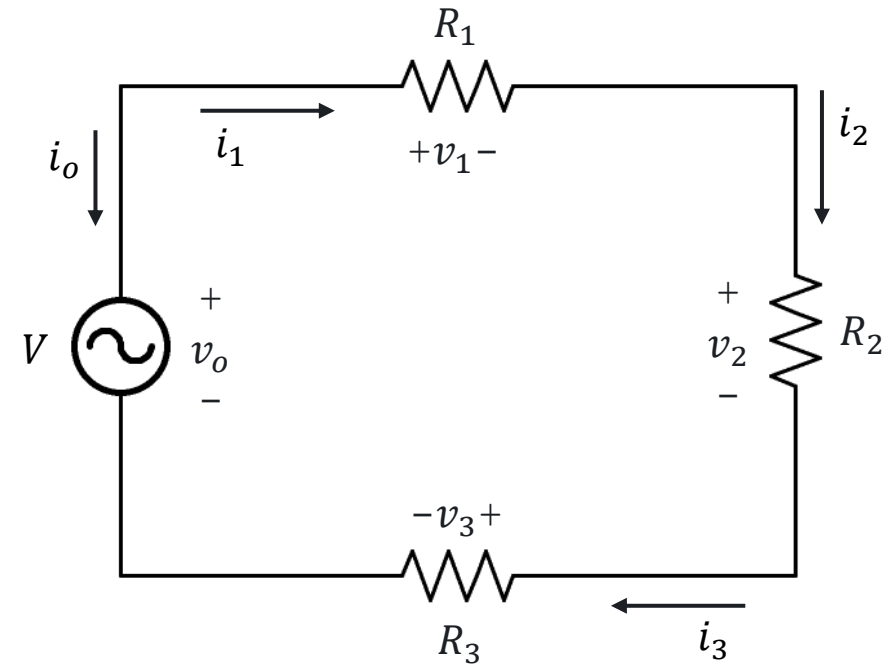


# VOLTAGE

In a series network, the total voltage is the sum of the voltages across each individual component.

Mathematical representation


$$v_o = v_1 + v_2 + v_3 + \cdots v_n$$

Series Network

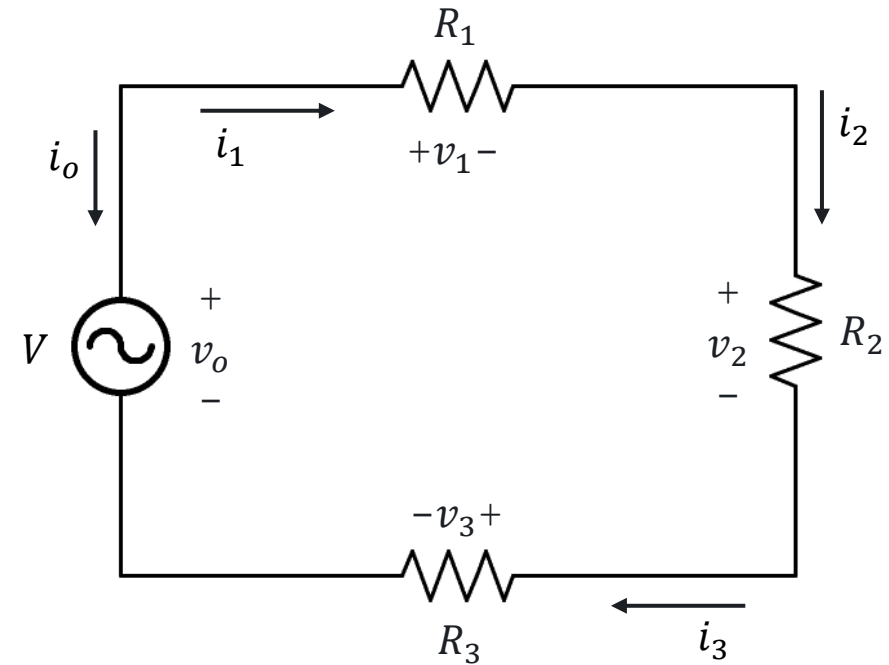
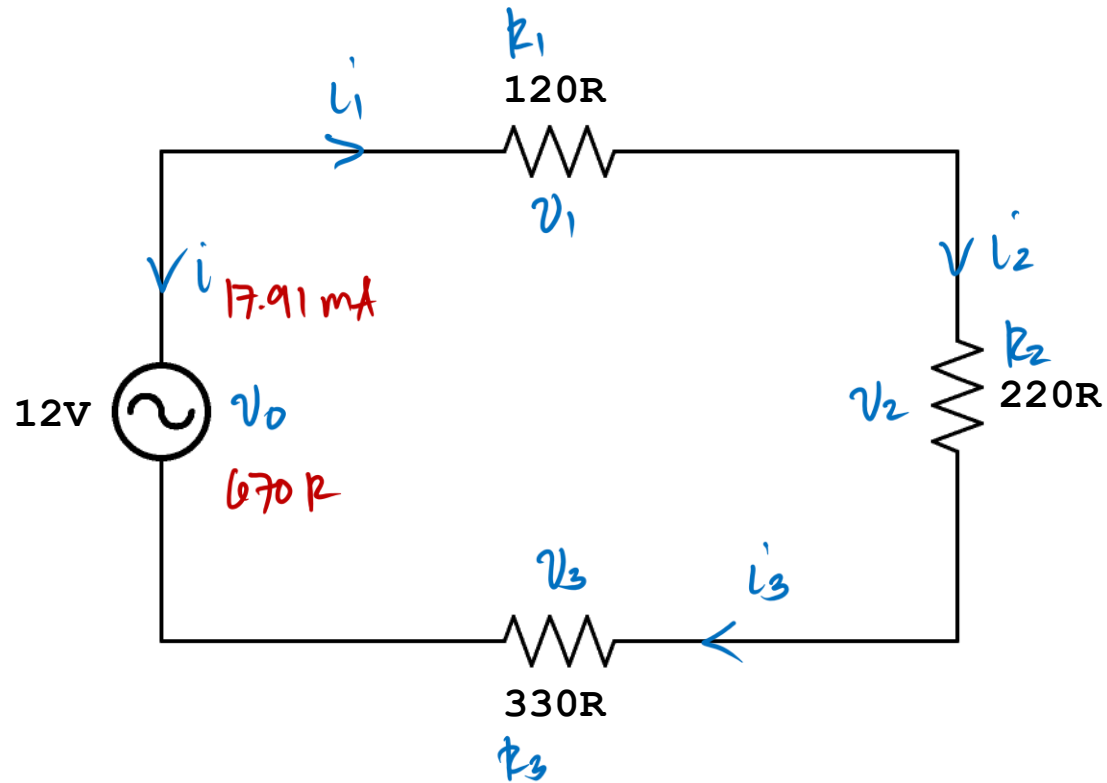
## EXERCISE

For the given series circuit, determine the voltage drops across each individual resistor.



Solution

Total resistance

$$R_0 = R_1 + R_2 + R_3$$

$$R_0 = 120 + 220 + 330$$

$$R_0 = 670 \Omega$$

Total Current


$$i_0 = \frac{v_0}{R_0}$$

$$i_0 = \frac{12}{670}$$

$$i_0 = 17.91 \text{ mA}$$
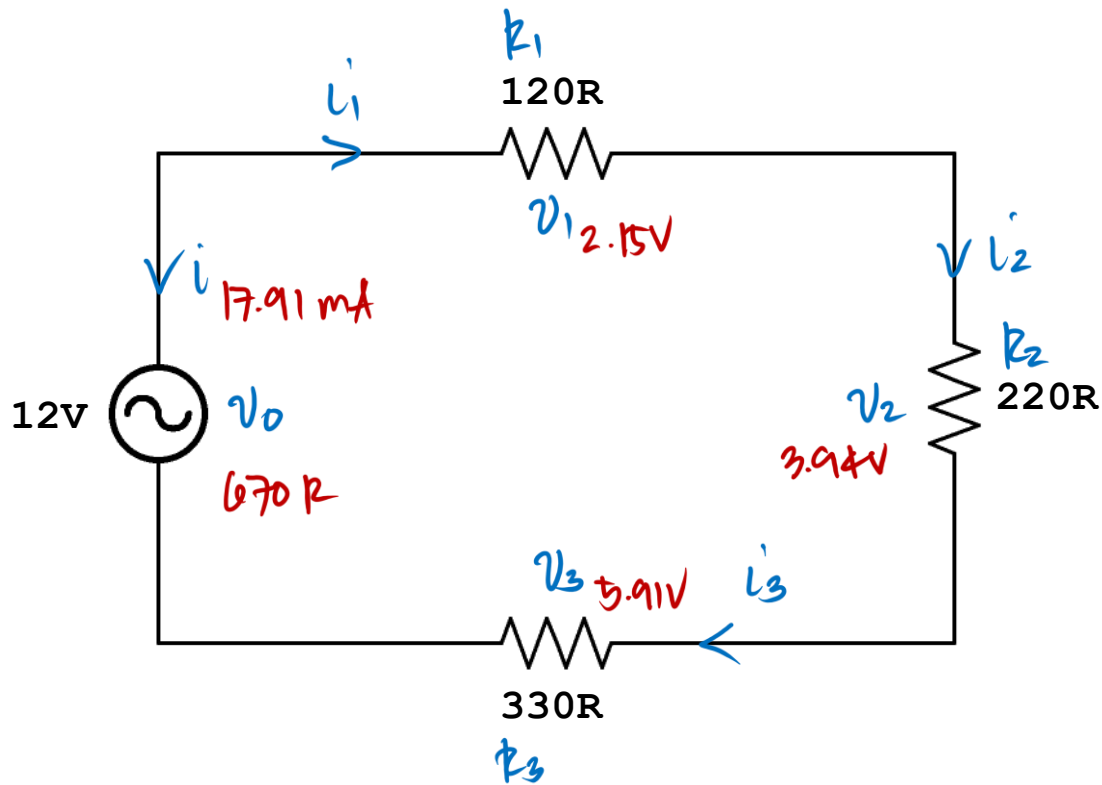
## EXERCISE

For the given series circuit, determine the voltage drops across each individual resistor.



Solution

Series network

$$i_0 = i_1 = i_2 = i_3$$

$$V_1 = i_1 R_1$$

$$V_1 = 17.91 \text{ m}(120)$$

$$V_1 = 2.15 \text{ V}$$

ans

$$V_2 = i_1 R_2$$

$$V_2 = 17.91 \text{ m}(220)$$

$$V_2 = 3.94 \text{ V}$$

ans

$$V_3 = i_3 R_3$$

$$V_3 = 17.91 \text{ m}(330)$$

$$V_3 = 5.91 \text{ V}$$

ans

$$V_0 = V_1 + V_2 + V_3$$

$$V_0 = 2.15 + 3.94 + 5.91$$

$$V_0 = 12 \text{ V} \checkmark$$




# PARALLEL NETWORK

---

A parallel network is a configuration where components are connected across the same two points, providing multiple paths for current to flow.

Parallel Network

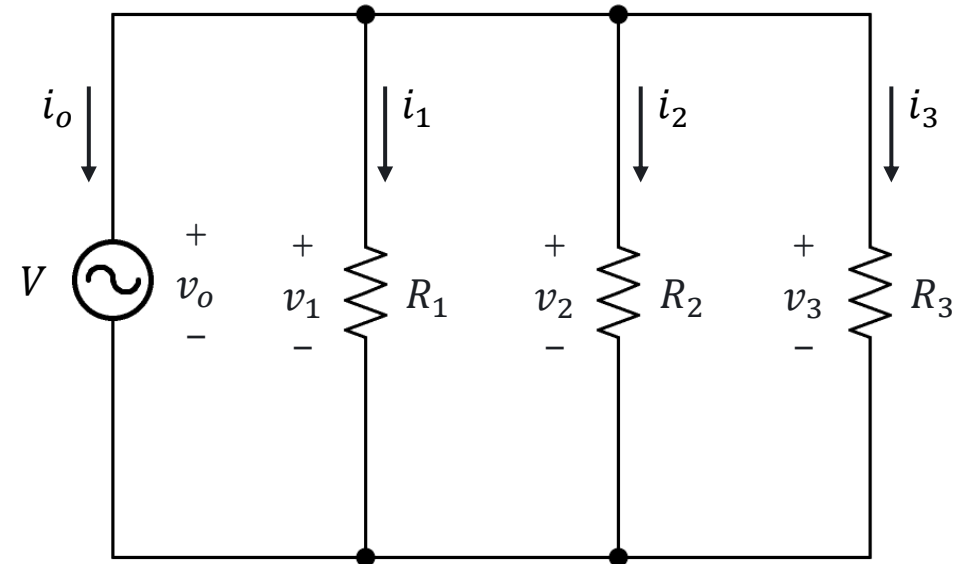

# VOLTAGE


---

In a parallel network, the voltage is the same across all components.

Mathematical representation

$$v_o = v_1 = v_2 = v_3 = \cdots v_n$$

## Parallel Network

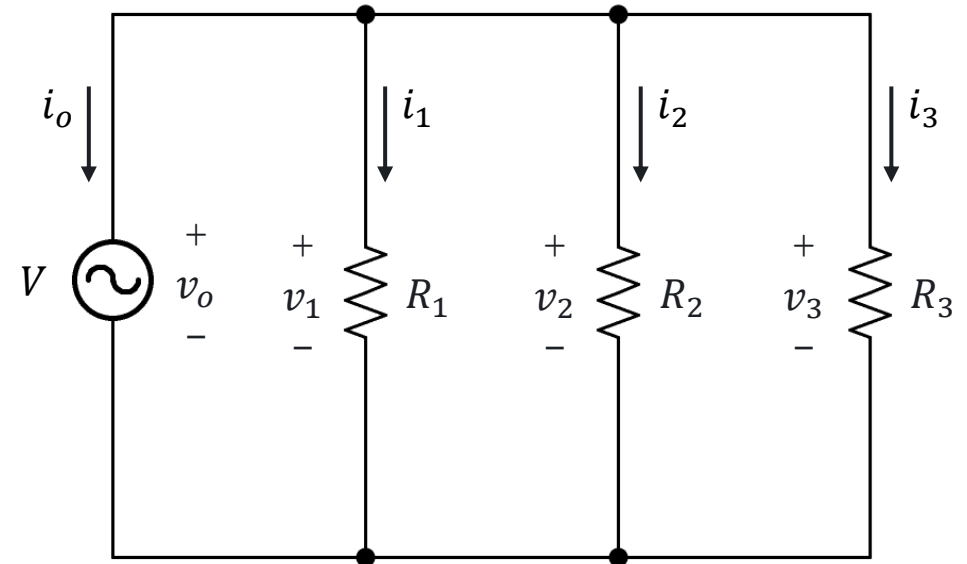


# CONDUCTANCE

Conductance refers to the ability of the network to allow the flow of electric current. It is the reciprocal of resistance and is measured in siemens ( $\mathcal{S}$ ).

Mathematical representation

$$G = \frac{1}{R}$$

Parallel Network

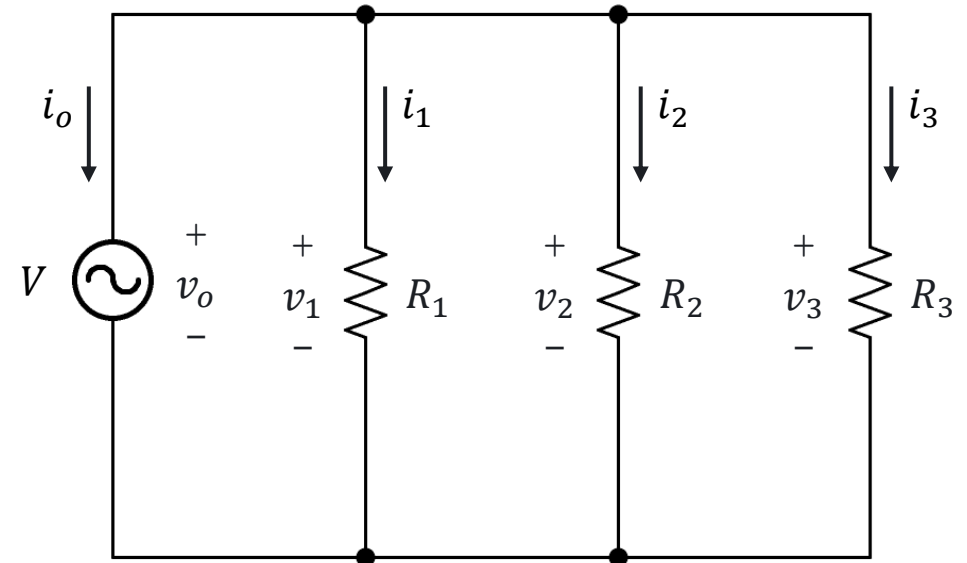


# CONDUCTANCE

In a parallel network, the total conductance is the sum of the individual conductance of each resistor.

Mathematical representation

$$G_o = G_1 + G_2 + G_3 + \cdots G_n$$

Parallel Network

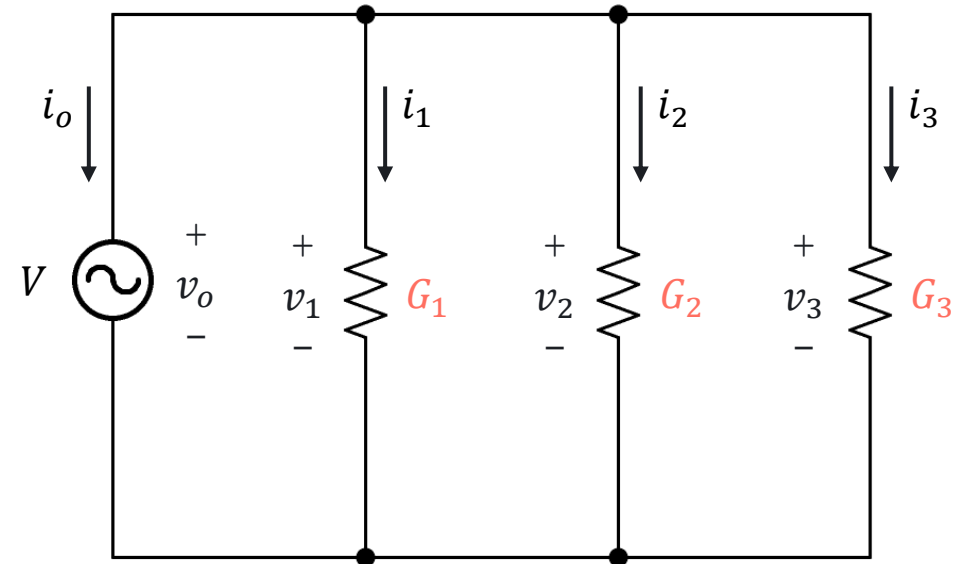


# CURRENT

In a parallel network, the total current is the sum of the current flowing through each individual component.

Mathematical representation


$$i_o = i_1 + i_2 + i_3 + \cdots i_n$$

Parallel Network

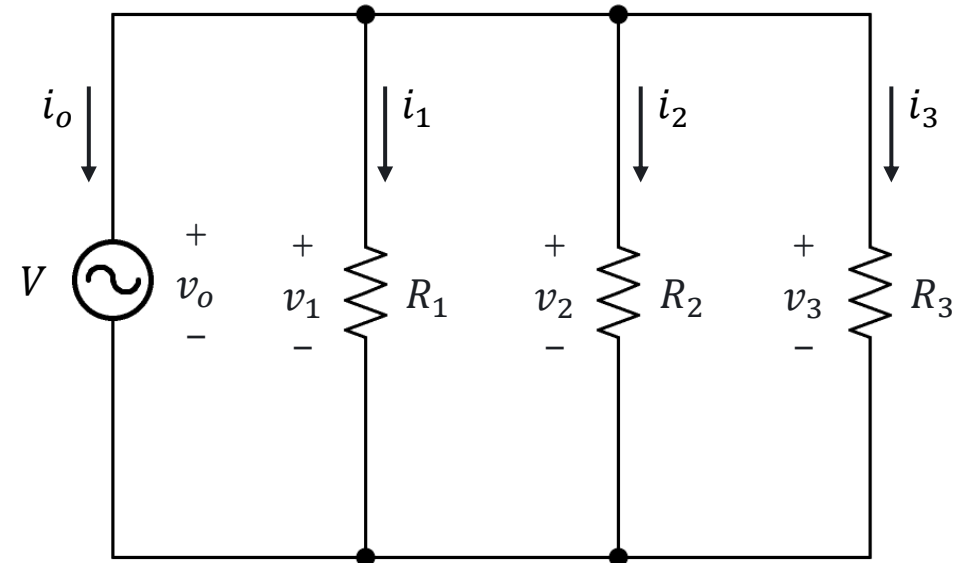
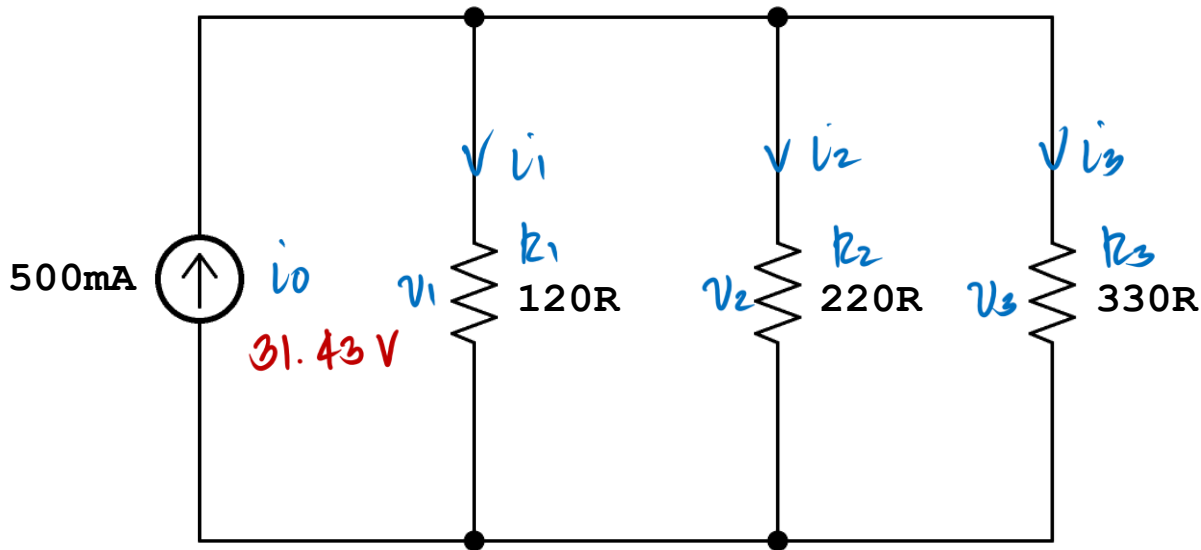
## EXERCISE

For the given parallel circuit, determine the current flowing through each individual resistor.



Solution

Total Conductance

$$G_0 = G_1 + G_2 + G_3$$

$$G_0 = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$G_0 = \frac{1}{120} + \frac{1}{220} + \frac{1}{330}$$

$$G_0 = \frac{7}{440} \text{ S}$$

Total Resistance

$$R_0 = \frac{1}{G_0}$$

$$R_0 = \frac{440}{7} \Omega$$

Total Voltage


$$V_0 = i_0 R_0$$

$$V_0 = 500 \text{ m} \left( \frac{440}{7} \right)$$

$$V_0 = 31.43 \text{ V}$$
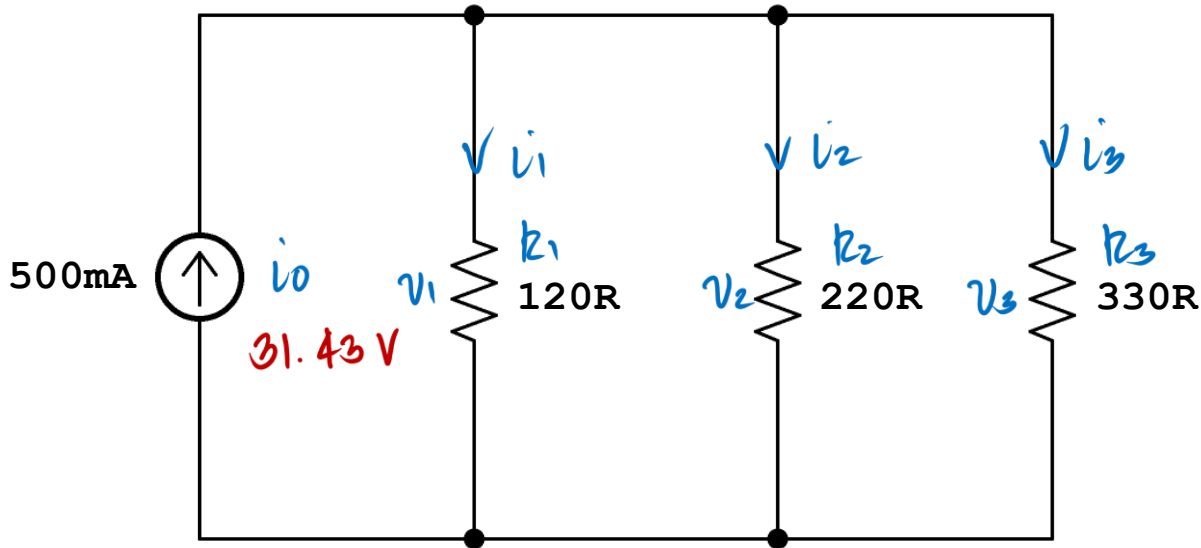
## EXERCISE

For the given parallel circuit, determine the current flowing through each individual resistor.



$$i_0 = 261.92 + 142.86 + 95.24 = \underline{500.02 \text{ mA}} \checkmark$$

Solution

Parallel Network

$$v_0 = v_1 = v_2 = v_3$$

$$i_1 = \frac{v_1}{R_1}$$

$$i_1 = \frac{31.43}{120}$$

$$i_1 = 261.92 \text{ mA}$$

ans

$$i_2 = \frac{v_2}{R_2}$$
$$= \frac{31.43}{220}$$

$$i_2 = 142.86 \text{ mA}$$

ans

$$i_3 = \frac{v_3}{R_3}$$
$$= \frac{31.43}{330}$$

$$i_3 = 95.24 \text{ mA}$$

ans



# SERIES PARALLEL NETWORK






# SERIEL-PARALLEL NETWORK


A series-parallel network is a type of electrical network that combines elements of both series and parallel circuits. These networks are commonly used in electrical and electronic systems to achieve desired voltage, current, and resistance characteristics.

Series-Parallel Network

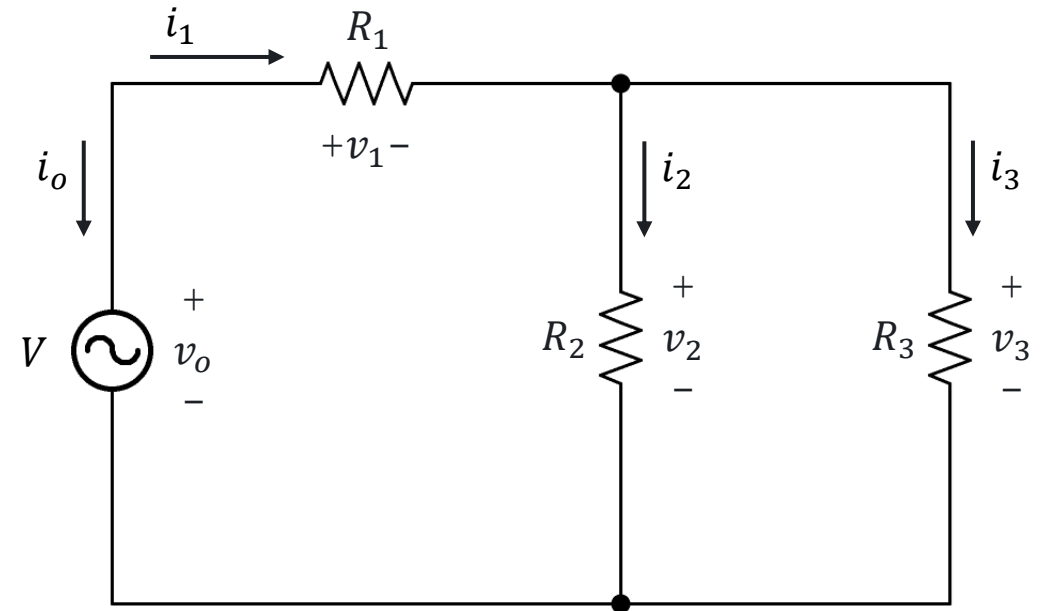

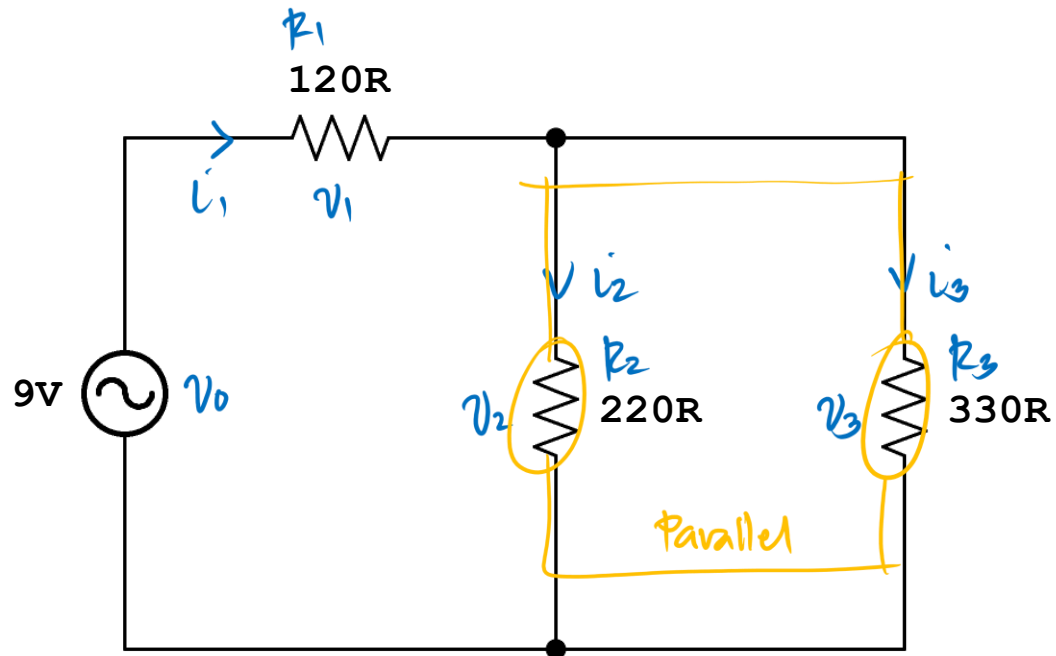
## EXERCISE

Analyze the given circuit to determine both the current through and the voltage drop across each resistor.



Solution

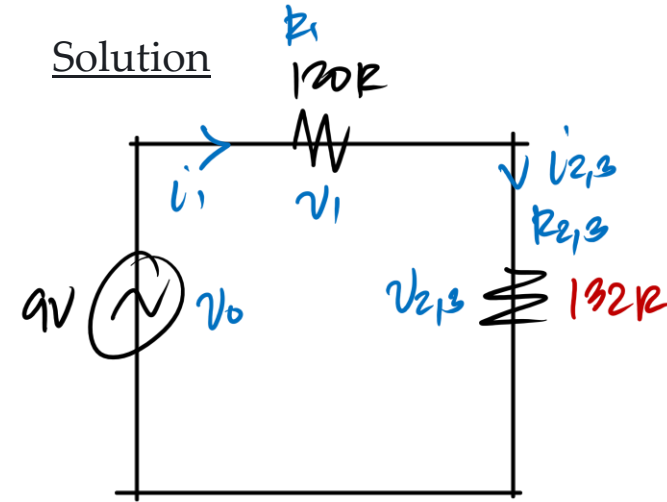

Equivalent resistance of  $R_2 // R_3$

$$G_{2,3} = G_2 + G_3$$



$$\frac{1}{R_{2,3}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{2,3}} = \frac{1}{220} + \frac{1}{330}$$

$$\underline{R_{2,3} = 132 \Omega}$$
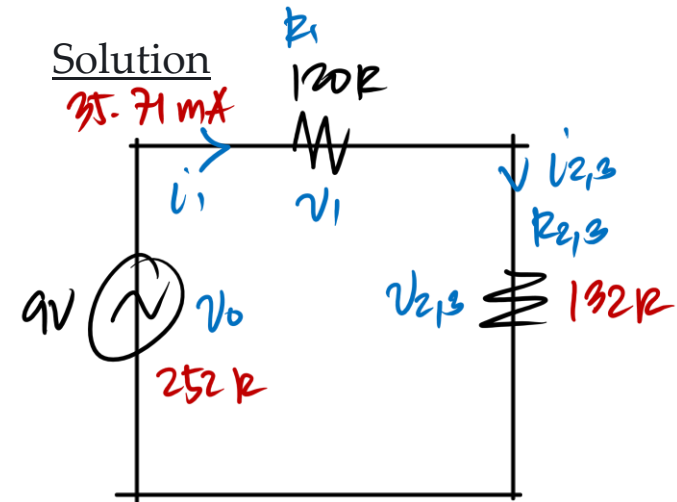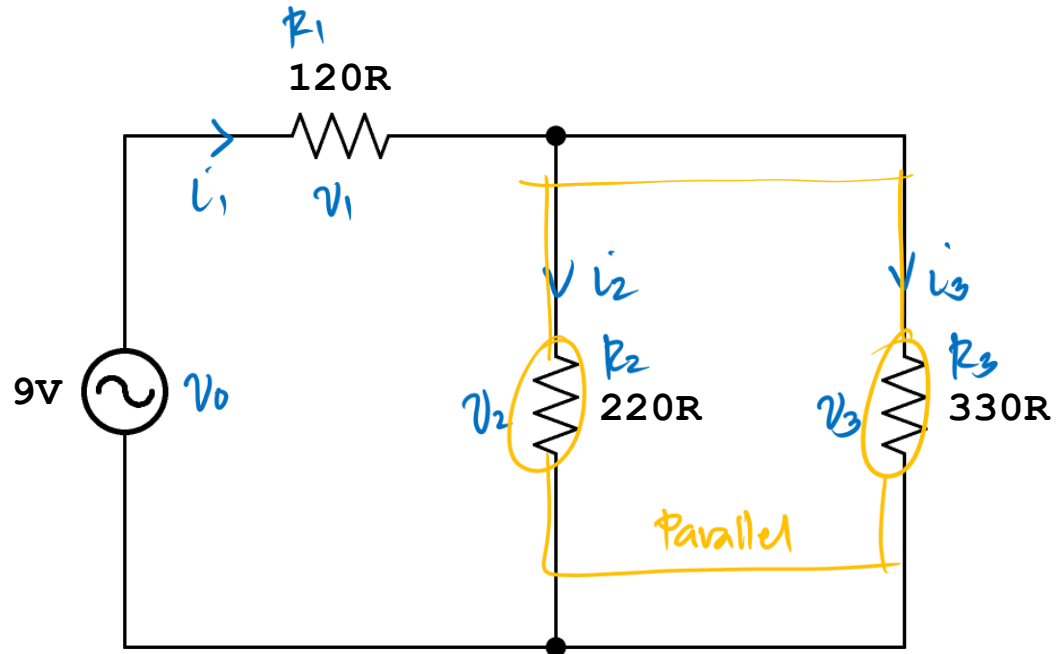
## EXERCISE

Analyze the given circuit to determine both the current through and the voltage drop across each resistor.



Total Resistance

$$R_0 = R_1 + R_{2,3}$$

$$R_0 = 120 + 132$$

$$\underline{R_0 = 252\ \Omega}$$

Total Current



$$i_0 = \frac{V_0}{R_0}$$

$$= \frac{9}{252}$$

$$\underline{i_0 = 35.71\text{ mA}}$$
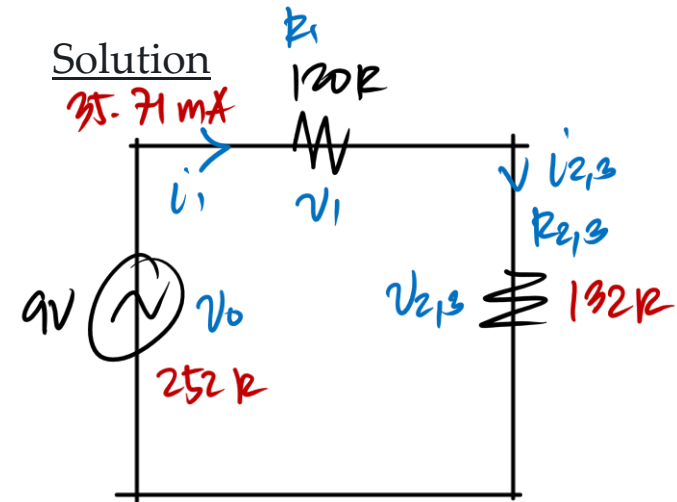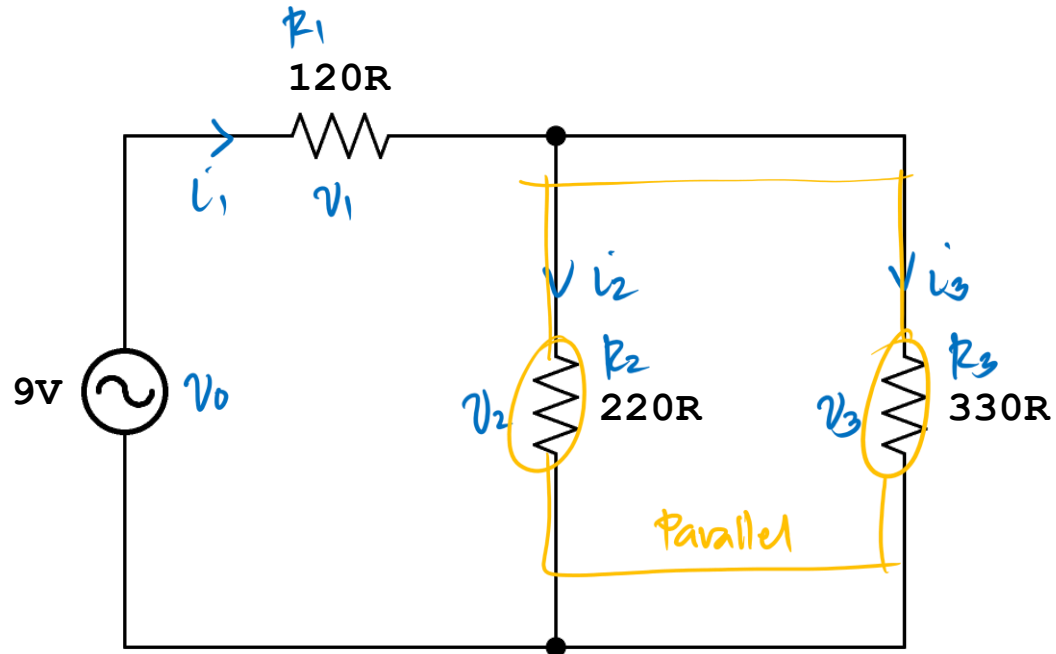
## EXERCISE

Analyze the given circuit to determine both the current through and the voltage drop across each resistor.



$$V_1 = i_1 R_1$$

$$V_1 = 35.71 \text{ m} (120)$$

$$V_1 = 4.28 \text{ V}$$

ans

$$V_2 = 4.71 \text{ V}$$

ans

$$V_{2,3} = i_{2,3} R_{2,3}$$

$$V_{2,3} = 35.71 \text{ m} (132)$$


$$V_{2,3} = 4.71 \text{ V}$$

ans


$$V_3 = 4.71 \text{ V}$$
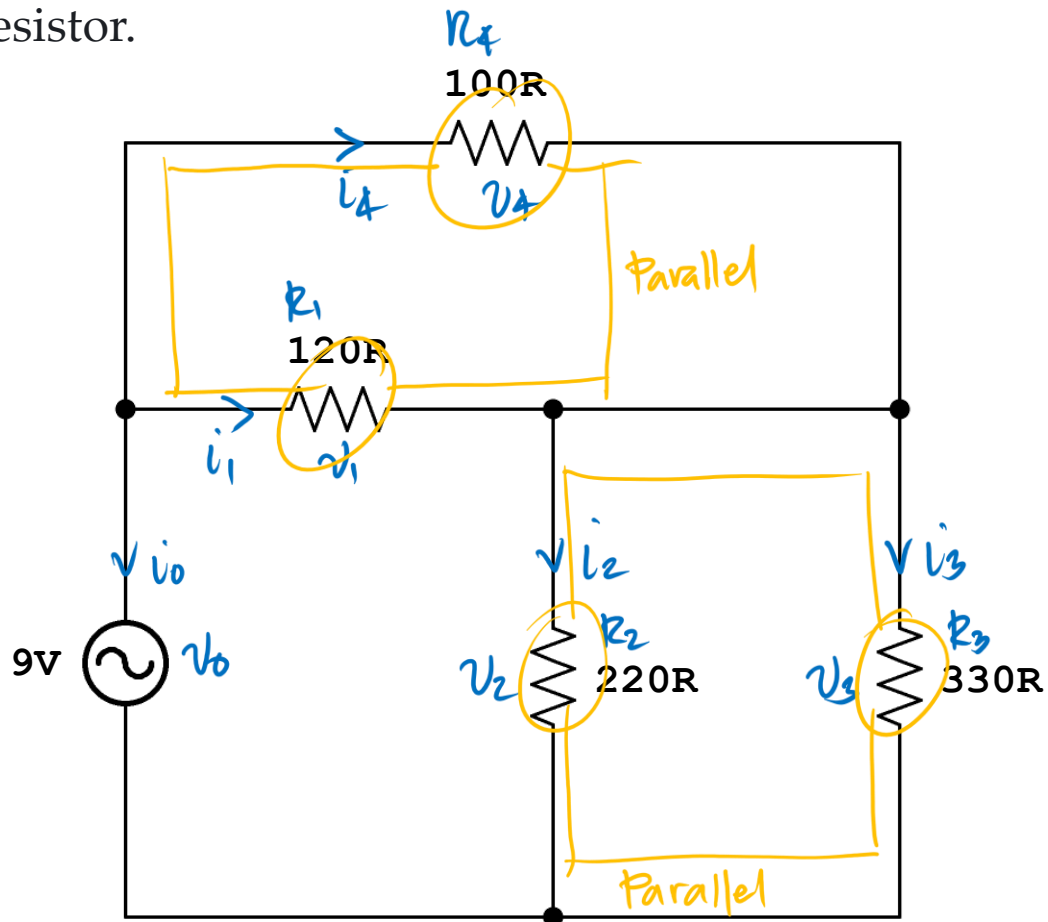
## EXERCISE

Analyze the given circuit to determine both the current through and the voltage drop across each resistor.



Solution

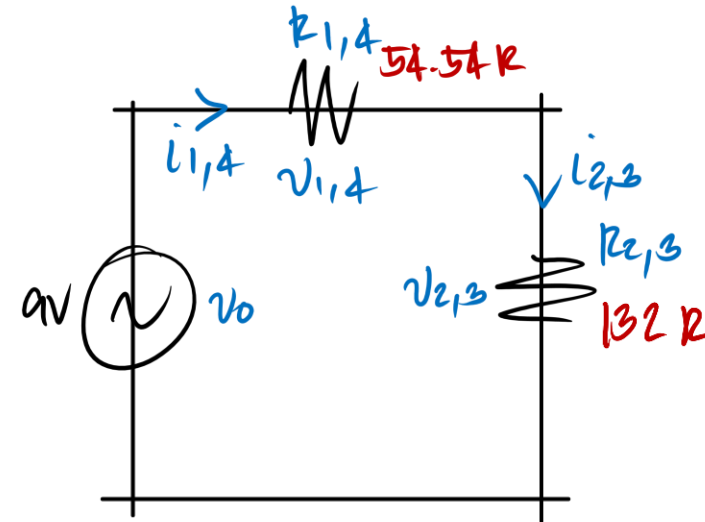


$$G_{1,4} = G_1 + G_4$$
$$\frac{1}{R_{1,4}} = \frac{1}{R_1} + \frac{1}{R_4}$$
$$\frac{1}{R_{1,4}} = \frac{1}{120} + \frac{1}{100}$$

$$\underline{R_{1,4} = 54.54\Omega}$$


$$G_{2,3} = G_2 + G_3$$
$$\frac{1}{R_{2,3}} = \frac{1}{R_2} + \frac{1}{R_3}$$
$$\frac{1}{R_{2,3}} = \frac{1}{220} + \frac{1}{330}$$
$$\underline{R_{2,3} = 132\Omega}$$
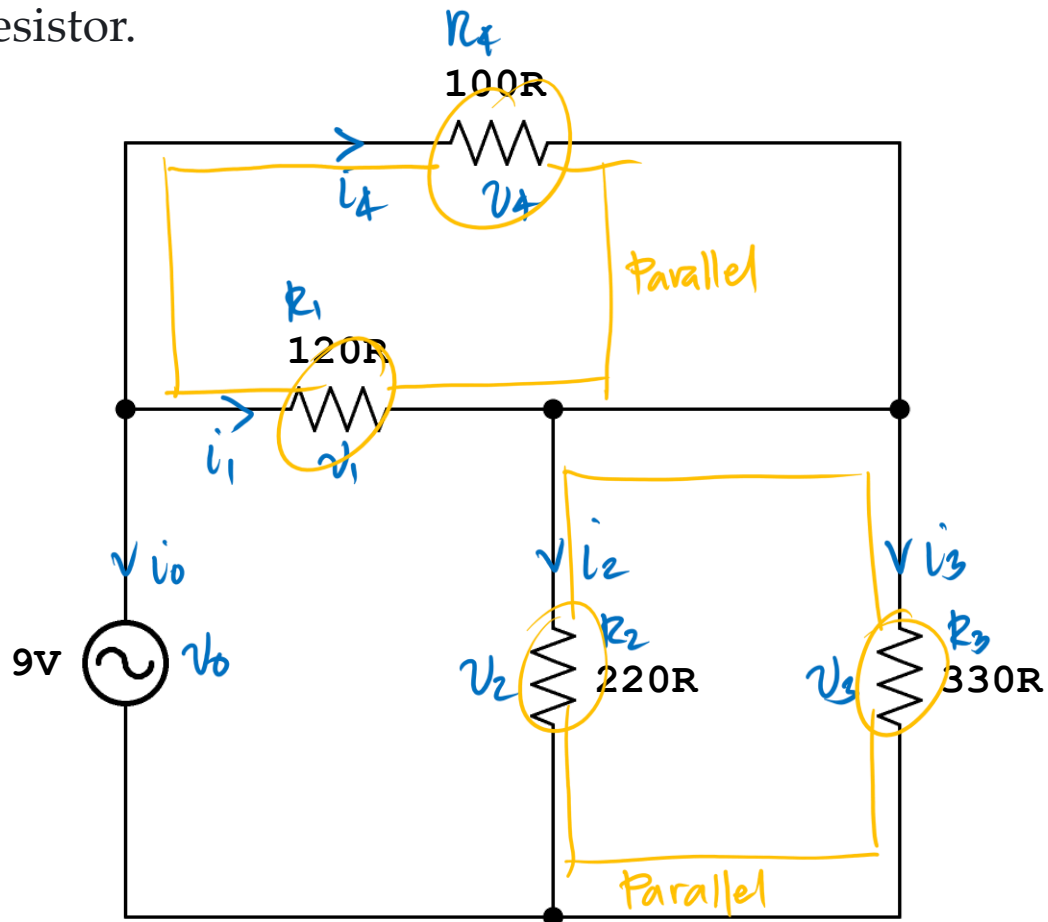
## EXERCISE

Analyze the given circuit to determine both the current through and the voltage drop across each resistor.



Solution

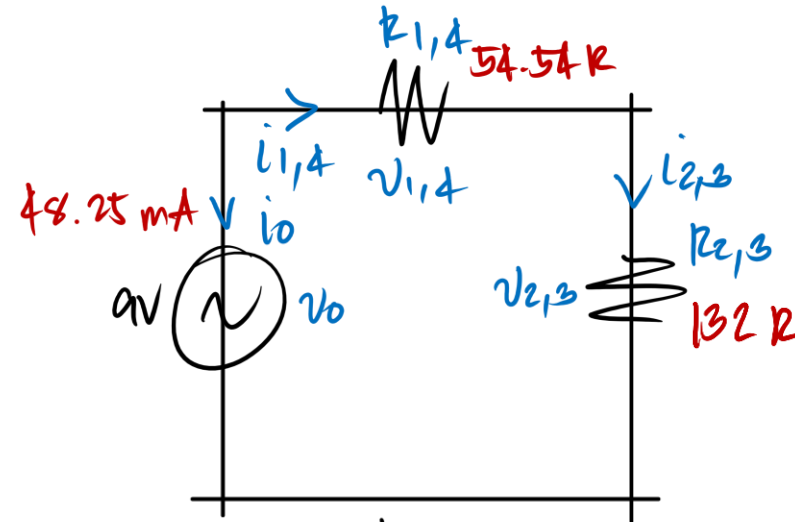

$$i_0 = \frac{v_0}{R_0}$$


$$i_0 = \frac{v_0}{R_{1,4} + R_{2,3}}$$

$$i_0 = \frac{9}{54.54 + 132}$$


$$i_0 = \underline{48.25 \text{ mA}}$$
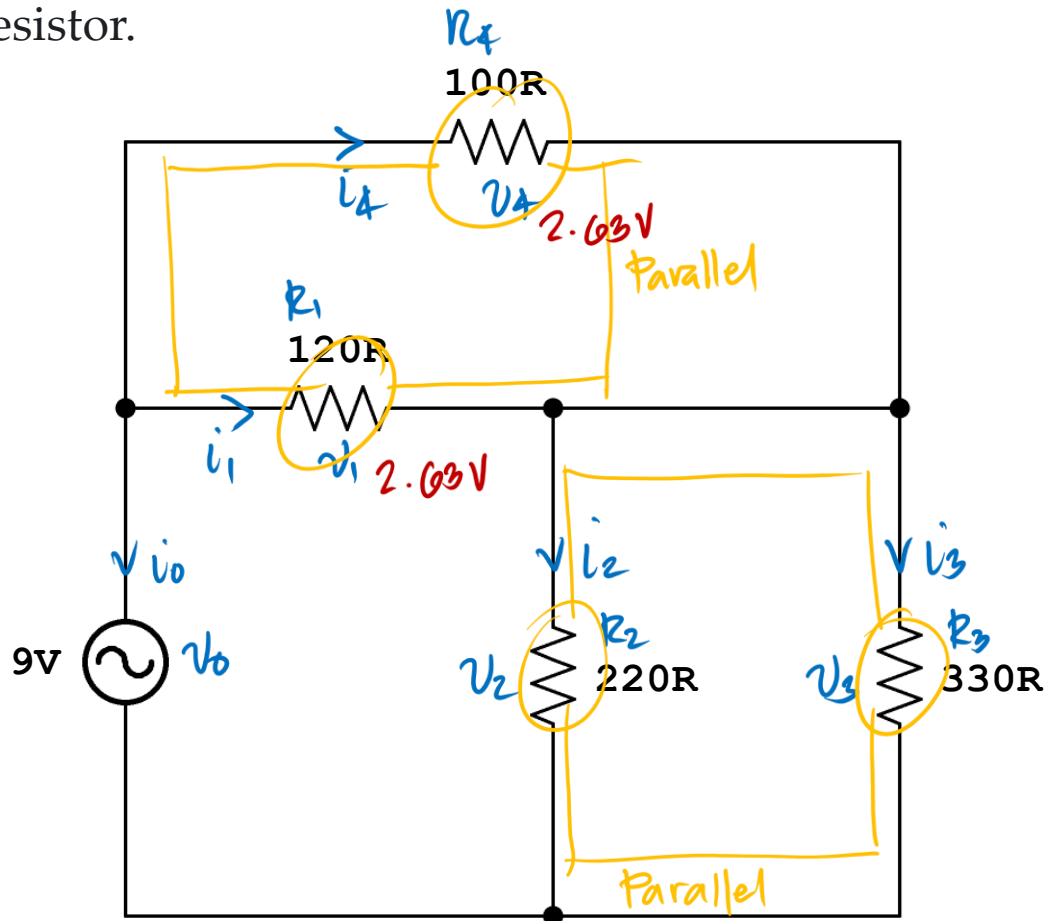
## EXERCISE

Analyze the given circuit to determine both the current through and the voltage drop across each resistor.



Solution

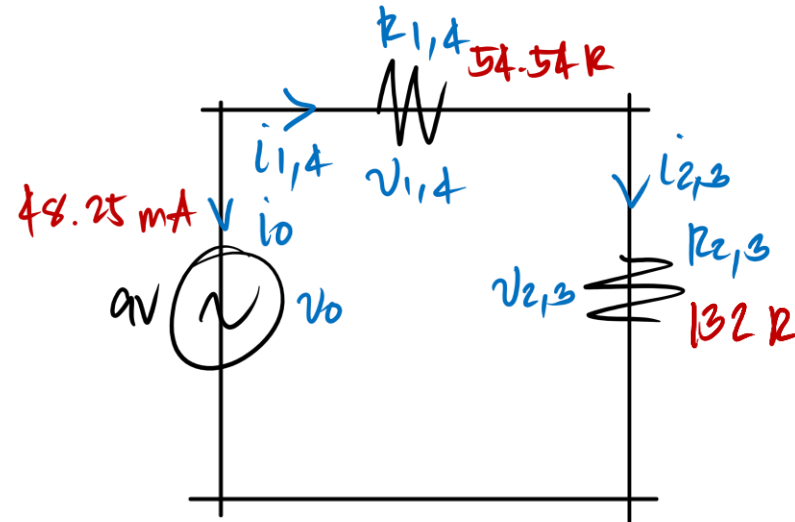

$$\begin{aligned} V_{1,4} &= i_{1,4} R_{1,4} \\ &= 48.25 \text{ m} (54.54) \end{aligned}$$


$$V_{1,4} = \underline{2.63 \text{ V}}$$

$$\boxed{V_1 = 2.63 \text{ V}} \quad \text{ans}$$


$$\boxed{V_4 = 2.63 \text{ V}} \quad \text{ans}$$
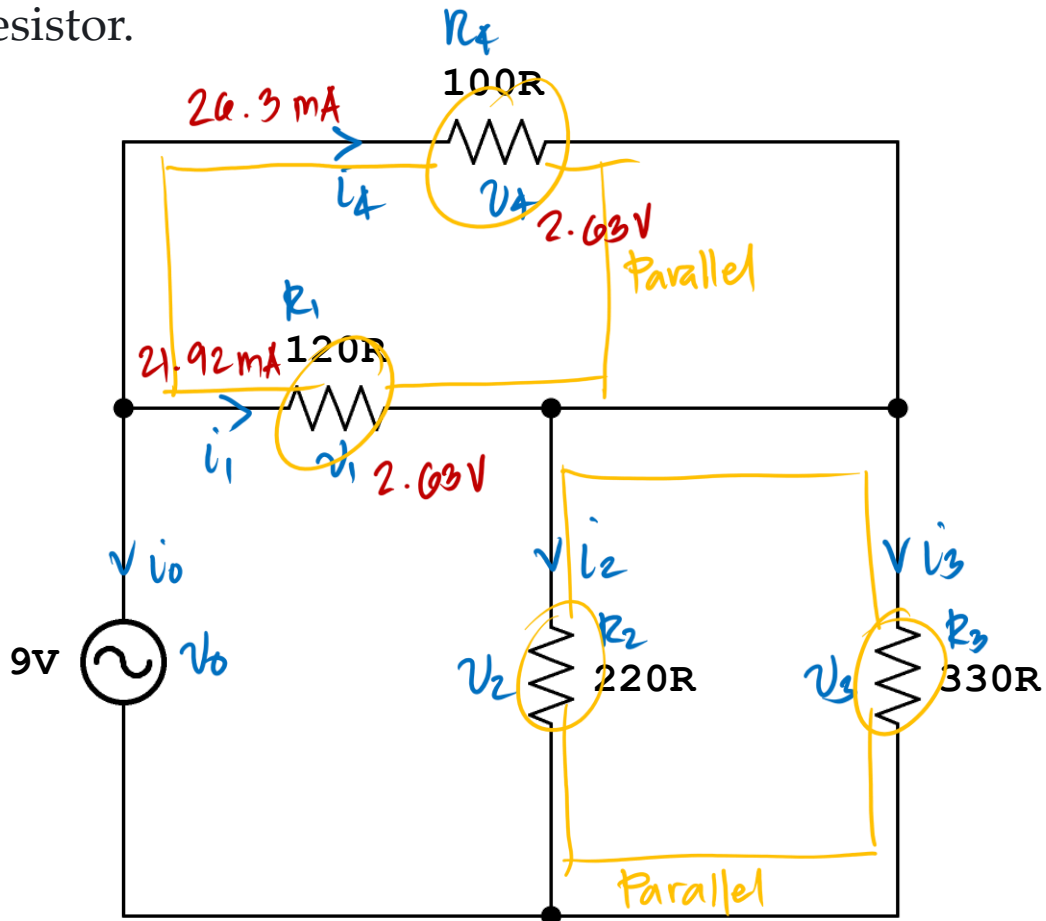
## EXERCISE

Analyze the given circuit to determine both the current through and the voltage drop across each resistor.



Solution

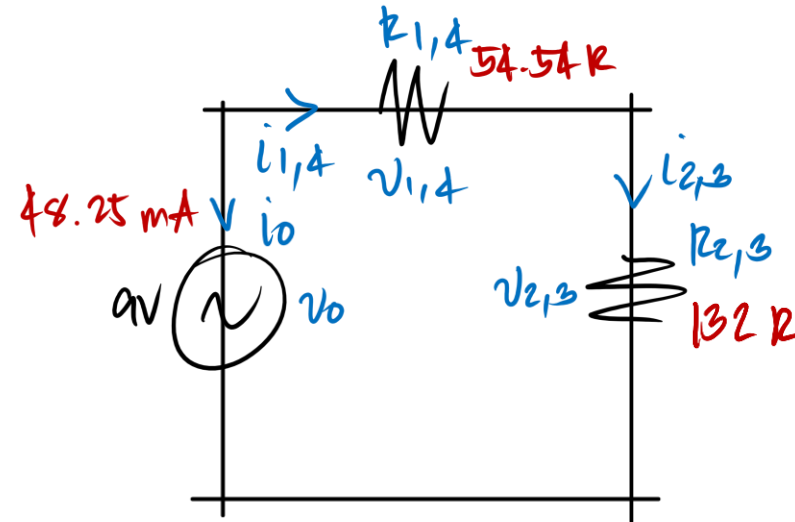

$$i_1 = \frac{v_1}{R_1}$$

$$i_1 = \frac{2.63}{120}$$

$$i_1 = 21.92 \text{ mA}$$

ans

$$i_2 = \frac{v_2}{R_2}$$

$$i_2 = \frac{2.63}{100}$$


$$i_2 = 26.3 \text{ mA}$$

ans



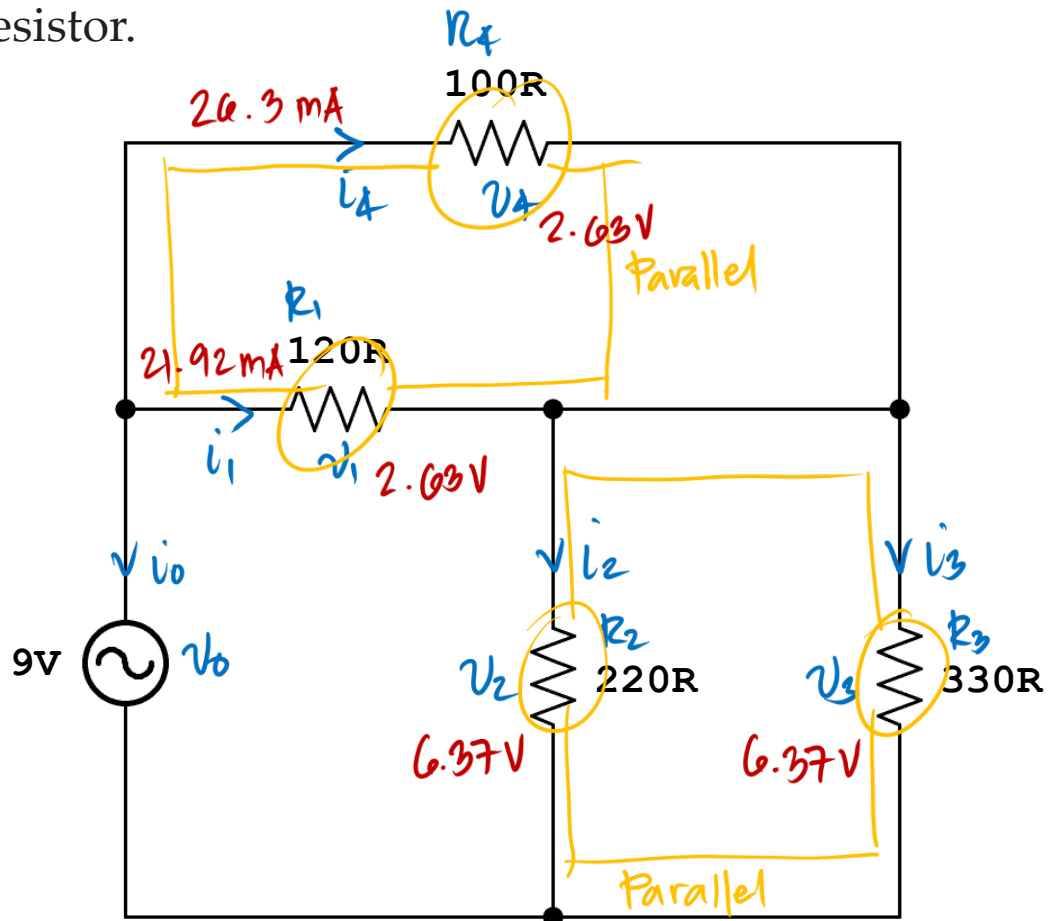
## EXERCISE

Analyze the given circuit to determine both the current through and the voltage drop across each resistor.



## Solution

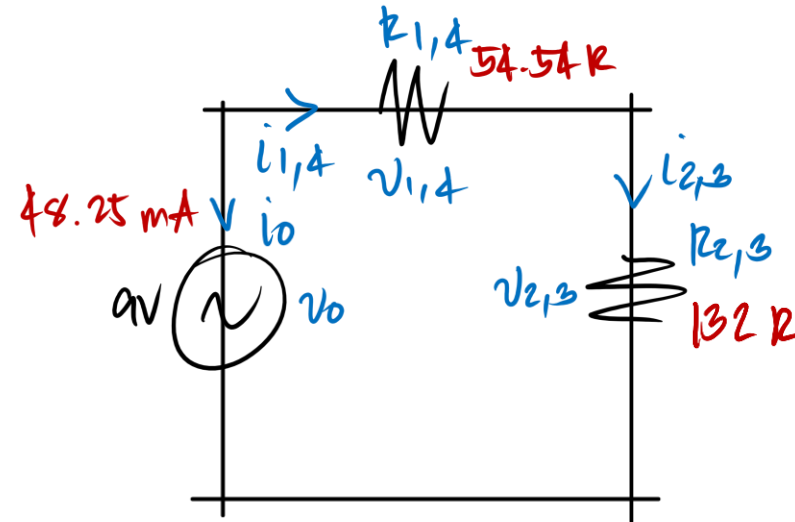

$$v_{2,3} = i_{2,3} R_{2,3}$$

$$v_{2,3} = 48.25 \text{ m} (132)$$


$$\underline{v_{2,3} = 6.37 \text{ V}}$$

$$\boxed{v_2 = 6.37 \text{ V}}_{\text{ans}}$$


$$\boxed{v_3 = 6.37 \text{ V}}_{\text{ans}}$$
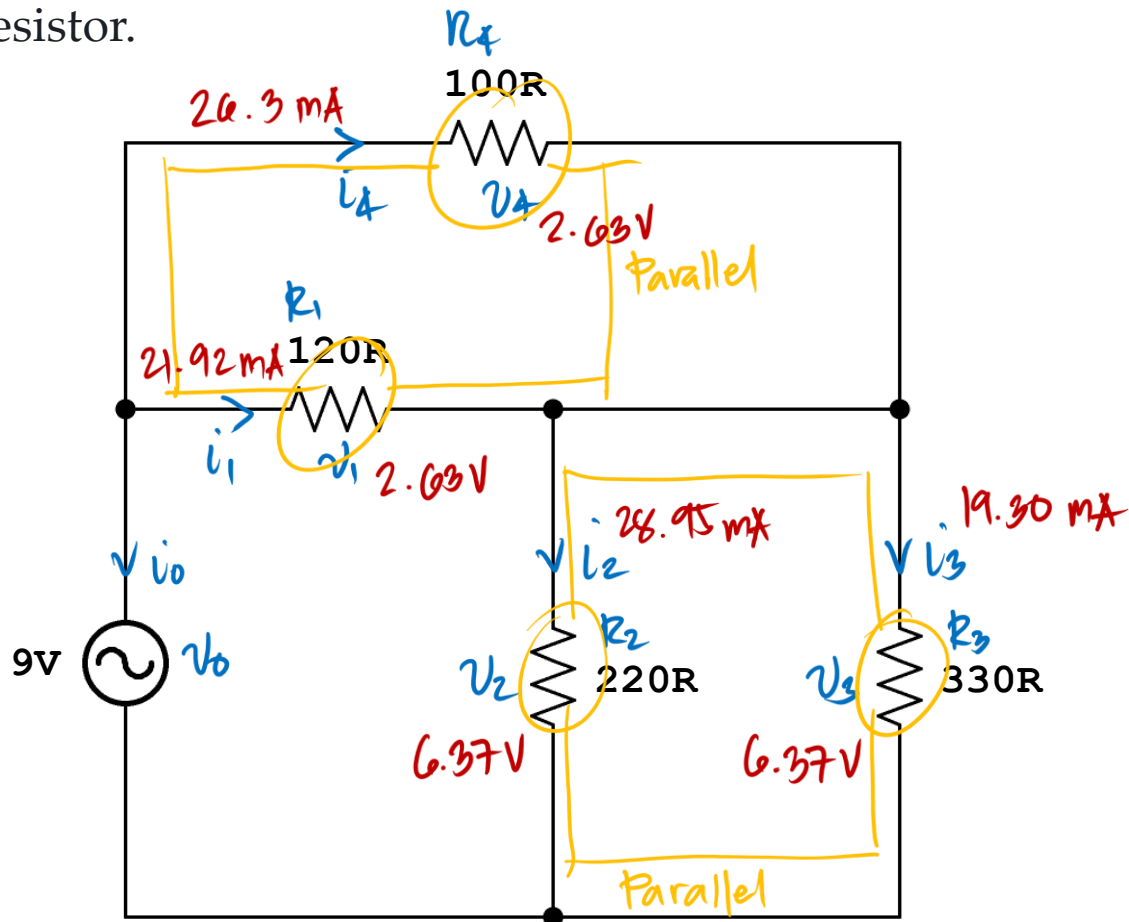
## EXERCISE

Analyze the given circuit to determine both the current through and the voltage drop across each resistor.



Solution

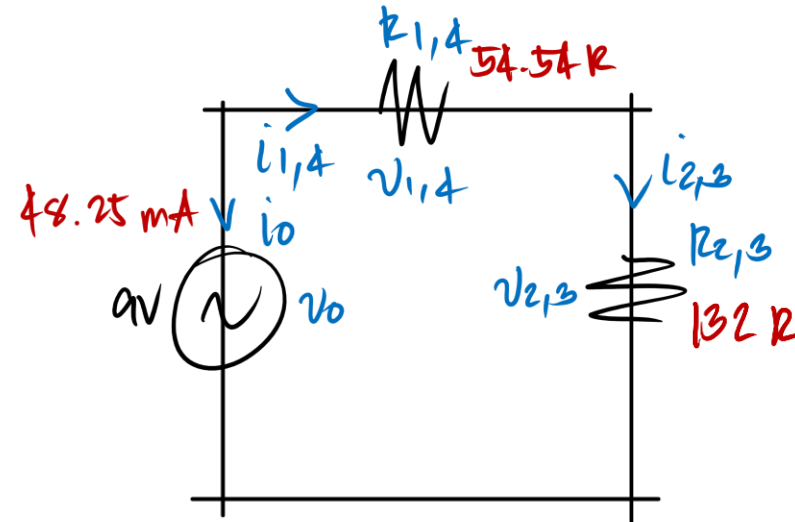

$$i_2 = \frac{v_2}{R_2}$$

$$i_2 = \frac{6.37}{220}$$

$$i_2 = 28.95 \text{ mA}$$

ans

$$i_3 = \frac{v_3}{R_3}$$


$$i_3 = \frac{6.37}{330}$$

$$i_3 = 19.30 \text{ mA}$$

ans
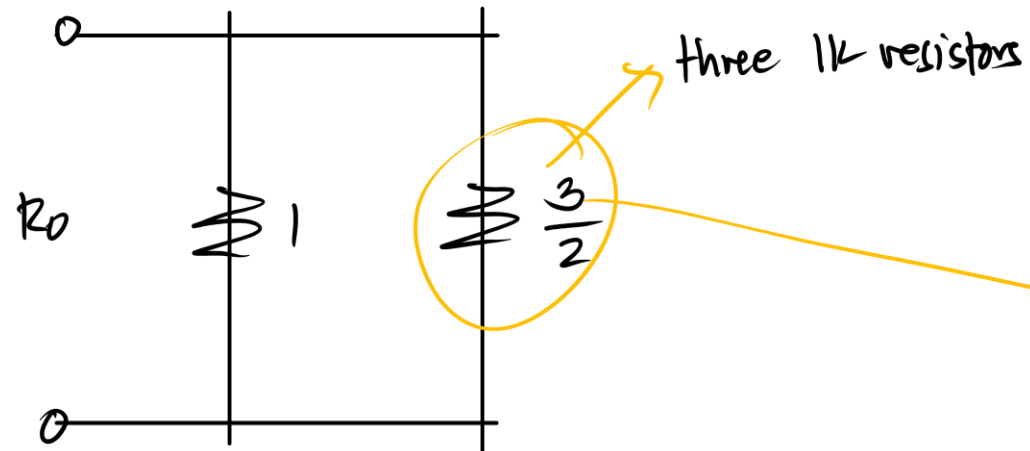
## EXERCISE

Using only  $1K$  resistors, synthesize a resistor of  $3/5K$  and  $5/3K$ . Use no more than four  $1K$  resistors.



Solution

$$R_0 = \frac{3}{5}$$

$$G_0 = \frac{5}{3}$$

$$G_0 = \frac{3}{3} + \frac{2}{3}$$

$$G_0 = 1 + \frac{2}{3}$$

parallel

conductance  
↓  
resistance =  $\frac{3}{2}$

equivalent resistance

$$R_{3T} = \frac{3}{2}$$


$$R_{3T} = \frac{2}{2} + \frac{1}{2}$$

$$R_{3T} = 1 + \frac{1}{2}$$

series
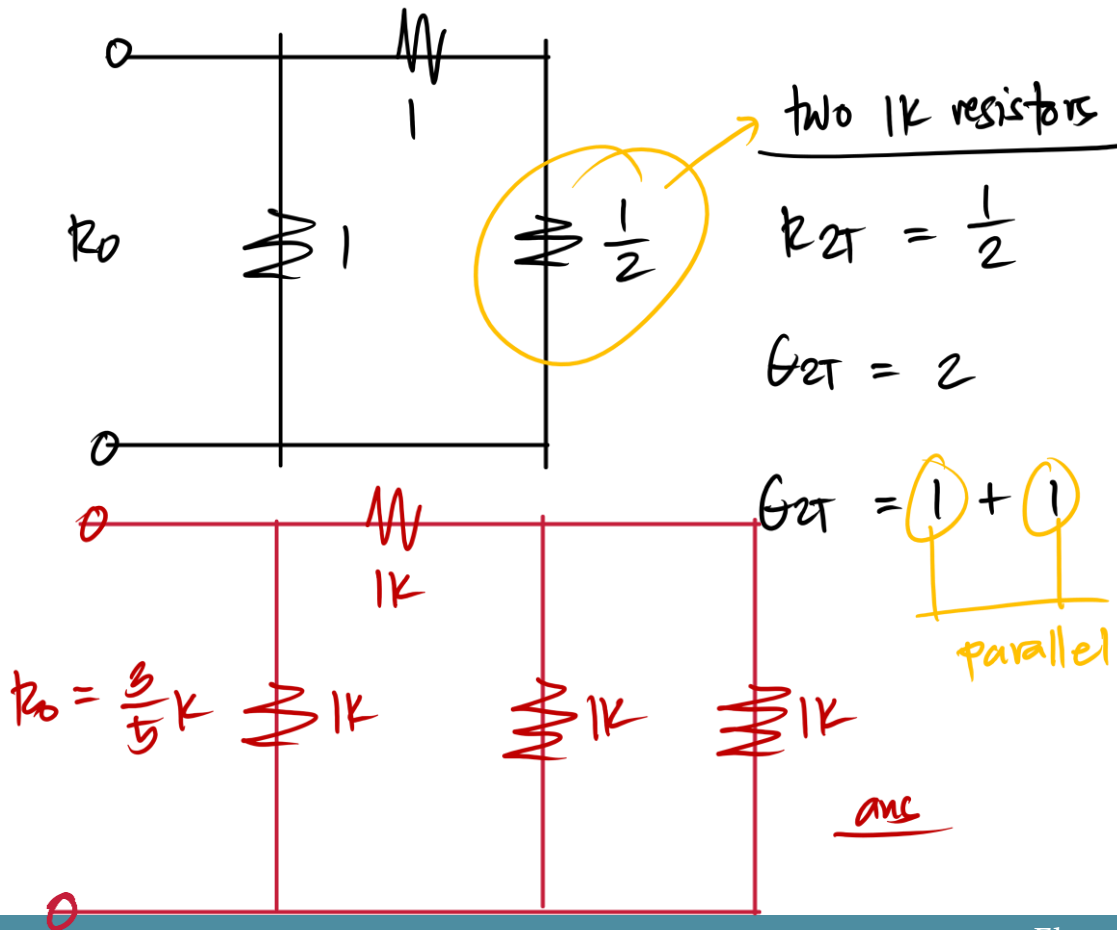
## EXERCISE

Using only 1K resistors, synthesize a resistor of  $\frac{3}{5}K$  and  $\frac{5}{3}K$ . Use no more than four 1K resistors.



Solution

$$R_0 = \frac{3}{5}$$

$$G_0 = \frac{5}{3}$$

$$G_0 = \frac{3}{3} + \frac{2}{3}$$

$$G_0 = 1 + \frac{2}{3}$$

parallel

conductance  
↓  
resistance =  $\frac{3}{2}$

Equivalent resistance

$$R_{3T} = \frac{3}{2}$$

$$R_{3T} = \frac{2}{2} + \frac{1}{2}$$


$$R_{3T} = 1 + \frac{1}{2}$$

series


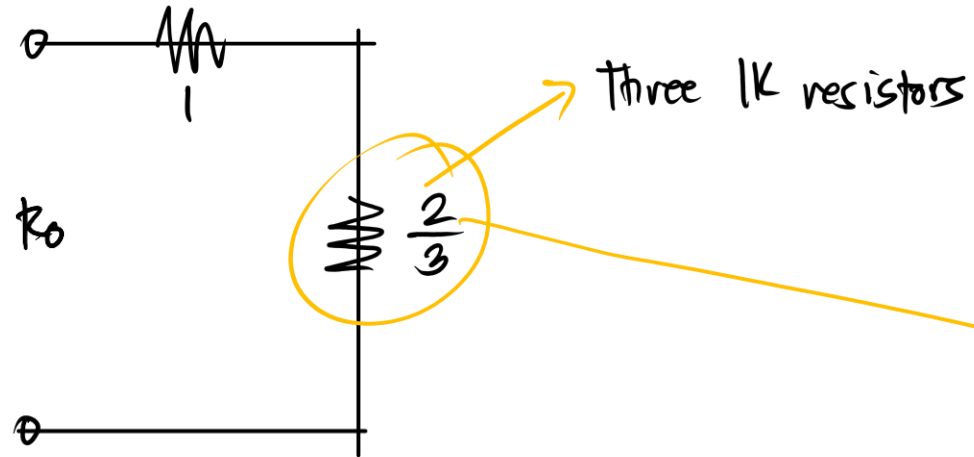
## EXERCISE

Using only 1K resistors, synthesize a resistor of  $3/5K$  and  $5/3K$ . Use no more than four 1K resistors.



Solution

$$R_0 = \frac{5}{3}$$

$$R_0 = \cancel{\frac{3}{3}} + \frac{2}{3}$$

$$R_0 = 1 + \frac{2}{3}$$

series

Equivalent resistors

$$R_{ST} = \frac{2}{3}$$

$$G_{ST} = \frac{3}{2}$$

$$G_{ST} = \cancel{\frac{2}{2}} + \frac{1}{2}$$

$$G_{ST} = 1 + \frac{1}{2}$$

parallel

Conductance  
↓  
Resistance = 2

## EXERCISE

Using only 1K resistors, synthesize a resistor of  $\frac{3}{5}K$  and  $\frac{5}{3}K$ . Use no more than four 1K resistors.

Solution

$$R_0 = \frac{5}{3}$$

$$R_0 = \cancel{\frac{3}{3}} + \frac{2}{3}$$

$$R_0 = 1 + \frac{2}{3}$$

series

Equivalent resistors

$$R_{ST} = \frac{2}{3}$$


$$G_{ST} = \frac{3}{2}$$

$$G_{ST} = \cancel{\frac{2}{2}} + \frac{1}{2}$$

$$G_{ST} = 1 + \frac{1}{2}$$

parallel

Conductance  
↓  
Resistance = 2

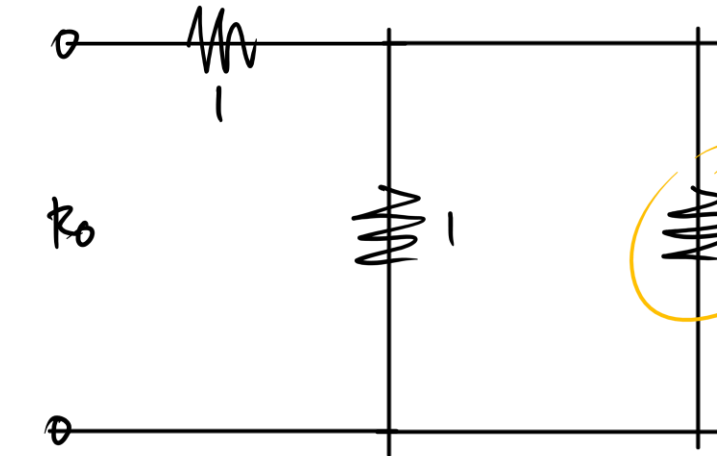


Two 1K resistors

$$R_{ST} = 2$$

$$R_{ST} = 1 + 1$$

series

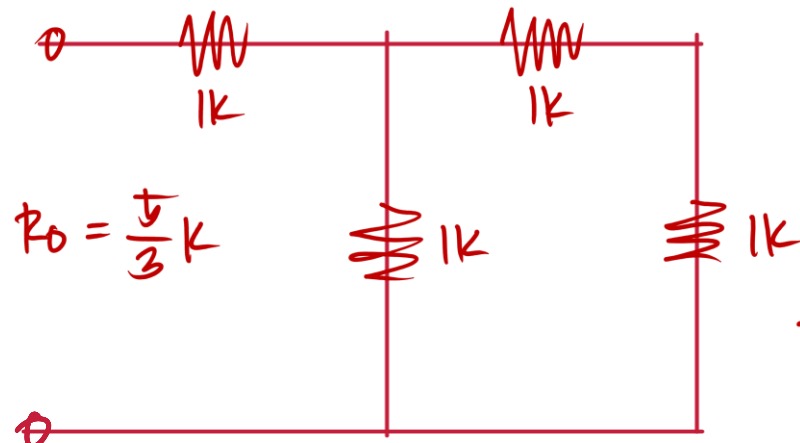


$$R_0 = \frac{5}{3} K$$


ans
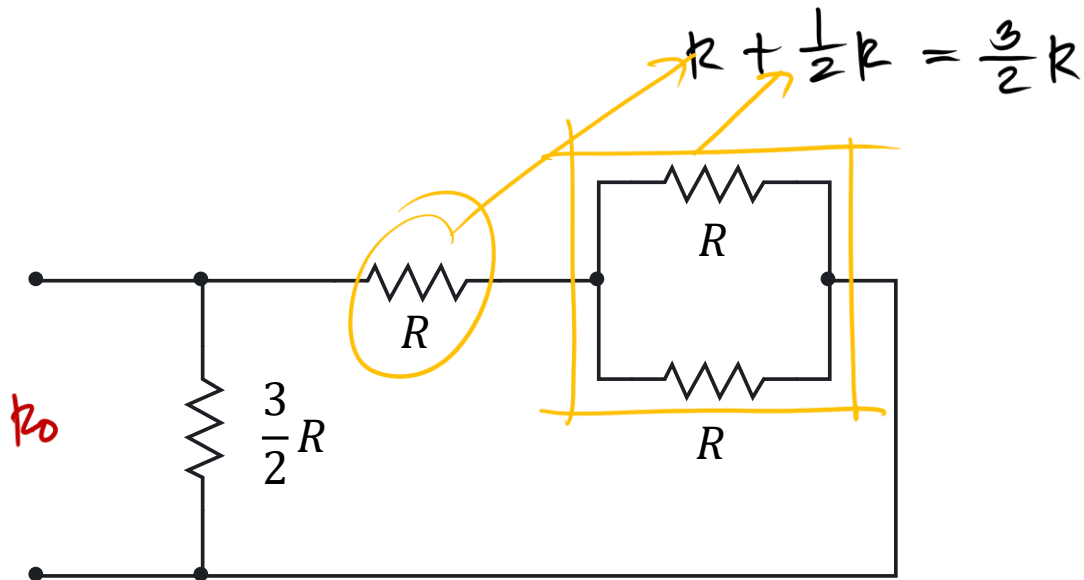
## EXERCISE

Find the equivalent resistance of the given network as viewed from its port.



Solution

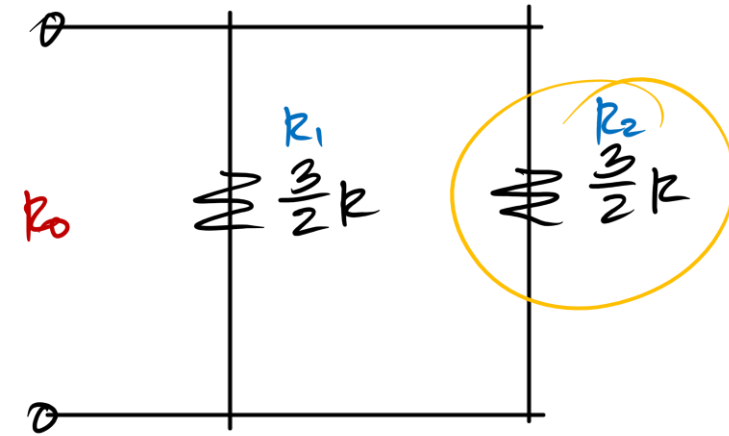

$$G_0 = G_1 + G_2$$

$$G_0 = \frac{2}{3} + \frac{2}{3}$$

$$G_0 = \frac{4}{3}$$

$$R_0 = \frac{3}{4}R$$

ans

## EXERCISE

You are given a black box with three terminals, as shown in Fig.1. The box is known to contain five 1-ohm resistors.

Using an ohm-meter, you measure the resistance between terminals to be the following:

A–B: 1.5 ohms

B–C: 3 ohms

A–C: 2.5 ohms

Determine the configuration of the five resistors inside the box.

## Solution

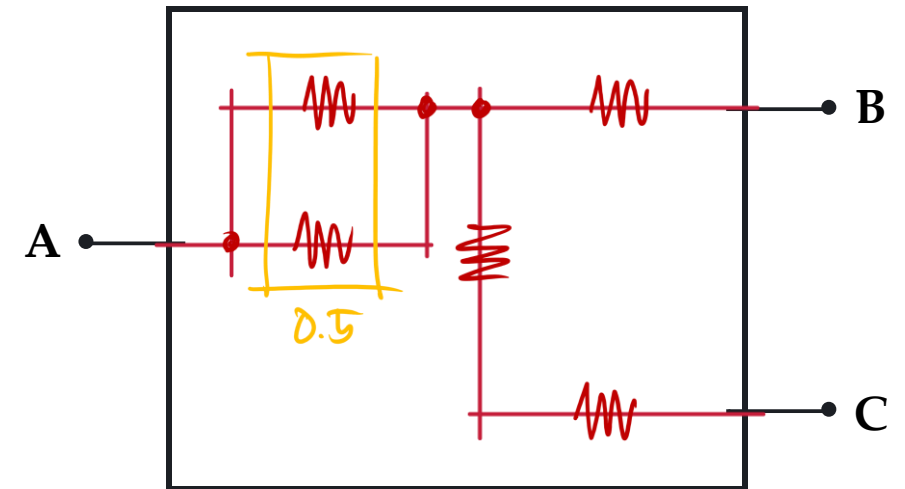


Fig.1. Black box





# LABORATORY

