



# **FILTER CAPACITOR**

## **POWER SUPPLY BUILDING BLOCKS**

---

*prepared by:*

**Gyro A. Madrona**  
Electronics Engineer

# TOPIC OUTLINE

Filter Capacitor

Smoothing Pulsating DC




# FILTER CAPACITOR




# FILTER CAPACITOR

A filter capacitor charges up when the voltage rises and discharges when the voltage drops, filling in the gaps of the pulsating DC waveform. This results in a smoother DC output.


Power Supply Block Diagram

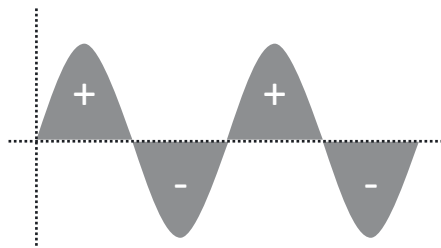

AC signal

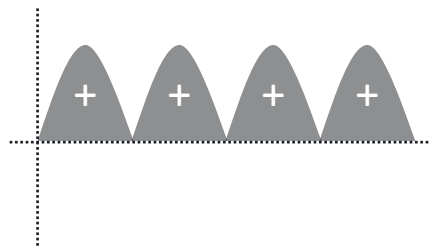

Pulsating DC

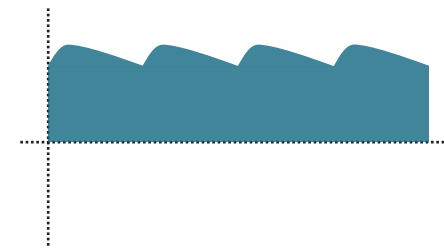

DC  
with AC ripple



# SMOOTHING PULSATING DC



# SMOOTHING HALF-WAVE

Discharging equation

$$v_c(t) = v_o e^{-\frac{t}{\tau}}$$

where:  $\tau = RC$


Let  $\tau = 10\Delta t$

$$v_c(\Delta t) = v_o e^{-\frac{\Delta t}{10\Delta t}}$$

$$v_c(\Delta t) = 0.905v_o$$

For half-wave, if the discharge time constant for the capacitor is 10 times the pulse duration, the average DC output level is approximately **90% of  $v_p$** .


DC with AC Ripple

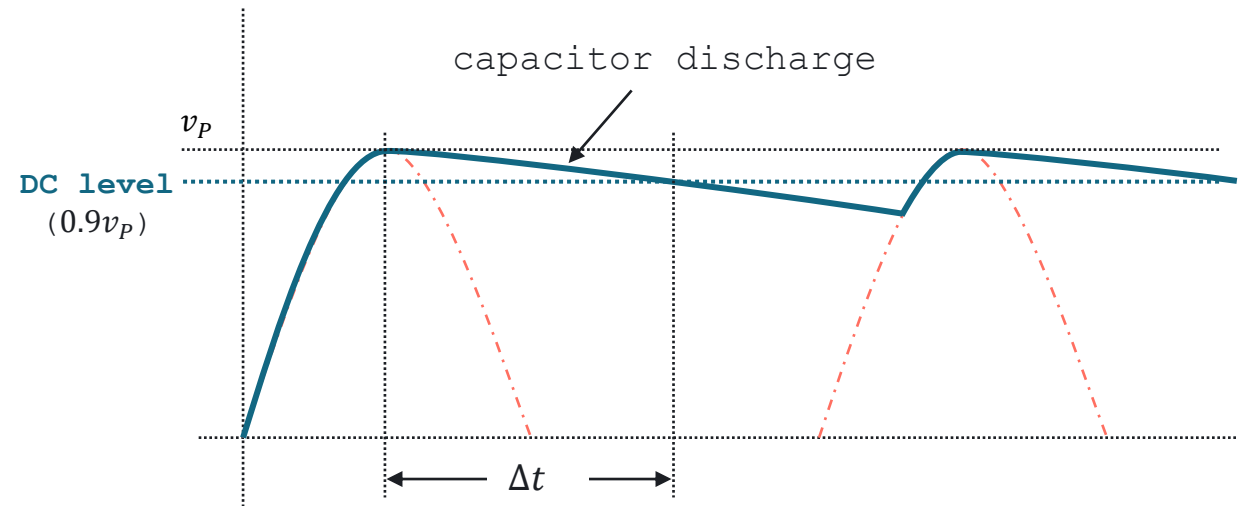

## EXERCISE

The AC input to the given rectifier circuit is a  $12V_{RMS}$ , 60Hz sine wave. For this circuit, you need 9V DC across the  $100\Omega$  load resistor. Determine the value of  $R_1$  and  $C_1$ .

Solution

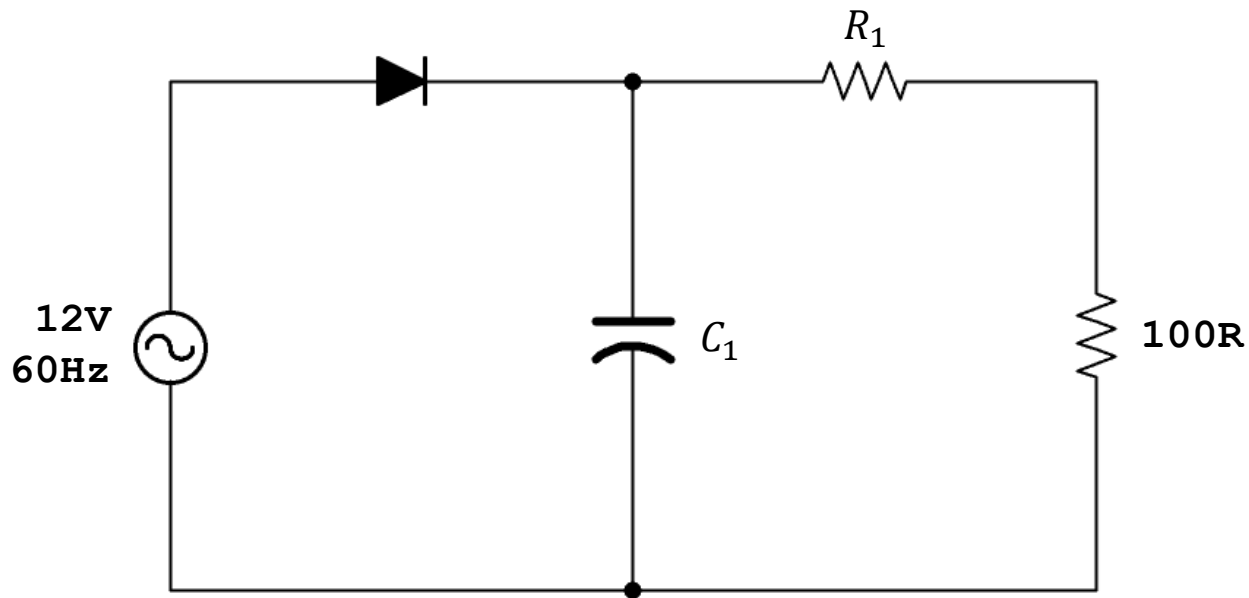

# SMOOTHING FULL-WAVE

Discharging equation

$$v_c(t) = v_o e^{-\frac{t}{\tau}}$$

where:  $\tau = RC$


Let  $\tau = 10\Delta t$

$$v_c(\Delta t/2) = v_o e^{-\frac{\Delta t/2}{10\Delta t}}$$

$$v_c(\Delta t/2) = 0.95v_o$$

For full-wave, if the discharge time constant for the capacitor is 10 times the pulse duration, the average DC output level is approximately **95% of  $v_p$** .

DC with AC Ripple

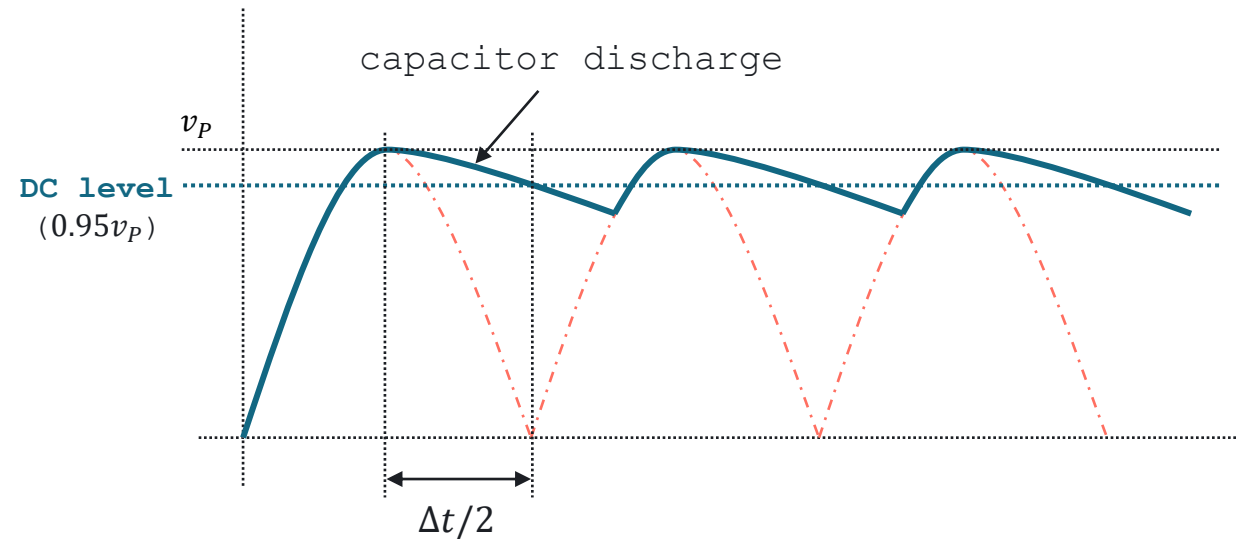




## EXERCISE

The AC input to the given rectifier circuit is a  $12V_{RMS}$ , 60Hz sine wave. For this circuit, you need 9V DC across the  $100\Omega$  load resistor. Determine the value of  $R_1$  and  $C_1$ .

Solution

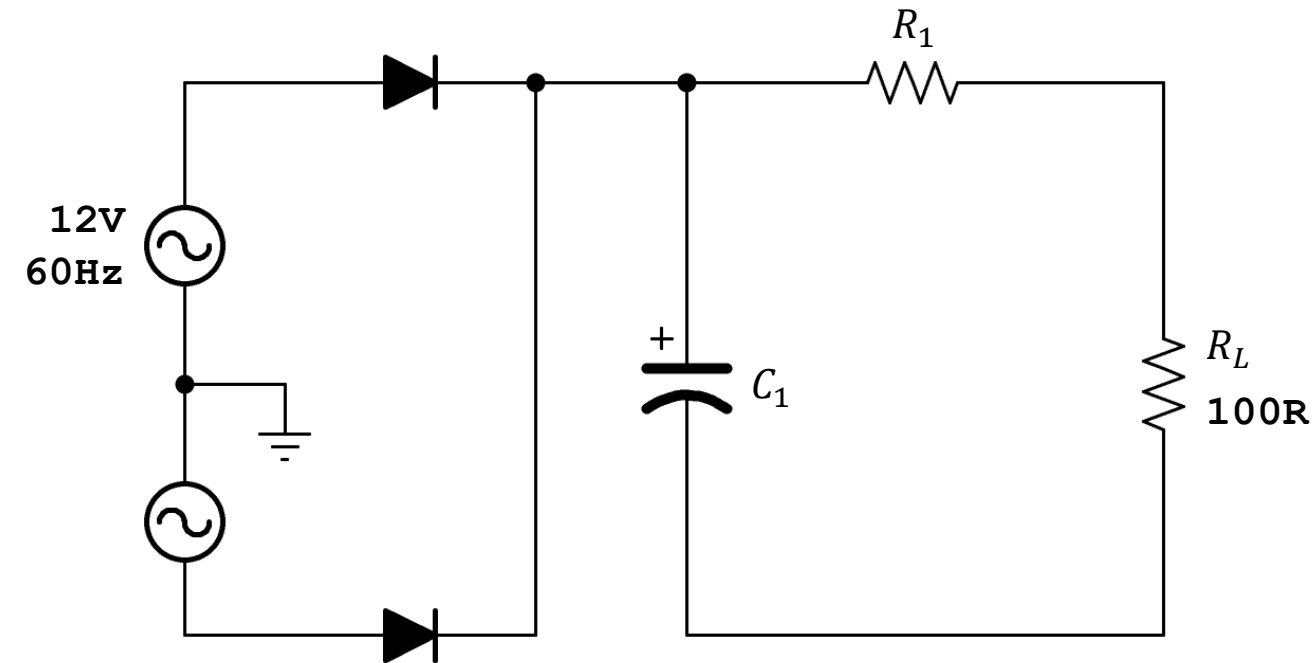

# LABORATORY

