



# SYNTHESIS OF LOGIC FUNCTIONS

## COMBINATIONAL LOGIC CIRCUITS

---

*prepared by:*

**Gyro A. Madrona**

Electronics Engineer

## TOPIC OUTLINE

Synthesis of XOR/XNOR Gate

Synthesis of Logic Functions



# SYNTHESIS OF XOR/XNOR GATE



# SYNTHESIS

---

## Cooking process analogy



high-level  
description

Synthesis is the process of transforming a high-level description of a desired functional behavior into a corresponding **hardware circuit** that implements that behavior.




logic circuit



# EXCLUSIVE-OR GATE


## Logic Symbol

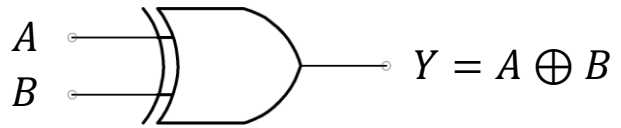

## Truth Table


A	B	Y	Minterm
0	0	0	
0	1	<u>1</u>	$\bar{A}B$
1	0	<u>1</u>	$A\bar{B}$
1	1	0	

## Equivalent Logic Circuit

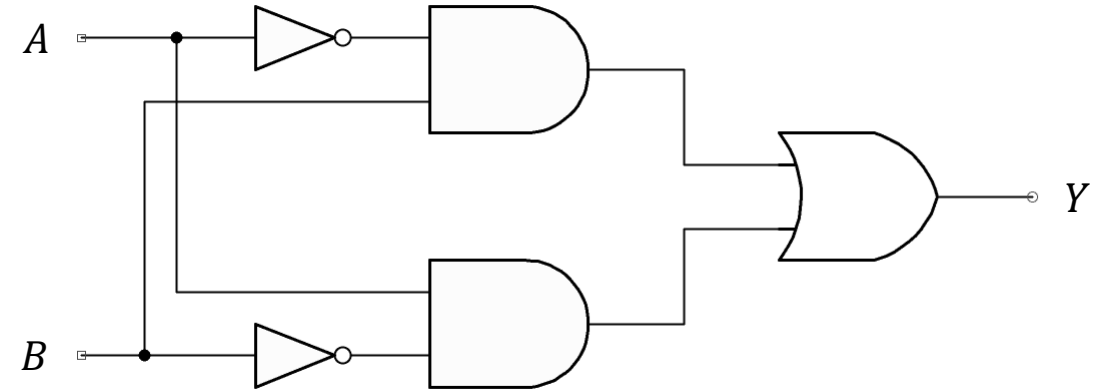

# EXCLUSIVE-NOR GATE


## Logic Symbol

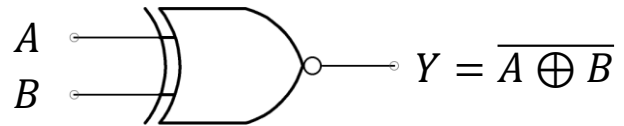

## Truth Table

A	B	Y	Minterm
0	0	<u>1</u>	$\bar{A}\bar{B}$
0	1	0	
1	0	0	
1	1	<u>1</u>	$AB$

## Equivalent Logic Circuit

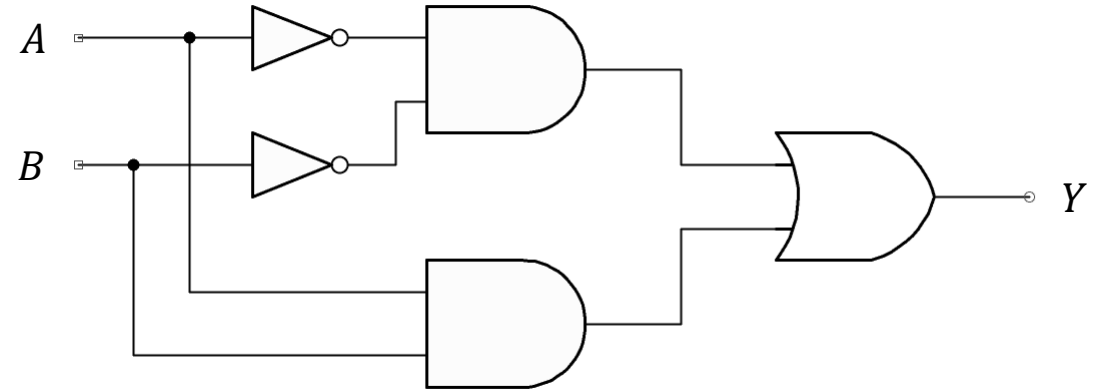

# SYNTHESIS OF LOGIC FUNCTIONS



## EXERCISE

Synthesize the logic function describe by the truth table.

A	B	C	f
0	0	0	0
0	0	1	<u>1</u>
0	1	0	<u>1</u>
0	1	1	0
1	0	0	<u>1</u>
1	0	1	0
1	1	0	0
1	1	1	<u>1</u>

Minterm

$\bar{A}\bar{B}C$

$\bar{A}B\bar{C}$


$A\bar{B}\bar{C}$

$ABC$

Solution

$$f = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \underline{A\bar{B}\bar{C}} + \underline{ABC}$$
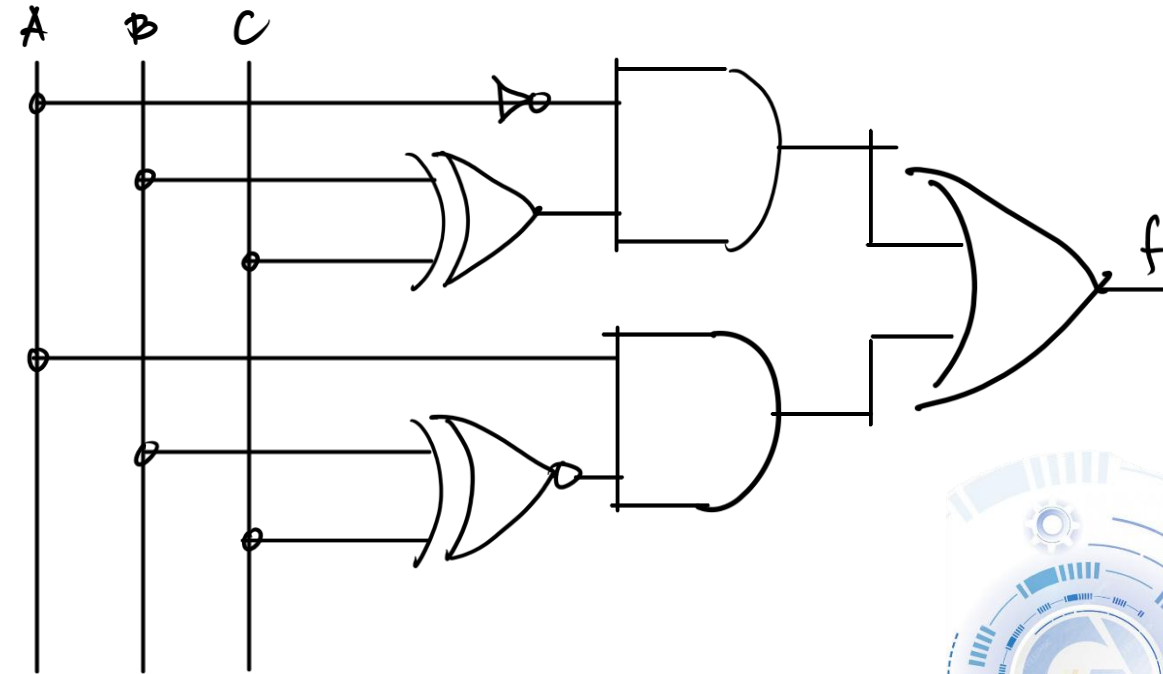
$$f = \bar{A}(\underbrace{\bar{B}C + B\bar{C}}_{\text{XOR}}) + A(\underbrace{\bar{B}\bar{C} + BC}_{\text{XNOR}})$$





## EXERCISE

A section of a bubble gumball factory uses a conveyor system equipped with three sensors— $s_1$ ,  $s_2$ , and  $s_3$  to inspect each gumball.


- $s_1 = 1$  if the gumball is too light.
- $s_2 = 1$  if the gumball is too small in diameter.
- $s_3 = 1$  if the gumball is too large in diameter.

The conveyor moves gumballs over a trap door that rejects defective ones. A gumball should be rejected if:

- It is too large ( $s_3 = 1$ ), or
- It is both too light and too small ( $s_1 = 1$  &  $s_2 = 1$ ).

Synthesize a logic circuit that activates the trap door based on the sensor outputs.

### Conveyor and Sensors

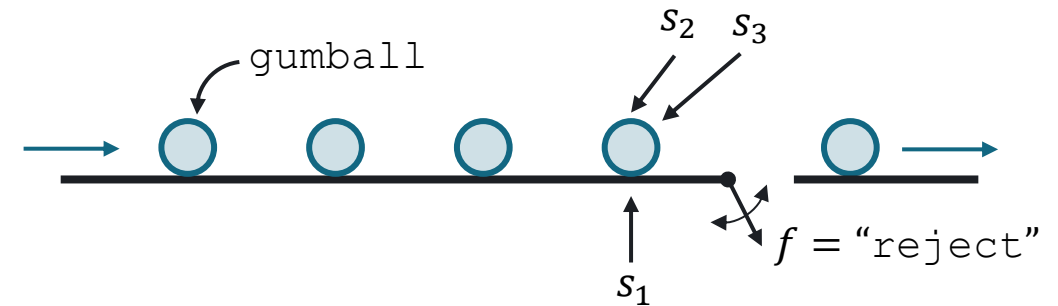


# EXERCISE

## Solution

$S_1$	$S_2$	$S_3$	$f$	Minterm
0	0	0	0	
0	0	<u>1</u>	1	$\bar{S}_1 \bar{S}_2 S_3$
0	1	0	0	
0	1	<u>1</u>	1	$\bar{S}_1 S_2 S_3$
1	0	0	0	
1	0	<u>1</u>	1	$S_1 \bar{S}_2 S_3$
<u>1</u>	<u>1</u>	0	1	$S_1 S_2 \bar{S}_3$
<u>1</u>	<u>1</u>	<u>1</u>	1	$S_1 S_2 S_3$

## Conveyor and Sensors

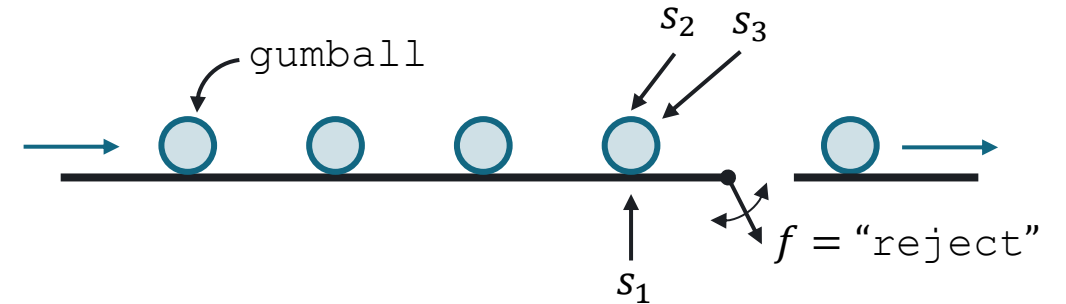

$$f = \bar{S}_1 \bar{S}_2 S_3 + \bar{S}_1 S_2 S_3 + S_1 \bar{S}_2 S_3 + S_1 S_2 \bar{S}_3 + S_1 S_2 S_3 + S_1 S_2 S_3$$


$$f = \bar{S}_1 S_3 (\cancel{\bar{S}_2} + S_2) + S_1 S_3 (\cancel{\bar{S}_2} + S_2) + S_1 S_2 (\cancel{\bar{S}_3} + S_3)$$

$$f = \bar{S}_1 S_3 + S_1 S_3 + S_1 S_2$$


$$f = S_3 + S_1 S_2$$

# EXERCISE

## Solution

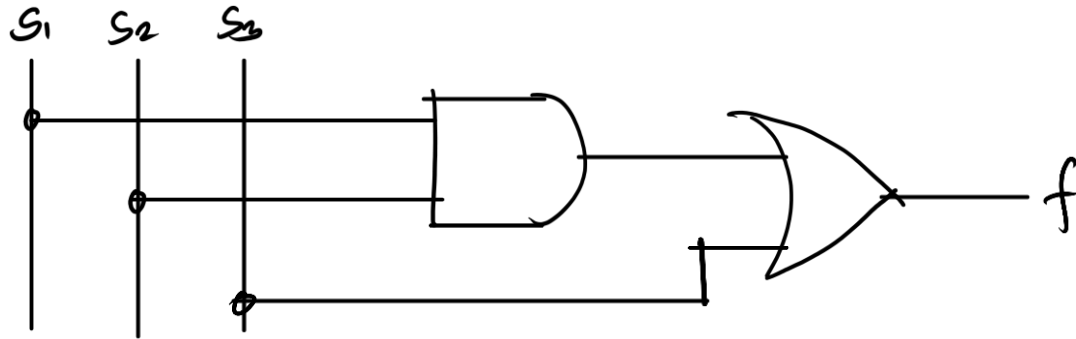

## Conveyor and Sensors

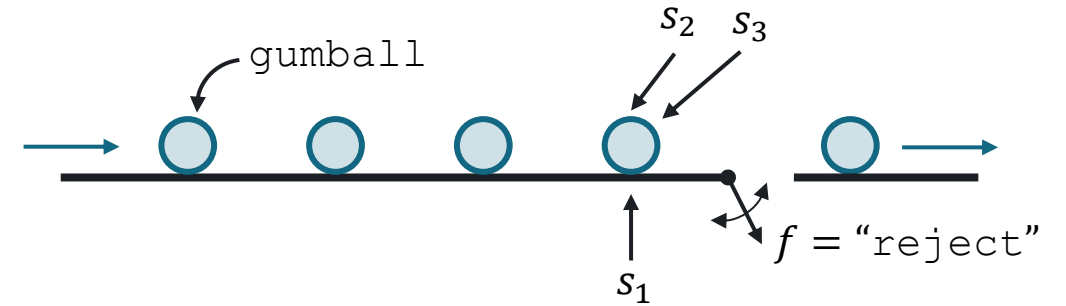

$$f = \underline{\bar{S}_1} \bar{S}_2 \underline{S_3} + \underline{\bar{S}_1} S_2 \underline{S_3} + \underline{S_1} \bar{S}_2 \underline{S_3} \\ + \underline{S_1} \underline{S_2} \bar{S_3} + \underline{S_1} \underline{S_2} S_3 + \underline{S_1} \underline{S_2} \underline{S_3}$$

$$f = \bar{S}_1 S_3 (\cancel{\bar{S}_2} + \cancel{S_2}) + S_1 S_3 (\cancel{\bar{S}_2} + \cancel{S_2}) \\ + S_1 S_2 (\cancel{\bar{S}_3} + \cancel{S_3})$$

$$f = \bar{S}_1 \underline{S_3} + S_1 \underline{S_3} + S_1 S_2$$

$$\underline{f = S_3 + S_1 S_2}$$

## EXERCISE

Synthesize a logic circuit that controls a single light in a large room with three entry points, each equipped with a switch. The behavior of this three-way light control are as follows:

$$A=0, B=0, C=0$$

1. The light is OFF when all three switches are open.
2. Closing any one of the switches turns the light ON.
3. If two switches are closed simultaneously, the light turns OFF.

$$A=1, B=1, C=1$$

4. If all three switches are closed, the light turns ON again.

Input

0 - open

1 - closed

Output

0 - OFF

1 - ON


### Solution

A	B	C	f	Minterm
<u>0</u>	<u>0</u>	<u>0</u>	0	
0	0	<u>1</u>	1	$\bar{A}\bar{B}C$
0	<u>1</u>	0	1	$\bar{A}B\bar{C}$
0	<u>1</u>	<u>1</u>	0	
<u>1</u>	0	0	1	$A\bar{B}\bar{C}$
<u>1</u>	0	<u>1</u>	0	
<u>1</u>	<u>1</u>	0	0	
<u>1</u>	<u>1</u>	<u>1</u>	1	$ABC$

$$f = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$



## EXERCISE

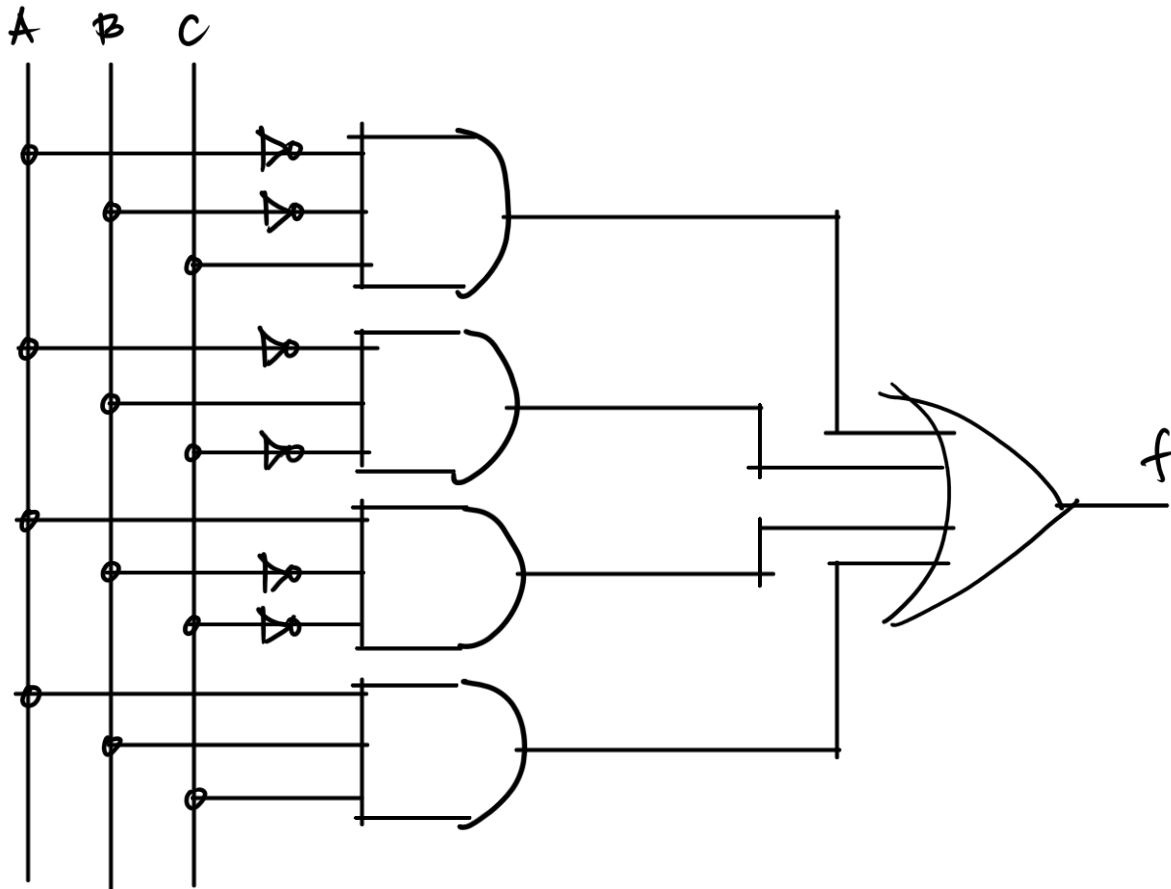

### Solution

A	B	C	f	Minterm
<u>0</u>	<u>0</u>	<u>0</u>	0	
0	0	<u>1</u>	1	$\bar{A}\bar{B}C$
0	<u>1</u>	0	1	$\bar{A}B\bar{C}$
0	<u>1</u>	<u>1</u>	0	
<u>1</u>	0	0	1	$A\bar{B}\bar{C}$
<u>1</u>	0	<u>1</u>	0	
<u>1</u>	<u>1</u>	0	0	
<u>1</u>	<u>1</u>	<u>1</u>	1	$ABC$

$$f = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$



# LABORATORY

