



# RESONANCE FREQUENCY

## AC CIRCUITS

---

*prepared by:*

**Gyro A. Madrona**

Electronics Engineer

# TOPIC OUTLINE

Series Resonance

Parallel Resonance




# SERIES RESONANCE



# SERIES RESONANCE


## Circuit Diagram

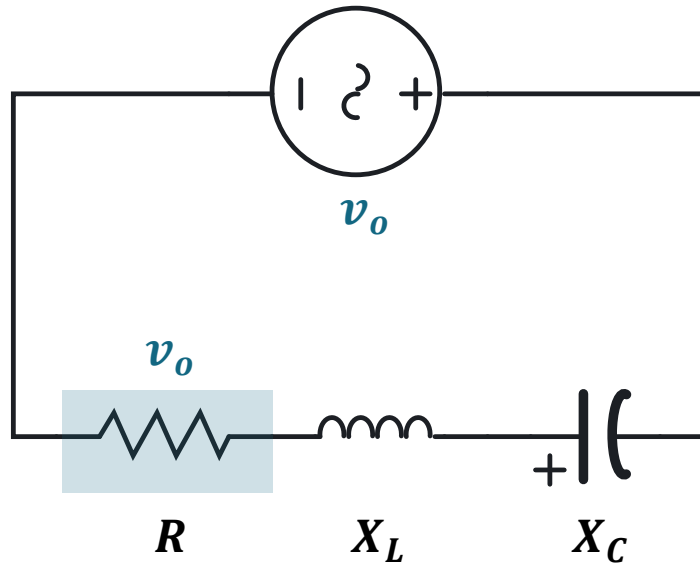

## Formula

$$f_R = \frac{1}{2\pi\sqrt{LC}}$$

Let  $X_L = X_C$

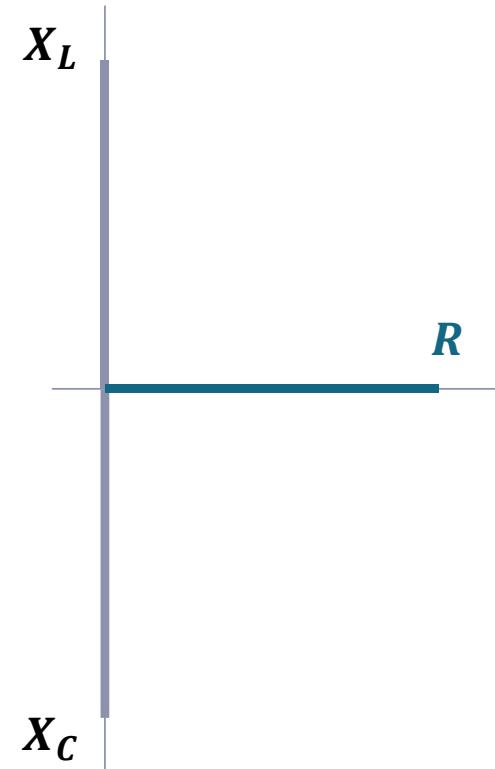

## EXERCISE

---

A series circuit consists of a  $30\ \Omega$  resistor, a  $0.104\ H$  inductor, and a  $40\ \mu F$  capacitor. If a variable-frequency  $120\ V$  source is connected across its terminals, for the condition of resonant determine the following:

- The resonant frequency ( $f_R$ )
- The circuit current ( $i_R$ ) and power ( $P_R$ )
- The voltage drop across the resistor ( $v_R$ ), the inductor ( $v_L$ ), and the capacitor ( $v_C$ )

Solution




# PARALLEL RESONANCE




# PARALLEL RESONANCE

## Circuit Diagram

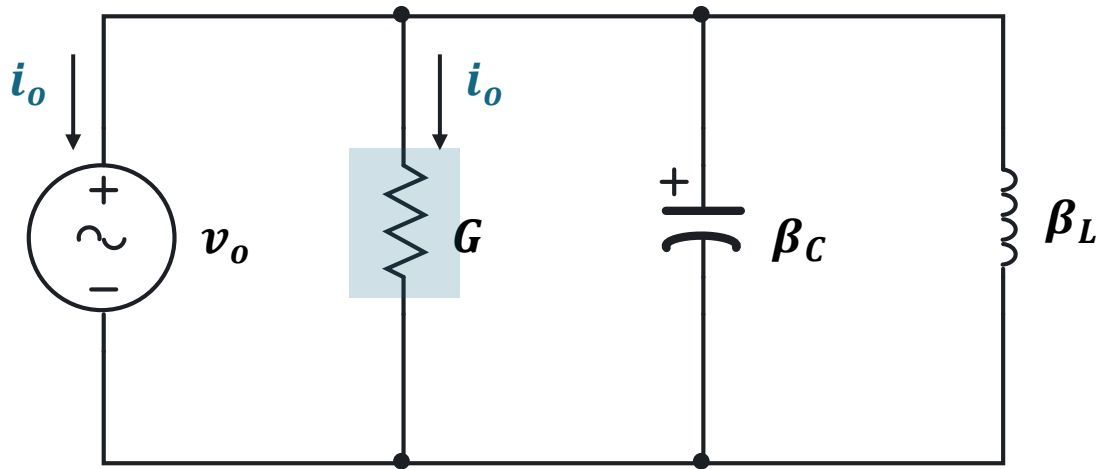

Let  $\beta_L = \beta_C$

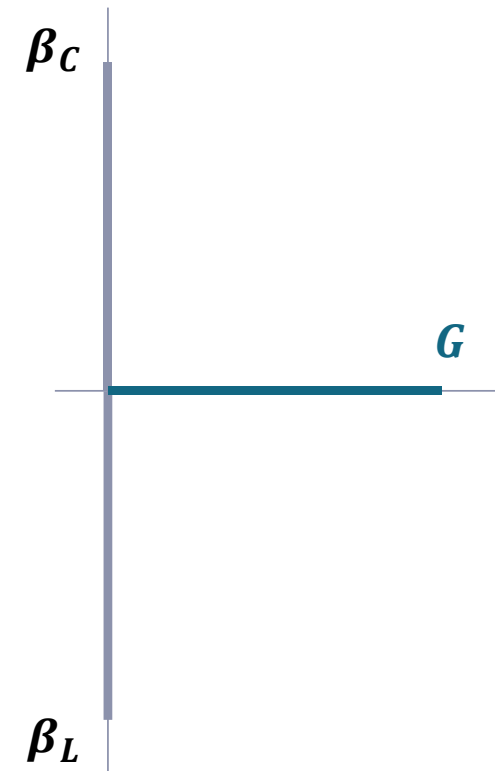

## Formula

$$f_R = \frac{1}{2\pi\sqrt{LC}}$$



## EXERCISE

---

A parallel circuit consists of a  $10\ \Omega$  resistor, a  $2\ H$  inductor, and a  $50\ \mu F$  capacitor. If a variable-frequency  $1\ V$  source is connected across its terminals, for the condition of resonant determine the following:

- The resonant frequency ( $f_R$ )
- The circuit current ( $i_R$ ) and power ( $P_R$ )
- The voltage drop across the resistor ( $v_R$ ), the inductor ( $v_L$ ), and the capacitor ( $v_C$ )

Solution





# RESONANCE FREQUENCY

---

$$f_R = \frac{1}{2\pi\sqrt{LC}}$$

Resultant reactance is zero [ $X_L = X_C$ ]

Circuit behaves like a **pure resistance**

Total current is **in phase** with the impressed voltage

Power factor is **unity**



# LABORATORY

