



# **MULTIPLIER CIRCUIT**

## **COMBINATIONAL LOGIC CIRCUITS**

---

*prepared by:*

**Gyro A. Madrona**  
Electronics Engineer

# TOPIC OUTLINE

## Multiplier Circuit



# MULTIPLIER CIRCUIT



# MULTIPLICATION

---

## Decimal Multiplication

$$\begin{array}{r} 8 \text{ Multiplicand} \\ \times 3 \text{ Multiplier} \\ \hline 24 \text{ Product} \end{array}$$

## Binary Multiplication

$$\begin{array}{r} 1000 \text{ Multiplicand} \\ \times 0011 \text{ Multiplier} \\ \hline 1000 \text{ Partial product 0} \\ + 1000 \text{ Partial product 1} \\ \hline 11000 \text{ Product} \end{array}$$



## EXERCISE

---

Create a block-level representation of a 2-bit binary multiplier.

Solution



## EXERCISE

---

Synthesize a 2-bit parallel binary multiplier, and design a corresponding printed circuit board (PCB) layout for its implementation.

### note

The use of XOR or XNOR gates is not allowed.

### Solution



# LABORATORY

