

VOLTAGE AND CURRENT DIVIDER THEOREM

BASIC CIRCUIT ANALYSIS METHOD

prepared by:

Gyro A. Madrona

Electronics Engineer

TOPIC OUTLINE

Voltage Divider Theorem (VDT)

Current Divider Theorem (IDT)



VOLTAGE DIVIDER THEOREM




VOLTAGE DIVIDER THEOREM

In a series circuit consisting of multiple resistors, the voltage across any resistor is proportional to its resistance relative to the equivalent resistance of the series combination.

Formula

$$v_N = v_{in} \frac{R_N}{R_{eq}}$$


Series Network

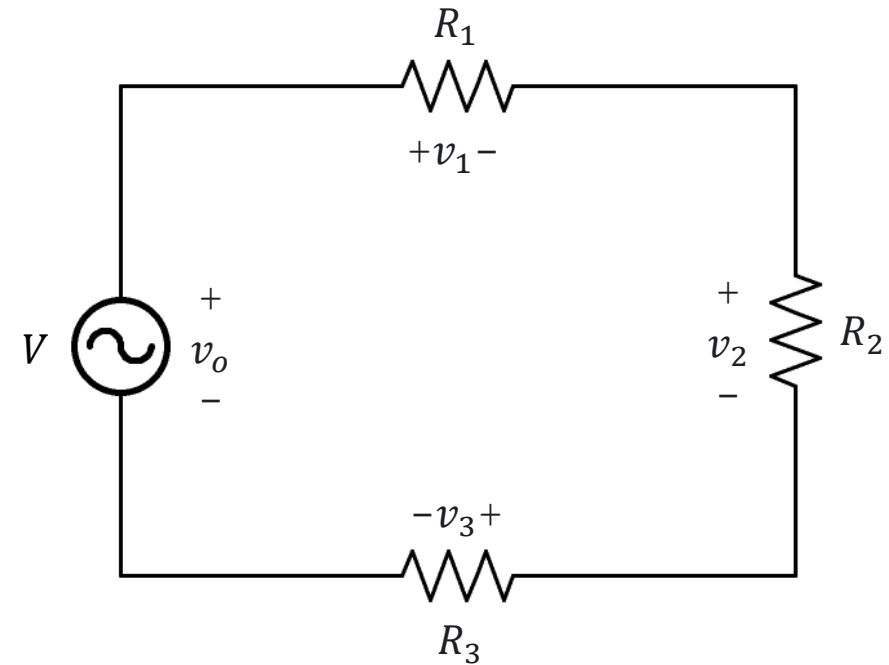

EXERCISE

For the given series circuit, determine the voltage drops across each individual resistor.

Solution

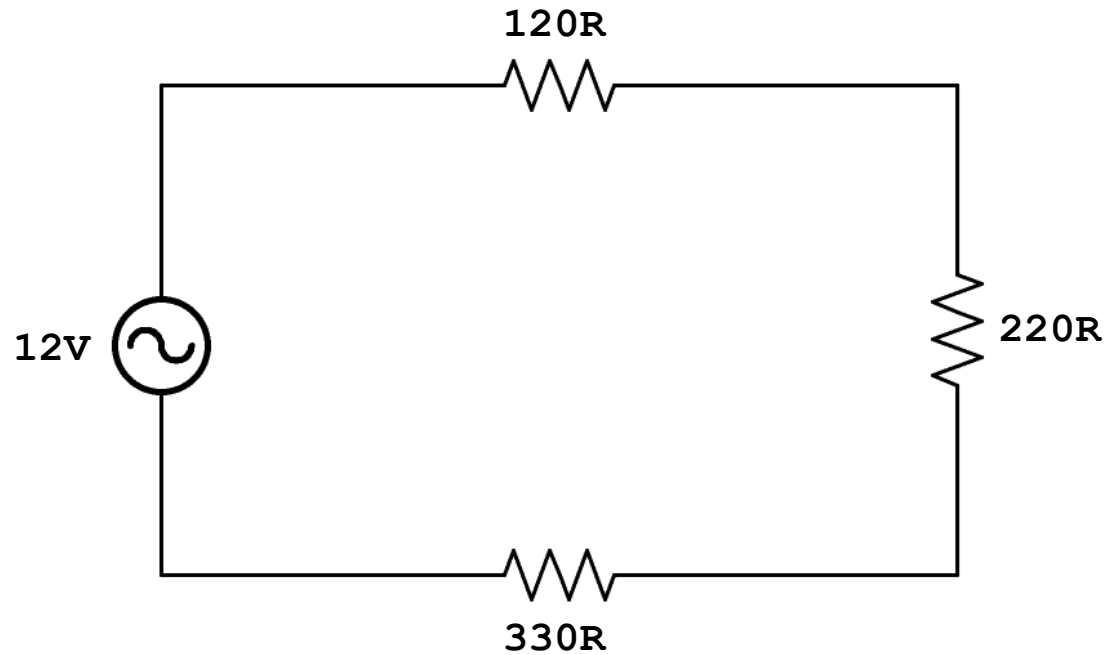

CURRENT DIVIDER THEOREM




CURRENT DIVIDER THEOREM

In a parallel circuit with multiple resistors, the current through any resistor is inversely proportional to its resistance relative to the equivalent resistance of the parallel combination.

Formula

$$i_N = i_{in} \frac{R_{eq}}{R_N}$$


Parallel Network

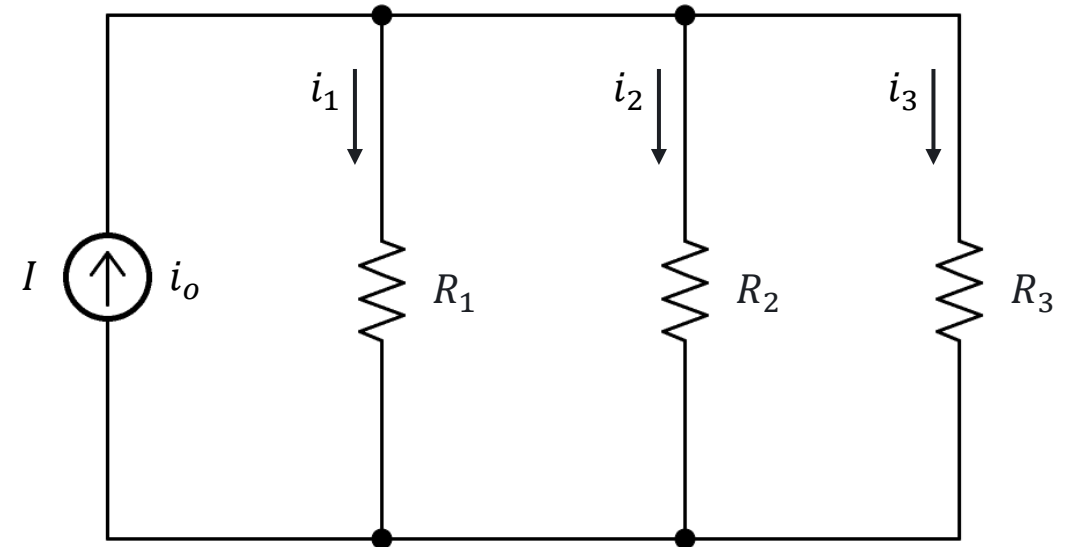

EXERCISE

For the given parallel circuit, determine the current flowing through each individual resistor.


Solution

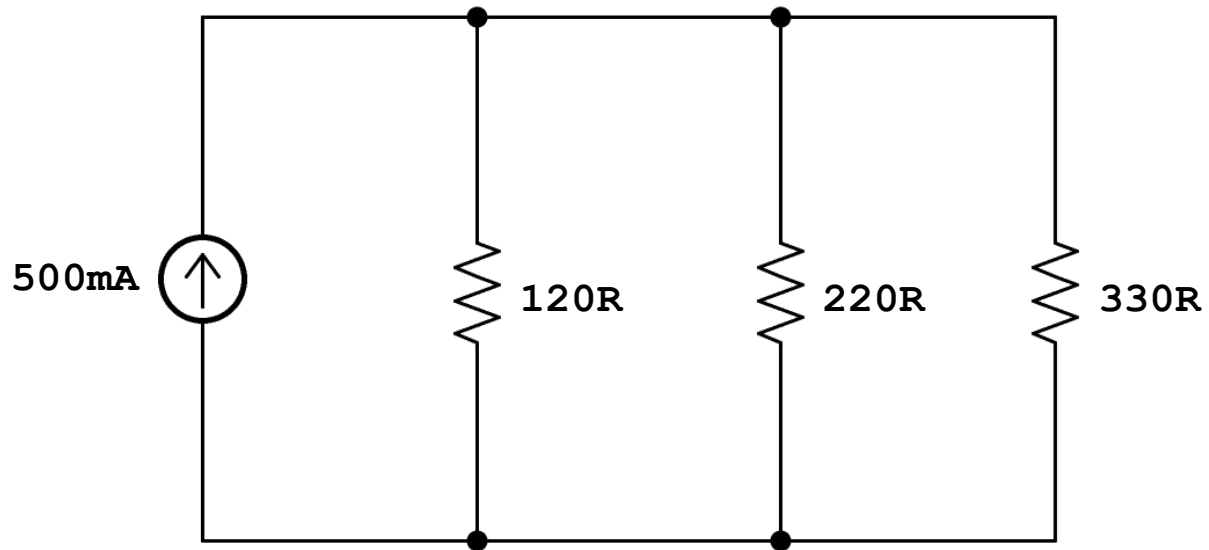

EXERCISE

Analyze the given circuit to determine both the current through and the voltage drop across each resistor.

Solution

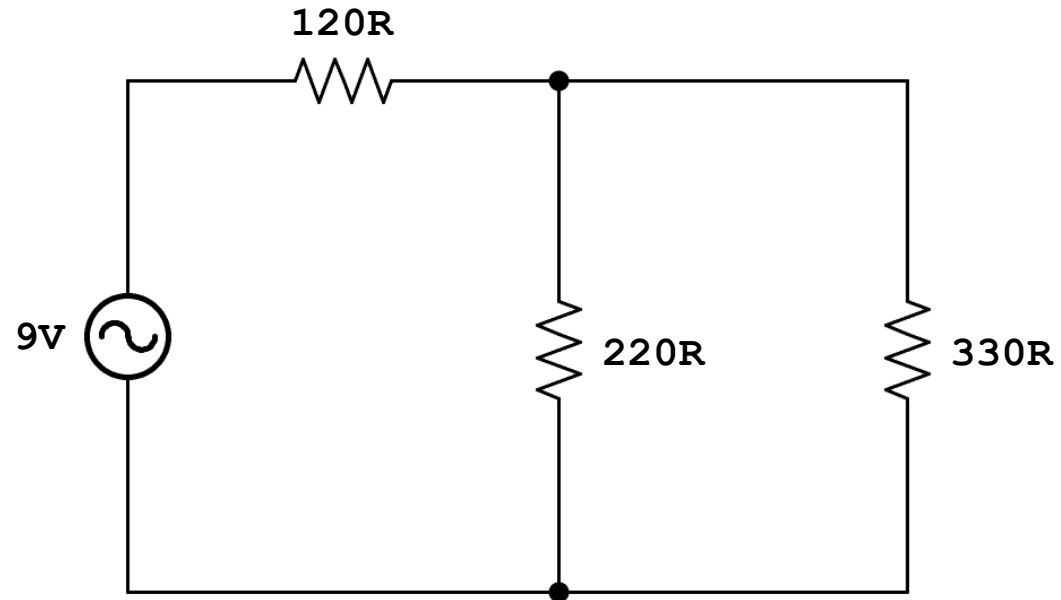

LABORATORY

