



BASIC OP-AMP **CONFIGURATIONS** **OPERATIONAL AMPLIFIER**

prepared by:

Gyro A. Madrona
Electronics Engineer

TOPIC OUTLINE

Basic Op-Amp Configurations

- Non-inverting Op-Amp
- Inverting Op-Amp
- Summing Op-Amp




BASIC OP-AMP CONFIGURATIONS



NON-INVERTING AMPLIFIER

Derivation

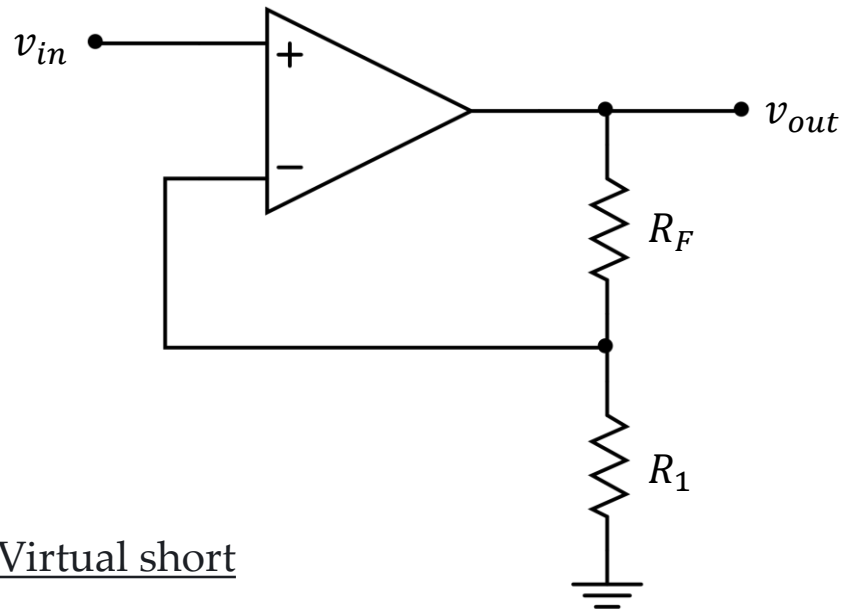

Virtual short


since $v^+ \approx v^-$



EXERCISE


What is the closed-loop gain and the output voltage of the given op-amp circuit?

Solution

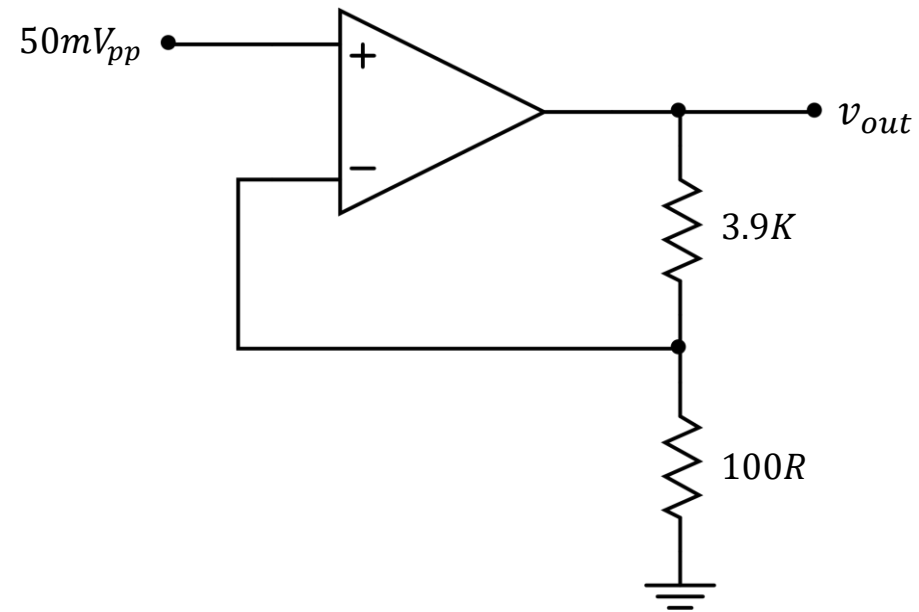

INVERTING AMPLIFIER

Derivation

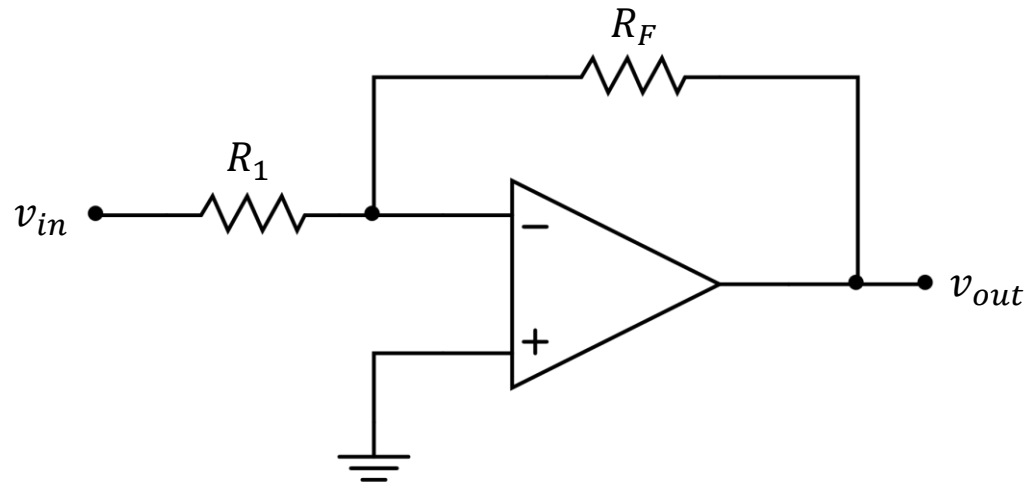

Virtual ground


since $v^+ \approx v^-$



EXERCISE


What is the closed-loop gain and the output voltage of the given op-amp circuit?

Solution

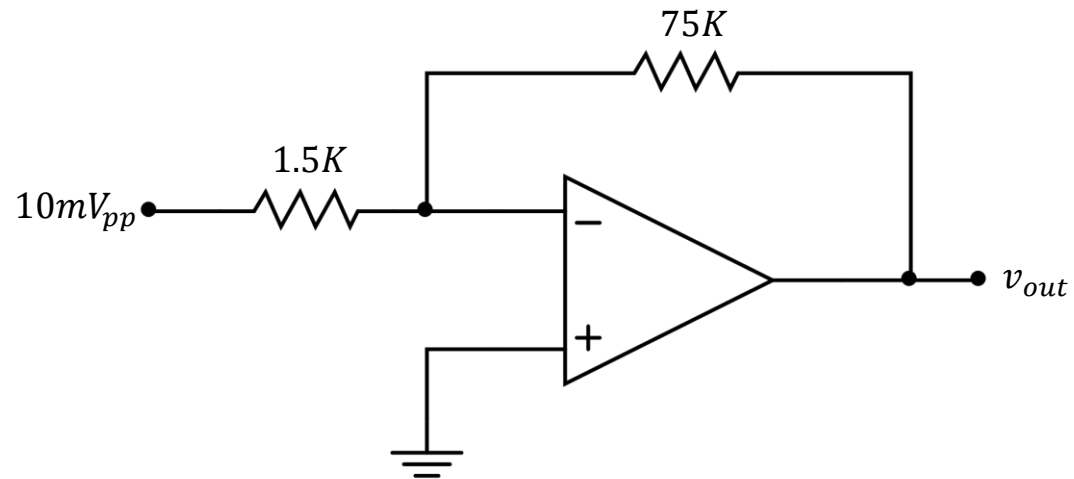

SUMMING AMPLIFIER

Derivation

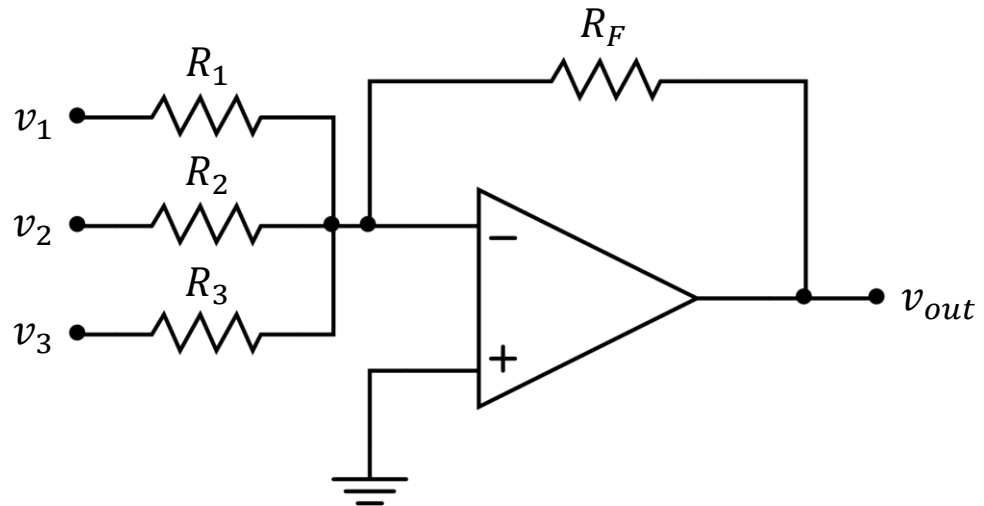

Virtual short


since $v^+ \approx v^-$



EXERCISE

What is the closed-loop gain and the output voltage of the given op-amp circuit?

Solution

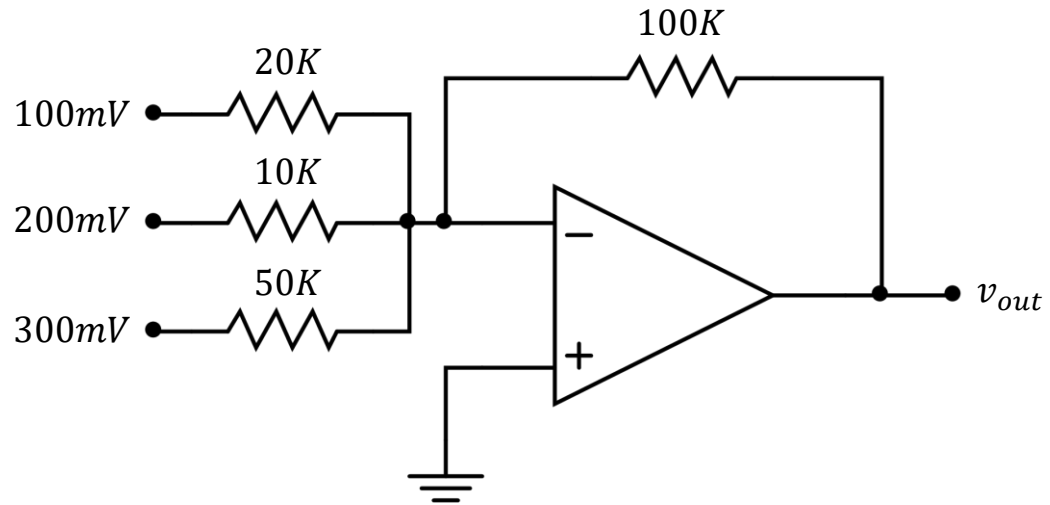

LABORATORY

