

THE THREE BASIC TYPES OF CIRCUIT

AC CIRCUITS

prepared by:

Gyro A. Madrona

Electronics Engineer

TOPIC OUTLINE

The R-Circuit

The C-Circuit

The L-Circuit




THE THREE BASIC TYPES OF CIRCUIT





THE R-CIRCUIT

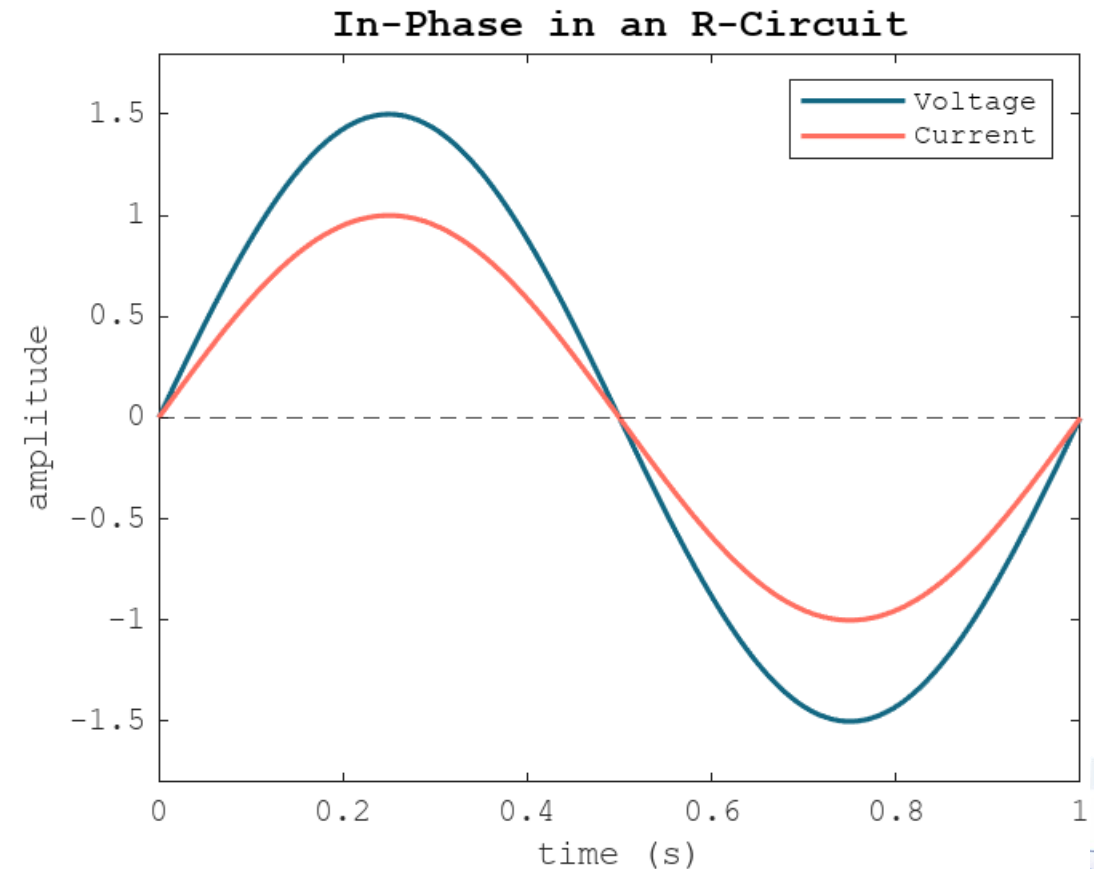In a purely resistive circuit, the voltage and current are in phase. Resistors are frequency-independent components, their behavior remains the same for both DC and AC circuits.




THE R-CIRCUIT

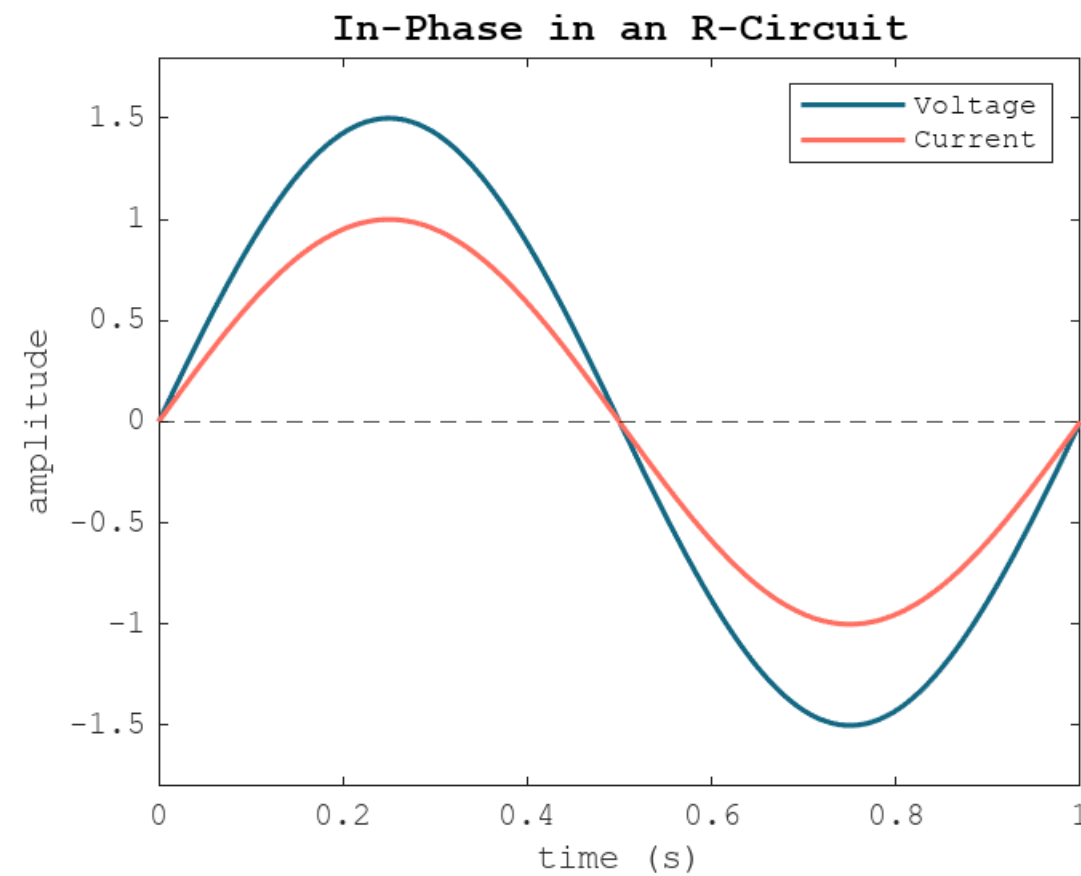
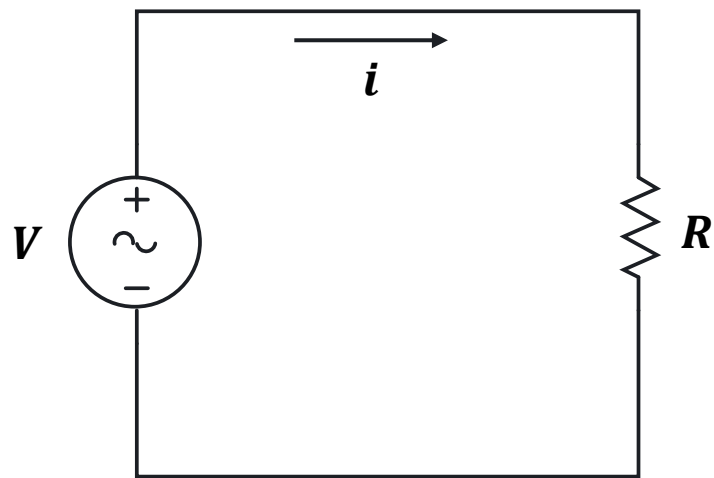


THE C-CIRCUIT

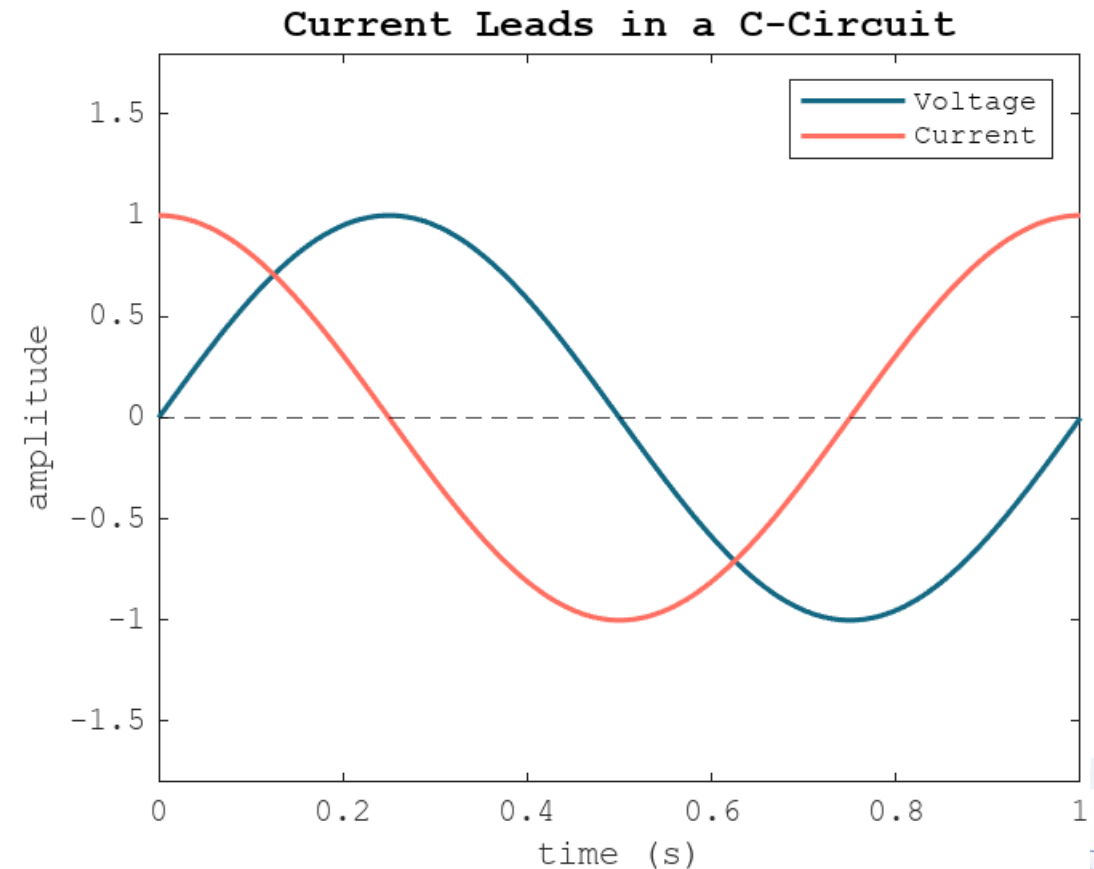In a purely **capacitive circuit**, the current leads the voltage by 90 degrees. This phase difference occurs because the capacitor resists changes in voltage.




THE C-CIRCUIT

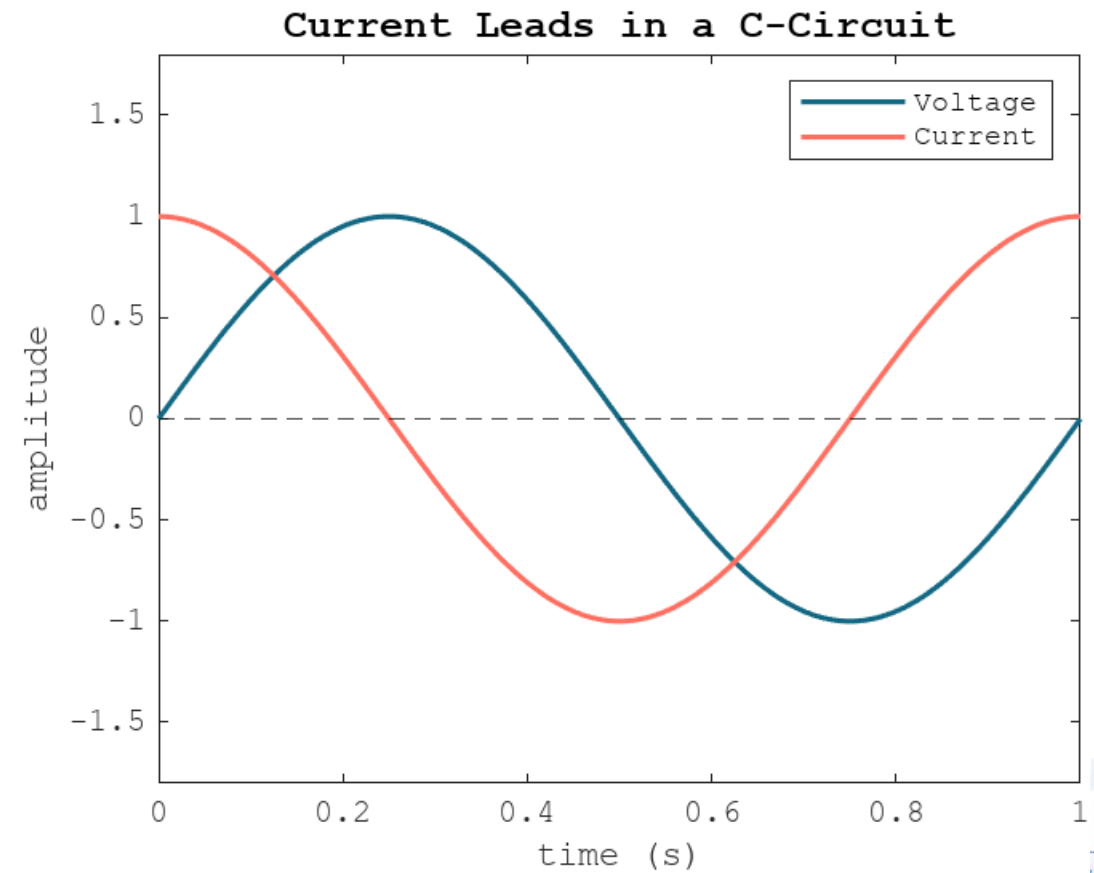
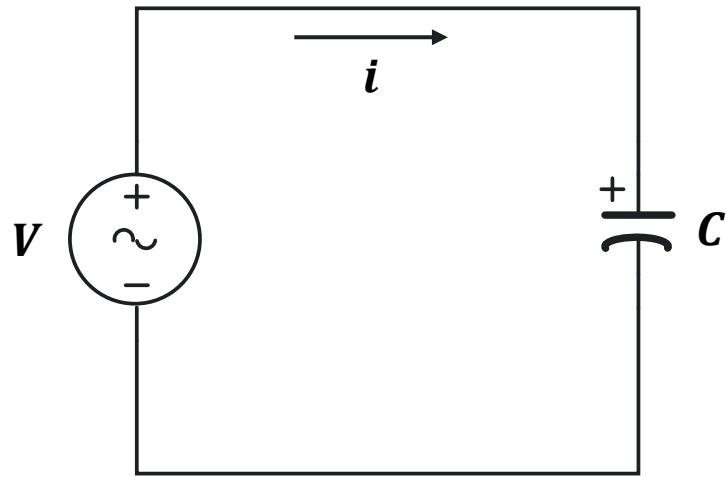


THE L-CIRCUIT

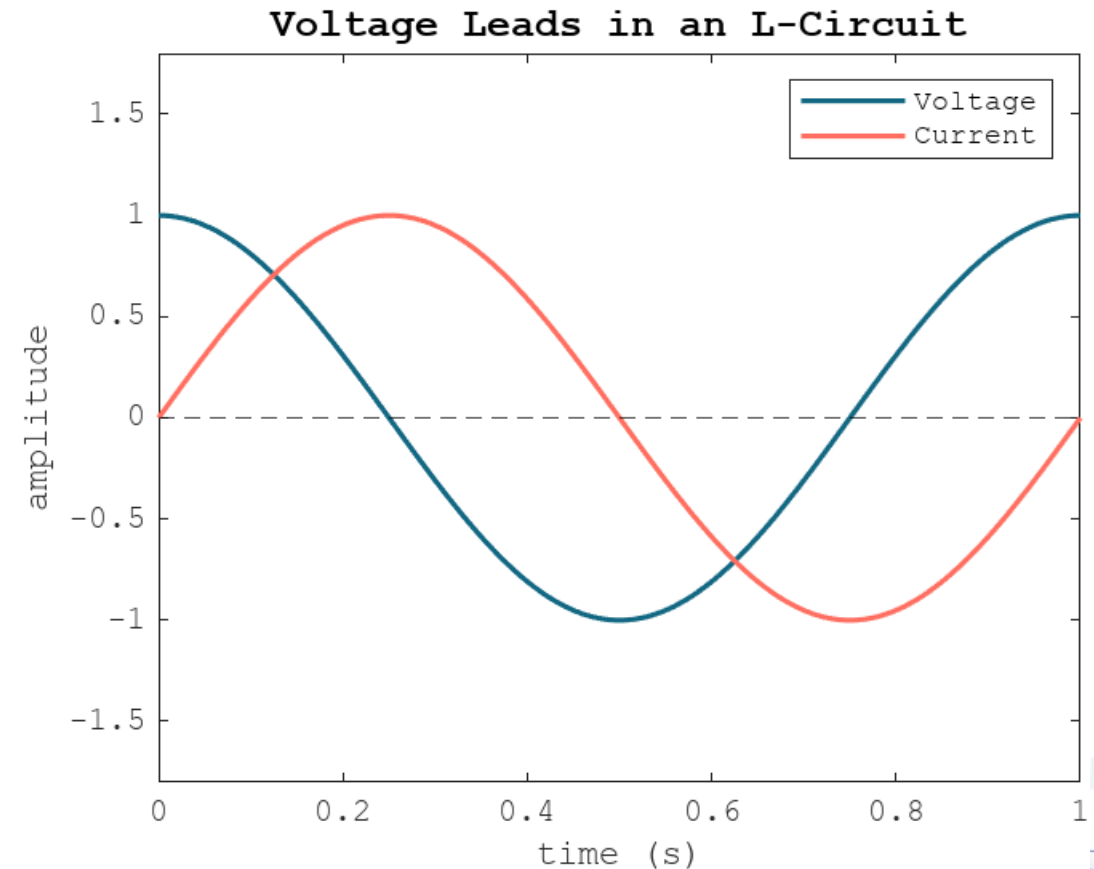In a purely inductive circuit, the voltage leads the current by 90 degrees. This phase difference occurs because the inductor resists changes in current.



THE L-CIRCUIT

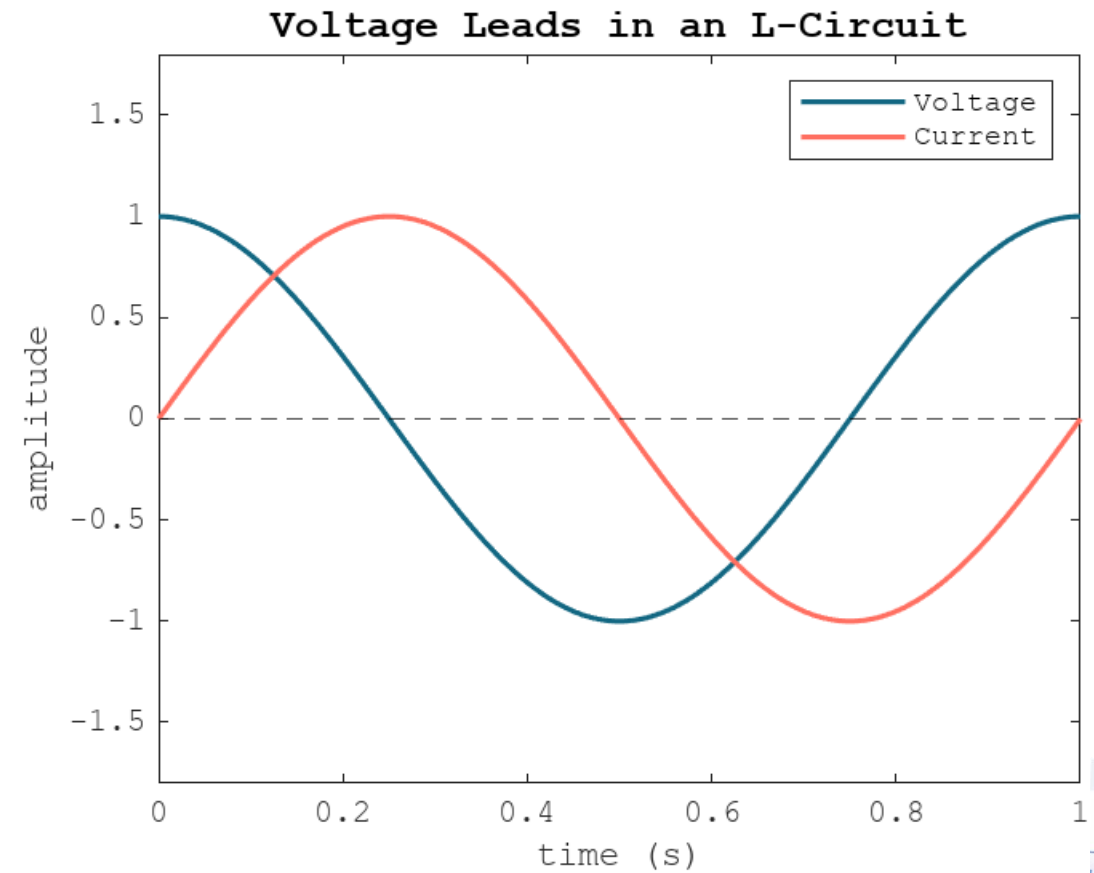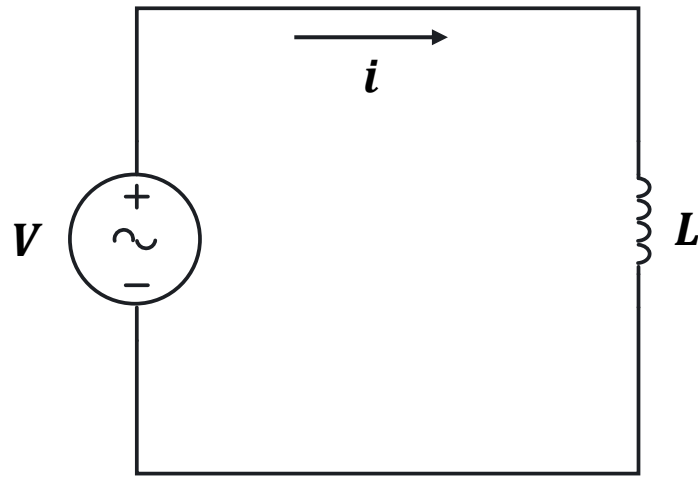

LABORATORY

