



CAPACITOR

TRANSIENT RESPONSE

prepared by:

Gyro A. Madrona
Electronics Engineer

TOPIC OUTLINE

RC Circuit

Charging a Capacitor

Discharging a Capacitor


Transient Response



CHARGING A CAPACITOR



RC CIRCUIT

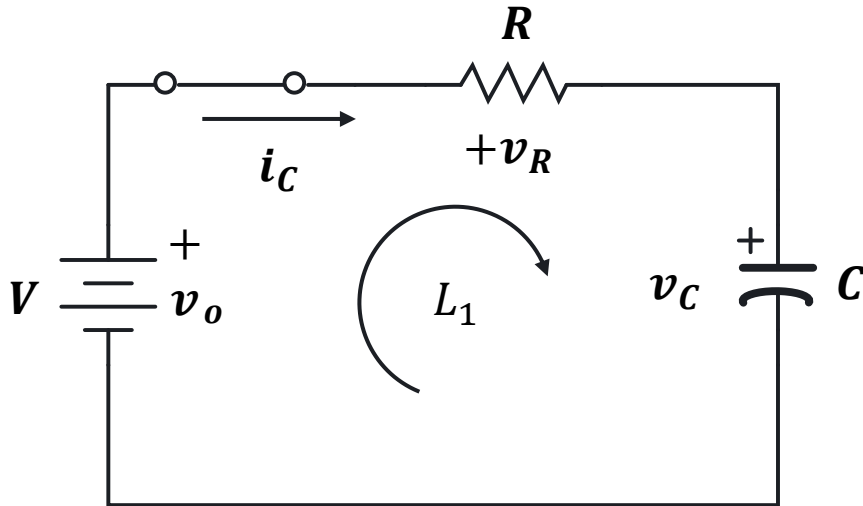

KVL @ L_1 :

$$-v_o + v_R + v_C = 0$$

$$v_R + v_C = v_o$$

$$i_C R + v_C = v_o \quad ; i_C = C \frac{d}{dt} v_C$$

$$RC \frac{d}{dt} v_C + v_C = v_o$$

$$\frac{d}{dt} v_C + \frac{1}{RC} v_C = \frac{v_o}{RC}$$

... first-order ODE

$$v_C(t) = v_o \left(1 - e^{-\frac{t}{RC}} \right)$$




CAPACITOR VOLTAGE

Charging equation:

$$v_c(t) = v_o \left(1 - e^{-\frac{t}{\tau}}\right)$$

where: $\tau = RC$

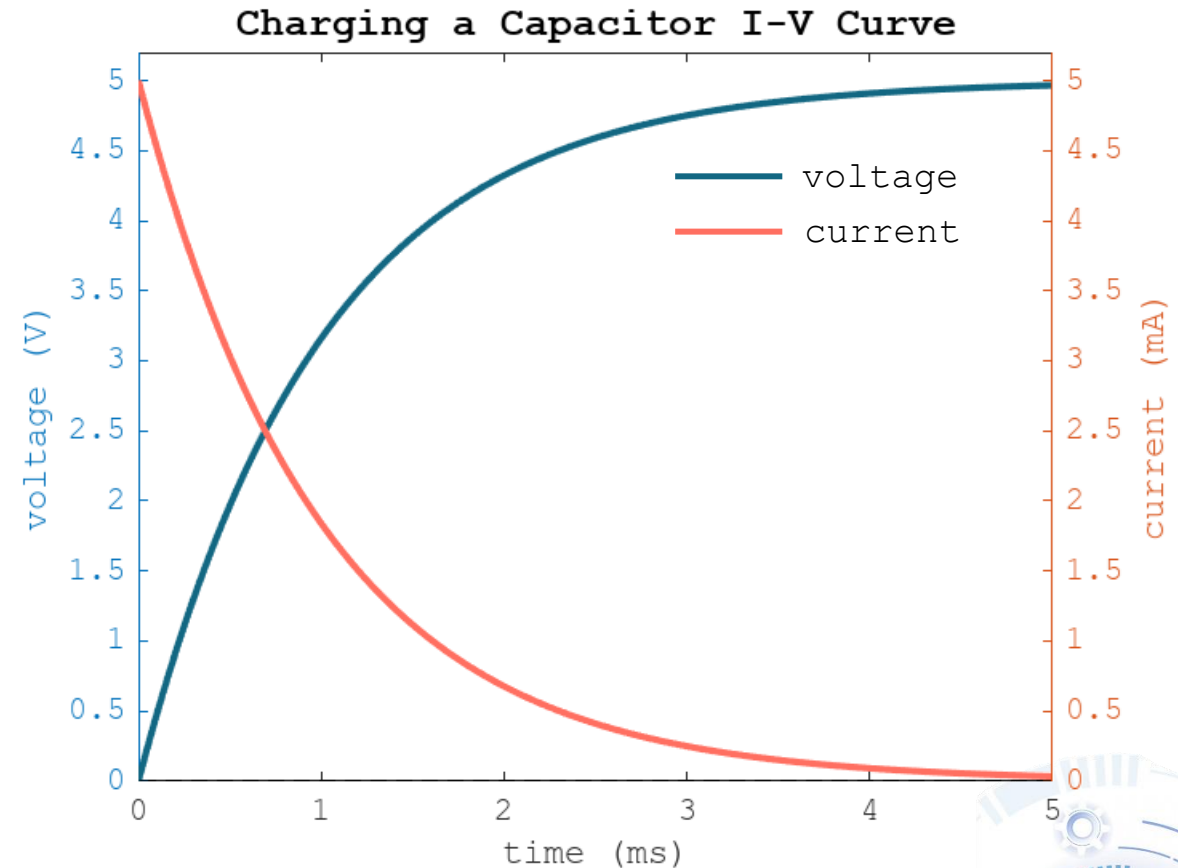The voltage across the capacitor starts at zero and exponentially increases to v_o volts (source voltage).




CAPACITOR CURRENT

Charging equation:

$$i_c(t) = \frac{v_o}{R} e^{-\frac{t}{\tau}}$$

where: $\tau = RC$

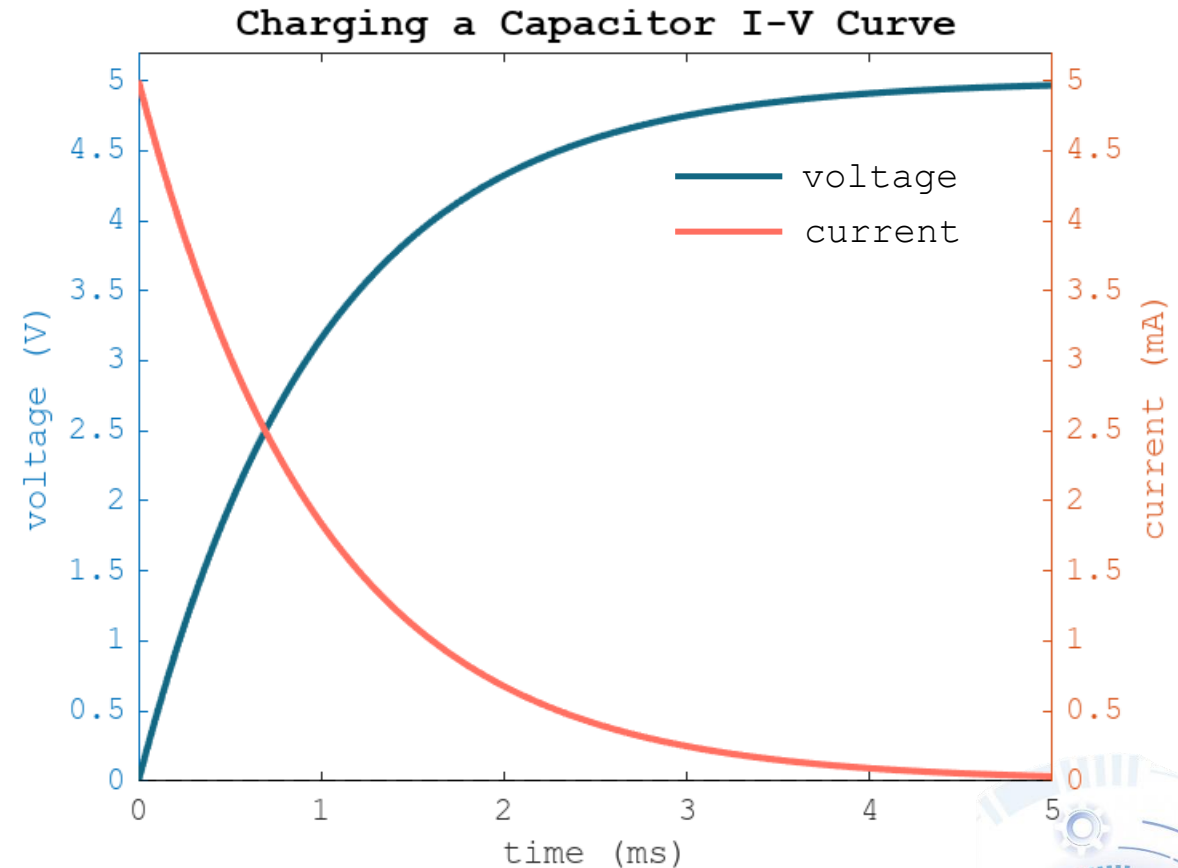The current through the capacitor instantly jumps to its maximum value of $\frac{v_o}{R}$ amperes then decays exponentially to zero.




TIME CONSTANT

The time constant τ is a measure of how quickly a capacitor charges or discharges in an RC circuit.

Formula:

$$\tau = RC$$

unit: second

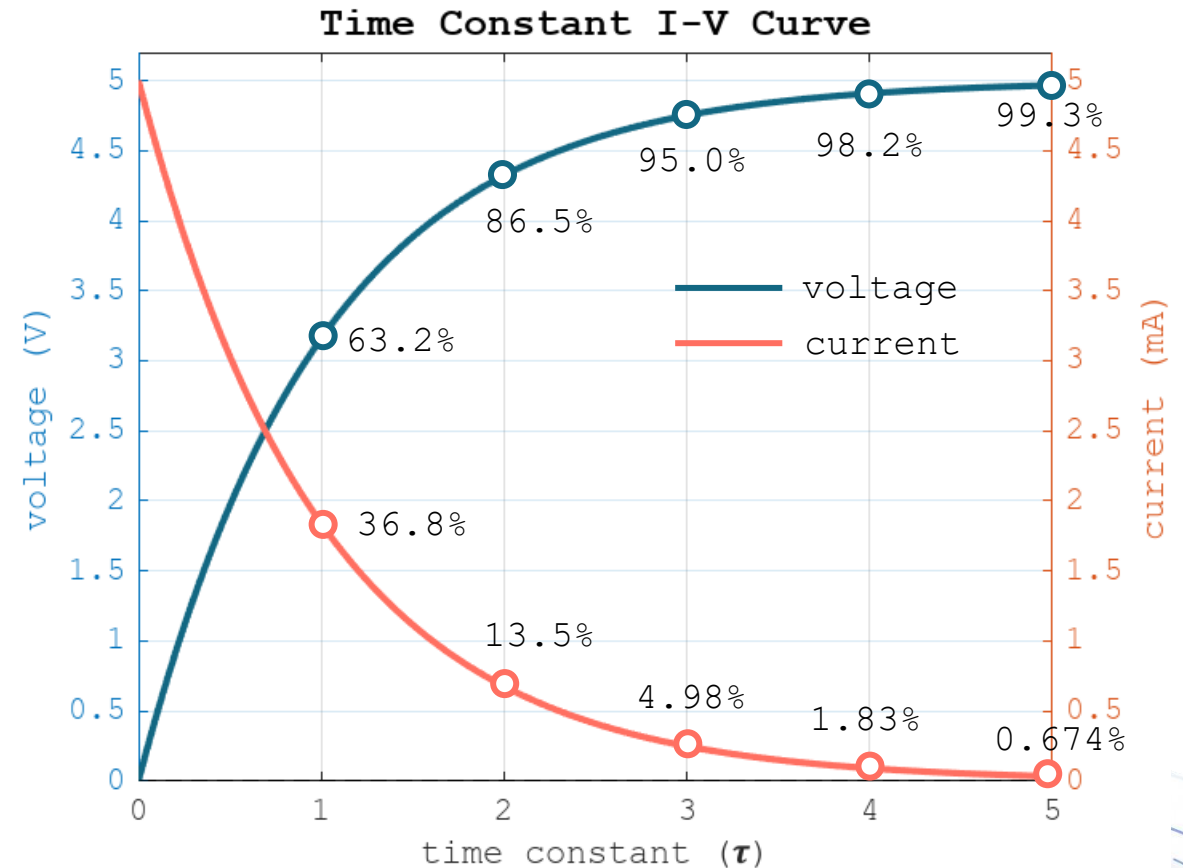

EXERCISE

A **100 μF** capacitor is connected to a **12 V** DC power supply through a resistor of **1 $K\Omega$** . Determine the time it takes for the capacitor to charge to **86.5%** of its maximum voltage.

Solution:



EXERCISE

A **$100\ \mu\text{F}$** capacitor is connected to a **$12\ \text{V}$** DC power supply through a resistor of **$1\ \text{k}\Omega$** . Determine the voltage across the capacitor after **$200\ \text{ms}$** of charging.


Solution:



DISCHARGING A CAPACITOR



RC CIRCUIT

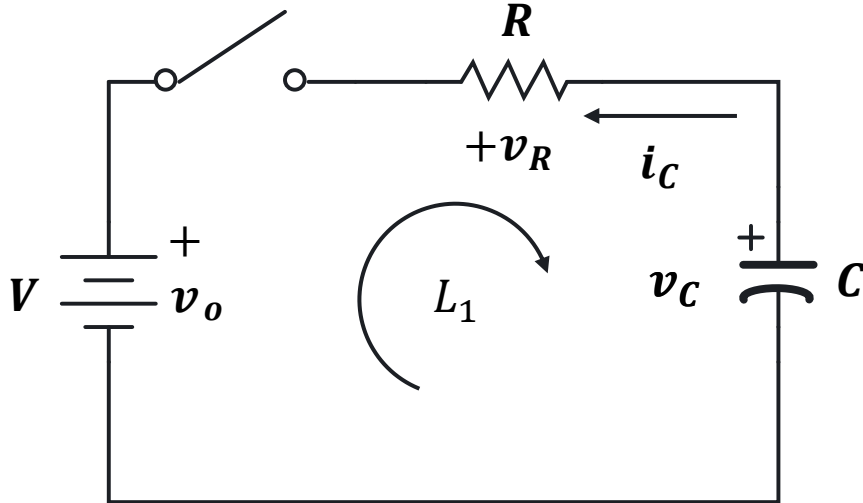

KVL @ L_1 :

$$v_R + v_C = 0$$

$$i_C R + v_C = 0 \quad ; i_C = C \frac{d}{dt} v_C$$

$$RC \frac{d}{dt} v_C + v_C = 0$$

$$\frac{d}{dt} v_C + \frac{1}{RC} v_C = 0$$

... first-order ODE

$$v_C(t) = v_o e^{-\frac{t}{RC}}$$




CAPACITOR VOLTAGE

Discharging equation:

$$v_c(t) = v_o e^{-\frac{t}{\tau}}$$

where: $\tau = RC$

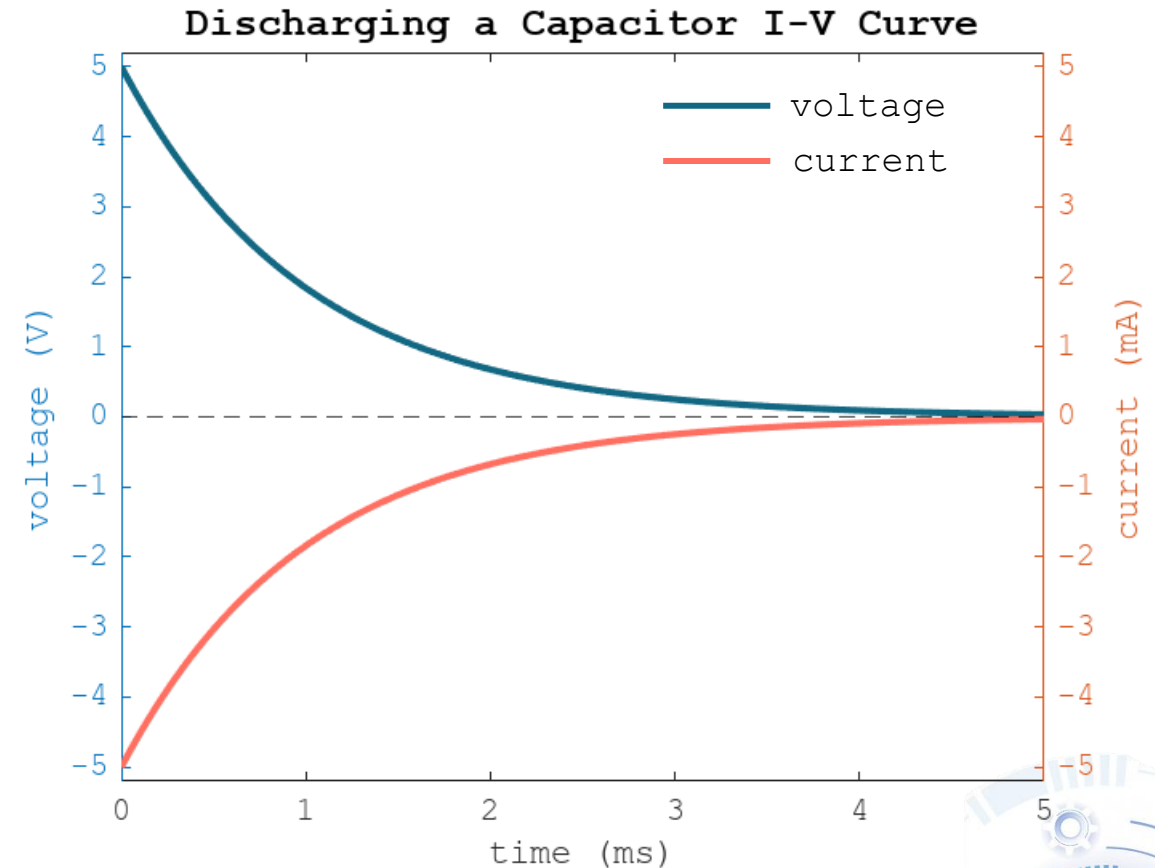The voltage across the capacitor starts at its maximum voltage v_o then decays exponentially to zero.




CAPACITOR CURRENT

Discharging equation:

$$i_c(t) = -\frac{v_o}{R} \left(e^{-\frac{t}{\tau}} \right)$$

where: $\tau = RC$

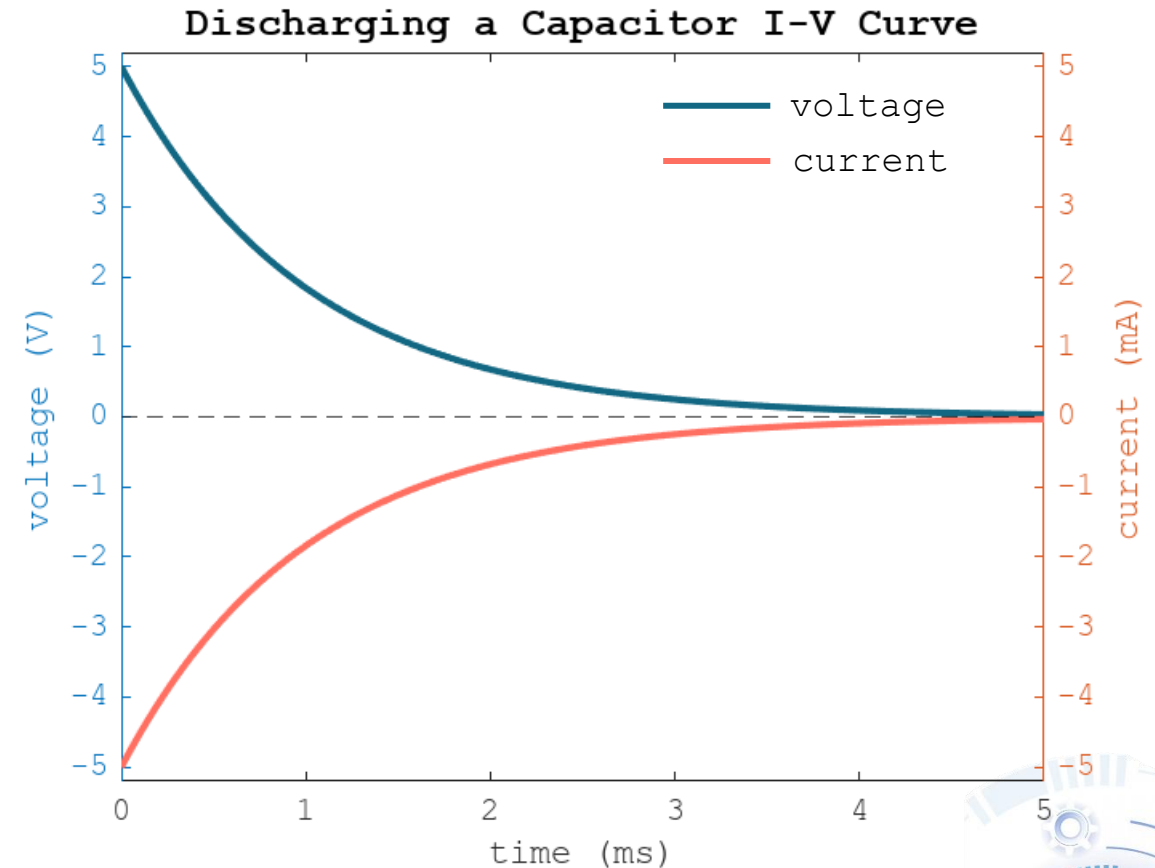The current through the capacitor instantly jumps to its maximum value, but in opposite direction of $-\frac{v_o}{R}$ then decays exponentially to zero.




EXERCISE

A **$200\ \mu\text{F}$** capacitor is initially charged to **$12\ \text{V}$** . It is then disconnected from the power supply and discharged a resistor of **$1.5\ \text{k}\Omega$** . Determine the **voltage** across the capacitor after **$0.1\ \text{s}$** of discharging.




TRANSIENT RESPONSE

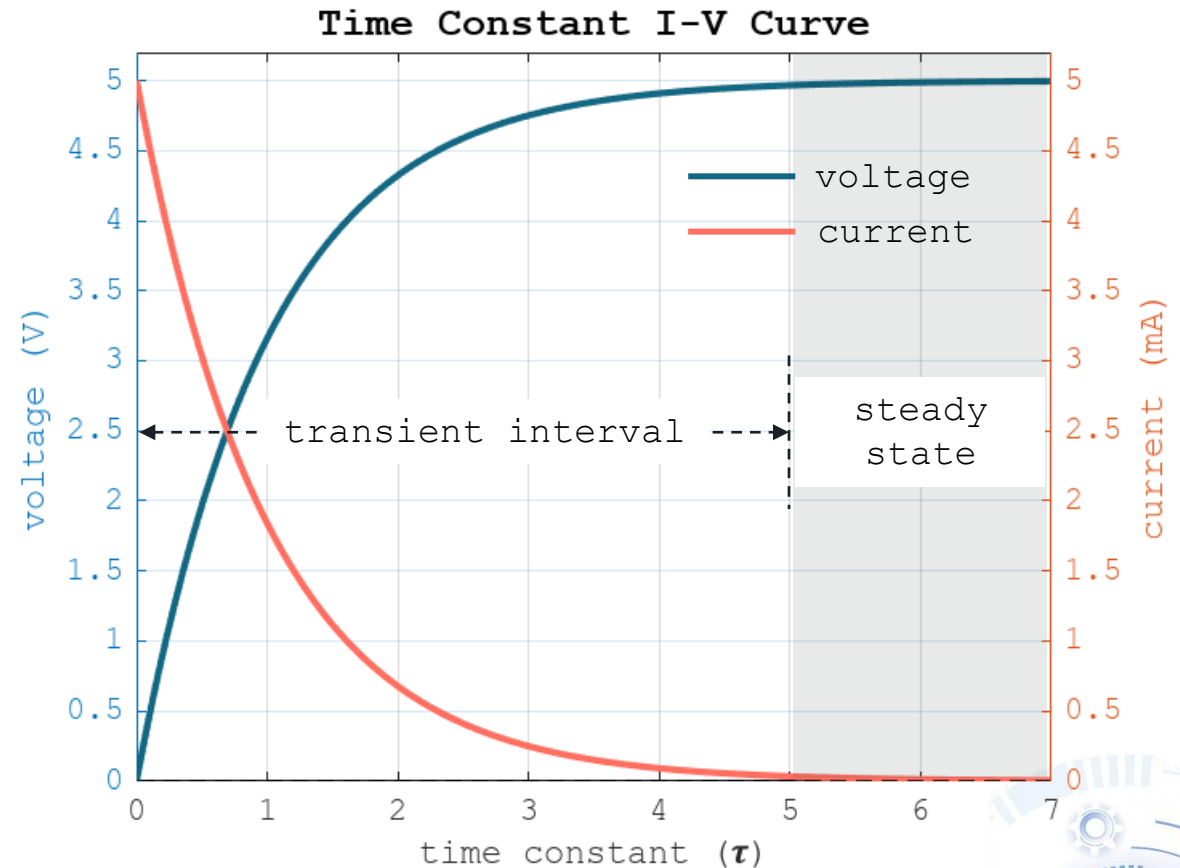The transient response of a capacitor describes the time-dependent changes in voltage across the capacitor and the current through it. The transient phase is typically considered to last for approximately five time constants 5τ after which the system is assumed to have reached steady-state conditions.



TRANSIENT RESPONSE

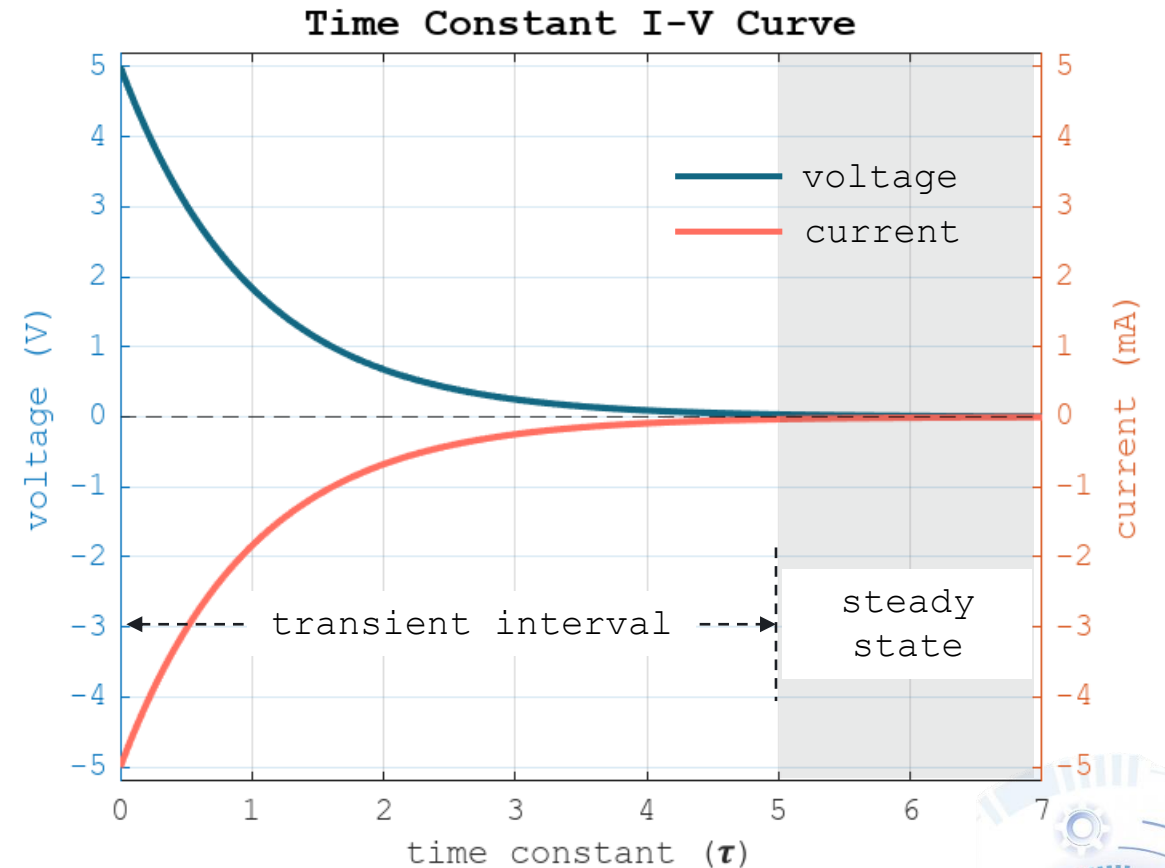The transient response of a capacitor describes the time-dependent changes in voltage across the capacitor and the current through it. The transient phase is typically considered to last for approximately five time constants 5τ after which the system is assumed to have reached steady-state conditions.



LABORATORY

