



# **ELEMENT COMBINATION** **RULE**

## **CIRCUIT ANALYSIS METHOD**

---

*prepared by:*

**Gyro A. Madrona**

Electronics Engineer

# TOPIC OUTLINE

Ohm's Law

Series Network

Parallel Network

Series-Parallel Network



# OHM'S LAW



# OHM'S LAW

---

Ohm's Law states that the ratio of voltage ( $V$ ) to current ( $I$ ) is **constant** ( $R$ ).

Mathematical Representation:

$$R = \frac{V}{I}$$

Basic Electrical Quantities:

1. Voltage (  $V$  ):

The measure of electrical potential energy per unit charge. It is the "**push**" or "force" that drives electric current through a circuit.

Formula:

$$V = IR$$

unit: Volt (  $V$  )



# OHM'S LAW

---

Ohm's Law states that the ratio of voltage ( $V$ ) to current ( $I$ ) is **constant** ( $R$ ).

Mathematical Representation:

$$R = \frac{V}{I}$$

Basic Electrical Quantities:

## 2. **Current ( I ):**

The flow of electric charge, typically carried by electrons in a conductor. It represents the rate at which charge flows through a point in a circuit.

Formula:

$$I = \frac{V}{R}$$

unit: Ampere ( A )



# OHM'S LAW

---

Ohm's Law states that the ratio of voltage ( $V$ ) to current ( $I$ ) is **constant** ( $R$ ).

Mathematical Representation:

$$R = \frac{V}{I}$$

Basic Electrical Quantities:

### 3. **Resistance ( $R$ ):**

The **opposition** to the flow of electric current in a material or component. It determines how much current will flow for a given voltage.

Formula:

$$R = \frac{V}{I}$$

unit: Ohm (  $\Omega$  )




## EXERCISE

---

Determine the current flowing through a circuit with **4 ohms** resistance when a voltage of **12 volts** is applied.

Solution:

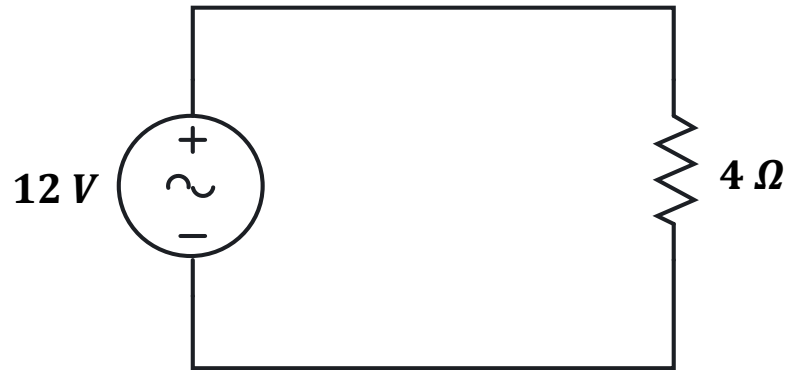


## EXERCISE

---

Determine the voltage drop across a circuit with a resistance of **5 ohms** when a current of **2 amps** flows through it.

Solution:

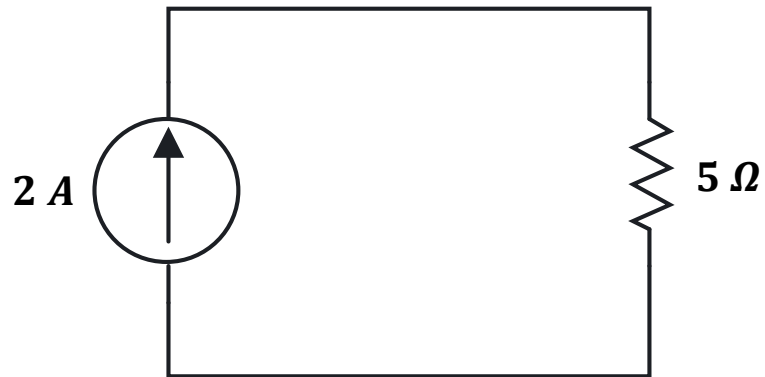




## EXERCISE

---

Determine the resistance of a circuit if a **9-volt** applied voltage results in a current flow of **1-ampere**.

Solution:

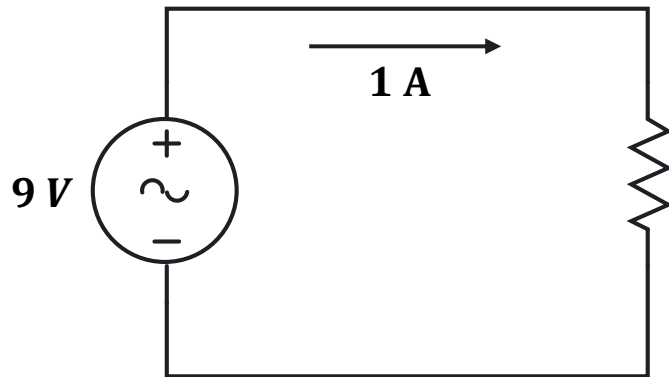


# SERIES NETWORK



# SERIES NETWORK

A series network refers to a configuration where components are connected end-to-end, forming a single path for current to flow.

Series Network:

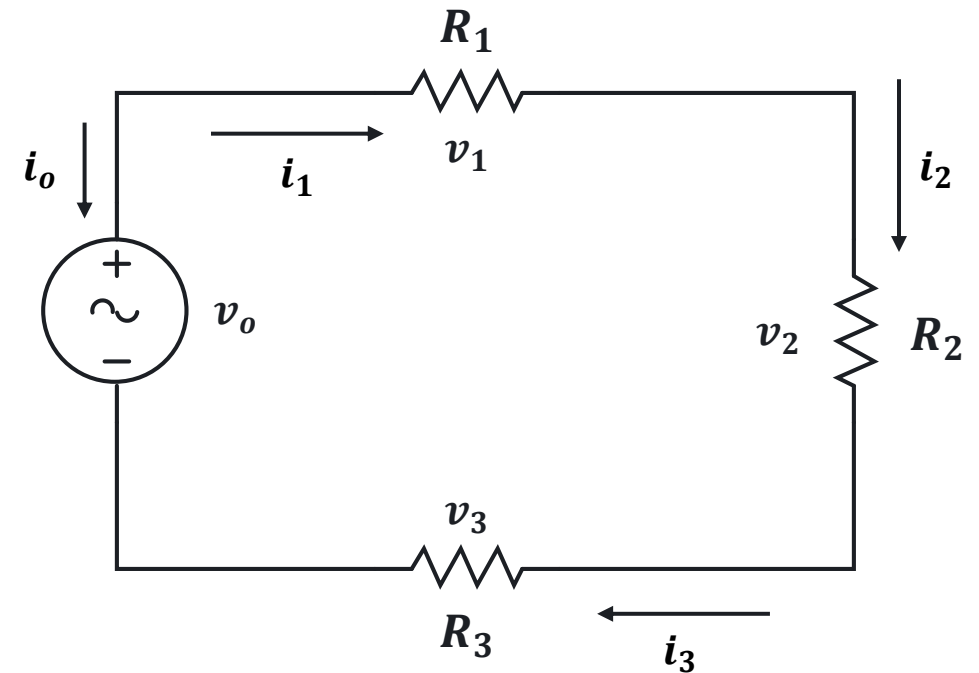


# CURRENT

In a series network, the same current flows through all components.

Mathematical Representation:

$$i_o = i_1 = i_2 = i_3 = \cdots i_n$$

Series Network:

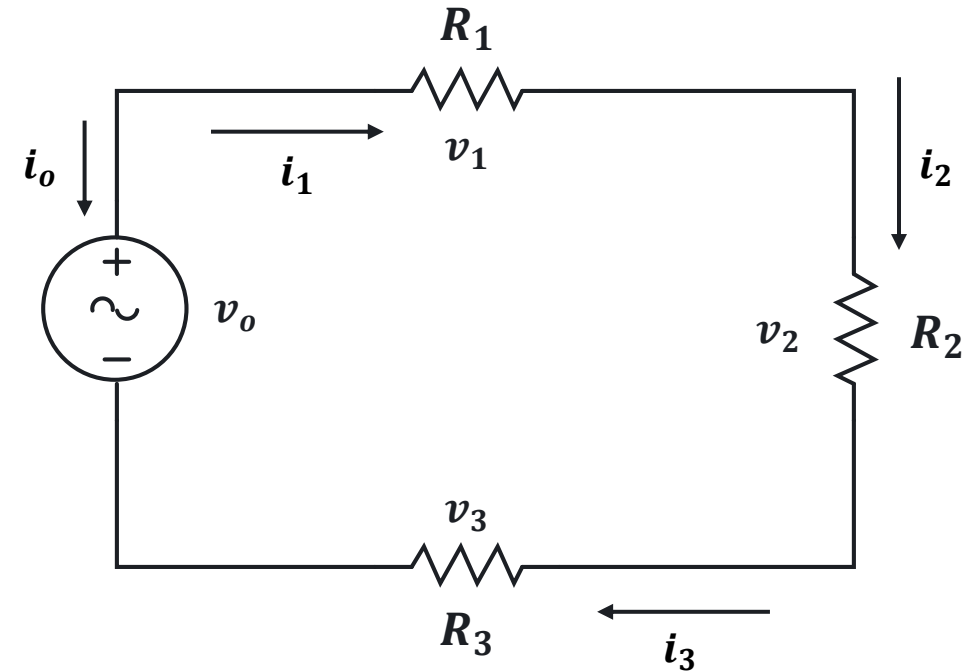


# RESISTANCE

In a series network, the total resistance is the sum of the individual resistances.

Mathematical Representation:

$$R_o = R_1 + R_2 + R_3 + \cdots R_n$$

Series Network:

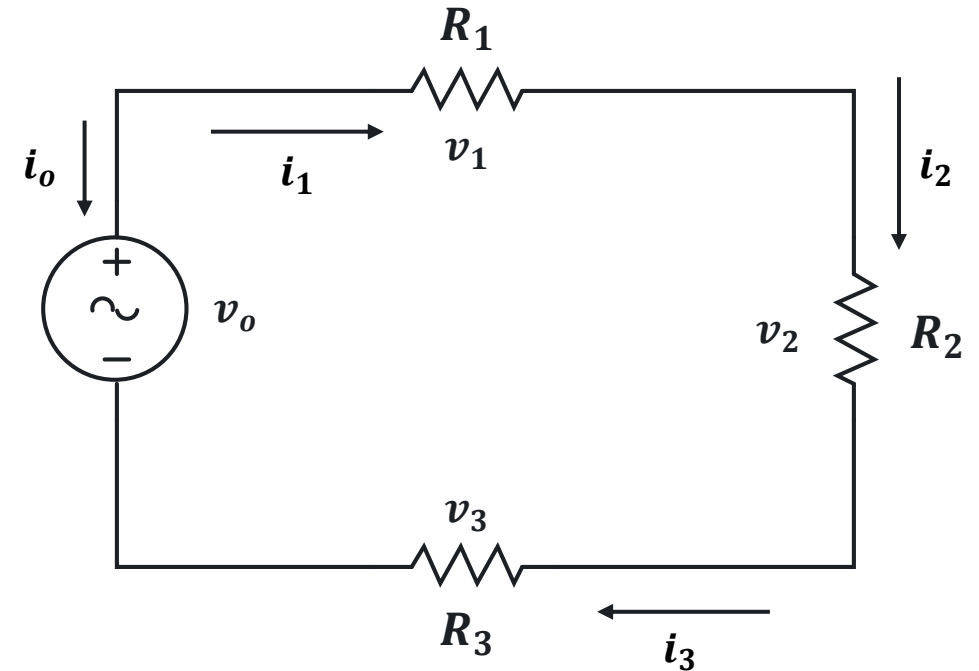


# VOLTAGE

In a series network, the total voltage is the sum of the voltages across each individual component.

Mathematical Representation:

$$v_o = v_1 + v_2 + v_3 + \cdots v_n$$

Series Network:

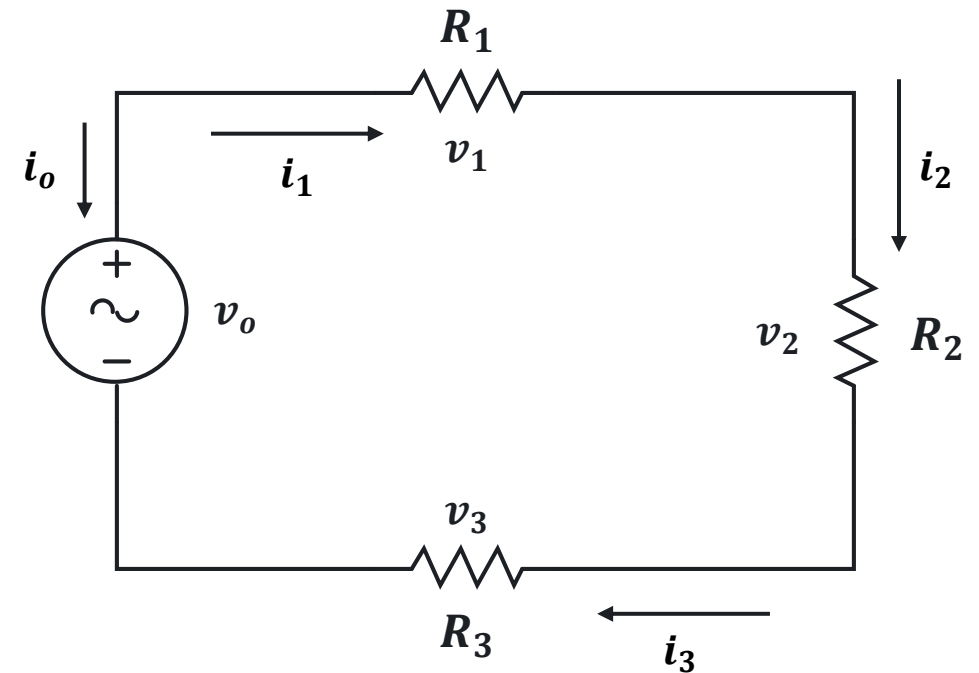


## EXERCISE

---

Determine the voltage drop across each resistor of the given circuit.

Solution:

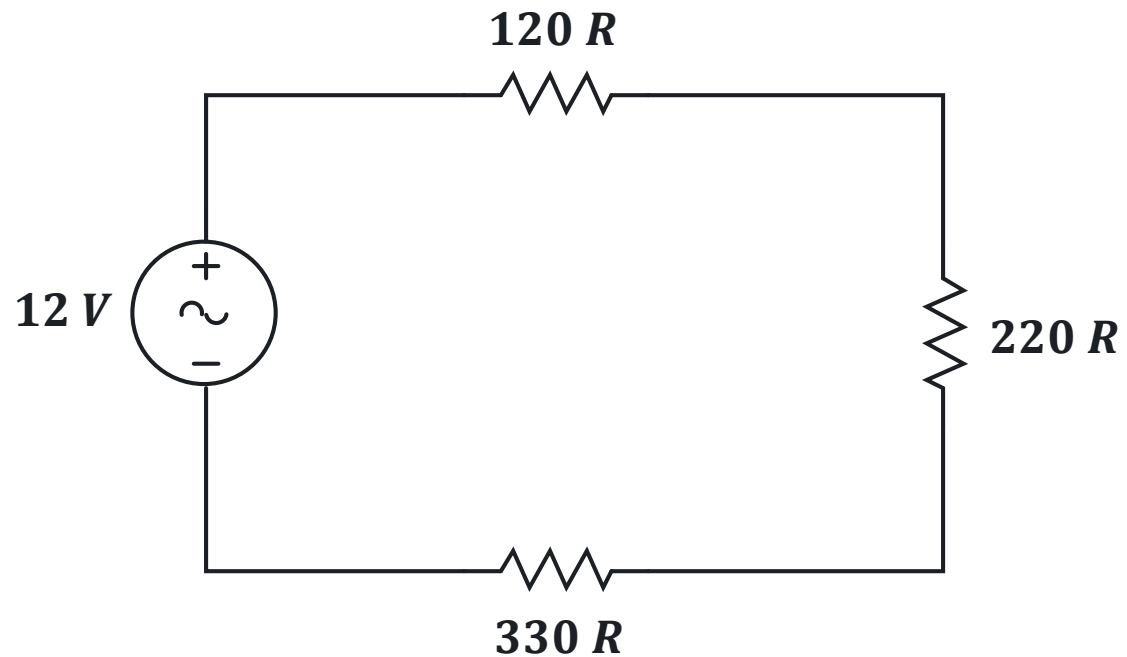


# PARALLEL NETWORK

---

A parallel network is a configuration where components are connected across the same two points, providing multiple paths for current to flow.

Parallel Network:

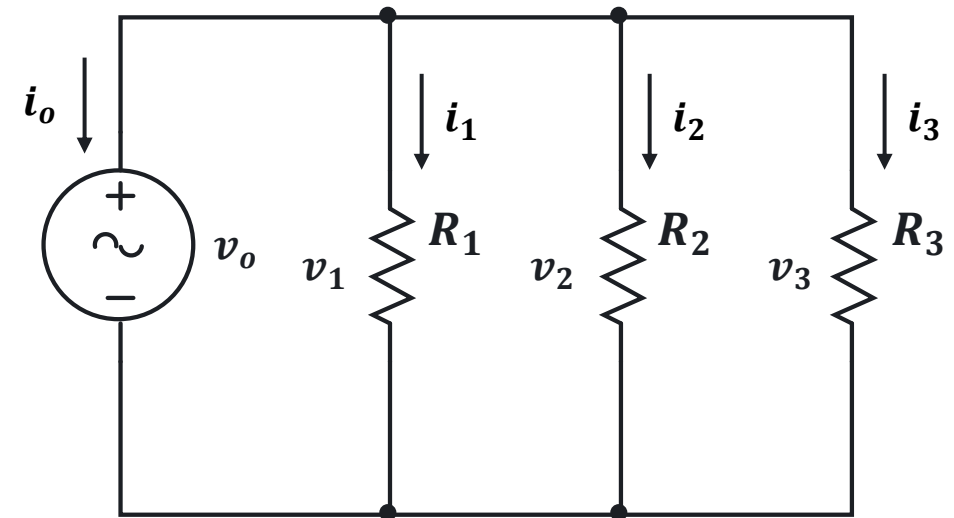



# VOLTAGE


---

In a parallel network, the voltage across all components is the same.

Mathematical Representation:

$$v_o = v_1 = v_2 = v_3 = \cdots v_n$$

Parallel Network:

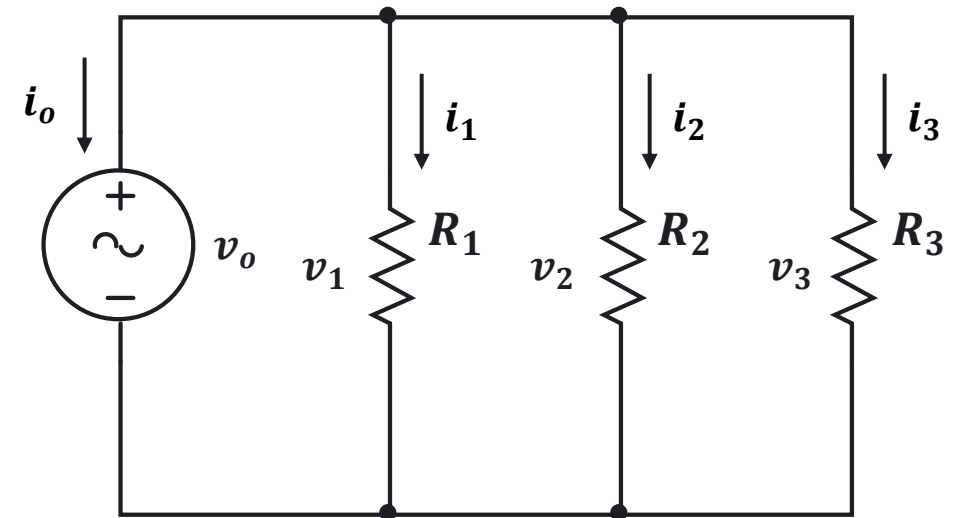

# CONDUCTANCE


---

Conductance refers to the ability of the network to allow the flow of electric current. It is the reciprocal of resistance and is measured in siemens ( $S$ ).

Mathematical Representation:

$$G = \frac{1}{R}$$

Parallel Network:

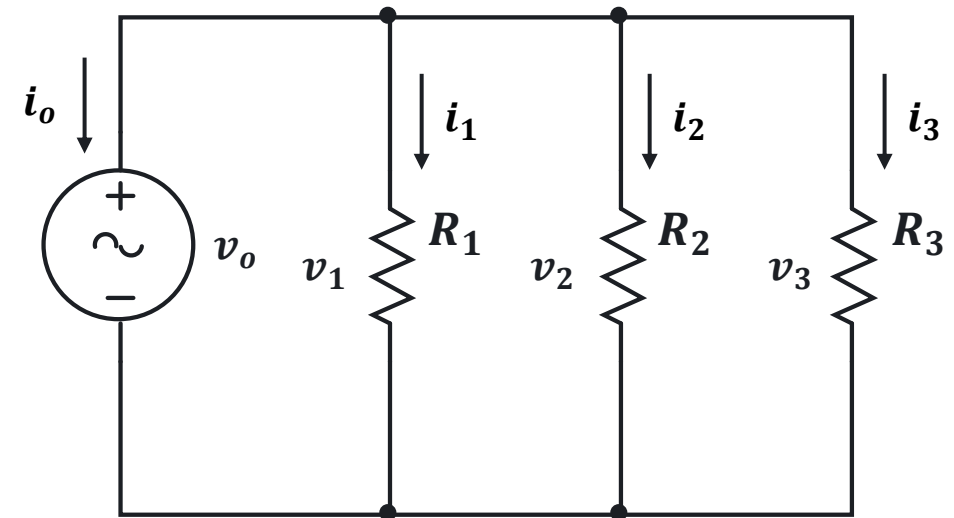

# CONDUCTANCE


---

In a parallel network, the total conductance is the sum of the individual conductance of each resistor.

Mathematical Representation:

$$G_o = G_1 + G_2 + G_3 + \cdots G_n$$

Parallel Network:

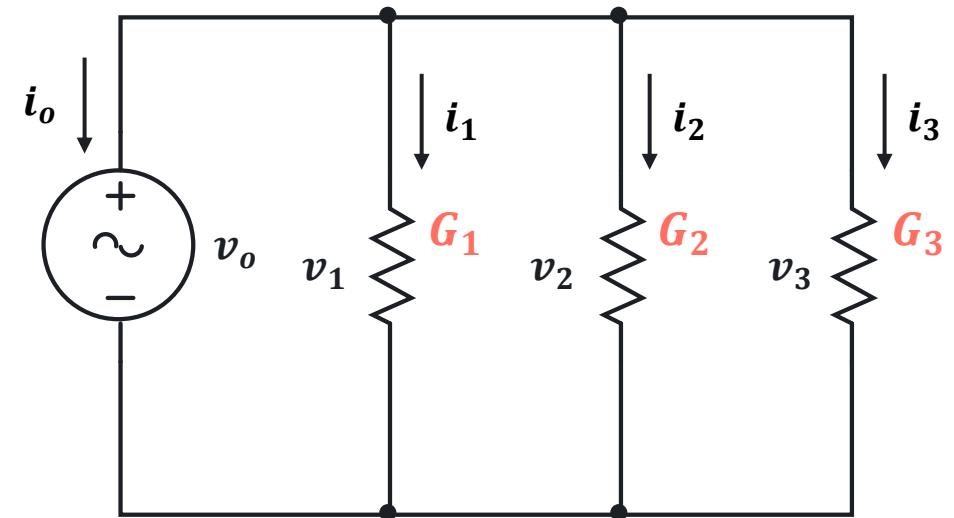

# CURRENT


---

In a parallel network, the total current is the sum of the current flowing through each individual component.

Mathematical Representation:

$$i_o = i_1 + i_2 + i_3 + \cdots i_n$$

Parallel Network:

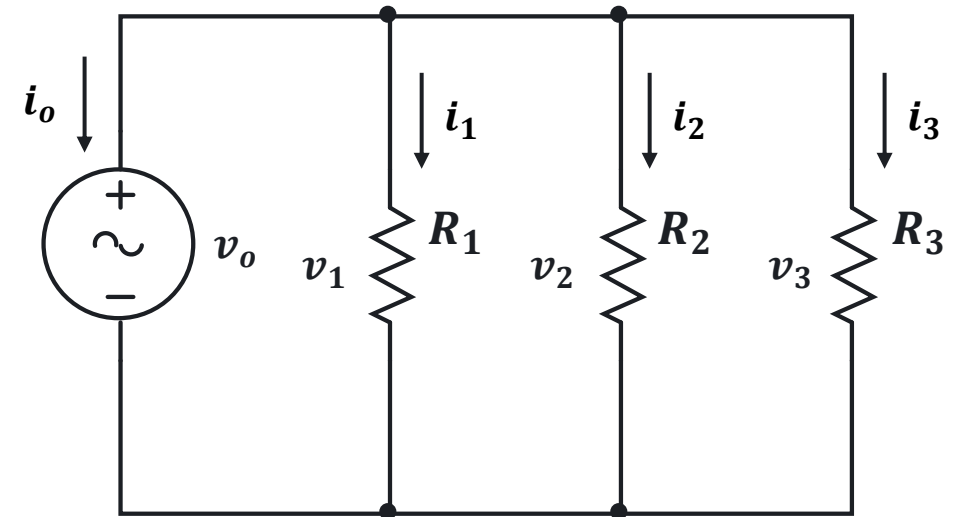


## EXERCISE

---

Determine the current flowing through each resistor of the given circuit.

Solution:

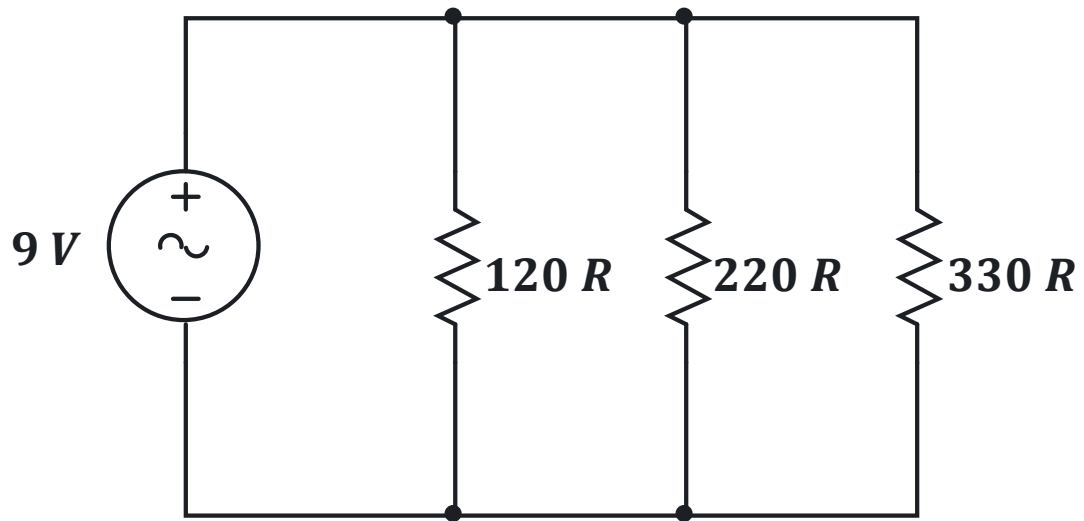

# **SERIES PARALLEL** **NETWORK**



# SERIAL-PARALLEL NETWORK

A series-parallel network is a type of electrical network that combines elements of both series and parallel circuits. These networks are commonly used in electrical and electronic systems to achieve desired voltage, current, and resistance characteristics.




## EXERCISE

---

Determine the current flowing through each resistor and the voltage drop across each resistor of the given circuit.

Solution:

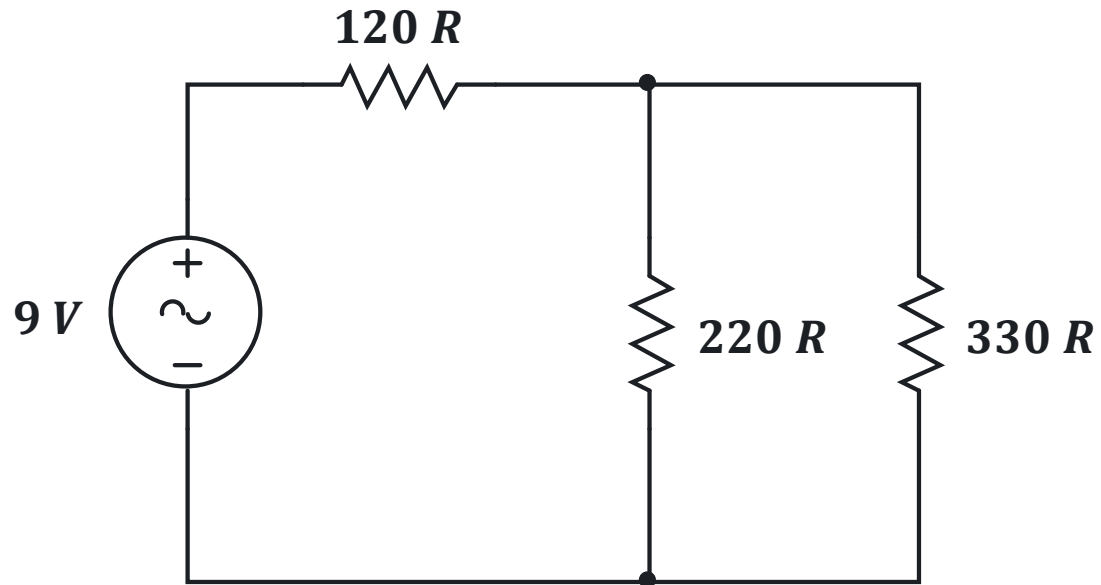




## EXERCISE

Determine the current flowing through each resistor and the voltage drop across each resistor of the given circuit.


Solution:

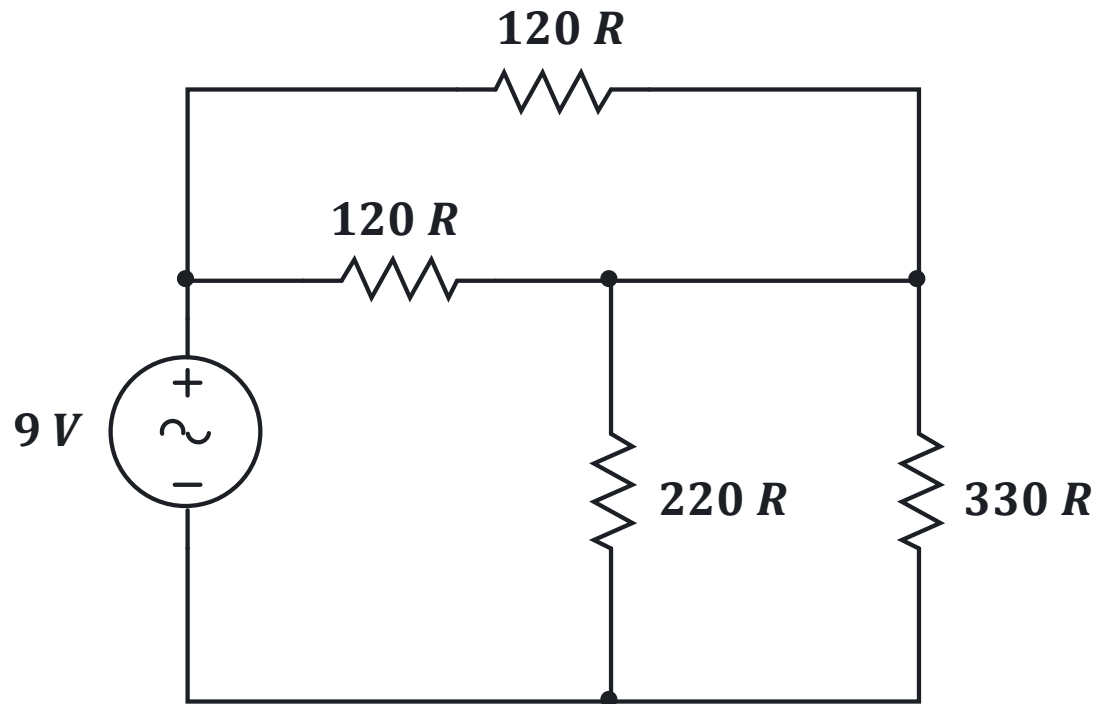

## EXERCISE

Determine the current flowing through each resistor and the voltage drop across each resistor of the given circuit.

Solution:

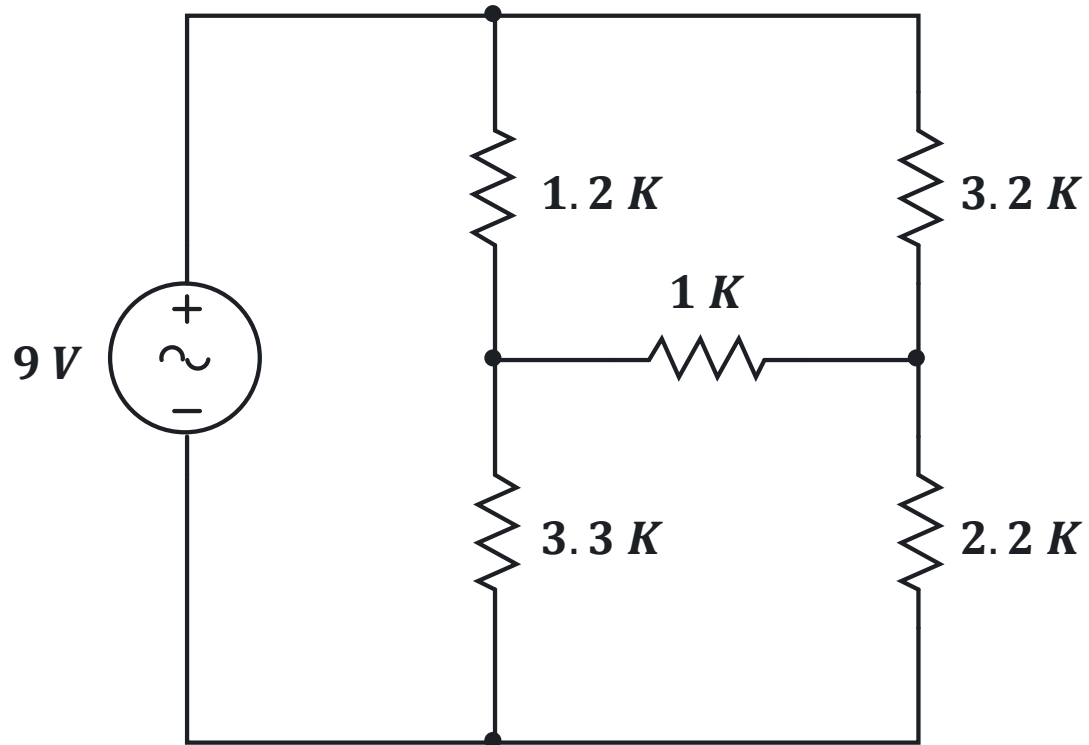

# LABORATORY



# LABORATORY 1

---

Reference File:

[student notes \laboratory exercises \L1-Lab 1  
Measuring Voltage-Current-Resistance.pdf](#)

