

VOLTAGE AND CURRENT DIVIDER THEOREM

BASIC CIRCUIT ANALYSIS METHOD

prepared by:

Gyro A. Madrona

Electronics Engineer

TOPIC OUTLINE

Voltage Divider Theorem (VDT)

Current Divider Theorem (IDT)



VOLTAGE DIVIDER THEOREM




VOLTAGE DIVIDER THEOREM

In a series circuit consisting of multiple resistors, the voltage across any resistor is proportional to its resistance relative to the equivalent resistance of the series combination.

Formula


$$v_N = v_{in} \frac{R_N}{R_{eq}}$$

Series Network

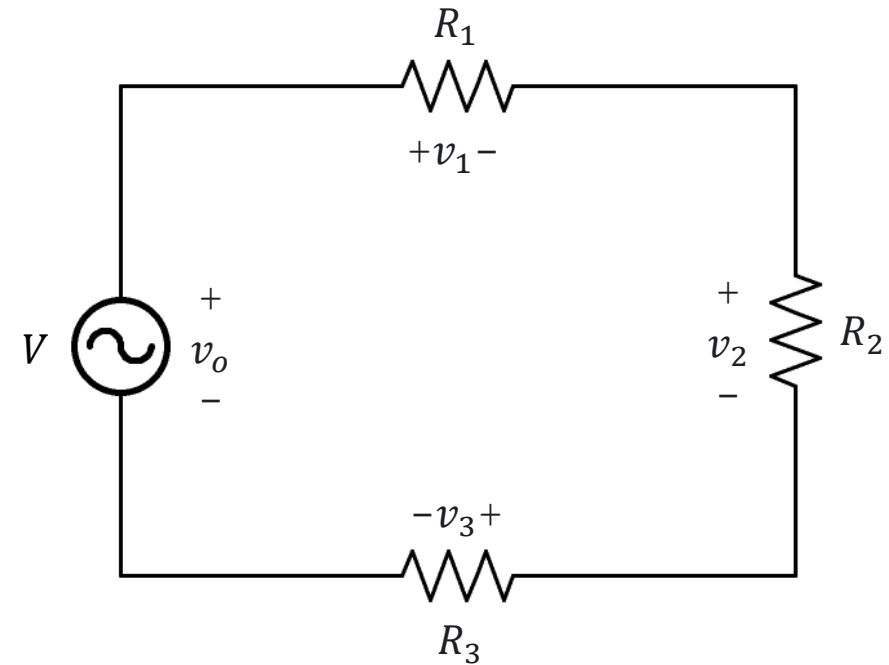

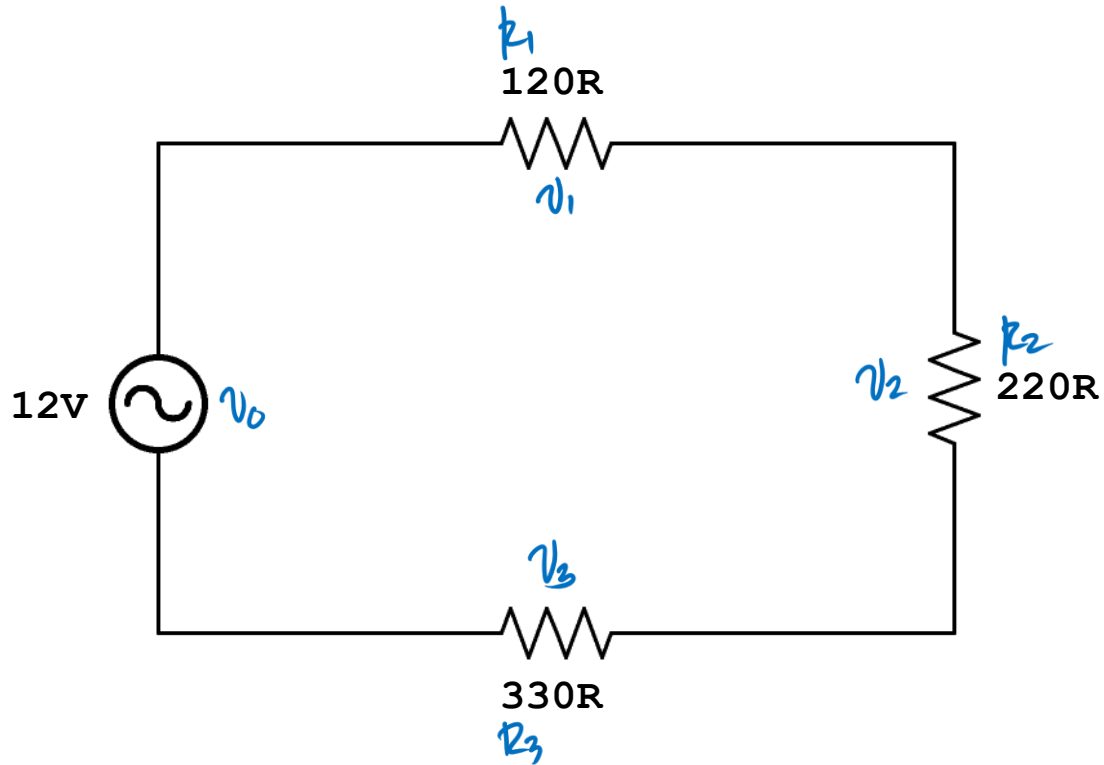EXERCISE

For the given series circuit, determine the voltage drops across each individual resistor.



Solution

Total Resistance

$$R_0 = R_1 + R_2 + R_3$$

$$R_0 = 120 + 220 + 330$$

$$R_0 = 670\Omega$$

VPT

$$V_1 = V_0 \frac{R_1}{R_0}$$

$$V_2 = V_0 \frac{R_2}{R_0}$$

$$V_3 = V_0 \frac{R_3}{R_0}$$

$$V_1 = 12 \frac{120}{670}$$

$$V_2 = 12 \frac{220}{670}$$

$$V_3 = 12 \frac{330}{670}$$

$$V_1 = 2.15V$$

$$V_2 = 3.94V$$

$$V_3 = 5.91V$$

ans

ans

ans

$$V_0 = 2.15 + 3.94 + 5.91 = 12V \checkmark$$

CURRENT DIVIDER THEOREM




CURRENT DIVIDER THEOREM

In a parallel circuit with multiple resistors, the current through any resistor is inversely proportional to its resistance relative to the equivalent resistance of the parallel combination.

Formula


$$i_N = i_{in} \frac{R_{eq}}{R_N}$$

Parallel Network

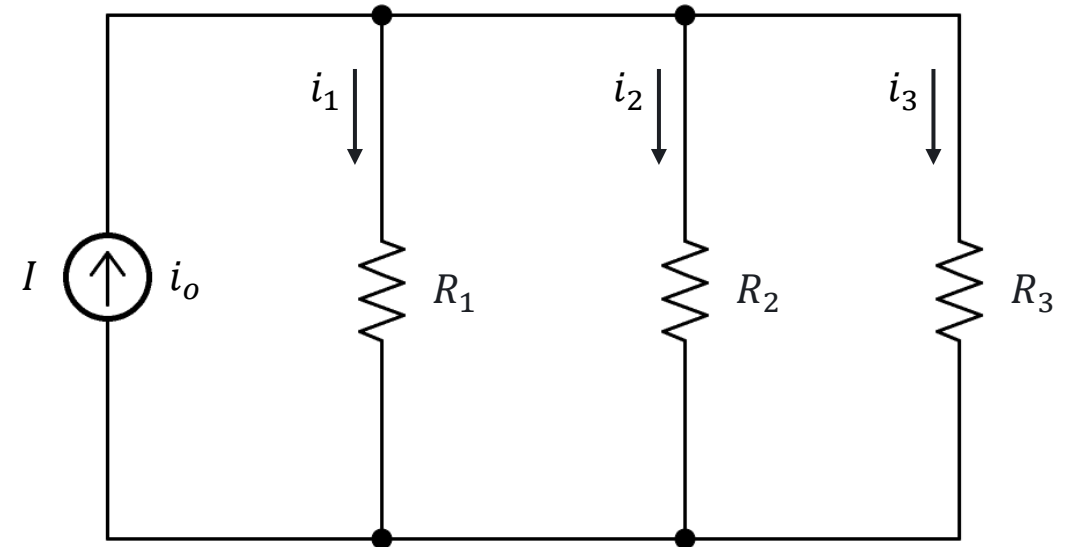

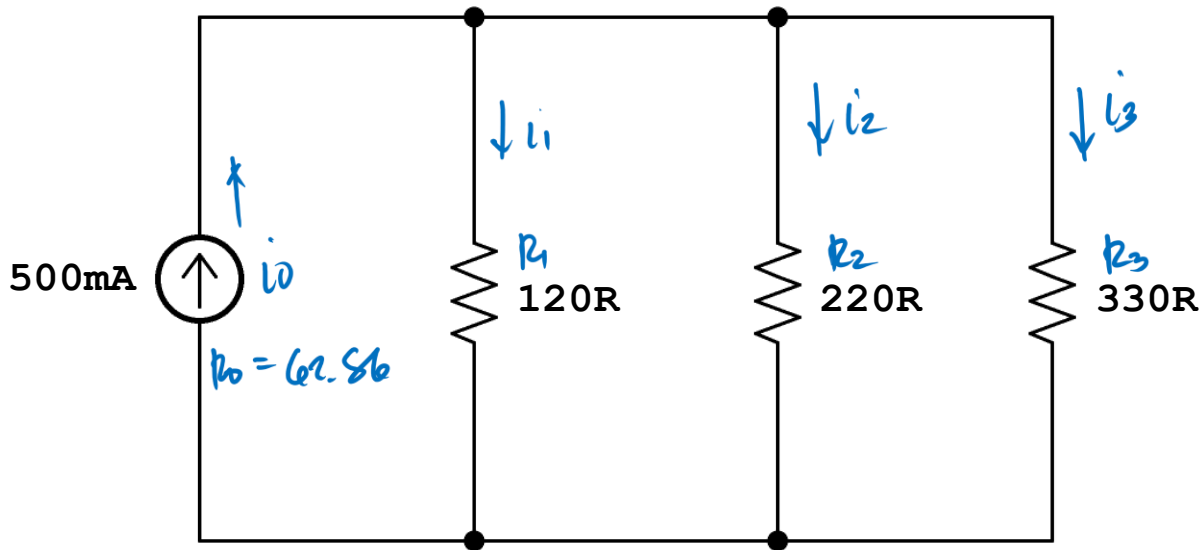EXERCISE

For the given parallel circuit, determine the current flowing through each individual resistor.



Solution

Total Resistance

$$G_0 = G_1 + G_2 + G_3$$

$$\frac{1}{R_0} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_0} = \frac{1}{120} + \frac{1}{220} + \frac{1}{330}$$

$$\frac{1}{R_0} = \frac{7}{440}$$


$$R_0 = \frac{440}{7}$$

$$\underline{R_0 = 62.86 \Omega}$$



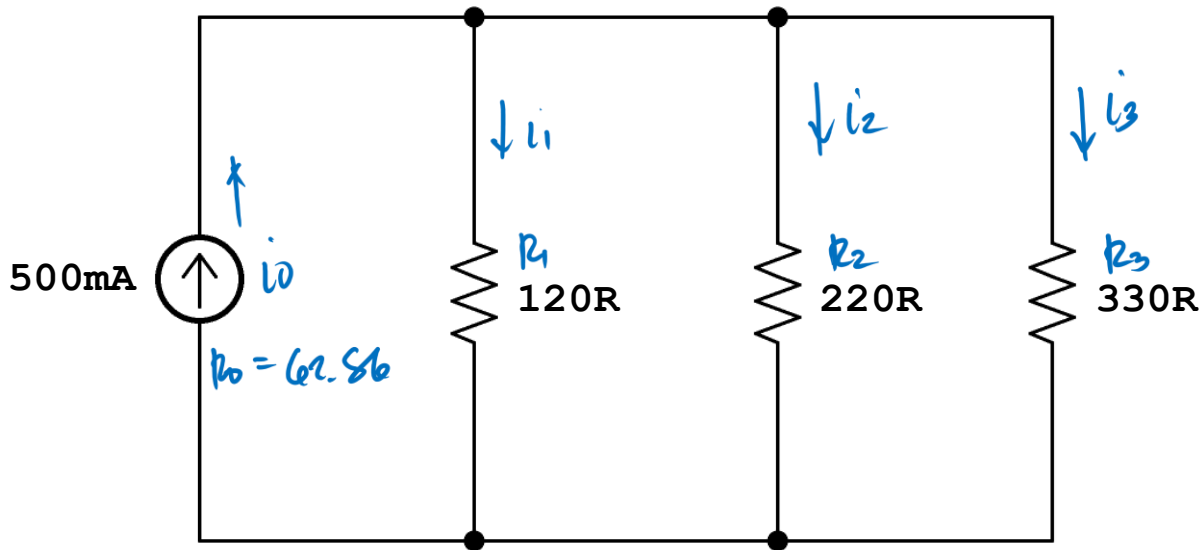EXERCISE

For the given parallel circuit, determine the current flowing through each individual resistor.



$$i_0 = 261.92 + 146.86 + 95.24$$

$$i_0 = \underline{500.02 \text{ mA}} \checkmark$$

Solution

10T

$$i_1 = i_0 \frac{R_0}{R_1}$$

$$= 500 \text{ m} \frac{62.86}{120}$$

$$i_1 = 261.92 \text{ mA}$$

ans

$$i_2 = i_0 \frac{R_0}{R_2}$$

$$= 500 \text{ m} \frac{62.86}{220}$$

$$i_2 = 142.86 \text{ mA}$$

ans

$$i_3 = i_0 \frac{R_0}{R_3}$$

$$= 500 \text{ m} \frac{62.86}{330}$$


$$i_3 = 95.24 \text{ mA}$$

ans



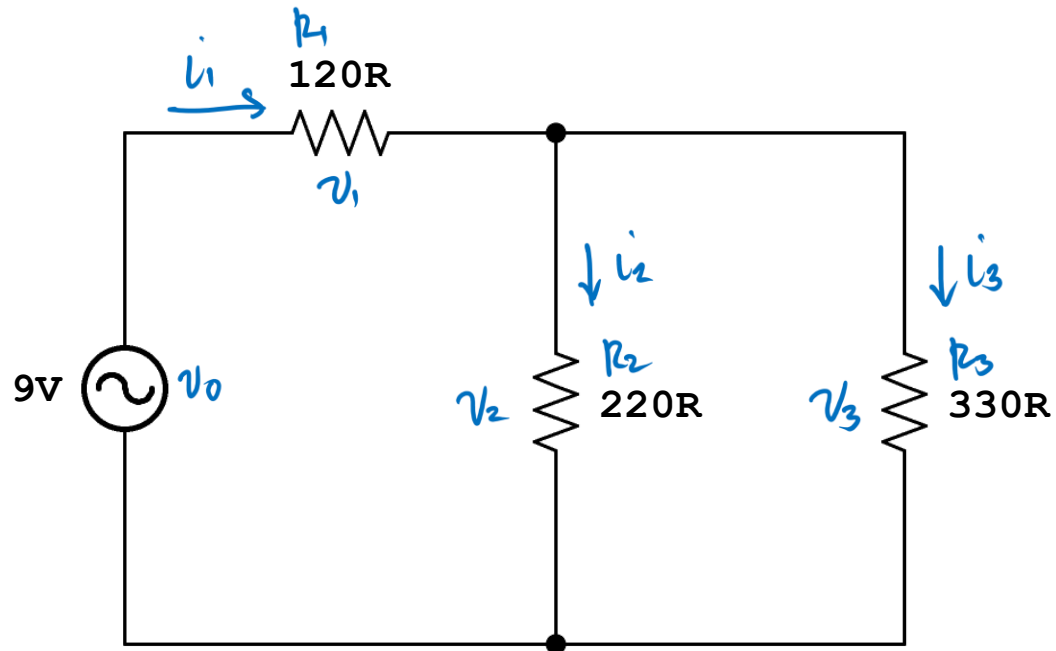EXERCISE

Analyze the given circuit to determine both the current through and the voltage drop across each resistor.



Solution


$$G_{2,3} = G_2 + G_3$$

$$\frac{1}{R_{2,3}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{2,3}} = \frac{1}{220} + \frac{1}{330}$$


$$\frac{1}{R_{2,3}} = \frac{1}{132}$$

$$\underline{R_{2,3} = 132\Omega}$$

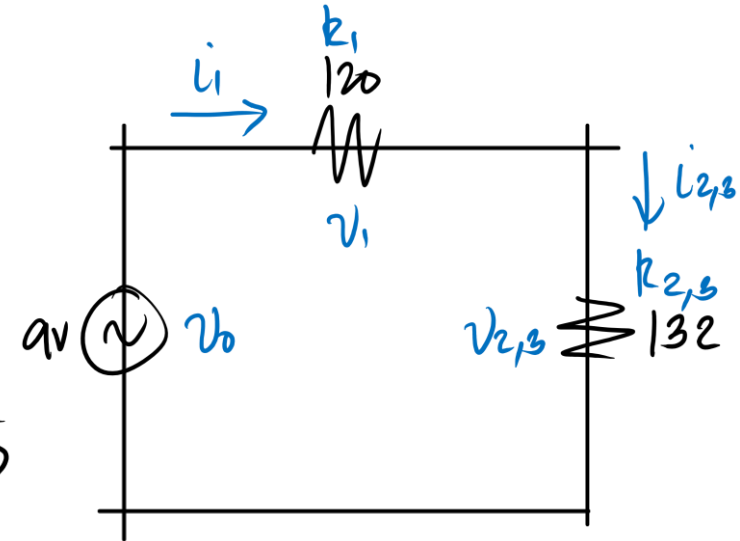

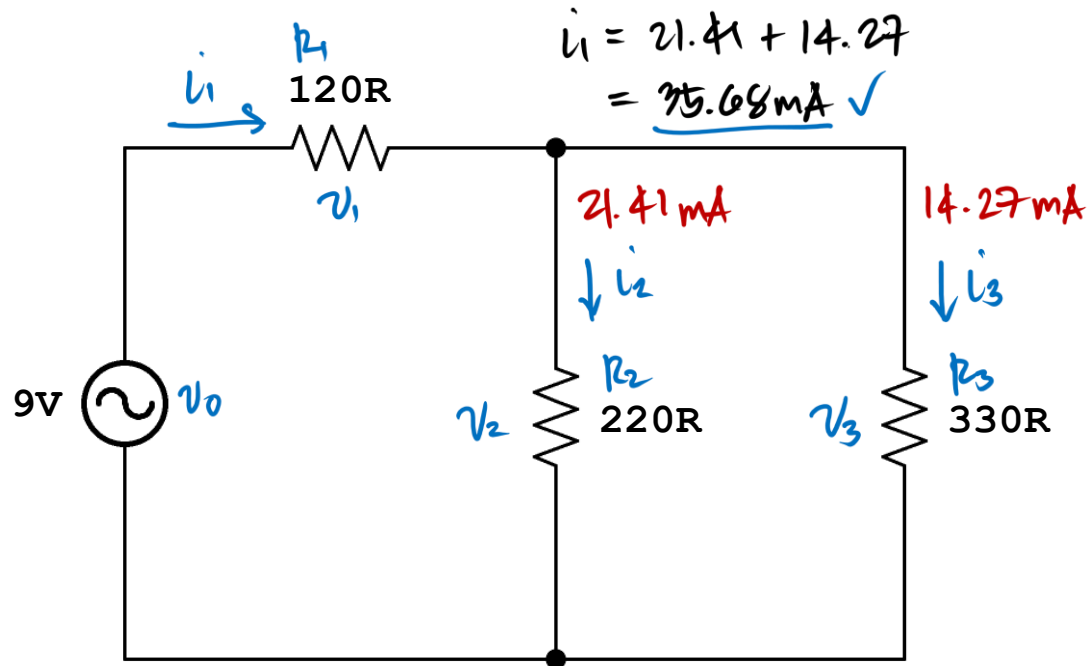EXERCISE

Analyze the given circuit to determine both the current through and the voltage drop across each resistor.



Solution

VDT

$$v_1 = v_0 \frac{R_1}{R_0}$$


$$v_1 = 9 \frac{120}{120 + 132}$$

$$v_1 = 4.29 \text{ V}$$

ans

$$i_1 = \frac{v_1}{R_1} = \frac{4.29}{120}$$

$$i_1 = 35.75 \text{ mA}$$

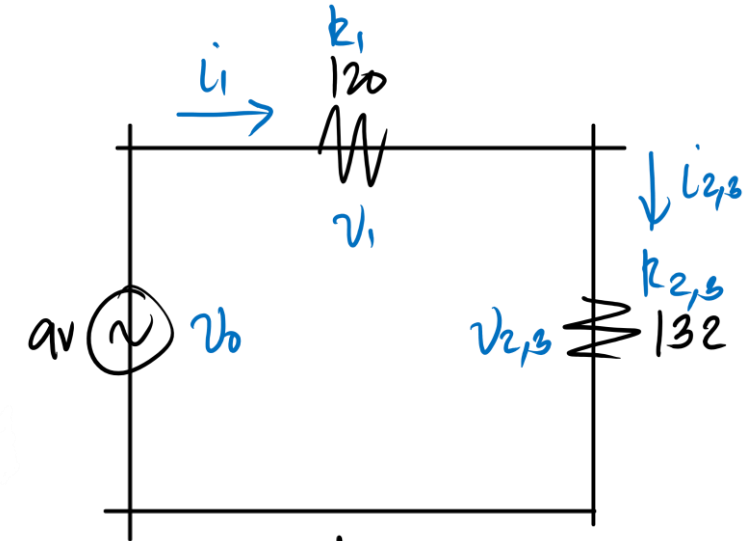

$$v_{2,3} = v_0 \frac{R_{2,3}}{R_0} = 9 \frac{132}{120 + 132}$$

$$v_2 = 4.71 \text{ V}$$

ans

$$v_3 = 4.71 \text{ V}$$

ans

LABORATORY

