



VOLTAGE-DIVIDER BIAS

BJT DC BIASING

prepared by:

Gyro A. Madrona

Electronics Engineer

TOPIC OUTLINE

Voltage-Divider Bias Circuit

- Base-Emitter Loop
- Collector-Emitter Loop
- Load Line Analysis



VOLTAGE-DIVIDER BIAS CIRCUIT



CURRENT GAIN

The current gain parameters alpha (α) and beta (β) describe the relationship between currents in the transistor's three terminals (emitter, base, and collector).

Alpha (α) is the ratio of the collector current to the emitter current.

Formula

$$\alpha = \frac{i_C}{i_E}$$

α is always less than 1 (typically 0.95 to 0.995)


Beta (β) is the ratio of the collector current to the base current.

Formula

$$\beta = \frac{i_C}{i_B}$$




VOLTAGE-DIVIDER BIAS CIRCUIT

 

The voltage-divider bias uses a pair of resistors (R_1 and R_2) to form a voltage divider that sets the base voltage. This configuration is less sensitive to variations in transistor beta (β) and offers a more stable operating point.



THEVENIN EQUIVALENT CIRCUIT

 

Thevenin Voltage

$$v_{TH} = v_{CC} \frac{R_2}{R_1 + R_2}$$


Thevenin Resistance

$$G_o = G_1 + G_2$$

$$\frac{1}{R_{TH}} = \frac{1}{R_1} + \frac{1}{R_2}$$



THEVENIN EQUIVALENT CIRCUIT

 

Thevenin Voltage

$$v_{TH} = v_{CC} \frac{R_2}{R_1 + R_2}$$


Thevenin Resistance

$$G_o = G_1 + G_2$$

$$\frac{1}{R_{TH}} = \frac{1}{R_1} + \frac{1}{R_2}$$



BASE-EMITTER LOOP

 

KVL @B-E

$$-v_{TH} + v_{RTH} + v_{BE} + v_{RE} = 0$$

$$v_{RTH} + v_{RE} = v_{TH} - v_{BE}$$

$$i_B R_{TH} + i_E R_E = v_{TH} - v_{BE}$$


$$i_B R_{TH} + i_B (\beta + 1) R_E = v_{TH} - v_{BE}$$

$$i_B (R_{TH} + (\beta + 1) R_E) = v_{TH} - v_{BE}$$

$$i_B = \frac{v_{TH} - v_{BE}}{R_{TH} + (\beta + 1) R_E}$$



COLLECTOR-EMITTER LOOP

 

KVL @C-E

$$-v_{CC} + v_{RC} + v_{CE} + v_{RE} = 0$$

$$v_{CE} = v_{CC} - v_{RC} - v_{RE}$$


$$v_{CE} = v_{CC} - i_C R_C - i_E R_E$$

$$i_E \approx i_C$$

$$v_{CE} = v_{CC} - i_C (R_C + R_E)$$



EXERCISE

 


For the given voltage-divider bias network, determine:

- Base current (i_{BQ})
- Collector current (i_{CQ})
- Collector-Emitter voltage (v_{CEQ})
- Emitter voltage (v_E)
- Collector Voltage (v_C)




EXERCISE

Solution

 

EXERCISE

Solution

 

LOAD LINE ANALYSIS




SATURATION POINT

The saturation point is the operating state where BJT conducts the maximum collector current ($i_{C(sat)}$) with zero collector-emitter voltage ($v_{CE} = 0$).


In this region the transistor acts like a closed switch (zero resistance between collector-emitter).

Collector Characteristic Curve

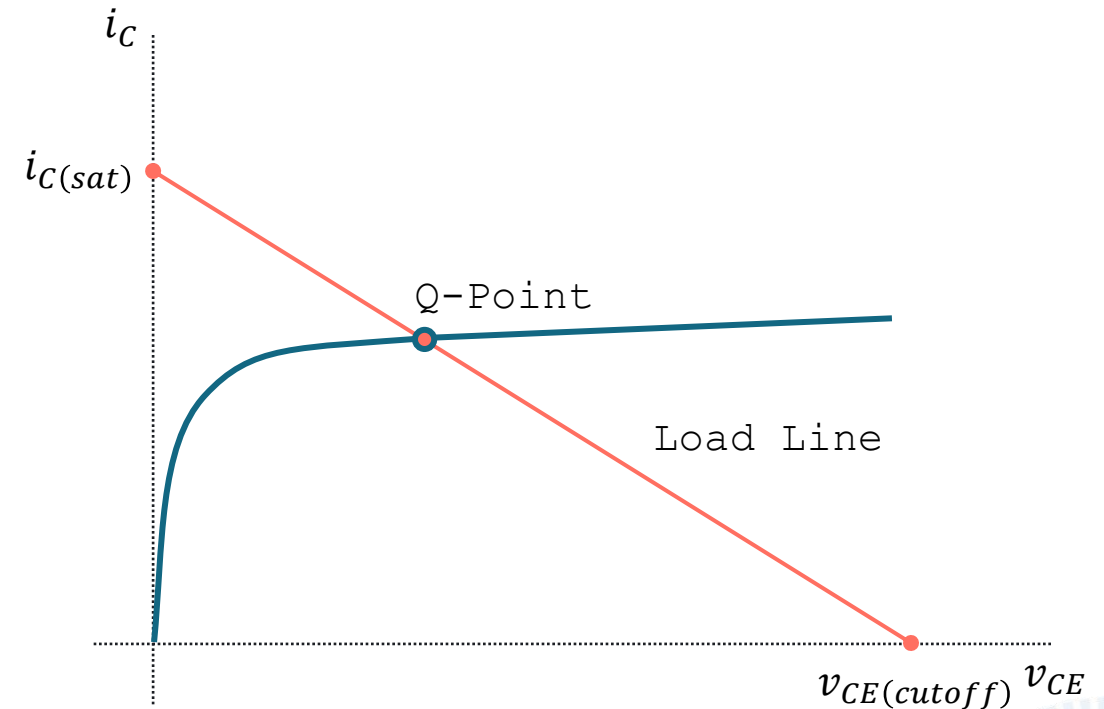


SATURATION POINT

Mentally Short

 

Collector Characteristic Curve

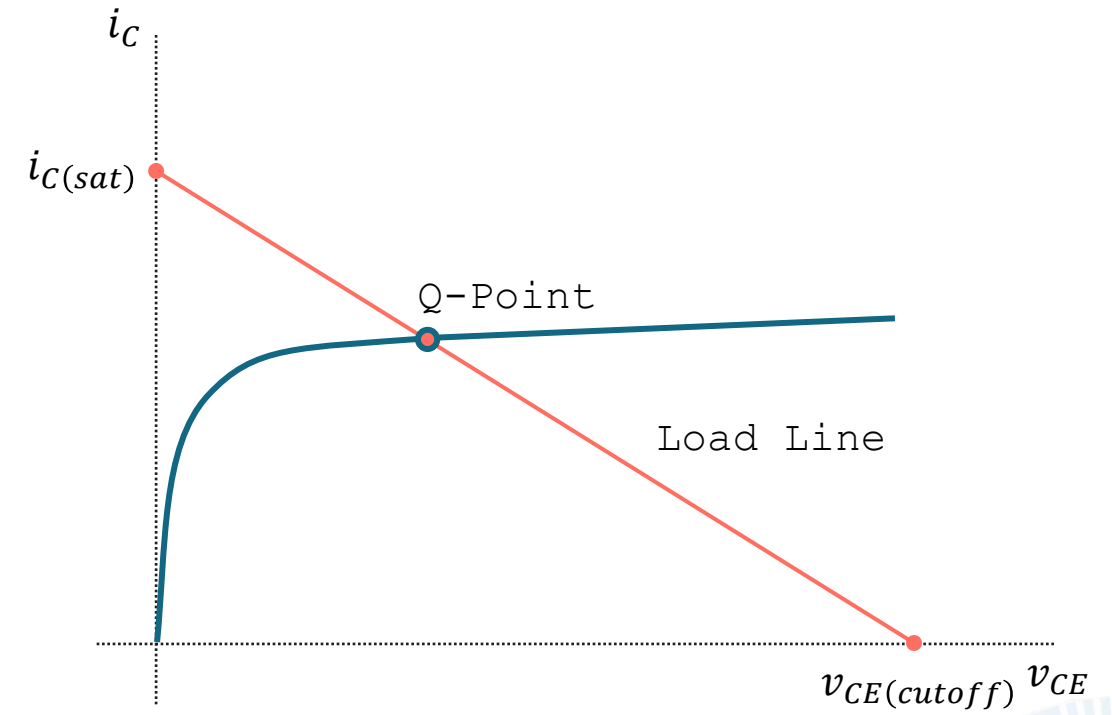


CUTOFF POINT

The cutoff point is the operating state where BJT conducts zero collector current ($i_C = 0$) with v_{CE} at its maximum ($v_{CE} = V_{CC}$).


In this region the transistor acts like an open switch (infinite resistance between collector-emitter).

Collector Characteristic Curve

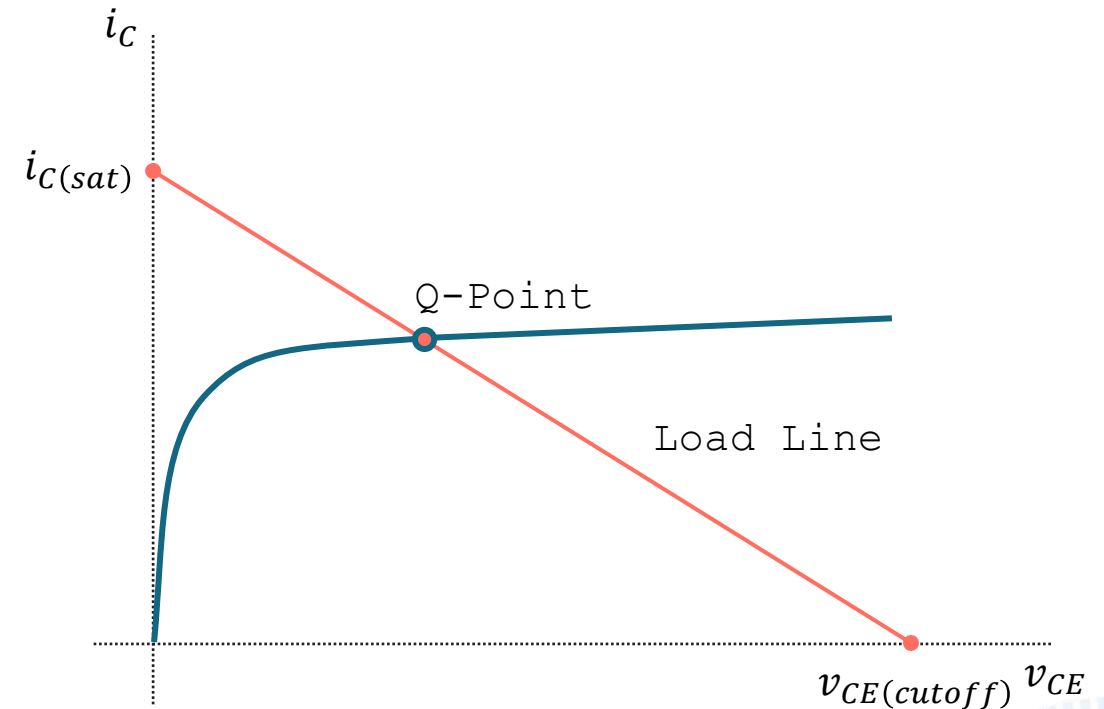


CUTOFF POINT

Mentally Open

 


Collector Characteristic Curve

 


QUIESCENT POINT

The Q-point is the stable DC operating condition characterized by specific value of collector current (i_C) and collector-emitter voltage (v_{CE}).

Collector Characteristic Curve

 

EXERCISE

 


Plot the DC load line analysis for the voltage-divider bias network, indicating:

- Saturation current ($i_{C(sat)}$)
- Cutoff voltage ($v_{CE(cutoff)}$)
- Operating Point (Q-Point)




EXERCISE

Solution

 


EXERCISE

Load Line Analysis

 

EXERCISE

 

For the given voltage-divider bias network, determine:

- Base current (i_{BQ})
- Collector current (i_{CQ})
- Collector-Emitter voltage (v_{CEQ})


And plot the DC load line analysis indicating:

- Saturation current ($i_{C(sat)}$)
- Cutoff voltage ($v_{CE(cutoff)}$)
- Operating Point (Q-Point)




EXERCISE

Solution

 


EXERCISE

Solution

 

EXERCISE

Load Line Analysis

 

INDEPENDENT OF THE TRANSISTOR BETA

Bias	β	$i_B (\mu A)$	$i_C (mA)$	$v_{CE} (V)$	$\% \Delta v_{CE}$
Fixed-Bias	50	47.08	2.35	6.83	-76%
	100	47.08	4.71	1.64	
Emitter-Stabilized	45	23.74	1.07	14.54	-31.16%
	90	37.04	3.33	10.01	
Voltage-Divider Bias					



LABORATORY

