CPE134 [Fundamentals of Electrical Circuits]

THEVENIN'S THEOREM

LABORATORY EXERCISE 5

Leader: _____

Date: _____ Rating: _____

Members: _____

_____

_____

_____

NEW MESSAGE

From: **Dana Modelle** (Quality Assurance Manager)

Subject: **Applying Thevenin's Theorem**

Good day, _____

I wanted to extend my appreciation for the exceptional work on the voltage divider design. It has significantly contributed to our cost-saving efforts by eliminating the need for purchasing a new power supply.

We are once again in need of your expertise for a new task. We currently have a motor driver module, but our primary focus lies on evaluating the motor's performance independently. Hence, we are planning to conduct tests on the motor external to its driver.

Could your team assist us in converting the motor driver circuit into its **Thevenin's Equivalent Circuit**? This would make a significant difference in our testing process.

Please refer to the attached files for further details regarding this request.
Thank you for consistently supporting us and for your commitment.

Best Regards,
Dana

Motor Driver Module,

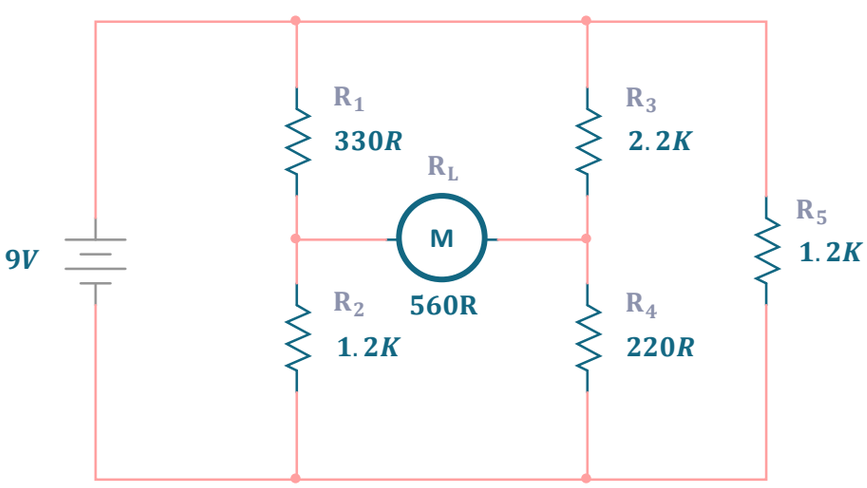

Reply: