SOLVING SYSTEMS OF LINEAR EQUATIONS BY MATRIX

LINEAR ALGEBRA

prepared by:

Gyro A. Madrona

Electronics Engineer

GRADING SYSTEM

FINAL GRADE

30%

PRELIM

30%

MIDTERM

40%

ENDTERM

TERM GRADE

70%

WEEKLY

30%

EXAM

WEEKLY GRADE

70%

LONG QUIZ

30%

SEATWORK

PENALTY

0

ABSENT

3

45-min LATE

7 max

15-min LATE

TOPIC OUTLINE

Solving System of Linear Equations by Matrix

SOLVING SYSTEM OF LINEAR EQUATIONS BY MATRIX

Solve the system of linear equations using matrix

$$-2a + 3b + 4c = 1$$

$$a + b + 5c = 2$$

$$b = 2a + c$$

Determine the voltages v_1, v_2 and v_3 of the given network.

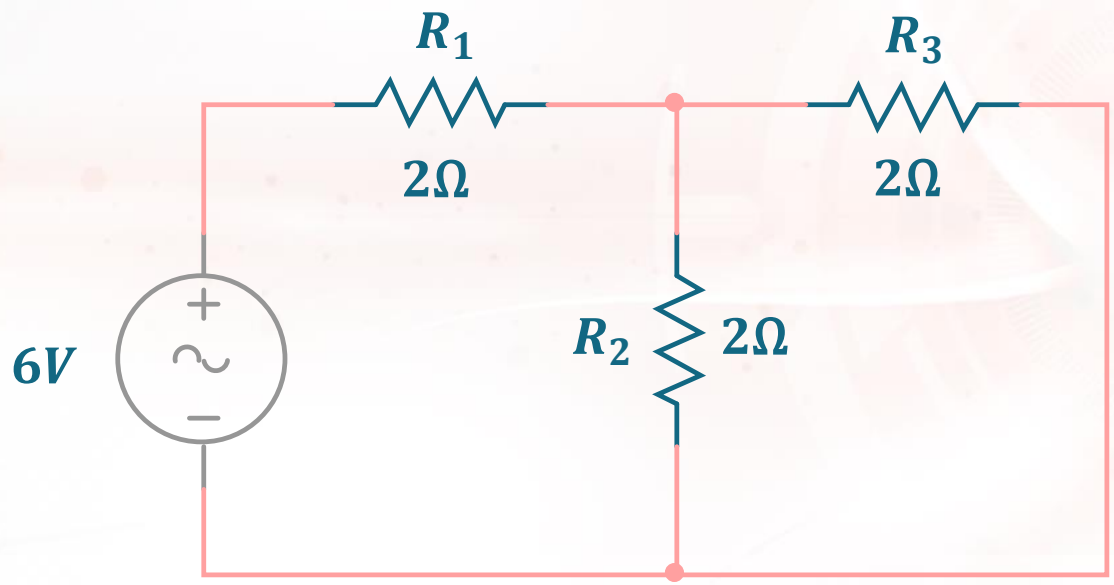

$$-\frac{v_1}{2} + \frac{v_2}{2} + \frac{v_3}{2} = 0$$

$$v_1 + v_2 + 0 = 6$$

$$0 - v_2 + v_3 = 0$$

SEATWORK